

2

~~350~~

(350)

-: HAND WRITTEN NOTES:-

OF

ELECTRICAL ENGINEERING

(1)

-: SUBJECT:-

ELECTRICAL MACHINES

2

②

$$R = \frac{\rho l}{A}$$

$$\propto \frac{l}{A}$$

$$\propto \frac{l}{V_{\text{of}}/l}$$

$$\propto l^2$$

(3)

$$I = \frac{V}{R}$$

$$= \frac{V}{\rho \frac{l}{A}}$$

$$I = \sigma \left(\frac{V}{l} \right) \times A$$

$\Rightarrow I = \sigma \cdot E$ → Point form of Ohm's law or microscopic form.

$$P = \frac{V^2}{R}$$


$$[P \propto V^2]$$

When connected with same supply :-

$$\frac{1}{P} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3} \rightarrow \text{series}$$

$$P = P_1 + P_2 + P_3 \rightarrow \text{parallel}$$

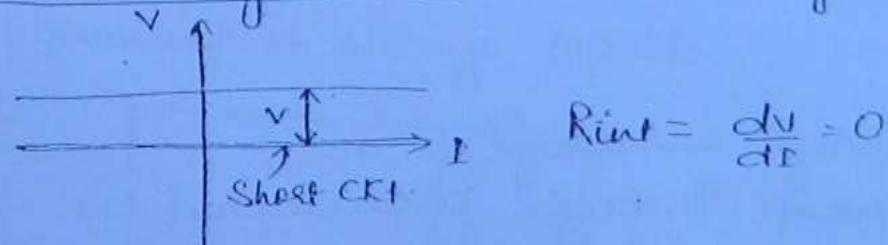Ideal Voltage Source → Const Voltage irrespective of current




Short CKT →

$$V = 0 \text{ for all } I$$

$$R = \frac{dV}{dI} = 0$$

Ideal Current Source →

const current irrespective of voltage.

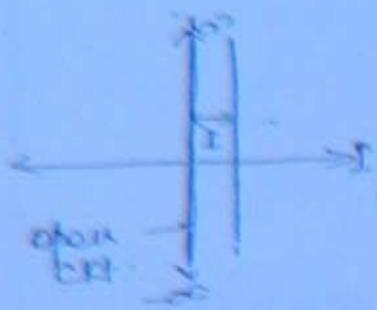


$$R_{int} = \frac{dV}{dt} = \infty$$

(9)


Open Ckt \rightarrow

$I=0$ for all V .

$$R_{eq} = \frac{dV}{dt} = \infty$$

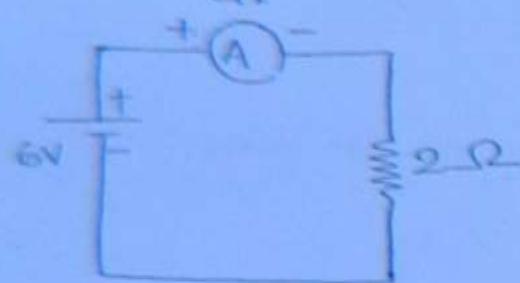


element is source.

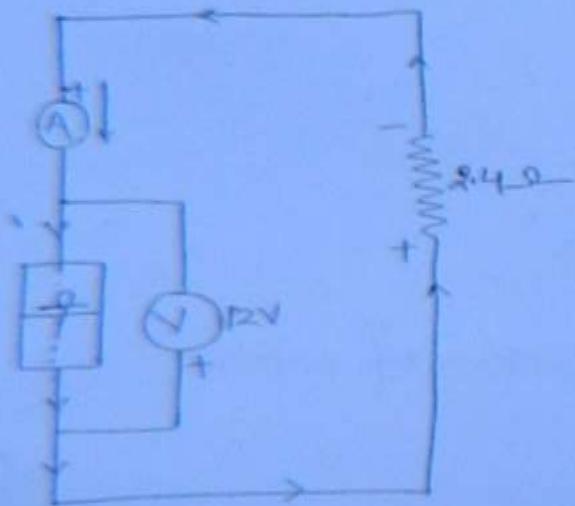

\rightarrow Pot. energy stored in the charge \rightarrow voltage


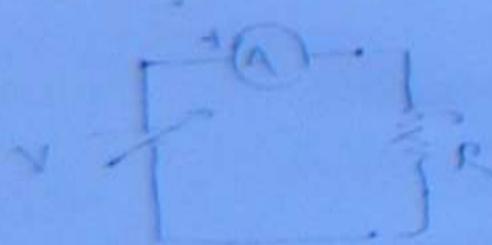
\rightarrow Amount of the charge flowing through a conductor is called current.




$$I = \frac{V}{R}$$

$\propto V$ when R is const
or

$\propto \frac{1}{R}$ when V is const

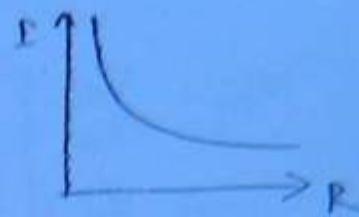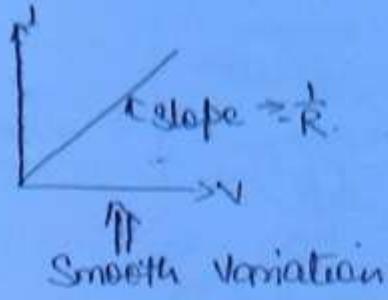


(5)

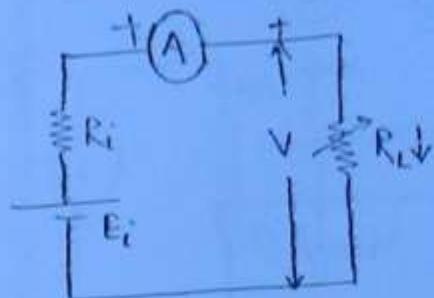


$$I = \frac{E}{R_i + R_L}$$

$$V = \frac{ER_L}{R_i + R_L}$$
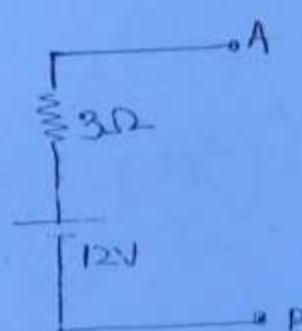
$$\downarrow V = \frac{E}{1 + \frac{R_i}{R_L}}$$



⇒

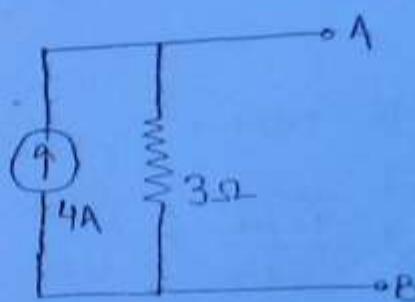



They are equivalent not identical.


For O.O. ⇒

Current in $3\Omega = 0$

Current in $3\Omega = 4A$

Equivalent is always outside.

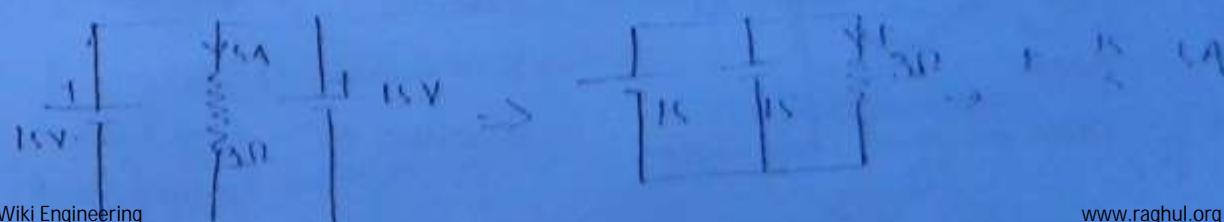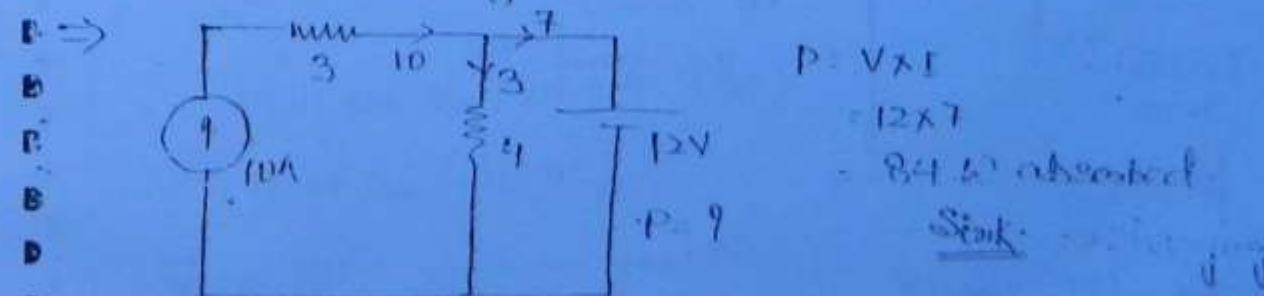


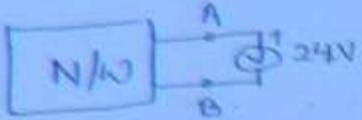

$$R_{eq} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{24}{8} = 3\Omega$$

(6)

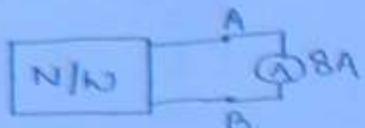


$$I_L = \frac{V_{oc}}{R_{eq} + R_L} = \frac{24}{3+5}$$

$$= 3A$$




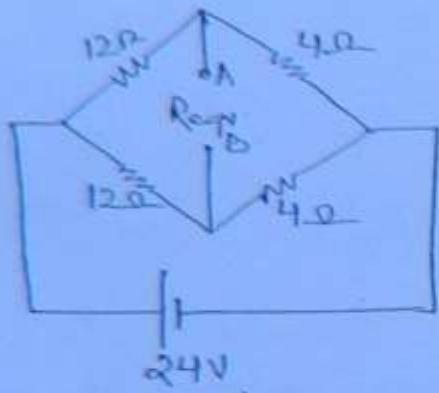
Q: $R_{eq} = \frac{V_{oc}}{I_{sc}}$ when $V_{oc} \neq 0$




$$R_{AB} = \frac{12 \times 4}{12+4} + \frac{12 \times 4}{12+4}$$

$$= 3+3$$



$$= 6\Omega$$

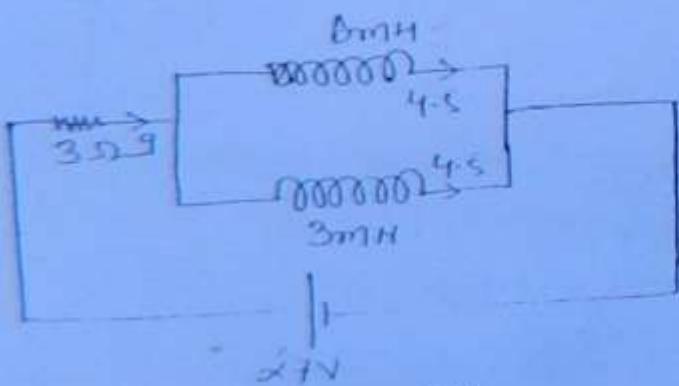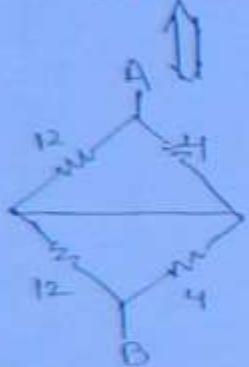


At S.C. \rightarrow
4.5 and 4.5

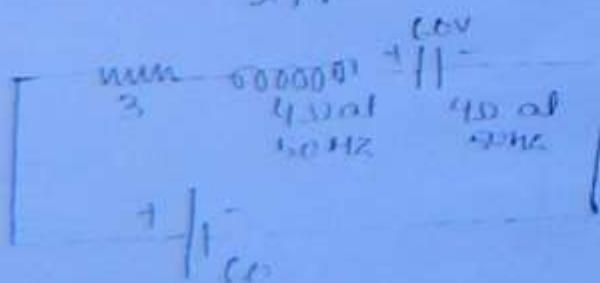

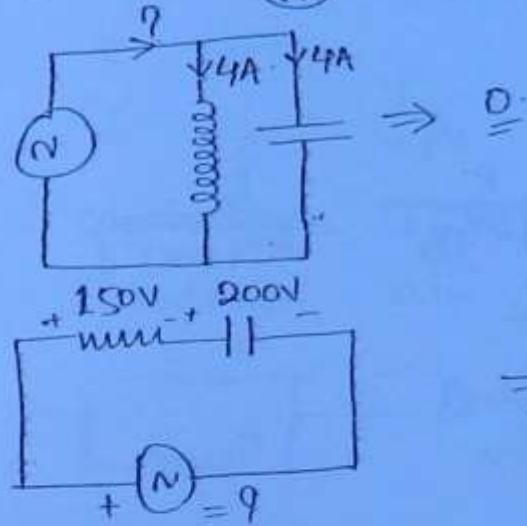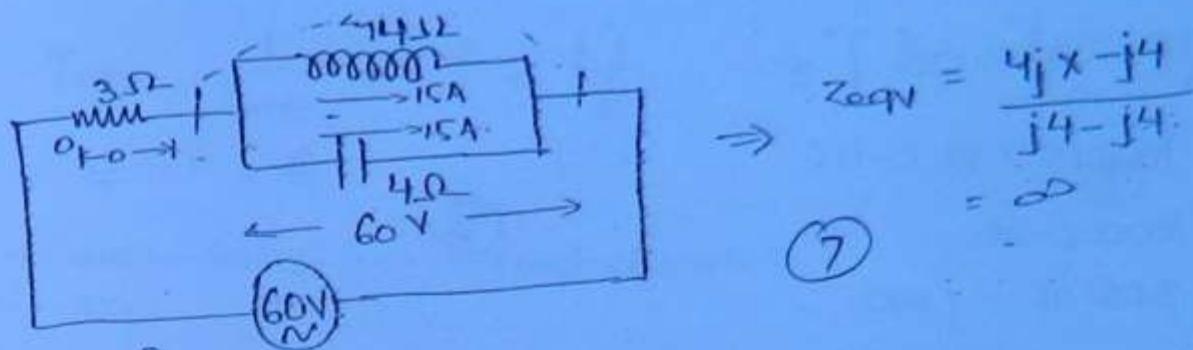
At S.C., $V_{ACROSS 3} = 0$.
 $V_{ACROSS L} = 0$.
 $V_{ACROSS BC} = 60V$ with
given polarity.


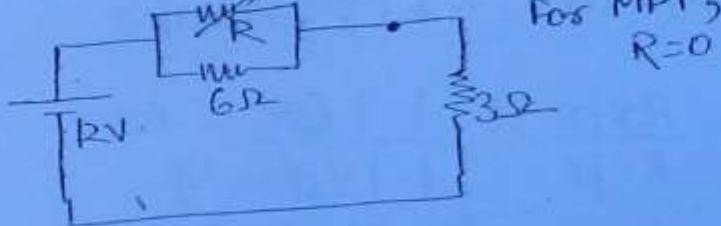
$$\Rightarrow \sqrt{150^2 + 200^2} = 250$$



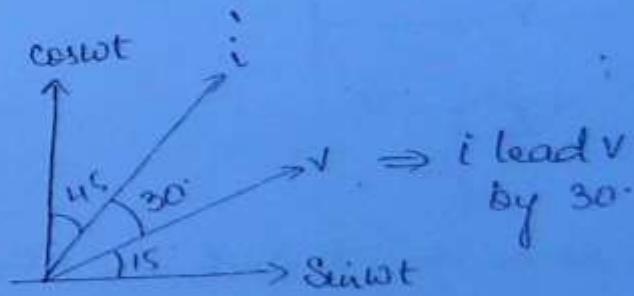MPT Applicable Only
When R_L is Variable
Not R variable.



$$v = 141.4 \sin(\omega t + 15)$$

$$i = 14.14 \cos(\omega t - 45)$$

$$\text{complex power} = 9$$

$$P = Vi$$

$$i = 14.14 \cos \sin(\omega t - 45 + 90)$$

$$= 14.14 \sin(\omega t + 45)$$

$$\sqrt{V} = \frac{141.4}{\sqrt{2}} \angle 115^\circ = 100 \angle 115$$

$$I = \frac{14.14}{\sqrt{2}} \angle 45^\circ = 10 \angle 45$$

$$\left| S = P_1 j Q = V I^* \right| Q \text{ is +ve for lagging VAR}$$

100 $\angle 115^\circ$

or $10 \angle 45$

$$S = 100 \angle 15^\circ [10 \angle 45^\circ]$$


$$= 100 \angle 15^\circ \times 10 \angle -45^\circ$$

$$= 1000 \angle -30^\circ$$

$$= 866.02 - j 500$$

(8)

$Q = 500$ VARs leading in nature.

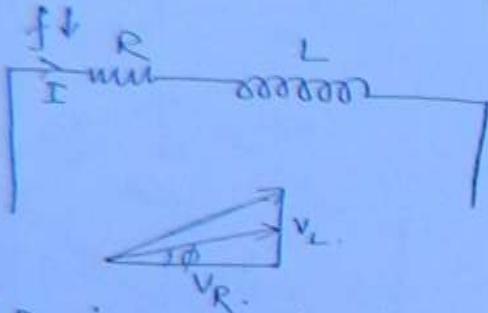

$$\uparrow P_f = \cos \phi = \frac{R}{\sqrt{R^2 + X_L^2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$


$$\tan \phi = \frac{R}{X_L}$$

Γ is same for R and L , so, $V = \Gamma Z$,

$$\text{for } R, V_R = \Gamma R$$

$$\text{for } L, V_L = \Gamma X_L = \Delta \omega f L$$

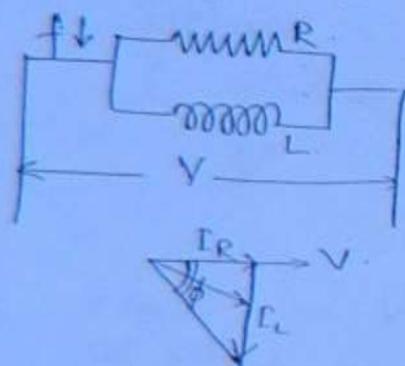$f \downarrow, X_L \downarrow, V_L \downarrow, \phi \downarrow, \cos \phi \uparrow$



$$Z_{eqv} = \frac{R + jX}{R + jX} = \frac{1 + j\tan^{-1} \frac{X}{R}}{1 + \tan^{-1} \frac{X}{R}}$$


$$f \downarrow, X \downarrow, \tan^{-1} \frac{X}{R} \downarrow, 90 - \tan^{-1} \frac{X}{R} \downarrow$$

$$\cos(90 - \tan^{-1} \frac{X}{R}) \downarrow$$

V is same for R and L , so, $I = \frac{V}{Z}$

$$\text{for } R, V_R = \Gamma R \Rightarrow I_R = \frac{V_R}{R}$$
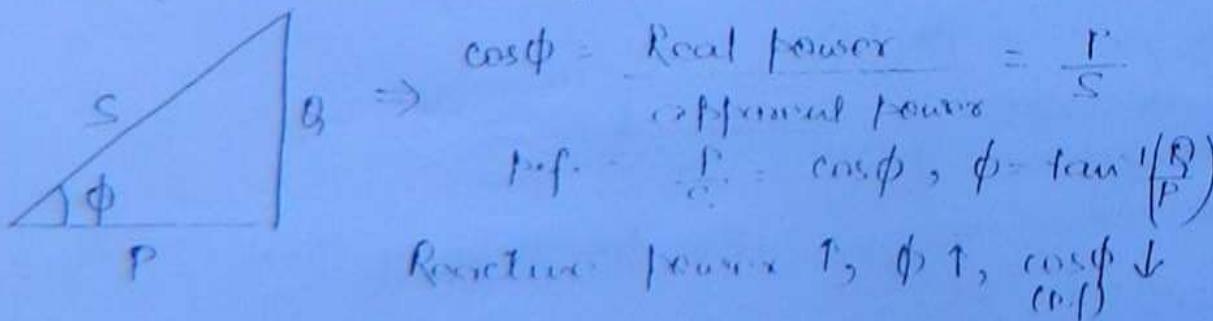
$$\text{for } L, I_L = \frac{V_L}{X_L} = \frac{V_L}{\Delta \omega f L} \quad f \downarrow, I_L \uparrow, \phi \uparrow, \cos \phi \downarrow$$



$$Y_{eqv} = \frac{1}{Z_{eqv}} = \frac{1}{R + j\frac{1}{X}} = \frac{1}{R} - j\frac{1}{R} = G - j\frac{1}{R}$$

~~If $X \downarrow$; G~~ (9)

~~num 80000~~ conductance = ?
~~3Ω~~ ~~4Ω~~

$$Z = 3+j4$$

$$Y = \frac{1}{Z} = \frac{1}{3+j4} = \frac{3-j4}{3^2+4^2} = \frac{3}{25} - j\frac{4}{25}$$

$$\text{conductance} = \frac{3}{25} = 0.12$$



$$\text{Susceptance} = 0.16$$

~~num 3~~ ~~80000~~ Resistance = ?

$$\begin{aligned} Z &= \frac{3+j4}{3+j4} \\ &= \frac{12j}{3+j4} \\ &= \frac{12j(3-j4)}{25} \\ &= \frac{36}{25}j + \frac{48}{25} \\ &= 1.92 + 1.44j \end{aligned}$$

$$\text{Resistance} = 1.92$$

$$X = 1.44$$

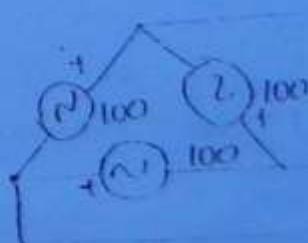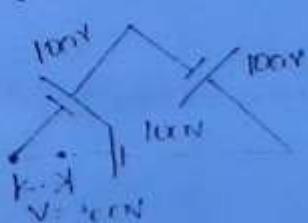

- If no load, no current in the internal legs.
- A closed delta has no fundamental loop current at no load.

2500 kVA, 2500V / 250 V. → for Transformer.
 ↑ ↑
 Rated O/P VA Rated O/P Voltage.

(10)

O/P will be rated delivered at rated VA.

1000W, 200V → bulb connected to 2nd side of transformer.

2000 / 200V

↓
180V

$P = \frac{V^2}{R}$ → R is constant for given bulb.

$P \propto V^2$

$$P = 1000 \times \left(\frac{\frac{180}{200}}{10} \right)^2$$

$$= 1000 \times \frac{81}{100}$$

$$= 810 \text{ W.}$$

Voltage regulation = $\frac{V_{NL} - V_{FL}}{V_{FL}}$ FL → Rated Voltage

Turns Ratio = $\frac{HV \text{ turns}}{LV \text{ turns}}$


Volt. Ratio = $\frac{\text{RMS terminal voltage at high voltage side}}{\text{RMS terminal voltage at low voltage side}}$

Lenz's Law →

Acc. to Lenz's law,

The direction of induced emf is such that it tends to oppose the cause to cause a current the current so produced opposes the cause.

$$e = - N \frac{d\phi}{dt}$$

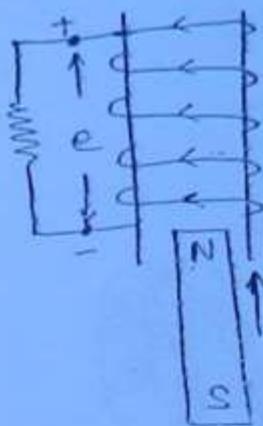


$$\Rightarrow e = + \frac{Nd\phi}{dt}$$

(1)

$$e = \pm \frac{d\lambda}{dt}, \lambda \rightarrow \text{flux links}$$


$$= \pm \frac{Nd\phi}{dt}$$

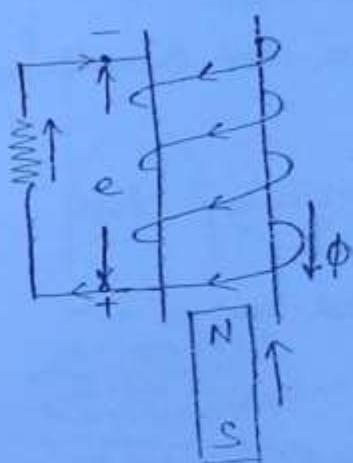where the sign depends on
Lenz law and which formula
is taken as true



$$\Rightarrow e = \frac{Nd\phi}{dt}$$


$\phi = \text{eff. flux}$

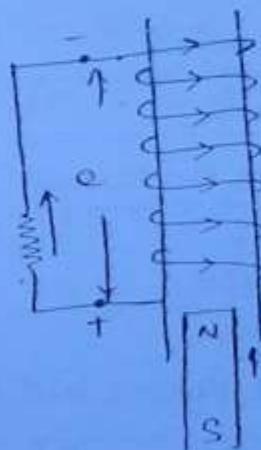


$$\Rightarrow e = - \frac{Nd\phi}{dt}$$



$$\Rightarrow e = - \frac{Nd\phi}{dt}$$

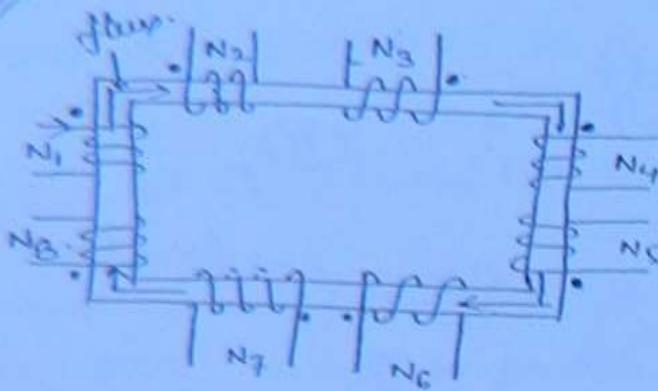

(12)

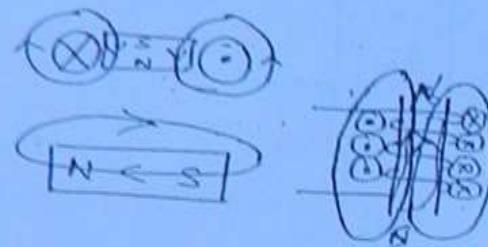

Dot convention :-

If the currents enter or leave through the dot simultaneous fluxes are additive.


Only the first dot can be assigned. Remaining dots follow automatically.

In II

Single phase transformer [dot assigned in the direction of original flux that is having +ve sign of e_1 and T tangent in case of opp. polarity of e_2 for the original flux]

AC response is always seen at $t=0$
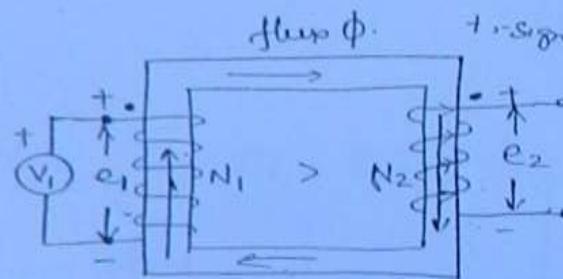
$$e_1 = N_1 \frac{d\phi}{dt} \quad \text{when } e_1 \text{ is expressed as voltage drop}$$



ideal transformer on No load

$$= -N_1 \frac{d\phi}{dt} \quad \text{when } e_1 \text{ is expressed as voltage rise.}$$

$$e_2 = N_2 \frac{d\phi}{dt} \quad \text{when polarity of } e_2 \text{ directly satisfies lenz's law.}$$

Ideal transformer \rightarrow

- ▷ No losses
- ▷ No leakage flux
- ▷ $H = \infty \rightarrow$ Excitation is 0 when flux ϕ is $\neq 0$

$$\text{mmf} = 0, \quad \text{when } \phi \neq 0. \quad \phi = \frac{\text{mmf}}{\text{reluctance}} = \frac{\text{mmf}}{l/160A} \quad \phi = \frac{\text{mmf} \cdot 160A}{l}$$


$$\phi = \frac{N_1 E_0}{\text{Reluctance}}$$

$$= \frac{N_1 E_0}{l/\mu A}$$

$$= \frac{(N_1 E_0) \mu A}{l}$$

$$\Rightarrow E_0 = \frac{\phi \times l}{\mu A N_1} = 0.$$

$$\phi = \phi_m \sin \omega t$$

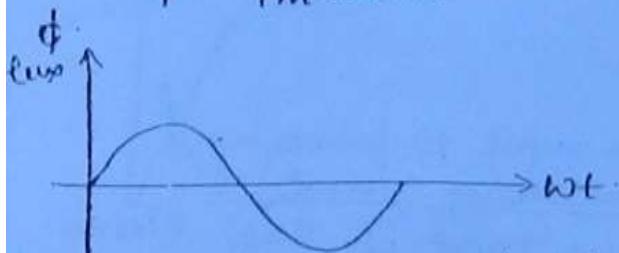

$$\phi = \phi_m \sin \omega t$$

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$= N_1 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= N_1 \phi_m \omega \cos \omega t$$

$$[e_1 = N_1 \phi_m \omega \sin(\omega t + 90^\circ)]$$

$$\vec{V}_1 = \vec{E}_1$$

$$\vec{V}_2 = \vec{E}_2$$

\rightarrow flux $\phi \rightarrow$

ideal transformer on no loss

$$e_2 = N_2 \frac{d\phi}{dt}$$

$$= N_2 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= N_2 \phi_m \omega \cos \omega t$$

$$[e_2 = N_2 \phi_m \omega \sin(\omega t + 90^\circ)]$$

$I_{1,\text{rms}} = \frac{N_1 \phi_m \omega}{J_s}$ \rightarrow $\propto \int \phi_m N_1$ \rightarrow induced emf at 1st


$I_{2,\text{rms}} = \frac{N_2 \phi_m \omega}{J_s}$ \rightarrow $\propto \int \phi_m N_2$ \rightarrow induced emf at 2nd

on load current or exciting current \Rightarrow no load ! —

mmf balance of ideal transformer

$$= N_1 \bar{E}_1 - N_2 \bar{E}_2 = 0$$
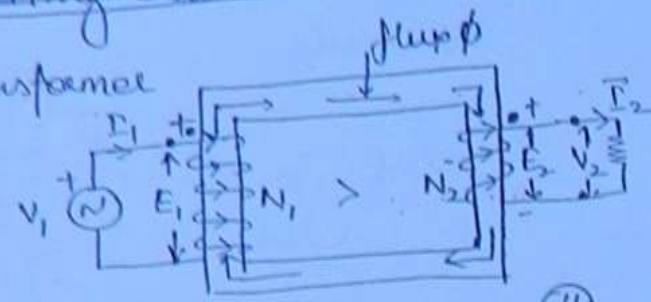
$$\Rightarrow \bar{E}_1 = \frac{N_2}{N_1} \bar{E}_2 \\ = \bar{E}'_2$$



(14)

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2} = \frac{\bar{E}_2}{\bar{E}_1} = a = \text{turns ratio} \approx \text{voltage ratio.}$$

$$\bar{E}_1 = \frac{\bar{E}_2}{a}$$

$= \bar{E}'_2$. [Secondary current with refer to primary]
Also called balancing current]

Dot convention—


As applied to transformers this means that if the current enters through the dot in primary wedg then it should leave through the dot from the secondary wedg,
In other words for transformers when dots represent same instantaneous polarity

$$\frac{V_1}{V_2} = \frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2} = a = \frac{\bar{E}'_2}{\bar{E}_1}$$

$$\Rightarrow V_1 I_1^* = V_2 I_2^*$$

$$\text{or}, E_1 I_1^* = E_2 I_2^*$$

$$\text{or}, \bar{S}_1 = \bar{S}_2$$

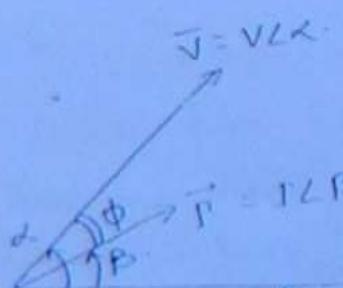

Reference axis or Datum

$$P_1 j\theta : V I^* = V L \angle(\alpha - \beta) = V_1 (\phi - V_1 \cos \phi + j V_1 \sin \phi)$$

$\nabla \times \vec{B} = \vec{J}$

F

$$P = \frac{d}{dt} (\text{work})$$

$$= \frac{dt}{dt} m$$

$$= \frac{vdq}{dt}$$

$$= vi$$

$\Rightarrow Q$ is fine for lagging VARs.

$$Q = VI \sin \phi.$$




$$\bar{S}^* = P - jQ \therefore \bar{V}^* \bar{I}$$

$$= VI - j IL + P$$

$$= VI \angle -\phi.$$

$$= VI \cos \phi - j VI \sin \phi.$$

(15)

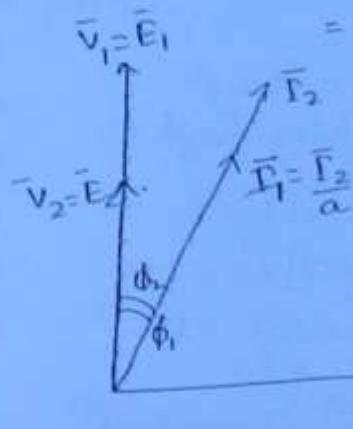

\Rightarrow ideal transformers on lagging Pf load.

Towards a PRACTICAL transformer

Departure from ideal transformer.

a) $M \neq \infty$

On no load

$$V_1 = E_1$$

$$V_2 = E_2$$

$90^\circ \rightarrow I_0 \rightarrow \text{flux } \phi$

tosless core X'mal on No-load
($M \neq \infty$)

$\phi \neq 90^\circ$ because $\cos \phi \rightarrow -ve$

Active = -ve so, from wdg to

Source, P is taken which is not practically possible.

Lossy core X'mal on No load

$\phi \neq 90^\circ$

$\phi \neq 90^\circ$

$\phi_0 \sim 75 \text{ to } 90^\circ$

$$V_1 = E_1$$

$$V_2 = E_2$$

$\phi_0 > 90^\circ$

$\phi_0 < 90^\circ$

$\phi \neq 90^\circ$

Angle of magnetization

$I_\phi \rightarrow$ net responsible for loss.

$I_o \rightarrow$ exciting current or No load current.

$\Gamma_{sc} \rightarrow \Gamma_o \cos \phi_o \rightarrow$ core loss component of Γ_o . (16)


$\Gamma_\phi \rightarrow \Gamma_o \sin \phi_o \rightarrow$ magnetising component of Γ_o .

$$\boxed{\Gamma_o \rightarrow 2 \text{ to } 5\% \text{ of } \Gamma_{PL}}$$

$$\boxed{N_1 I_1 - N_2 I_2 = N_1 \Gamma_o} \leftarrow \text{mmf balance on load. When } \Gamma_o \neq 0.$$

$$\bar{\Gamma}_1 = \frac{\bar{\Gamma}_2}{a} + \bar{\Gamma}_o$$


on lagging pf load \rightarrow

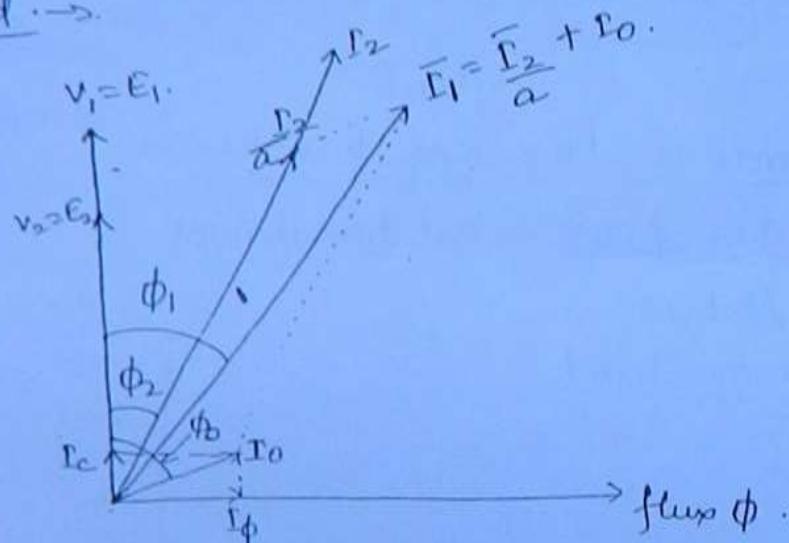


lossy core & m.e on lagging pf load:

leakage flux is that which is not a common flux or mutual flux.

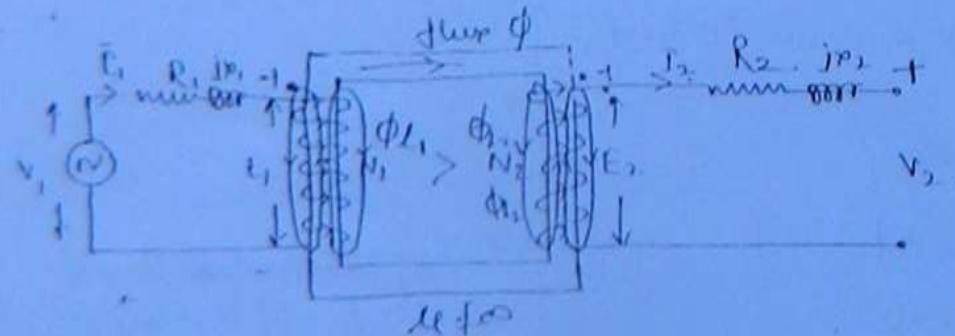common flux or mutual flux is that which links both windings.



Analogy b/w main flux and leakage flux -

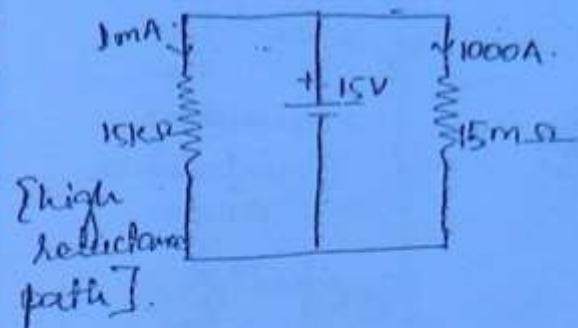

Flux cannot be confined inside one dirⁿ
current can be confined along one dirⁿ.

(17)

$$\bar{A} \propto \bar{B}$$


$$a \propto b$$

$$a = Kb$$

$$= K[B \sin \omega t]$$

$$a = KB \sin \omega t$$

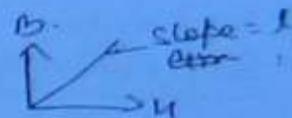$\phi_{\text{leakage}} \propto i$ [because of air.] BH curve



E_{11} → primary flux voltage

E_{12} → secondary leakage flux voltage

Leiman lit,
phase seq.
is BPP.


→ flux ϕ

X_1 → Primary leakage reactance

X_2 → Secondary leak reactance

Z_1 → primary leakage impedance

Z_2 → secondary leakage impedance

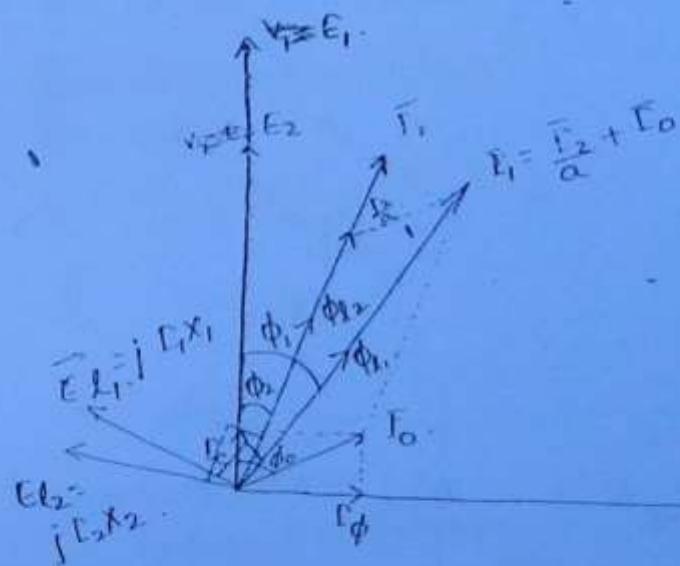

$$E_1 = V_1 + I_1 R_1 + j I_1 X_1$$


$$I_1 = \frac{P_2}{Z_1} = \frac{P_2}{R_1 + j X_1}$$

$$I_1 = \frac{P_2}{\alpha} + \bar{I}_o$$

$$V_1 = I_1 R_1 + I_1 X_1$$

$$= I_1 (R_1 + j X_1)$$

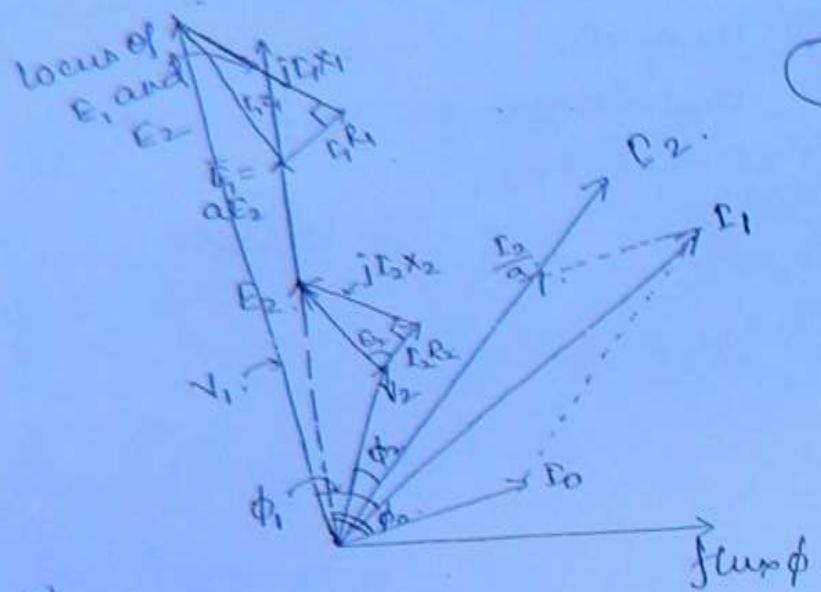Step down mode and lagging pf load \rightarrow



$$D_2 = \tan^{-1} \frac{X_2}{R_2}$$

D_2 = secondary impedance angle

$$D_1 = \tan^{-1} \frac{X_1}{R_1}$$

\Rightarrow complete phasor diagram.




Step down mode and leading pf load \rightarrow

$$E_2 = V_2 + I_2 R_2 + j I_2 X_2$$


$$E_1 = a E_2$$

$$V_1 = \frac{E_2}{a} + E_0$$

$$V_1 = E_1 + I_1 R_1 + j I_1 X_1$$

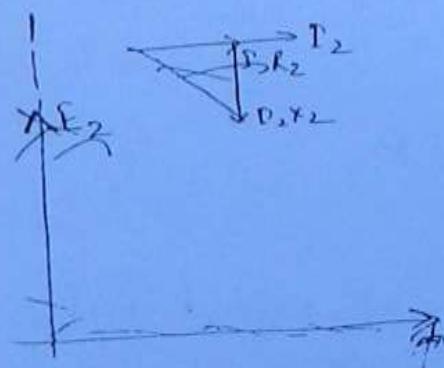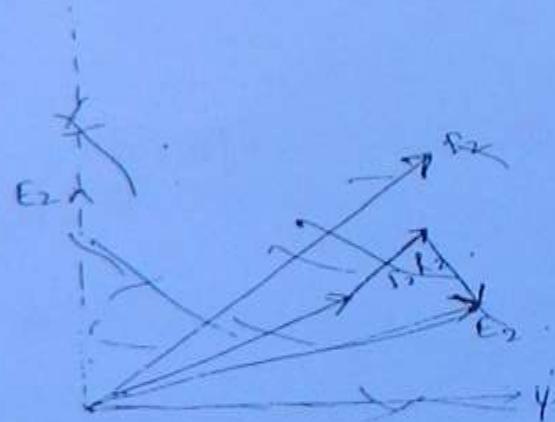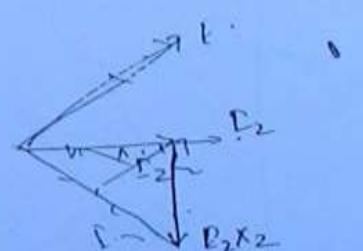

(19)

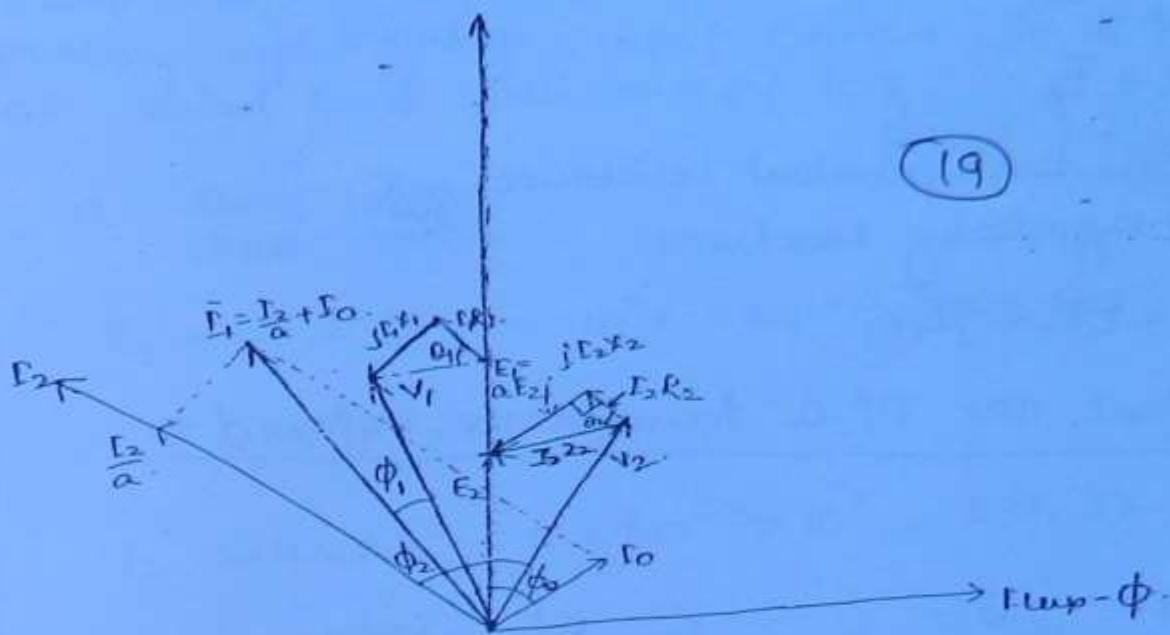

Representation of a device by a standard active and passive circuit elements that can be used to analyse the performance of the device is known as its equivalent C.R.T.

$$\bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$$

$$\bar{E}_1 = \alpha \bar{E}_2$$

$$\bar{I}_1 = \frac{\bar{P}_2}{\alpha} + \bar{I}_0 \quad [i.e. \bar{I}_2' + \bar{I}_0]$$

$$\bar{E}_0 = \bar{I}_0 R_0 + j \bar{I}_0 X_0$$

$$\bar{V}_1 = \bar{E}_1 + \bar{I}_1 R_1 + j \bar{I}_1 X_1$$

Equivalent C.R.T. \rightarrow

Referred to primary

$$\bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$$

$$\Rightarrow \text{multiply by } \alpha = \frac{N_1}{N_2}$$

$$\alpha \bar{E}_2 = \alpha \bar{V}_2 + \alpha \bar{I}_2 R_2 + \alpha j \bar{I}_2 X_2 \alpha$$

$$\Rightarrow \bar{I}_1 - \bar{I}_2' = \bar{V}_2' + \left(\frac{\bar{I}_2}{\alpha} \right) \alpha^2 R_2 + j \left(\frac{\bar{I}_2}{\alpha} \right) \alpha^2 X_2$$

$$\Rightarrow \bar{I}_1 - \bar{I}_2' = \bar{V}_2' + \bar{I}_2' R_2' + j \bar{I}_2' X_2'$$

\bar{V}_2' : Secondary terminal voltage referred to primary

$$\bar{I}_1 = \bar{I}'_2 + \bar{I}_0$$


$$\bar{I}_0 = \bar{I}_c + \bar{I}_{\phi}$$

R_c → core loss equivalent resistance. (20)

X_{ϕ} → magnetising reactance.

$$\bar{V}_1 = \bar{E}_1 + \bar{I}_1 R_1 + j \bar{I}_1 X_1$$

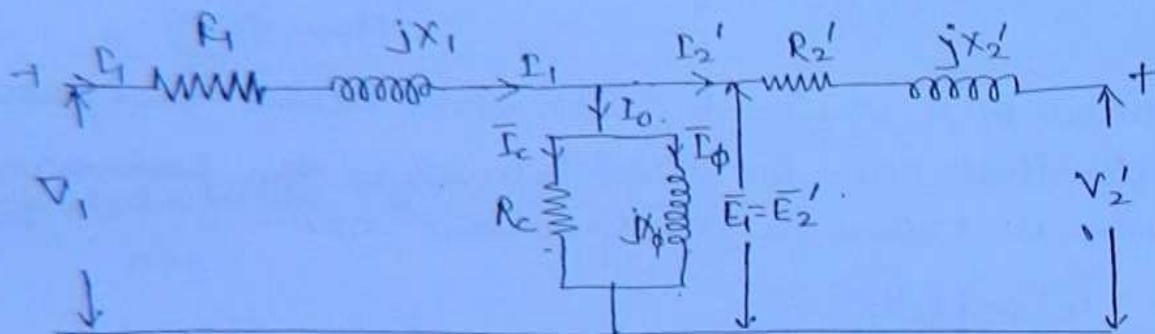exact equivalent circuit of a transformer referred to primary:



$$\begin{aligned} \text{Secondary copper loss} &= I_2'^2 R_2 \\ &= \left(\frac{I_2}{a}\right)^2 \times a^2 R_2 \\ &= I_2'^2 R_2' \end{aligned}$$

Solution

Q. 150 kVA, 2400 V / 240 V transformer

$$R_1 = 0.2$$

$$R_2 = 2 \text{ m}\Omega$$

$$X_1 = 0.1 \text{ m}\Omega$$

$$X_2 = 4.5 \text{ m}\Omega$$

$$R_c = 10 \text{ k}\Omega$$

$$X_{\phi} = 1.55 \text{ k}\Omega$$

The parameters of eq. circ of above transformer are shown above.

Using the cut referred to primary, determine the primary input voltage, input current, pf of X-mor ^{above} at rated load with 0.8 pf lag.

$$\alpha = \frac{2400}{2400} = 10$$

(2)

$$R_2' = \alpha^2 R_2 = 10^2 \times 2 \times 10^{-3} = 0.2 \Omega$$

$$E_1 = V_2' + I_2' Z_2'$$

$$X_2' = 10^2 \times 4.5 \times \alpha^2 = 4.5 \times 10^{-3} \times 10^2 = 0.45 \Omega$$

$$E_1 = 2400V$$

$$R_2' =$$

$$V_2' = E_1 - I_2' Z_2'$$

$$= 2400 - I_2' (0.2 + j0.45)$$

$$= 2400 -$$

$$V_2' =$$

$$E_1 = V_2' + I_2' Z_2'$$

$$= 2400 + I_2' (0.2 + j0.45)$$

$$V_2' = 240V$$

$$= 2400 + 62.5 L - 36.87 (0.2 + j0.45) = 2400$$

$$V_2' = \alpha V_2$$

$$I_2' = \frac{100 \times 10^3}{240}$$

$$E_1 = 2426.92 L 0.354$$

$$= 625$$

$$I_C = \frac{E_1}{R_C} = 0.2427 L 0.354$$


$$I_2' = 62.5 L - 36.87$$

$$I_\phi = \frac{I_1}{jX_\phi} = \frac{2426.92}{j1.5658 \times 10^3}$$

B

$$= 1.5658 \times 10^{-3} L - 36.87$$
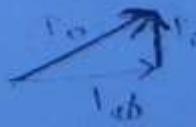
$$I_O = 1.5658 L 20.94 = 0.671 \text{ of } I_2'$$



$$E_1 = E_2' + E_\phi \\ = 63.66 \angle -37.85^\circ$$

$$V_1 = E_1(R_1 + jX_1) + E_1 \\ = 2454.68 \angle 0.69^\circ \quad \text{Ans}$$






$$R_1 = R_2' \\ X_1 = X_2'$$


← equal allocation of R and X in one side

$$\text{Input PT angle} = \angle V_1 - \angle E_1 \\ = 0.69 - (-37.86) \\ = 38.55 \text{ lag}$$

$$\text{Input PT} = \cos 38.55 \text{ lag} \\ = 0.7821 \text{ lag}$$

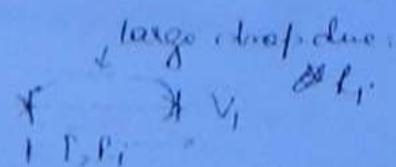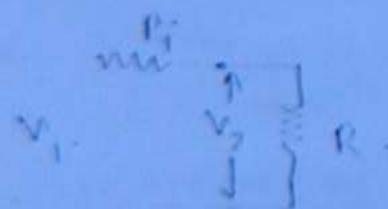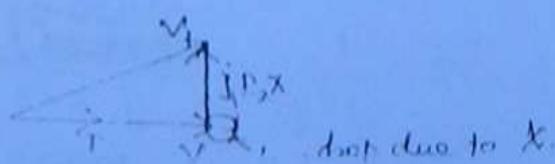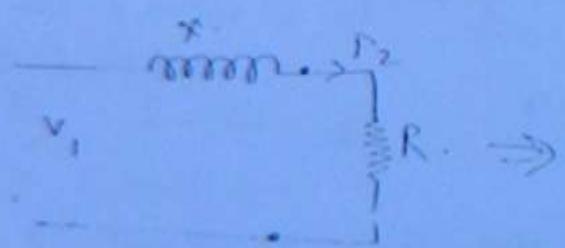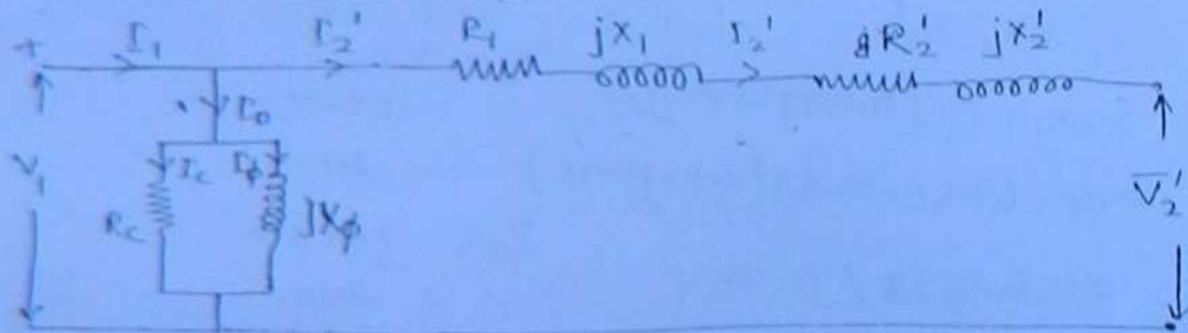First approximate equivalent circuit \Rightarrow



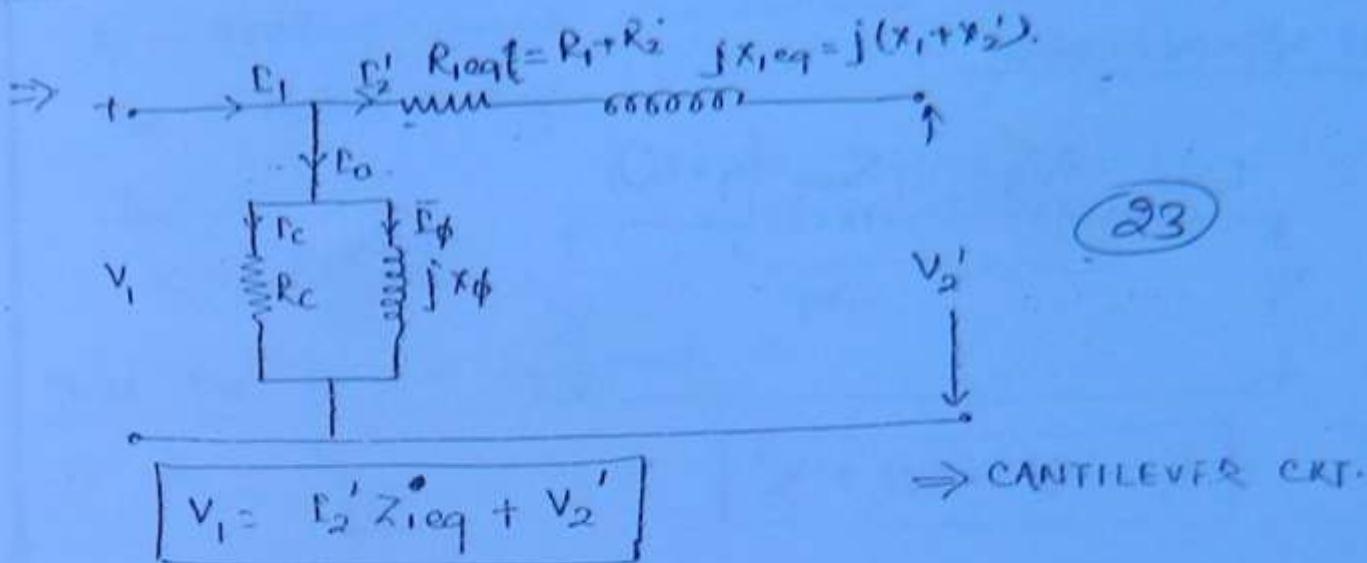

Name plate Voltage - O/P voltage on PL

At 1st approximation, let the equivalent circuit is as shown
Find all the values.

Aus $R_2' = 0.2$.

$$R_{1,eq} = 0.2 + 0.2 \\ = 0.4$$

$$X_{1,eq} = 0.45 + 0.45 \\ = 0.9j$$

$$Z_{1,eq} = (R_{1,eq} + jX_{1,eq}) \\ = (0.4 + 0.9j)$$

$$I_2' = 62.5 \angle -26.87$$

$$V_2' = 2400$$

V_2' → rated Voltage

$$V_1 = V_2' + I_2' Z_{1,eq}$$

$$= 2400 \angle 0.70$$

$$I_c = \frac{V_1 / R_p}{R_C}$$

$$= \frac{2400 \angle 0.70 \times 10^3}{10 \times 10^3}$$

$$= 0.2400 \angle 0.70$$

$$I_p = \frac{V_1}{R_p}$$

$$= 1.5832 \angle 0.93$$

$$I_O = I_c + I_d$$


$$= 1.6021 \angle -80.49$$

$$I_I = 63.6034 \angle -37.8$$

$$\left| \tan \alpha \right| = \frac{0.11}{37.81}$$

$$V_f = \cos 37.81 \times 0.787 \log$$



Final Approximation →

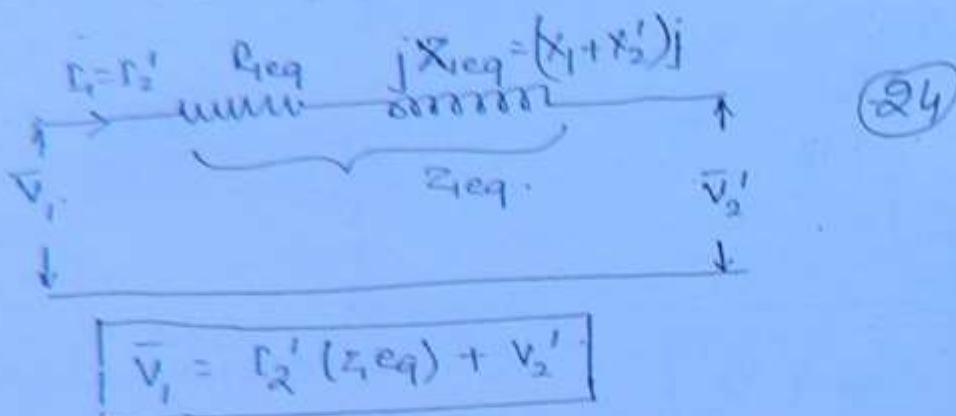

To predict the performance of the transformer without actual loading? → For D.C. and S.C test.

Open Circuit Test →

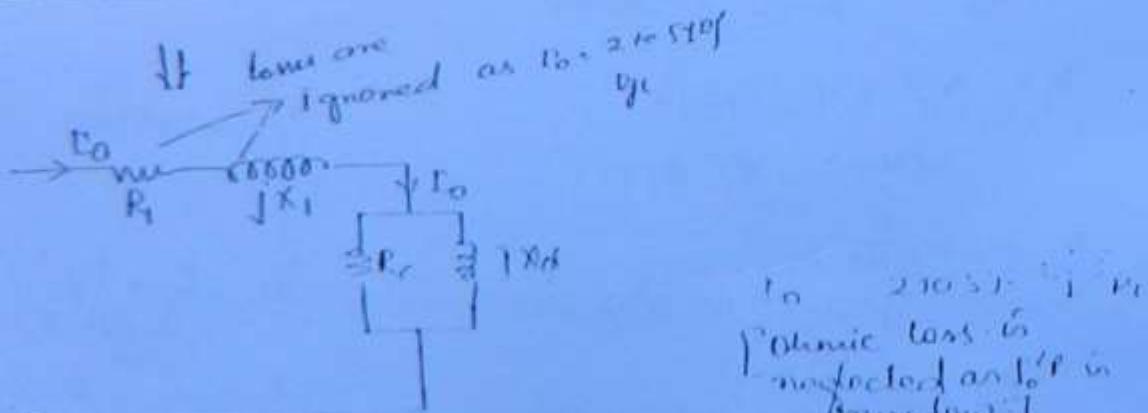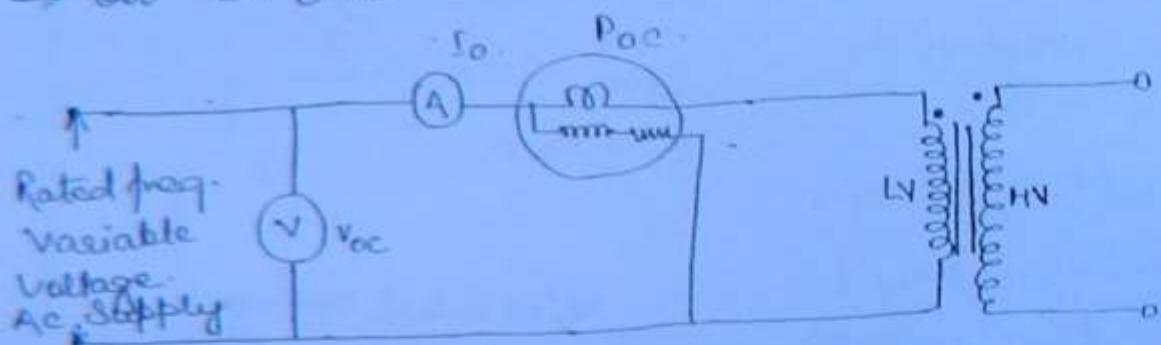- Carried out rated Voltage and freq becoz of rated flux.
- core loss and $\frac{\text{core}}{\text{loss}}$ const and carried out at rated flux.
- On LV side.



P_{oc} = core loss. [Later treated as const].

may be corrected for primary losses $I_o^2 R_p$.

I_o → exciting current

ie no load current

V_{oc} → Rated voltage

$$P_{oc} = I_o^2 R_c$$

$$R_c = \frac{P_{oc}}{I_o^2}$$

Best and Quickest approach →


$$1) R_c = \frac{V_{oc}^2}{P_{oc}}$$

$$2) \phi_o = \cos^{-1} \left[\frac{P_{oc}}{V_{oc} I_o} \right]$$

$$3) \tan \phi_o = \frac{R_c}{X_\phi}$$

$$\Rightarrow X_\phi = \frac{R_c}{\tan \phi_o}$$

(25)

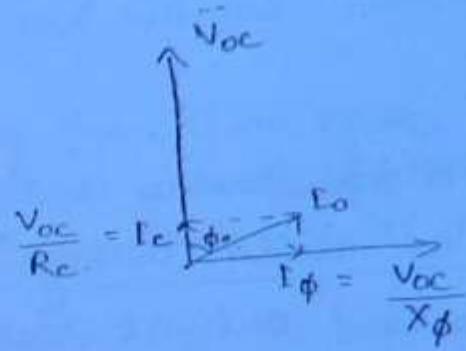

$$\tan \phi_o = \frac{I_o \phi}{I_c}$$

$$= \frac{V_{oc} / X_\phi}{V_{oc} / R_c}$$

$$\boxed{\tan \phi_o = \frac{R_c}{X_\phi}}$$

Alternative method →

$$1) R_c = \frac{V_{oc}^2}{P_{oc}}$$

$$2) I_c = \frac{V_{oc}}{R_c}$$

$$3) I_\phi = \sqrt{I_o^2 - I_c^2}$$

$$4) X_\phi = \frac{V_{oc}}{I_\phi}$$

Alternative

$$1) I_c = \frac{P_{oc}}{V_{oc}}$$

$$\propto$$

$$I_c = \frac{V_{oc}}{R_c}$$

$$\propto$$

$$X_\phi = \frac{V_{oc}}{I_\phi}$$

$$2) I_\phi = \sqrt{I_o^2 - I_c^2}$$

Alternative 3 -

$$1) \phi_0 = \cos^{-1} \frac{P_{oc}}{V_{oc} I_0}$$

$$2) I_c = I_0 \cos \phi_0$$

$$\& I_\phi = I_0 \sin \phi_0.$$

$$3) R_c = \frac{V_{oc}}{I_c}$$


$$X_\phi = \frac{V_{oc}}{I_\phi}$$

(26)

> O.C. test on a transformer is carried out to determine the 'core loss at rated voltage and freq'? Accordingly the test is carried out at rated voltage and freq. with the instruments placed on L.V. side and the H.V. side is left open circled. Since the no load current of a transformer is 2% to 5% of the full load value the primary wdg copper loss may be ignored. Similar the voltage drop across the primary leakage impedance on no load may also be neglected because primary impedance is low and also dominately inductive. This test is carried out on L.V. side because ranging rated volt. Supply at L.V. level is much easier than on H.V. level. Also a instruments required would be cheap and would be safe to work on L.V. side.


Ans 11: ammeter is costly than high pf wattmeter
the wattmeter required should be a low pf as the no load pf is very low of the order of 0.2 pf lag.

Short Cut Test →

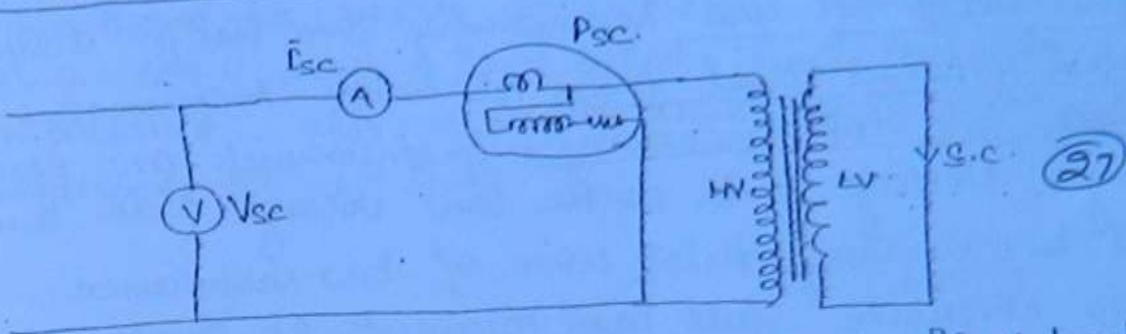

→ to determine core loss at rated current. If full load core loss

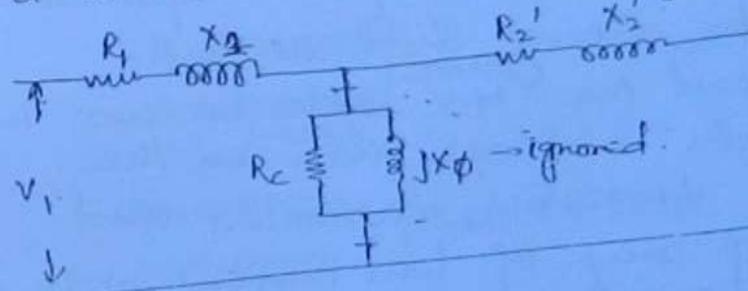$I^2 R$
 → Resistance is not affected by freq. if we ignore skin effect
 So, we can conduct the test instead of rated freq as it
 so, it is not essential to carry the test at rated freq.



$P_{sc} \rightarrow$ full load cur loss

$\Gamma_{\text{sc}} \rightarrow$

$$V_{CC} \rightarrow$$

Quickest and best method

$$Z_{eq} = \frac{V_{SC}}{I_{SC}} \cdot (\cos^{-1} \frac{P_{SC}}{V_{SC} I_{SC}})$$

$$= \rho_{eq} + j \chi_{eqn}$$

Alternative method

i) Req = $\frac{P_{SC}}{P_{SC}}$

$\Rightarrow Z_{\text{eff}} = \frac{V_{\text{c}}}{V_{\text{e}}}$

⇒ $\text{Var} = \int x^2 P(x)$

$$\begin{aligned} & \text{For } R_1 \text{ and } R_2 \\ & \text{parallel combination} \\ & \text{Req. } Z_{eq} = (R_1 + R_2) \\ & \text{For } X_1 \text{ and } X_2 \\ & \text{parallel combination} \\ & \text{Req. } Z_{eq} = (X_1 + X_2) \\ & \text{Total } Z_{eq} = R_{eq} + jX_{eq} \end{aligned}$$

Short Ckt test is carried out on a transformer to determine full load core loss. Accordingly this test is carried out at rated current and freq, although requirement of rated freq. is not necessary. Instruments are placed on the high voltage side with low voltage side being short ckted by a very thick wire of low resistance. In order to circulate full load current at short Ckt, an input voltage of 8% to 10% is usually sufficient and therefore the core loss during this test is ignored. Moreover the no load current at such reduced voltage also becomes negligible and therefore can be ignored. This means that the exciting part of the equivalent ckt may not be consider during short ckt test.

The instruments are placed on H.V. side because the rated current on HV side is lower than on the low voltage side. Hence Ammeters, wattmeters and instrument transformers if any of low current rating may be used.

high B wattmeter

Q. With the instruments connected on LV side, o.c., test readings for 10 KVA, 450 V / 120 V, 50 Hz transformer are 120 V, 4.2 A, 80 W. Find Resistance and reactance of eq. exciting ckt referred to the H.V. side.

$$\text{Ans. } P_{oc} = 80 \text{ W}$$

$$a = \frac{450}{120} = 3.75 \quad (28)$$

$$I_o = 4.2 \text{ A}$$

$$R_c' = \frac{180 \times (3.75)^2}{4.2^2} = 95.7 \Omega$$

$$V_{oc} = 120 \text{ V}$$

$$X_c = R^2 \times 58.9$$

$$R_c = \frac{V_{oc}}{P_{oc}} = 180$$

$$= 406.96$$

$$\phi_0 = \cos^{-1} \frac{P_{oc}}{V_{oc} I_o}$$

$$\cos^{-1} \left(\frac{80}{120 \times 4.2} \right) = 80.86^\circ$$

$$\tan \phi_0 = \frac{R_c}{j X_c} = 28.34 \Omega$$

Q. Instruments connected on HV side, the no load readings for 50 KVA, 2400V / 240V transformer are 48 V, 20.8 A and 617 W. Find leakage impedance, eff. resistance and leakage reactance referred to LV side.

(29)

Aus

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} \angle \cos^{-1} \frac{P_{sc}}{V_{sc} I_{sc}}$$

$$= \frac{48}{20.8} \angle \cos^{-1} \frac{617}{48 \times 20.8} = 1.426 + j1.8143 \Omega$$

$$= 2.3077 \angle 51.83^\circ$$

$\alpha = 10^\circ$

$$= 2.3077 + j0.0249 \Omega$$

$$R = \frac{2.3077 - 1.426}{200 \text{ kV}} \quad Z \text{ on LV side} = \frac{2.3077 + j0.0249}{\alpha^2}$$

$$X = \frac{0.0249}{1.8143} \quad = 0.0231 + j0.0002 \Omega$$

$$R = 0.0231 \quad \left. \begin{array}{l} \text{on HV side} \\ \text{on LV side} \end{array} \right\}$$

$$X = 0.00025$$

$$Z_{eq} [LV] = 0.0231 \angle 51.83^\circ \quad \Omega$$

$$Req [LV] = 0.0143 \Omega$$

$$Req [HV] = 0.0181 \Omega$$

~~Q. Part 16~~ A 2200/220 V, 50 Hz, 1-phi transformer has exciting current of 0.6 A and core loss of 361 W when its HV side is energised at rated voltage. Cal. the two comp. of exciting current.

Aus

$$I_0 = 0.6 \text{ A}$$

$$\psi = \cos^{-1} \frac{I_0}{I_m}$$

$$P_0 = 361 \text{ W}$$


$$V_{no load}$$

$$V_0 = 2200$$

$$\approx \cos^{-1} \frac{361}{2200 \times 0.6} \quad \{ = 74.12^\circ$$

$$I_\phi = 0.6 \cos 74.12^\circ = 0.141 \text{ A}$$

$$I_e = 0.1411 + j0.0002 \text{ A}$$

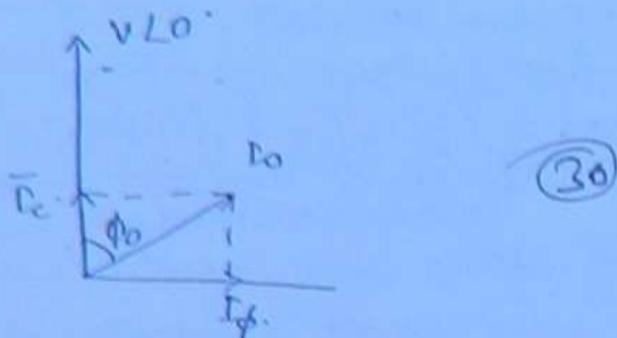

(30)

with voltage as reference phasor. —

$$\begin{aligned}
 \bar{I}_o &= I_o \angle -\phi_0 \\
 &= 0.6 \angle -\cos^{-1} \frac{P_o}{V_o I_o} \\
 &= 0.6 \angle -\cos^{-1} \frac{361}{2200 \times 0.6} \\
 &= 0.1641 - j 0.5771
 \end{aligned}$$

Part B:


If transformer of part A supplies a load current of 60 A at 0.8 pf lag on its LV side then cal. the primary current and its pf. Ignore leakage impedance drop.

Ans. $V = 220 \text{ V}$.

$$I_2 = 60 \text{ A}$$

~~$$\text{For. } P_2 = V I_2 \cos$$~~

~~$$\phi_2 = 6.48^\circ$$~~

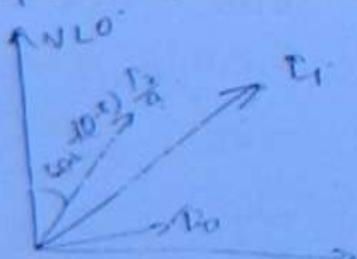

$$I_1 = I_2 + I_o$$

$$= \frac{I_2}{a} + I_o$$

$$= \frac{60}{10} \angle^{10.8^\circ} (0.1641 - j 0.5771)$$

$$\begin{aligned}
 &\approx 6 \angle -\cos^{-1} 0.8 + 0.1641 \\
 &\quad - j 0.5771 \\
 &\approx 6.419 \text{ A} - j 0.5771
 \end{aligned}$$

$$\begin{aligned}
 \text{Primary pf} &= \cos(40.08^\circ) \text{ lag} \\
 &= 0.7671 \text{ lag}
 \end{aligned}$$

4V

Base QTY. →
Srated, Vrated (4V) (3)

$$Z_{base}(4V) = \frac{[V_{rated}[4V]]^2}{S_{rated}}$$

$$Z_{base}(4V) = \alpha^2 \frac{[V_{rated}(1V)]^2}{S_{rated}} \\ = \alpha^2 Z_{base}(1V)$$

$$Z_{pu}(4V) = \frac{Z_{eq}(4V)}{Z_{base}(4V)} \\ = \frac{\alpha^2 Z_{eq}(1V)}{\alpha^2 Z_{base}(1V)}$$

1V

Srated, Vrated [1V]

$$Z_{base}(1V) = \frac{[V_{rated}[1V]]^2}{S_{rated}}$$

$$Z_{eq}(1V) \\ Z_{pu}(1V) = \frac{Z_{eq}(1V)}{Z_{base}(1V)}$$

$$\boxed{Z_{pu}(4V) = Z_{pu}(1V)}$$

~~$R_{pu} = \frac{R_{eq}}{Z_{base}}$~~

$$\frac{\Psi}{F} = Z_F$$

$$= \frac{R_{eq}}{V_{rated}/I_{rated}}$$

= $\frac{I_{rated} R_{eq}}{V_{rated}}$ → Rated ohmic drop in full & load

- Resistive drop on full load in pu

- pu ohmic drop

- $\frac{I_{rated} R_{eq}}{V_{rated}/I_{rated}}$ = Full load cu loss

Vrated/Irated = per unit full load cu loss

If R_{pu} or μ_{pu} more than $\frac{V_{rated}}{I_{rated}}$ cu loss in pu is zero

max efficiency (roughly) will be cu loss due to max

$$X_{pu} = \frac{Z_{eq}}{Z_{base}}$$

$$= \frac{X_{eq}}{(V_{rated}/P_{rated})}$$

$$= \frac{P_{rated} \times X_{eq}}{V_{rated}} \quad \text{Reactive drop on full load in pu.}$$

(32)

i.e. pu Reactive drop on full load

$$= \frac{V_{rated}^2 X_{eq}}{V_{rated} P_{rated}}$$

$$= \frac{full\ load\ Reactive\ loss\ in\ pu}{full\ load\ Reactive\ power}$$

$$Z_{pu} = \frac{Z_{eq}}{Z_{base}}$$

$$= \frac{Z_{eq}}{V_{rated}/P_{rated}}$$

$$= \frac{P_{rated} \cdot Z_{eq}}{V_{rated}} = \text{Impedance drop on full load in pu or pu impedance drop on full load}$$

$$= \frac{V_{rated}^2 Z_{eq}}{V_{rated} P_{rated}} = \text{Apparent power loss in pu on full load or pu full load Apparent power loss.}$$

$$R \approx 0.01 \text{ pu}$$

$$X \approx 0.1 \text{ pu}$$

$$R_c = 100 \text{ pu}$$

$$X_\phi = 25 \text{ pu}$$

$$N.R. = V_0^2 R_c$$

$$\frac{P_i}{P_i} = \frac{V_{rated}^2}{R_c}$$

$$\therefore 0.01 = \frac{V_{rated}^2}{R_c}$$

$$\therefore [R_c = 100 \text{ pu}]$$

$$X_\phi = 25 \text{ pu}$$

P

$$E_\phi = \frac{V_{\text{rated}}}{X_\phi}$$

$$0.04 = \frac{1.0}{X_\phi} = ?$$


$$X_\phi = 25 \text{ pu.}$$

Important of $\Sigma_0 = E_\phi$

(B3)

Voltage Regulation →

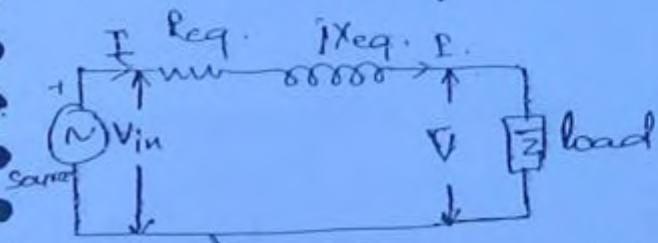Voltage Regulation of the transformer is defined as the change in secondary output voltage expressed as fraction of full load rated voltage when full load at a given pf is removed keeping primary input voltage const.



$$\text{Voltage Reg}^2 = \frac{|V_{\text{int}} - V|}{|V|}$$

where $|V| = \text{rated}$

$$= \frac{|V_{\text{int}}| - 1}{|V|}$$

$$= |V_{\text{in}}(\text{pu})| - 1$$

$$\bar{V}_{\text{in}} = \bar{V} + \bar{E}_{\text{eq}}$$

$$\% \text{Reg} = \frac{|V_{\text{in}}| - 1}{|V|} \text{ pu.}$$

- Q. A transformer has pu impedance of 0.10 and pu resistance 0.01. Cal. phase diff b/w O/P and P/F voltage on PL and also cal. V.R. at $\text{P.F.} > 0.8 \text{ Pf lag}$
- unity pf
 - 0.8 pf load

$$\text{Ans phase diff } \cos^{-1}\left(\frac{0.01}{0.1}\right) = 84.26^\circ$$

$$V_{Reg} = \frac{120 - 12.84 \angle 26^\circ}{0.8 \angle 90^\circ}$$

(34)

0.8 pf lag

$$V_{in} = 120 + 12 \angle -\cos^{-1} 0.8 \times 0.01 \angle \cos^{-1} \frac{0.01}{0.10}$$

$$= 1.0702 \angle 3.94^\circ$$

$$\text{Reg}^2 = V_{in}(\text{pu}) - 1$$

$$= 0.0702$$

$$= 7.02\%$$

1.0 pf

$$V_{in} = 1.0148 \angle 5.626^\circ$$

$$\text{Reg}^2 = 1.48\%$$

0.8 pf load

$$V_{in} = 1.94 \angle 21.13^\circ$$

$$V_{Reg}^2 = 1.94 \angle 05^\circ$$


$$V_{in} = 0.9522 \angle 5.16^\circ \text{ pu}$$

$$\text{Reg}^2 = 0.9522 - 1$$

$$= -0.0478 \text{ pu}$$

$$= -4.78\%$$

for lagging pf

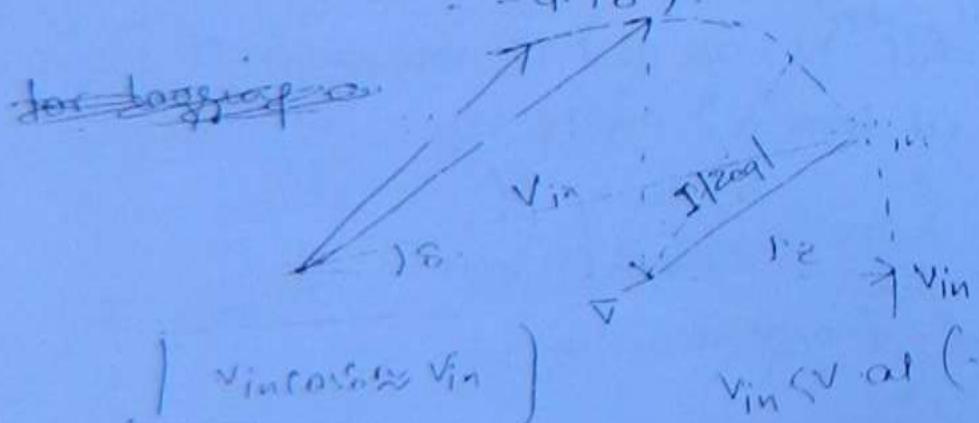


$|P_{Regulated}| = \text{const}$
but θ varies
differs

$V_{in} \propto \text{at } (-\text{ve Regulation})$

Approximate Regulation formula :→

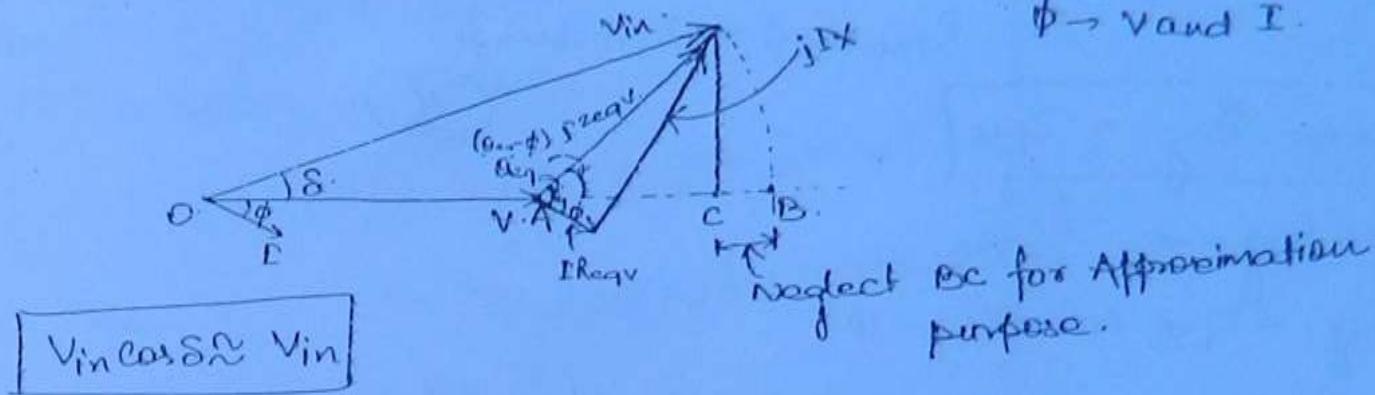(35)

$\theta_{eq} \rightarrow$ b/w θ_{reg} and
 $\phi \rightarrow V_a$ and I.



Approximation involves the assumption that

$$\phi \approx 0^\circ$$

$$\begin{aligned} R_{eq} &= \frac{|V_{in}| - |V|}{|V|} \\ &= \frac{OB - OA}{OA} = \frac{OB - OA}{|V|} \end{aligned}$$

$$\begin{aligned} \text{Approx } R_{eq} &\approx \frac{OC - OA}{|V|} \quad \text{for approximate regulation} \\ &\approx \frac{AC}{|V|} \end{aligned}$$

$$\begin{aligned} &\approx \frac{r_{eq} \cos(\theta_{eq} - \phi)}{|V|} \\ &\approx Z_{pu} \cos(\theta_{eq} - \phi) \quad \text{where } \phi \text{ is fine for lagging P.} \end{aligned}$$

Now for lagging:

$$\text{Approx } R_{eq} \approx \frac{0.1}{0.7} \cos(0.4261 - 108^\circ 0.8)$$

$\approx 6.7\%$.

Q1, Not enough + because we assume $\phi \approx 0^\circ$.

for leading P_{eq}! -5.161.

$$\begin{aligned}
 \text{Appx Reg} &= Z_{pu} \cos(\theta_{eq} - \phi) \\
 &= Z_{pu} [\cos \theta_{eq} \cos \phi + \sin \theta_{eq} \sin \phi] \\
 &= (Z_{pu} \cos \theta_{eq}) \cos \phi + (Z_{pu} \sin \theta_{eq}) \sin \phi \\
 &= R_{pu} \cos \phi + X_{pu} \sin \phi.
 \end{aligned}$$

$$\boxed{\text{max Reg} = Z_{pu}}$$

(36)

max Reg \rightarrow


$$\text{Reg.} = Z_{pu} \cos(\theta_{eq} - \phi)$$

Reg is max when $\theta_{eq} - \phi = 0$.
i.e. $\phi = \theta_{eq}$ lagging.

$$\text{max Reg} = Z_{pu}$$

$$\begin{aligned}
 \text{PF at max Reg} &= \cos \phi \Rightarrow \text{lagging} \\
 &= \cos \theta_{eq} \text{v. lagging} \\
 &= \frac{R_{pu}}{Z_{pu}} \text{ lagging}
 \end{aligned}$$

for max regulation \rightarrow

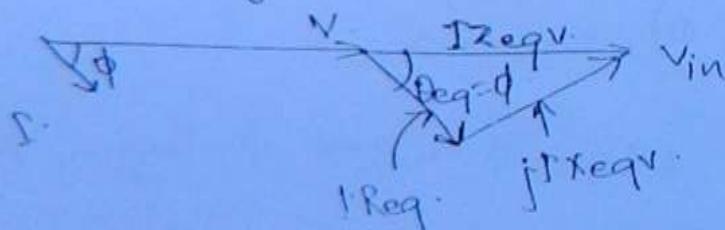

No approximation involved.

because $\delta = 0$

$$\bar{V} = V \angle 0^\circ$$

$$\bar{I} = I \angle -\phi$$

$$\bar{Z} = Z \angle 0^\circ$$

Analytical approach for approximate Results

(37)

$$\bar{V}_{in} = \bar{V} + \bar{I} Z_{eq}$$

$$\begin{aligned}\bar{V}_{in} &= V \angle 0^\circ + I \angle -\phi \times Z \angle 0^\circ \\ &= V \angle 0^\circ + I Z \angle 0^\circ \angle -\phi \\ &= V + I Z (\cos(0-\phi) + j \sin(0-\phi)) \\ \bar{V}_{in} - V &= I Z [\cos(0-\phi) + j \sin(0-\phi)] \\ \frac{\bar{V}_{in} - V}{V} &= \frac{I Z}{V} [\cos(0-\phi) + j \sin(0-\phi)]\end{aligned}$$

$$\Rightarrow V_{in} \angle \delta = V \angle 0^\circ + I \angle -\phi \times Z_{eq} \angle 0^\circ$$

$$\Rightarrow V_{in} (\cos \delta + j \sin \delta) = V + I Z_{eq} [\cos(0^\circ - \phi) + j \sin(0^\circ - \phi)]$$

equating real parts \rightarrow

$$V_{in} \cos \delta = V + I Z_{eq} \cos(0^\circ - \phi)$$

for approximate regulation

$$V_{in} \cos \delta \approx V_{in} \text{ as } \delta \approx 0^\circ$$

$$V_{in} - V = I Z_{eq} \cos(0^\circ - \phi)$$

$$\frac{V_{in} - V}{V} = \frac{I Z_{eq}}{V} \cos(0^\circ - \phi)$$

$$= Z_{pu} \cos(0^\circ - \phi)$$

for O-regulation

$$\cos(0^\circ - \phi) = 0$$

$$\theta_{inj}, \phi = 90^\circ$$

$$\phi = \frac{\theta_{inj} - \theta_{inj, \text{load}}}{\theta_{inj, \text{load}}} \times 90^\circ$$



$$\text{Req } \delta = 2pu \cos(\theta_{eq} - \phi) = 0$$

$$\Rightarrow \theta_{eq} - \phi = 90^\circ$$

$\phi = \theta_{eq} - 90^\circ$ lagging

$$= -(90^\circ - \theta_{eq}) \text{ lagging} \quad (38)$$

$\phi_+ = \text{leading } (90^\circ - \theta_{eq})$

Corresponding pf = $\cos \phi$ leading

$$= \cos(90^\circ - \theta_{eq}) \text{ leading}$$

$$= \sin \theta_{eq} \text{ leading}$$

i.e. $\text{pf} = \frac{x_{pu}}{2pu} \text{ leading}$

~~min Req \rightarrow~~


$\phi = 90^\circ$ leading

$$\text{Approx. Req} = 2pu \cos(\theta_{eq} - (-90))$$

$$= 2pu \cos(90 + \theta_{eq})$$


$$= -x_{pu}$$

at zero pf leading

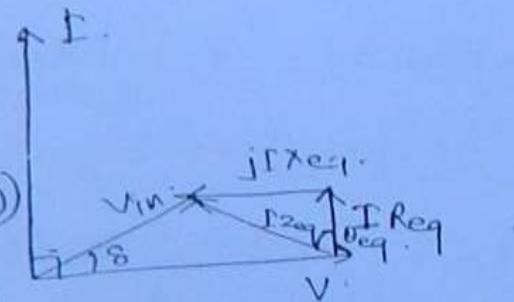

~~why~~

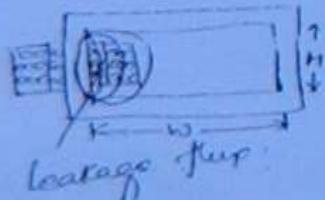
- LV wdg is placed near core because of insulation of LV is easier than HV. HV wdg is placed above LV



core type transformer

minimizes漏磁 to reduce leakage flux

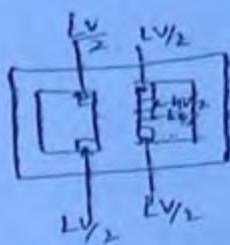To reduce leakage flux, the HV sides are placed close together



→ sandwiched wedg 39

P.T → operates on full load & used in transmission.

for distribution X-mer $\rightarrow 2pu = 1.5\%$
in 24 hr operation $\therefore \text{max Reg} = 1.5^\circ$

\therefore V.R. is not taken into account

$2pu \uparrow = 15\%$.

fault level decrease

$2pu$ of high rating transformer is high because wedg insulation is high. So, physically they are not close as low rating X-mer and leakage reactance increases so, $2pu \uparrow$

Improvement of voltage Regulation -

Regulation of transformers can be improved by reducing its equivalent impedance. Since the resistance of the wedg. decided based on off consideration, it leaves only the leakage reactance which must be reduced to improve regulation. leakage reactance absolutely can be reduced by keeping the HV wedg and low voltage wedg physical close together. This is accomplished by using concentric cylindrical wedgs in core type transformer. and by using sandwiched wedgs in shell type transformer. further, in a core type transformer, the window ht to width ratio can be increased to increase air gap path taken by leakage flux. This would result in reducing leakage reactance and consequent improvement in VR.

A HV transformer in general has a higher volt-regulation as compared to L.V. transformer because the thicker iron in H.V. X-mer makes the two wedg further apart thus in higher leakage flux.

Distribution X-mer fault line voltage & in commercial line

and therefore their V.R. is designed to be very low. Thus the leakage impedance may be as low as 0.015 pu. On the other hand, the variation of voltage from full to no load is not of great consideration in case of power transformer as they usually operate on full load or are switched off. Consequently pu impedance of power transformer is much higher as high as 0.15 pu. Such high value of pu impedance has an advantage that the fault level of the system becomes low.

(40)

A 10 KVA, 2000/200 V, 50 Hz - 1 ϕ transformer when working on rated voltage at no load takes an input of 125 watts at 0.15 pf. Its % leakage impedance based on its KVA rating is $0.5 + j1$. If it ~~mer~~ delivers 10 KW at 200 V at pf 0.8 lagging on its LV side. Determine the E/P and pf. ^{overloaded}.

Given - 10 KVA 50 Hz. 1- ϕ Transformer.
2000/200V.

$$P_{i2} = 125 \text{ W} = 0.2000 \times I_i^2 \times 0.15 \text{ pf}$$

$$\frac{125}{2000 \times 0.15} = I_i^2 = 0.416 \text{ A}$$

$$Z_{pe} = (0.5 + j1) \times 0.01$$

$$= 0.005 + 0.01j$$

$$= 0.012 + j0.013$$

$$V_1 = V_2 + I_i' Z_2$$

$$V_1 = 2000 + j(-0.416(-81.37 + j0.012 + j0.013))$$

On 2nd side 10' P-KVA.

$$P = 10 \text{ KVA}$$

$$V = 200 \text{ V}$$

$$\cos\phi = 0.8 \text{ lag.}$$

(41)


$$P = VI \cos\phi$$

$$I_2 = \frac{10 \times 1000}{200 \times 0.8}$$

$$I_2 = 62.5 \text{ A}$$

$$I_2' = \frac{62.5}{10} = 6.25, \bar{I}_2' = 6.25 \angle -\cos^{-1} 0.8$$
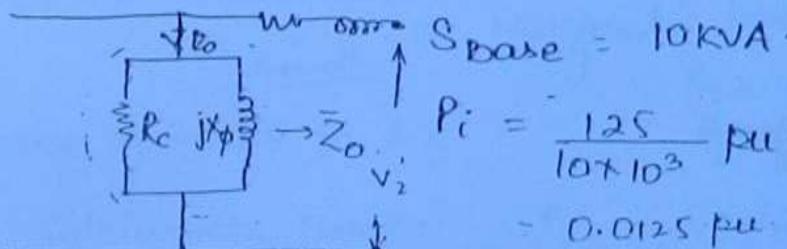
$$\rightarrow I_0 = 0.416 \quad \varphi$$



$$P_i = \frac{125}{10 \times 10^3} \text{ pu.}$$

$$P_i = V_o I_o \cos\phi$$

$$= 0.0125 \text{ pu.}$$

$$= V_o \left(\frac{Z_o}{2e} \right) \cos\phi_e$$

$$P_i = \frac{V_o^2}{Z_o} \cos\phi_b.$$

$$\Rightarrow 0.0125 = \frac{(1.0)^2}{Z_o} \times 0.15$$

$$Z_o = 12 \text{ pu.}$$

$$\bar{V}_1 = 120 + 1.25 \angle -\cos^{-1} 0.$$

$$\bar{Z}_o = 12 \angle \cos^{-1}(0.15)$$

$$\times (6.5 + j1) \times$$

$$= 12 \angle 81.37^\circ \text{ pu.}$$

$$\Rightarrow 1.01251 \angle -0.835$$

On load,

$$\text{Output KVA} = \frac{10}{0.8} \text{ KVA}$$

$$= 12.5 \text{ KVA}$$

$$= 1.56 \text{ pu.}$$

$$I_2' \text{ pu} = 1.25 \text{ pu.}$$

$$\Gamma_0 = \frac{V_1}{Z_0} -$$

$$= 0.08438 L - 81.02 \text{ pu.}$$

$$C_1 = \Gamma_2' + I_0^q$$

$$= 1.25 L - \cos^{-1} 0.8 + 0.08438 L - 81.02$$

$$= 1.31186 L - 39.44$$
(42)

$$S_{in} = V_1 C_1^*$$

$$= 1.02065 + j 0.85007$$

$$= 1.32828 L 39.79 \text{ pu.}$$

$$\Sigma IP \text{ pf} = \cos 39.79$$

$$= 0.7684 \text{ lagging}$$

$$P_{in} = 1.02065 \times 10 \text{ kW}$$

$$= 10.2065 \text{ kW}$$

Efficiency :-

$\omega \rightarrow$ Active power

$$\eta = \frac{\text{Output watt}}{\text{Input watt}}$$

$$= \frac{\text{Output}}{\text{Output + losses}}$$

$$= \frac{\text{Input - losses}}{\text{Input}}$$

$$\Rightarrow 1 - \frac{\text{losses}}{\text{Input}}$$

A 1-mw has 25% losses & losses are 1/4th of output.

$$\eta = \frac{\text{Output}}{\text{Output} + 0.25 \text{ Output}} \\ = \frac{1}{1+25} = 0.8$$

(43)

a.c test \rightarrow $I=0$
 $\eta \rightarrow 0$.

c.c test \rightarrow $V=0$
 $\eta \rightarrow 0$.

If losses are 100%.

$$\eta = \frac{\text{Output}}{\text{Output} + \text{Output} \rightarrow 100\%} \\ = \frac{1}{1+1} = 0.5$$

Only in Incandescent lamp
losses or rating in terms of HP.

Losses \rightarrow iron loss or core loss
 \downarrow const or magnetic loss.

Hysteresis loss
 $P_h \propto f B_m^2$
eddy current loss.

Where $n \rightarrow 1.5$ to 2.5

(3 to 4%)

0.35 thickness of lamination
is used for reduced
eddy current loss.

Steinmetz const.

Eddy current loss $= P_e \propto f^2 B_m^{n/2}$ Lamination should be
insulated.

Silicon used - to $f \uparrow$, $\sigma R T$
to reduce eddy current &
and also B-H curve becomes narrow by default

$$V = \sqrt{2} \pi f \phi_m N$$

$$V \propto \phi_m f$$

$$V \propto f B_m$$

$$P_e \propto f^2 B_m^2$$

$$\propto (f \cdot B_m)^2$$

$$\text{for } 220V/110V, 50Hz$$

$$f/p \rightarrow 220V, 4000Hz$$

$$P_e \propto \text{const}^2$$

$| P_e \propto V^2 | \rightarrow \text{eddy current loss}$

$$P_h \propto f B_m^n$$

$$\propto f (N)^n \propto \frac{V^n}{f^{n+1}} \propto \frac{1}{f^{n+1}}$$

$$\left| \begin{array}{l} \downarrow P_h \propto \frac{V^n}{f^{n+1}} \\ \uparrow f^{n+1} \end{array} \right|$$

copper loss $\rightarrow I^2 R$ loss.
or ohmic loss or resistive loss

$$\Rightarrow P_{Cu} = I^2 R_{Req}$$

$$\propto I^2$$

$$\propto V_{rated}^2 I^2$$

~~$P_{Cu} \propto S^2$~~ \rightarrow variable.

$$\begin{aligned}\eta &= \frac{VI \cos \phi}{VI \cos \phi + I^2 R_{Req} + \forall P_i} \\ &= \frac{VI \cos \phi}{VI \cos \phi + I^2 R_{Req} + \frac{P_i}{I}}\end{aligned}$$

where $P_i \rightarrow$ iron loss

for max η , denominator should be min.

$$\frac{d}{dI} (\text{denom}) = 0$$

$$\Rightarrow R_{Req} - \frac{P_i}{I^2} = 0$$

$$\Rightarrow P_i = I^2 R_{Req} = P_{Cu} \text{ at } \eta_{max}$$

$$\& \quad \eta_{max} = \sqrt{\frac{P_i}{R_{Req}}}$$

$$V_{rated} I_{\eta_{max}} = V_{rated} \sqrt{\frac{P_i}{R_{Req}}}$$

$S_{\eta_{max}}$ = output at which η is max.

$$\left| S_{\eta_{max}} = S_j \sqrt{\frac{P_i}{(P_{Cu})_j}} \right| \quad \left| \frac{P_i}{I_j^2 R_{Req}} \right| \quad I_j \rightarrow \text{any load current may be FL current}$$

$$\eta_{map} = \frac{V I_{n_{map}} \cos \phi}{V I_{n_{map}} \cos \phi + 2 P_i}$$

(45)

$$\boxed{\eta_{map} = \frac{S_{n_{map}} \cos \phi}{S_{n_{map}} \cos \phi + 2 P_i}}$$

when load P_f is constant.

$$\text{eff. } S_{n_{map}} = S_{FL} \times \sqrt{\frac{P_i}{P_{cu(f)}}}$$

After

If the load is constant and P_f is variable then map eff. is obtained at unity P_f .

Alternative approach to η_{map} →

$$P_{cu} \propto S^2$$

$$\frac{P_{cu}(\eta_{map})}{P_{cu}(j)} = \left[\frac{S_{n_{map}}}{S_j} \right]^2$$

$$\int \frac{P_{cu}(\eta_{map})}{P_{cu}(j)} = \frac{S_{n_{map}}}{S_j}$$

$$\Rightarrow \int \frac{P_i}{P_{cu(j)}} = \frac{S_{n_{map}}}{S_j}$$

$$\Rightarrow S_{n_{map}} = S_j \cdot \int \frac{P_i}{P_{cu(j)}}$$

losses and eff. → (46) $\frac{V_{eff}}{P_{loss}}$ → Xed unext magnetiz.
Transformer in general has a very high eff. because it does not have rotating parts. The core and the wings are all stationary. and therefore ~~not~~ only losses encountered in a transformer are ^{permeation} core loss and copper loss. Core loss is also known as magnetic loss or iron loss and depends upon the core material for the same operating conditions.

Magnetic losses are further subdivided into Hysteresis loss and eddy current loss. Hysteresis loss is due to magnetic reversal in the core material and is therefore reduced by proper selection of the core material. The usual core material for X-mos is core Rolled Grain Oriented (CGO) silicon steel with high permeability and no loss. Eddy current loss is minimised by laminating the core and adding silicon to the core material to increase its resistivity. The usual lamination thickness for X-mos is 0.35 mm and laminations are insulated from each other by an oxide layer on their surfaces or by a thin core of insulating enamel or varnish on both sides. The silicon content is not more than 3% or 4%. A higher value of silicon makes the core material brittle which may shatter like glass, in a const. volt X-mos, a core loss is treated as const despite minor variations in volt. and freq. during operation. Copper loss in PPR loss is of two types placed in the wings of X-mos. It is also known as ohmic loss or Resistive loss. Since the loss is proportional to P²R, it can be easily calculated. It is found that for a const. volt X-mos, it is proportional to the square of output KVA. Hyp. eff. of X-mos is obtained at a load at which the copper loss becomes equal to the iron loss.

η is unknown phenomena

$$\text{copper loss at } 1\text{-A} = \frac{1000}{\text{at } 70\%} = \frac{307^2 \times 100}{450 \mu\text{m}}$$

For the same rating of π -mer,

(iron to copper ratio = big
for distribution π -mer)

large size of π -mer \rightarrow distribution

small .. " \rightarrow P.T.

(47)

efficiency consideration in PT and distribution π -mer:-

A PT operated on full load or not at all. These π -mers are found in generating station or in large substation.

Distribution π -mer feed the ordinary low voltage consumers and therefore their loading depends upon the consumer demands at that time of the day. The av. loading or distribution π -mer is 70% to 75% of its

F.L. Capacity


The max. eff. of any π -mer is designed for its max operating load. Consequently, the max. eff. of PT is designed for full load operation and therefore the core loss of a PT is high as it is equal to full load cu loss so as to give max. eff. on full load.

On the other hand, since the av. loading on distribution π -mer is only 70% to 75% of its rated capacity, its max. eff. is designed at this reduced av. load. Consequently, the core loss in a distribution π -mer has to be kept low as it must equal cu loss at 70-75% of load. This is achieved by reducing flux density in the core which in turn requires the core cross-sectional area to be higher than that of a comparable power transformer. Thus the iron to copper ratio in a distribution π -mer is higher than that of P.T. of same capacity and voltage rating.

$$i_s = \frac{\Phi}{N} \times \frac{N_i}{1/100} \times \left(\frac{P_i}{V_{no}} \right) B \propto \Phi$$

Q. For 200 kVA, 4000/1000 V single phase transformer draw the eq. circuit referred to LV side and insert all the values. It is given that trans. eff. at unity pf is 97%. both at full load and at 60% of full load. The no load pf is 0.25 and full load regulation at lagging pf of 0.8. is 5%.

Ans.

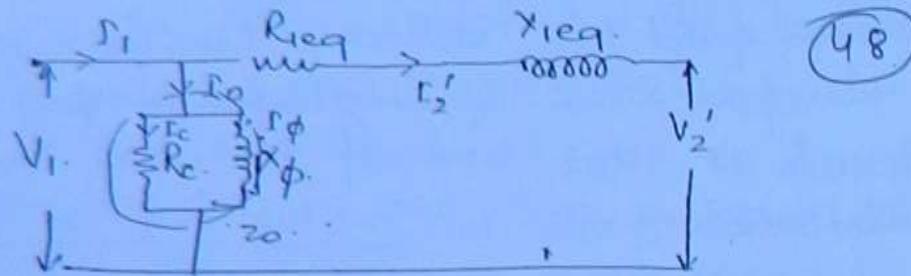

$$\eta = 0.97 \text{ at unity pf}$$

[on full load and on 60% of full load]

$$\text{No pf at no load} = 0.25$$

$$V\cdot \text{Reg}] \text{lagging pf } 0.8 = 0.05$$

$$0.05 = R_c \cos \phi + X_\phi \sin \phi$$

$$\therefore V\cdot R = Z_{pu} [\cos \theta_{eq} - \phi] \quad \theta_{eq} = \cos^{-1}$$

$$0.05 =$$

$$0.97 = \frac{1.71}{1.71 + P_i + P_{cu} \tan^2 \theta}$$

$$0.671 \\ 0.671 P_i \rightarrow P_{cu} [0.67]^2 \text{ reg.}$$

$$(P_i + P_{cu})^{0.367} = \frac{1}{0.97} - 1 = 0.03 DB3$$

$$\frac{P_i + P_{cu}}{P_i + P_{cu}} = \frac{1}{0.97} - 1 = 0.03 \approx \frac{P_i - 0.03}{P_{cu} - 0}$$

$$P_i + 0.36 P_{cu} \text{PF}_{LT} = 0.01856 \text{ pu}$$

$$\Rightarrow P_i = 0.0116 \text{ pu}$$

$I_{cu}(N) = 0.01933 \text{ pu}$ [this is P_{pu}]

$$0.05 = P_{pu} \cos\phi + X_{pu} \sin\phi$$

(49)

$$\therefore 0.05 = 0.01933 \times 0.8 + X_{pu} \sqrt{1-0.8^2}$$

$$\Rightarrow X_{pu} = 0.05756.$$

$$P_i = \frac{V_{oc}^2}{R_c} \cos\phi$$

$$R_c = \frac{V_{oc}^2}{P_i} \cancel{\cos\phi}$$

$$= \frac{1^2}{0.0116} \cancel{\cos\phi}$$

$$= 86.2069$$

$$X_\phi = \frac{R_c}{\tan\phi} = \frac{86.2069}{\tan \cos^{-1} 0.25} \\ = 22.2625$$

$$Z_{base LV} = \frac{[V_{base LV}]^2}{S_{rated}} = \frac{(1000)^2}{200} = 5$$

$$R_c = 431.0245$$

$$X_\phi = 22.2625 \times 5 = 111.3125$$

$$R_{req} = 0.0361 \Omega \approx 0.2878$$

$$X_{req} = 0.2878$$

- Q) Max η of 500 KVA, 3300 / 1500 V, 50 Hz \rightarrow 1-Q trans.
 is 97% and occurs at 75% of full load unity Pf
 Q) transformer impedance is 10% cat. Regulation
 at full load 0.8 Pf lagging.

Ans:

$$\eta = \frac{1 - I}{1 + 2P_i + P_i^2}$$

(50)

$$\eta = \frac{1}{L + 2P_i}$$

$$2P_i = \frac{1}{\eta} - L$$

$$= \frac{1}{0.97} - L = 0.03098$$

$$P_i = 0.01546 = P_{cu}$$

$$0.97 = \frac{0.75 \times 1}{0.75 + 2P_i}$$

$$P_i = 0.0116 \text{ pu.} = P_{cu}(75\%)$$

$$P_{cufl} = \frac{6.0116}{(0.75)^2} = 0.02062 \text{ pu}$$

$$= R_{pu}$$

$$Z_{pu} = 0.1 \angle \cos^{-1} \frac{0.0206}{0.10}$$

$$= 0.1 \angle 78.11^\circ$$

$$\text{Reg.} = Z_{pu} \cos(\theta_{eq} - \phi)$$

$$= 0.1 \cos(78.11^\circ - 36.84^\circ)$$

$$= 0.075195$$

$$= 7.5195$$

All day η. or energy efficiency:

$$\eta_{\text{all day}} = \frac{\text{kwh O/P in 24 hrs.}}{\text{kwh R/P in 24 hrs.}} \quad (51)$$
$$= \frac{\text{kwh O/P in 24 hrs.}}{\text{kwh O/P in 24 hrs} + \text{kwh Pout loss} + \text{kwh Pi loss}}$$

Q:- A 300 KVA transformer has max eff. of 98.6% at 300 KVA at unity pf. During the day it is loaded as follows.

6 hr : 300 KVA, 0.8 pf lag. \rightarrow ~~299.9~~ 290.

4 hr : 240 KW, 0.6 pf lead.

5 hr : No load.

9 hr : 225 KVA, unity pf

Cal. all day eff. of transformer.

A.m. $\eta_{\text{max}} = 0.986 = \frac{0.7 \times 1}{0.7 \times 1 + \text{Pout} + \text{Pi}}$

$\left\{ \begin{array}{l} \text{Pout} \\ \text{Pi} \end{array} \right\} \text{in J}$

$$2 \text{Pi} = \frac{0.7}{0.986} - 0.7$$

$$\text{Pi} = 0.0049696 \text{ Jm}^4$$

$$\text{Pi} = 2.4848 \text{ J} = 2.4848 \text{ kJ}$$

6 hr

$$\text{kwh O/P} = 300 \times 0.8 \times 6 = 1440 \text{ kwh.}$$

$$\text{kwh Pout loss} = 2.4848 \times \left(\frac{300}{300} \right)^2 \times 6 = 10.93 \text{ kwh.}$$

4 hr

$$\text{kWh O/P} = 240 \times 4 = 960 \text{ kWh}$$

$$\text{kWh Pcu loss} = 2.4848 \times \frac{(240/0.6)^2}{(350)^2} \times 4 \\ = 12.981 \text{ kWh}$$

(52)

8 hr \rightarrow

No load.

$$\text{kWh O/P} = 0$$

$$\text{kWh Pcu loss} = 0$$

] Only iron loss.

9 hr \rightarrow

$$\text{kWh O/P} = 225 \times 1 \times 9 \\ = 2025$$

$$\text{kWh O/P Pcu loss} = 2.4848 \times \frac{(225)}{(350)}^2 \times 9 \\ = 9.242 \text{ kWh}$$


$$\text{kWh O/P (total)} = 4425 \text{ kWh}$$

$$\text{kWh Pcu loss} = 33.176 \text{ kWh}$$

$$\text{kWh Ploss} = 2.4848 \times 24 \\ = 59.635$$


$$\eta = \frac{4425}{4425 + 33.176 + 59.635} \\ = 97.95\%$$

1.5 kVA, 120V / 100V - 2 wdg. T-mes

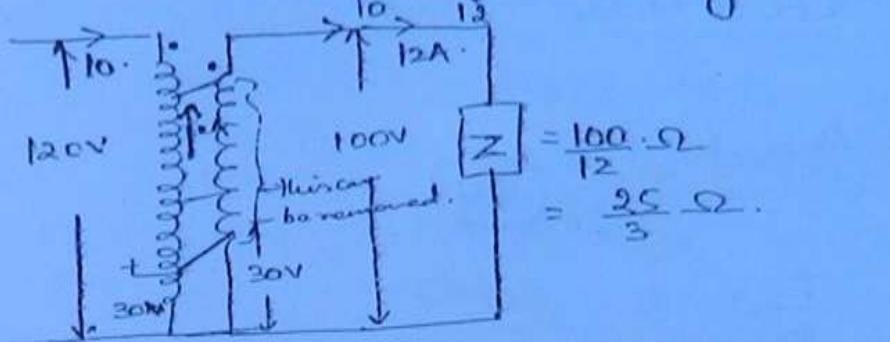

(53)

Auto-transformer :-

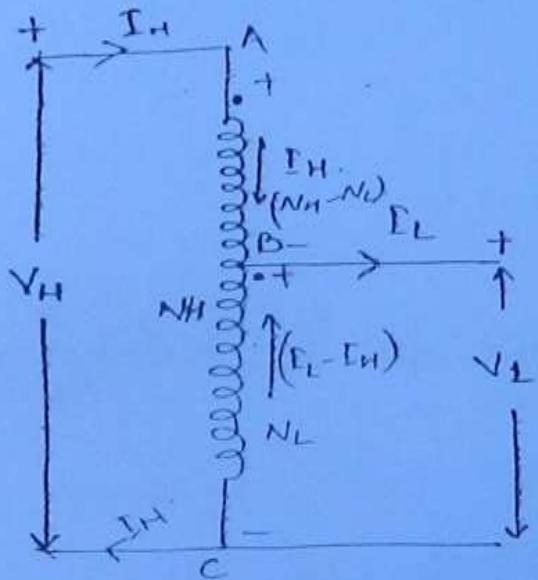

$$AC : N_H$$

$$BC : N_L$$

$$AB = N_H - N_L \rightarrow \text{Series wdg.}$$

Since flux is common

$$\frac{V_H}{N_H} = \frac{V_L}{N_L} = \frac{V_H - V_L}{N_H - N_L}$$

$$\frac{V_H}{V_L} = \frac{N_H}{N_L} = R_{\text{auto}} \rightarrow \text{volt. Ratio}$$

exciting current is neglected
mmf balance

$$(N_H - N_L) I_H = N_L (I_L + I_H)$$

When flux is same,
Voltage / turn is same

$$\Rightarrow N_H \Gamma_H - N_L \Gamma_H = N_L \Gamma_L - N_L \Gamma_H.$$

$$\Rightarrow N_H \Gamma_H \approx N_L \Gamma_L.$$


$$\Rightarrow \left[\frac{N_H}{N_L} = \frac{\Gamma_L}{\Gamma_H} \right] = \alpha_{auto}. \quad (54)$$

$$\frac{V_H}{V_L} = \frac{N_H}{N_L} = \alpha_{auto} = \frac{\Gamma_L}{\Gamma_H}$$

~~$$V_H \Gamma_H = V_L \Gamma_L$$~~

$$\Rightarrow S_{HV} = S_{LV}$$

comparison of copper : \rightarrow

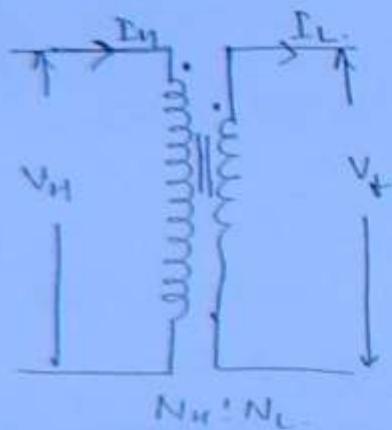

\rightarrow 2 wdg \times -mer for Same duty.

Copper wt = Copper Vol \times copper density

\propto copper ~~density~~ Vol.

\propto conductor \times -section \times conductor length

$$\downarrow \quad \quad \quad \downarrow \\ \propto E \quad \quad \quad \propto N$$

Cu wt \propto NF

\propto MMF.

$$\frac{\text{Cu (auto)}}{\text{Cu (2 wdg)}} = \frac{n_H (N_H - N_L) \Gamma_H + N_L (\Gamma_L - \Gamma_H)}{N_H \Gamma_H + N_L \Gamma_L}$$

$$= \frac{N_H E_L - N_L E_L + N_L E_L - N_L E_H}{N_H E_H + N_L E_L}$$

$$= \frac{N_H E_H - N_L E_H + N_L E_L - N_L E_H}{\partial N_H E_H}$$

$$= \frac{\partial N_H E_H - \partial N_L E_H}{\partial N_H E_H}$$

(55)

$$= 1 - \frac{N_L E_H}{N_H E_H}$$

$$= 1 - \frac{N_L}{N_H}$$

$$= 1 - \frac{1}{(\alpha_{auto})}$$

$$\boxed{Cu(\text{auto}) = \frac{\alpha_{auto} - 1}{\alpha_{auto}} \times Cu(2 \text{ wdg})}$$

for $\alpha = L$, 100% Cu saving -

$$Cu \text{ saving} = \frac{Cu(2 \text{ wdg}) - Cu(\text{auto})}{Cu(2 \text{ wdg})}$$

$$= 1 - \frac{Cu(\text{auto})}{Cu(2 \text{ wdg})}$$

$$= 1 - \left[1 - \frac{1}{\alpha_{auto}} \right]$$

$$\boxed{Cu \text{ saving} = \frac{1}{\alpha_{auto}}}$$

$\alpha_{auto} \approx 1$ for more saving

auto wdg number
no. of auto wdg
per unit

comps of P.T. →

(56)

$$S_{LV} = V_L E_L$$

$$= \underbrace{V_L (E_L - E_H)}_{\text{inductive transfer}} + \underbrace{V_L I_H}_{\text{conductive transfer}}$$

xmer or

transfer due to transformer action.

$$\begin{aligned} S_{LV} &= V_L (E_L - E_H) \\ &= V_L I_L - V_L I_H \\ &= V_H I_H - V_L I_H \\ &= (V_H - V_L) I_H \\ &= S_{AB}. \end{aligned}$$


$$\frac{V_L I_H}{V_L E_L} = \frac{E_H}{E_L} - \frac{1}{a_{auto}} = \frac{\text{conductive transfer}}{\text{total transfer.}} = \frac{V_L}{V_H}$$

⇒ If conductive transfer = 73%.

The saving of copper = 73%.

$$\frac{\text{Inductive transfer}}{\text{total transfer}} = \frac{V_L (E_L - E_H)}{V_L E_L} = \frac{E_L - E_H}{E_L}$$

$$= 1 - \frac{P}{a_{auto}}$$

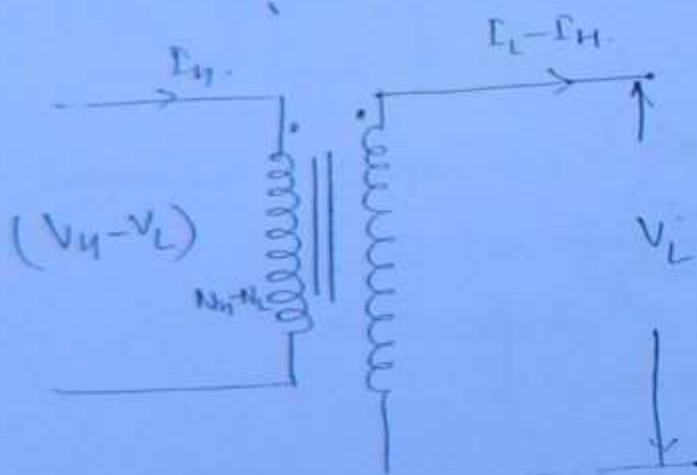

$$\frac{S_{auto}}{S_{wdg}} = \frac{V_H I_H}{(V_H - V_L) I_H} \quad \text{or} \quad \frac{V_L I_L}{V_L (I_L - I_H)}$$

$$= \frac{V_H}{V_H - V_L} \quad \text{or} \quad \frac{A L_L}{E_L - E_H}$$



$$\frac{S_{\text{auto}}}{S(\text{two-wdg})} = \frac{\alpha_{\text{auto}}}{\alpha_{\text{auto}} - 1} \quad (57)$$

losses are same, O/P inc., η ↑ of S auto & m.e.

Regulation is very low

I_{sc} ↑ due to decrease in Z

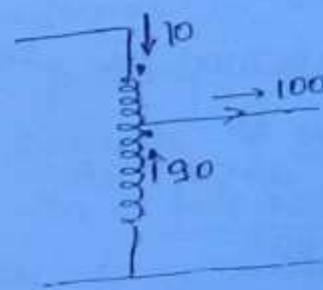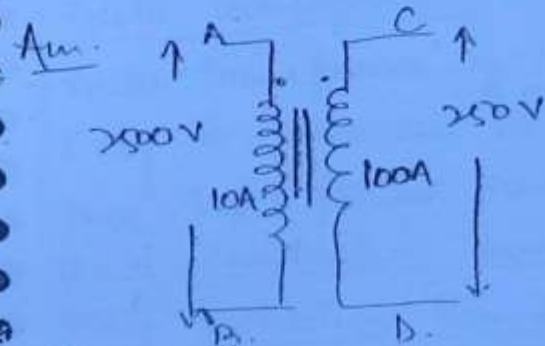→ A 45 kVA, 2500/250 V two-wdg x-mag is used to come if an auto transformer. What will be the voltage ratio and o/p with diff possible combination



$$1) V_H - V_L = 2500$$

$$V_L = 250$$

$$V_H = 2500 + 250 \\ = 2750$$


$$S_{\text{auto}}$$

$$S_{\text{auto}} = 25 \times \frac{10}{10-1}$$

$$= \frac{250}{9} = \frac{250}{9} = 27.78 \text{ MVA}$$

at 2750/250

→ 2750/250 at 27.78 MVA

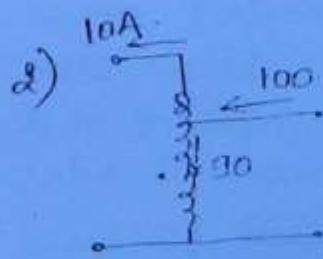

$$25 \times \frac{10}{10-1}$$

$$= 2.77$$

$$V_{250H} = 2500$$

$$V_H - V_L = 250$$


$$V_L = 2500 - 250$$

$$2250$$

2500/2250 at 2.77 MVA

Additive polarity →

1) Option (cont)

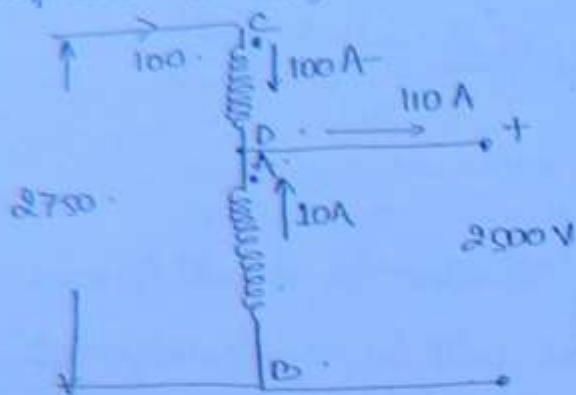


(58)

$$Q_{auto} = \frac{2750}{2500} = 1.1$$

$$S_{auto} = 2750 \times 100 \text{ or } 2500 \times 110 \text{ A}$$

$$\frac{4}{2750} \text{ KVA}$$

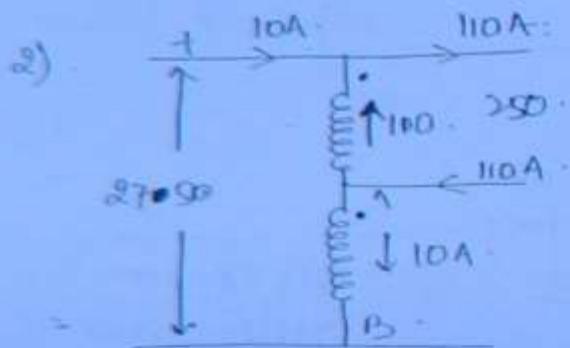


$$Q_{auto} = \frac{2750}{2500} = 1.1$$

$$S_{auto} = 2750 \times 10 \\ = 27.5 \text{ KVA}$$

3) Subtractive polarity →

100A for stepup

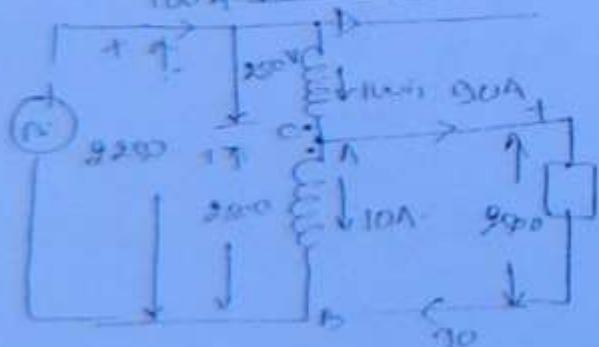


$$Q_{auto} = \frac{10}{9} = \frac{2500}{2250}$$

$$S_{auto} = \frac{2750 \times 10}{2250 \times 100} \\ = 22.5 \text{ KVA}$$

For Step down →

(59)

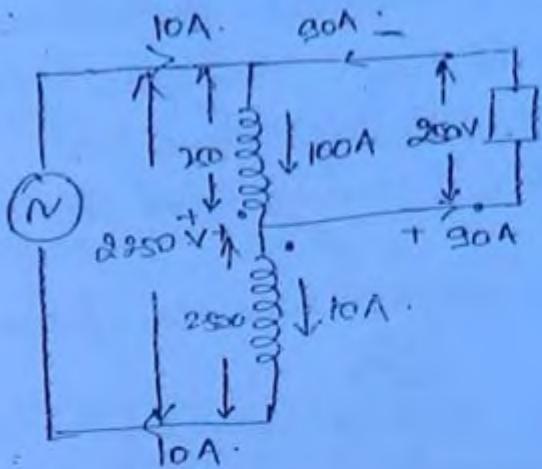

$$a_{auto} = \frac{2250}{250} = 9:1$$

$$S_{auto} = \frac{2250 \times 10}{250 \times 90} = 22.5 \text{ kVA}$$

Auto transformer —

Auto transformer is a transformer in which a part of wdg is common to both primary and secondary cts. The total power transfer consists of inductive transfer and conductive transfer. In a two wdg X-mer, there is only inductive transfer which is a transfer due to transformer action. In auto X-mer, there is additional power transfer on account of physical connection b/w the source and the load through the series wdg. The conductive transfer is the main factor responsible for massive cu saving and increased KVA O/P in an auto transformer as compared to a two wdg X-mer of the same capacity and voltage rating. This advantage is most visible when the ratio is close to 1. Accordingly auto transformers are seldom used when the voltage ratio is more than 2:1.

Some of the other advantages of auto transformer as compared to two wdg X-mer are higher efficiency, lower pu. impedance and therefore lesser voltage regulation. However the lower pu. impedance results into higher se current and therefore higher fault level.

The disadvantage of with auto π -mer is that if you step down mode, the common wdg develops o.c. Then load is subjected to almost full high voltage. flows series wdg. Moreover, an auto transformer does not provide electrical isolation b/w the primary and second chgs.

An auto transformers find their application in following areas :-

(6)

- 1) to interconnect two PS of diff. Voltage level where their ratio does not actually usually exceed 2:1. For eg 765 / 400 KV, 400 KV / 220 KV, and 220 KV / 132 etc.
- 2) For starting 3- ϕ induction motors usually of the squirrel cage type.
- 3) In automatic Voltage stabilizers for domestic use and in servo stabilizer for industrial, commercial and domestic use.
- 4) As Voltage booster in electric traction electrification scheme of traction system like railways to compensate for line voltage drop.
- 5) As continuously variable π -mer in laboratory applications.

When a 2 wdg π -mer is converted into an auto π -mer, the insulation of LV wdg of two wdg π -mer should be strengthened to withstand the HV rated of the auto π -mer.

✓


A_{2wdg}

(61)

S_{auto} = A_{2wdg} × S_{2wdg} ± S_{kwdg}) → a is close to L.

S_{auto} = S_{2wdg} ± $\frac{S_{2wdg}}{A_{2wdg}}$ → a ≠ close to L.

Tertiary wdg →

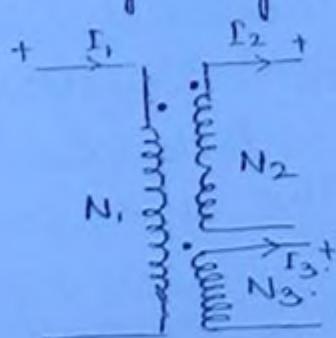

Since flux is common,

$$\frac{\bar{V}_1}{N_1} = \frac{\bar{V}_2}{N_2} = \frac{\bar{V}_3}{N_3}$$

Neglecting exciting current :—

$$N_1 \bar{I}_1 - N_2 \bar{I}_2 - N_3 \bar{I}_3 = 0.$$

considering exciting current :—

$$\boxed{N_1 \bar{I}_1 - N_2 \bar{I}_2 - N_3 \bar{I}_3 = N_1 I_0}$$

$$\Rightarrow \bar{I}_1 = \frac{N_2}{N_1} \bar{I}_2 + \frac{N_3}{N_1} \bar{I}_3 + \bar{I}_0$$

taking conjugates,

$$\Rightarrow \bar{I}_1^* = \frac{N_2}{N_1} \bar{I}_2^* + \frac{N_3}{N_1} \bar{I}_3^* + \bar{I}_0^*$$

$$\bar{V}_1 \bar{I}_1^* = \frac{N_2}{N_1} \bar{V}_1 \bar{I}_2^* + \frac{N_3}{N_1} \bar{V}_1 \bar{I}_3^* + V_1 I_0^R$$

$$\Rightarrow \boxed{\bar{V}_1 \bar{I}_1^* = \bar{V}_2 \bar{I}_2^* + \bar{V}_3 \bar{I}_3^* + \bar{V}_1 I_0^*}$$

$\bar{V}_1 I_0^*$ → complex power taken by excitation

Tertiary wdg is the 3rd wdg in addition to the usual primary and secondary wdg. The total power drawn from the supply is obviously the sum of the total power delivered to loads connected to

2nd and tertiary wdg if no internal losses are neglected. Tertiary wdg is usually used in following applications:-

(62)

- i) To connect 3 power system at diff. Volt. level.
 - 2) To provide an additional Volt level for specific purpose. for eg to supply power Analys in power plant and to connect reactive power compensating equipm.
 - 3) for reactive power compensation.
- 3) for Y-Y connected transformers and unloaded delta connected tertiary wdg may be used as a stabilizer wdg to prevent problems arising out of unbalance and harmonics. It also helps to reduce the value of the 0 seq. impedance.


Q: The ratio of the no. of turns /φ in the primary Secondary and tertiary wdg of X-mer is 10:2:L. with lagging currents of 45 A at pf 0.8 in the secondary and 50 A at pf 0.71 & in the tertiary wdg find the primary current and pf. neglect losses.

Ans. With V₀ as ref phasor.

| | | |
|----------------|----------------|----------------|
| N ₁ | N ₂ | N ₃ |
| 10 | 2 | L |

$$\begin{aligned} I_1^* &= \frac{N_2 I_2}{N_1} + \frac{N_3 I_3}{N_1} \\ &= \frac{2}{10} 45 L - \cos^{-1} 0.8 + \frac{1}{10} \times 50 L - \cos^{-1} 0.71 \\ &= 13.972 L - 39.50 \end{aligned}$$

| | |
|------------|---------|
| Pf = 0.772 | lagging |
|------------|---------|

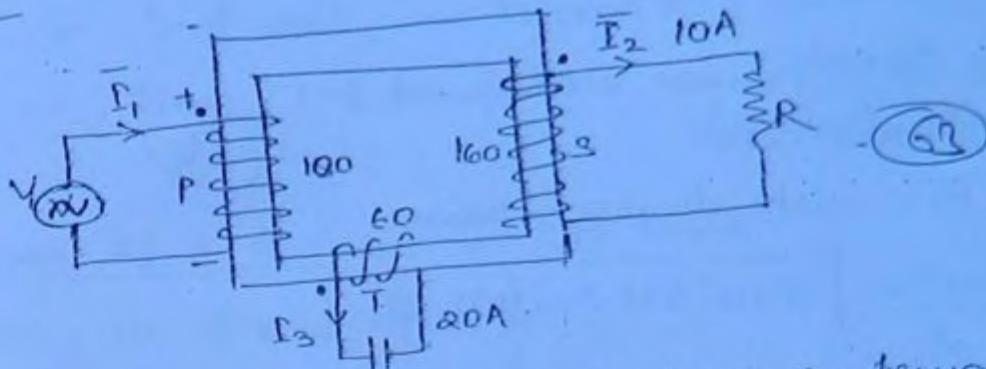

- An ideal X-mes has 3 wdg 100 turns on primary wdg P, 160 turns on 2nday wdg S, and 60 turns on T. wdg S feeds 10 A to a resistive load, whereas a capacitance load across wdg T takes 20 A.
- part A cat. current in primary wdg and its Pf in case X-mes magnetising segment is neglected.
- part B with the polarity markings on P as shown mark the polarities on wdg for S and T also.

Ans. $\bar{E}_1 = \frac{N_2}{N_1} \bar{I}_2 + \frac{N_3}{N_1} \bar{I}_3$

$$\frac{(160 \times 10) + (60 \times 20)}{100} \bar{E} = \cos 10^\circ$$

$$= 20$$

with Voltage as ref. phasor

$$V = \frac{160}{100} \times 10 / 0^\circ + \frac{60}{100} \times 20 / 90^\circ$$

$$= 20 \cos 136.87^\circ$$

Input Pf $\cos 26.87^\circ$
on 0.8 load.

Three phase X-mag :→.

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

$vi = P$ = instantaneous power

$$P = \frac{V_m I_m}{2} \left[2 \sin \omega t \sin(\omega t - \phi) \right].$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \left[\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi) \right]$$

$$= V_{rms} I_{rms} \left[\cos \phi - \cos(2\omega t - \phi) \right]$$

$$P_{\perp \phi} = VI \cos \phi - VI \cos(2\omega t - \phi)$$

\uparrow \uparrow
Independent pulsating twice the power
of time freq.

∴ Torque, noise, vibration ↑

∴ Single phase ~~motors~~^{m/c} vibrate more and produce noise much more than 3-φ m/c

$$P_{3-\phi} = 3VI \cos \phi$$

$$= \cos \phi$$

∴ $P_{3-\phi}$ is independent of time. So, less noise and vibration.

$$P_{1-\phi} = VI \cos \phi - VI \left[\cos \omega t \cos \phi + \sin \omega t \sin \phi \right]$$

$$= VI \cos \phi (1 - \cos \omega t) - VI \underbrace{\sin \phi \sin \omega t}_{Q}$$

3: $\phi - \chi$ -mer:

Option 1. \rightarrow 3- ϕ unit — 1×3000 kVA unit (B)

Option 2 \rightarrow Three 1- ϕ transformers connected in 3- ϕ bank.
 3×1000 kVA Bank.

Advantage of 1- ϕ x-mer in 3 ϕ bank:


- 1) Economy in spare capacity.
 - 2) Economy in spare part management.
 - 3) "Vee" connection is possible.
- Open delta

- 4) Ease of transfert (particularly in mines)

Disadv. \rightarrow


- 1) more costly
- 2) occupies more space at site
- 3) Overall η is lower.

Polarity test \rightarrow

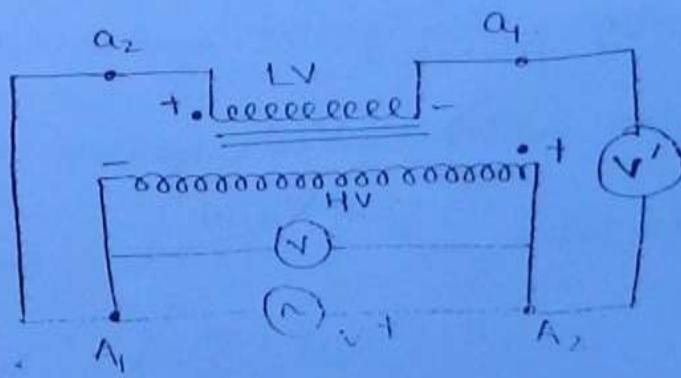

$$V' > V_2$$

additive polarity

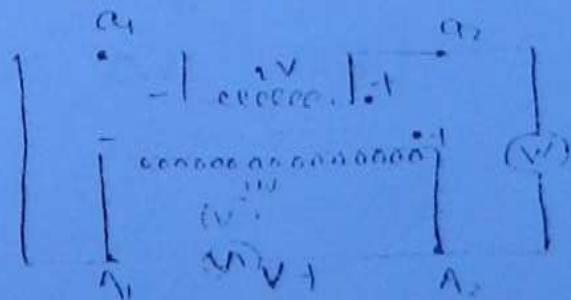

$$V' < V_2$$

subtractive polarity

Phase gp of connection →


gp 1: 0° → $Y_y 0, D_d 0$

gp 2: 180° → $Y_y 6, D_d 6$

gp 3: 30° lag (-30°) → $Y_d 1, Y_d D_y 1$


gp 4: 30° lead ($+30^\circ$) → $Y_d II, D_y II$

(66)

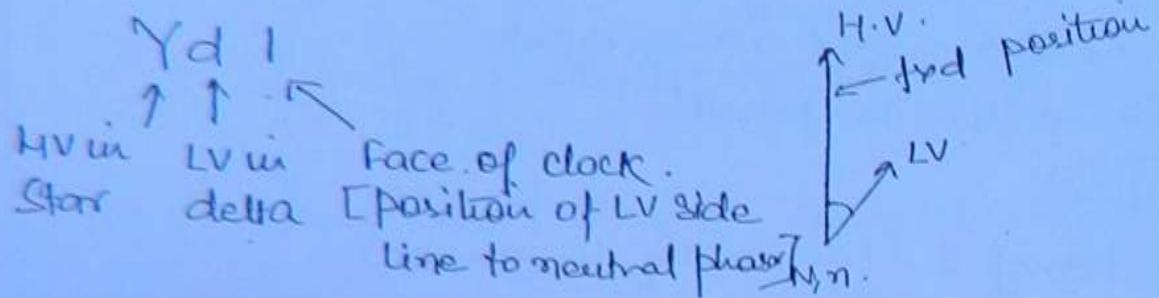


Conventions to be followed :

1) Phase seq. is ABC.

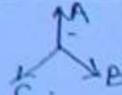

2) HV side A-N phasor at 0° o'clock position.

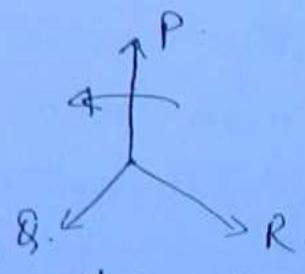
3) HV side A terminal to be taken from A_2 .



Φ seq. is PRQ. =
 $RQ_{R_N} = QPR$

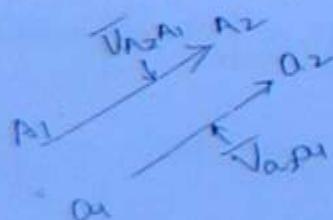4) $\bar{V}_{A_1 A_2}$ and $\bar{V}_{a_1 a_2}$ are in phase.

$$(\bar{V}_{A_2 A_1}) \quad (\bar{V}_{a_2 a_1})$$





$$\begin{aligned} &\rightarrow \bar{V}_{A_1 A_2} \\ &\rightarrow \bar{V}_{a_1 a_2} \end{aligned}$$

YyD →

$$a_t = \frac{N_{HV}}{N_{LV}}$$

(67)

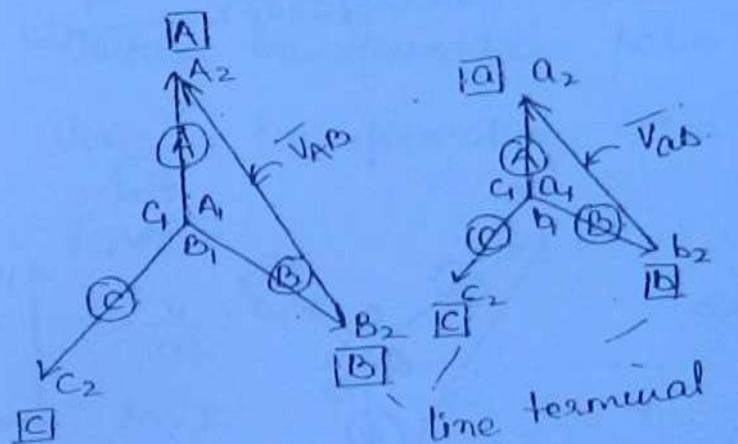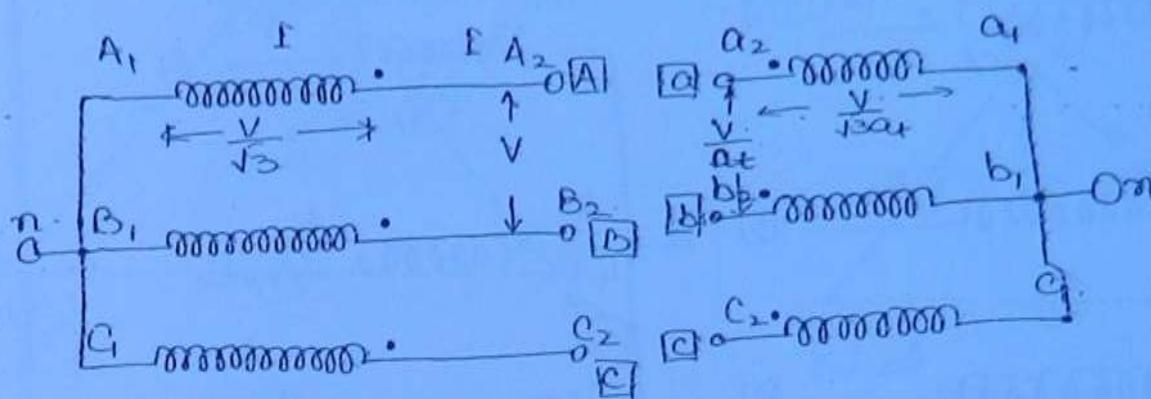

$$\bar{V}_{AB} = \bar{V}_{AN} - \bar{V}_{BN}$$

$$V_{AN} = V_{BN} + V_{AB}$$

→ Phase voltage transformation ratio = $\frac{V}{\sqrt{3}} : \frac{V}{\sqrt{3}a_t} = a_t : 1$

→ Line voltage transformation ratio = $\frac{V}{\sqrt{3}} : \frac{V}{a_t} = a_t : 1$



→ $S_{HV} = \sqrt{3}VI$ $\sqrt{3}VI \cos\phi \rightarrow \phi \rightarrow \text{angle b/w phase l and phase a}$

$$S_{LV} = \sqrt{3} \frac{V}{a_t} \cdot a_t I$$


$$S_{LV} = \sqrt{3}VI \quad S_{HV}$$

→ to transfer power from 1st level to 2nd level for

Yy G. →

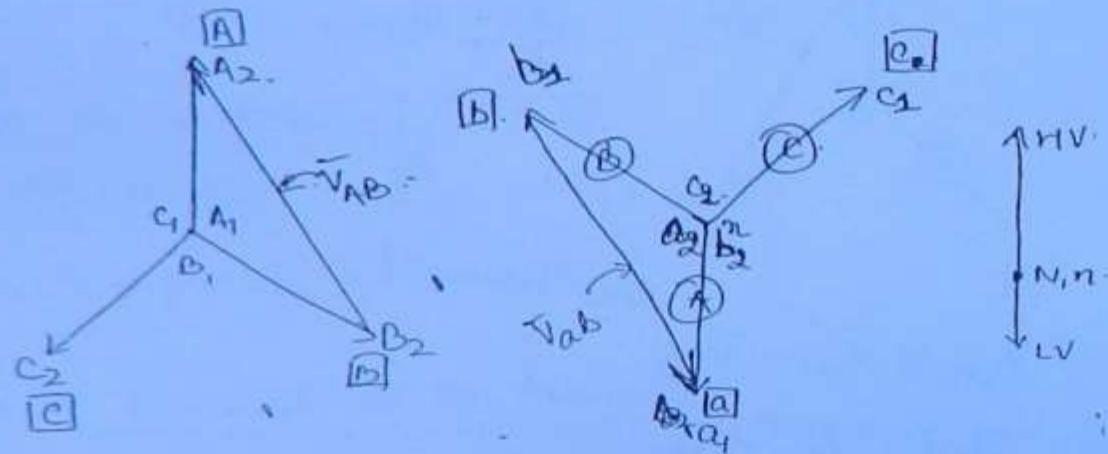
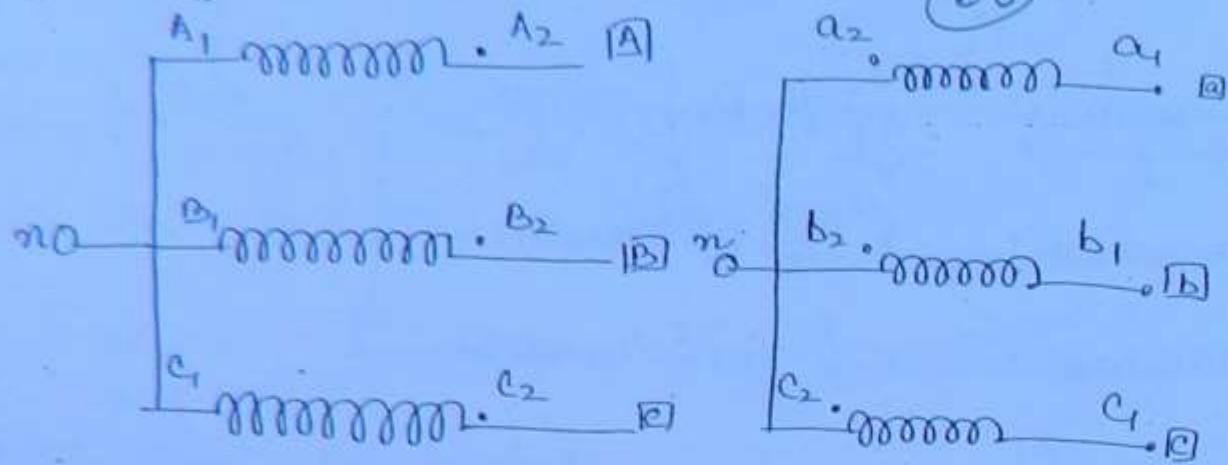


10

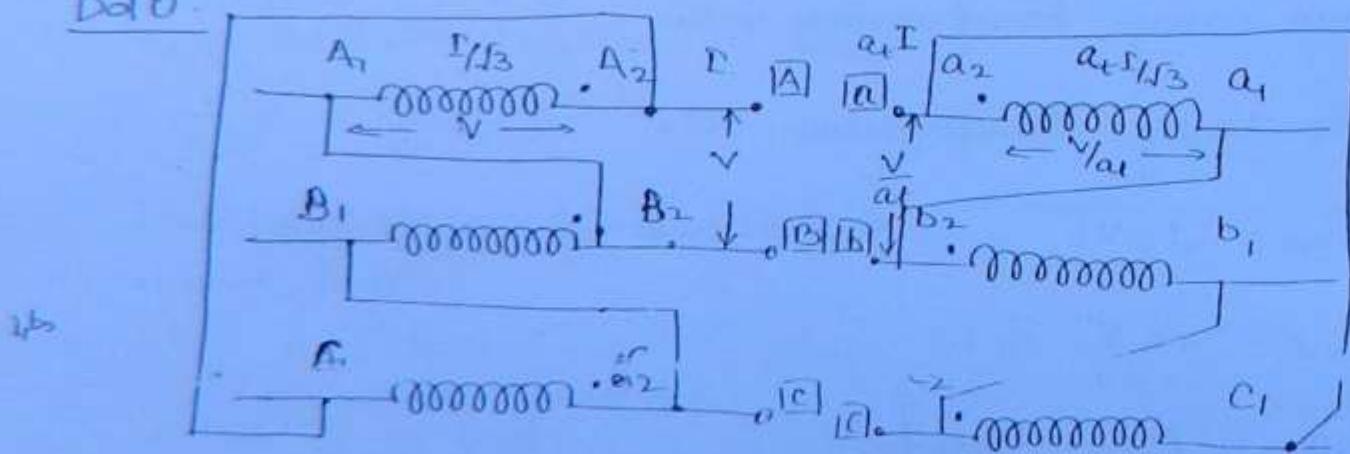

111

(69)

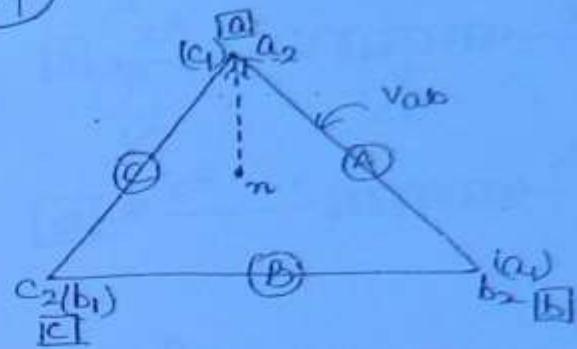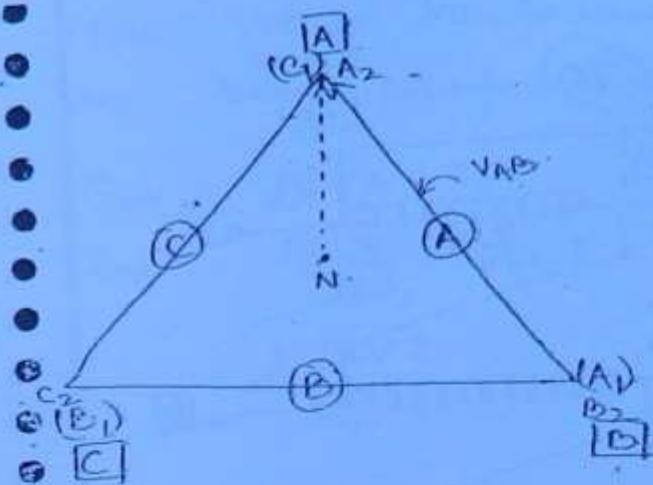

Phase Voltage transformation ratio = $V : \frac{V}{a_1} = a_1 : 1$

Line Voltage transformation ratio = $V : \frac{V}{a_1} = a_1 : 1$.



$$S_{HV} = \sqrt{3} V I$$

$$S_{LV} = \sqrt{3} \frac{V}{a_1} \cdot a_1 I$$


$$= \sqrt{3} V I$$

$$= S_{HV}$$


Ddg

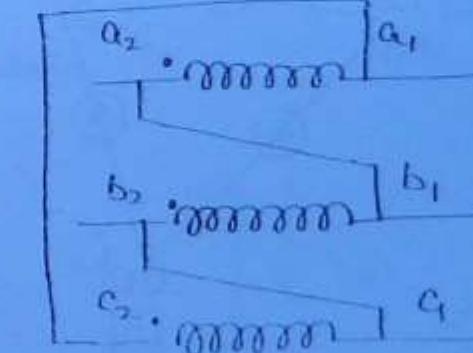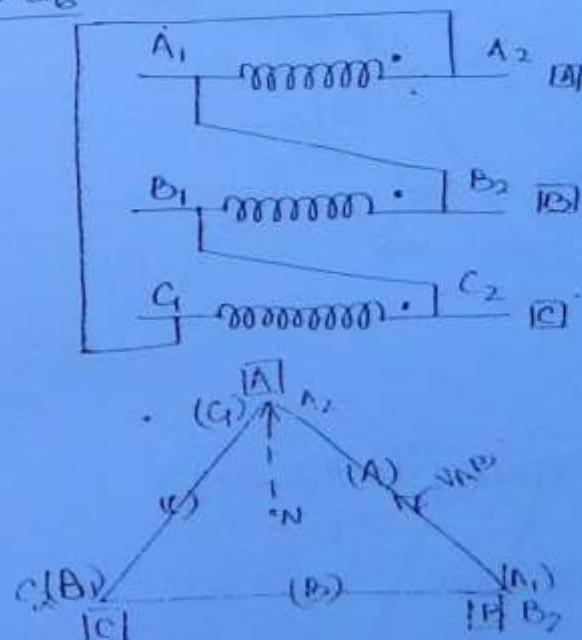



HV
N, n
LV

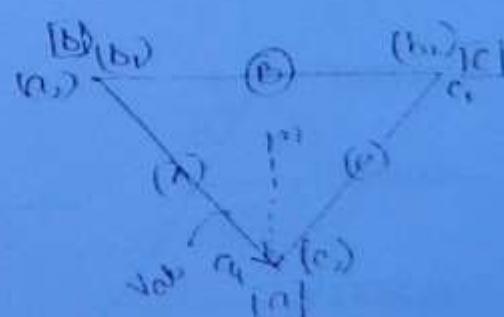


Yd1 →

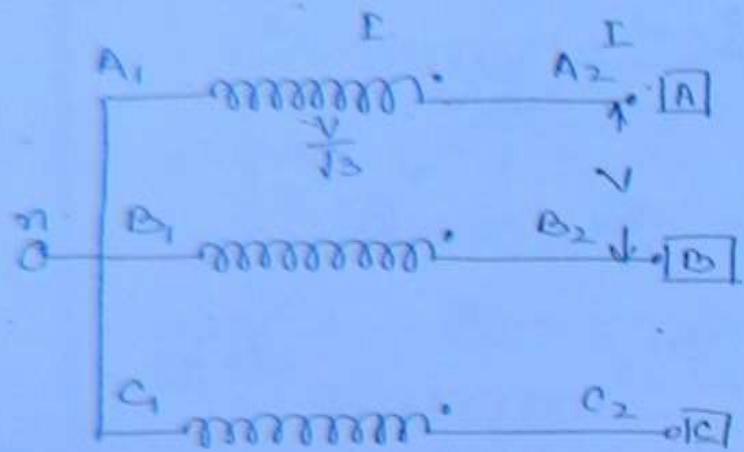



(70)

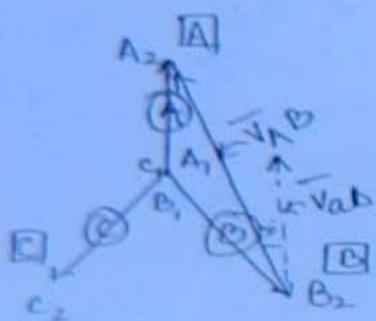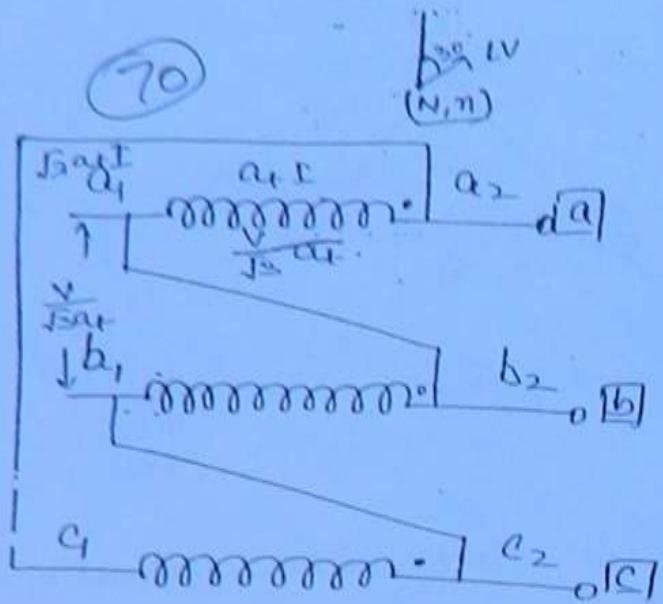

Yds →

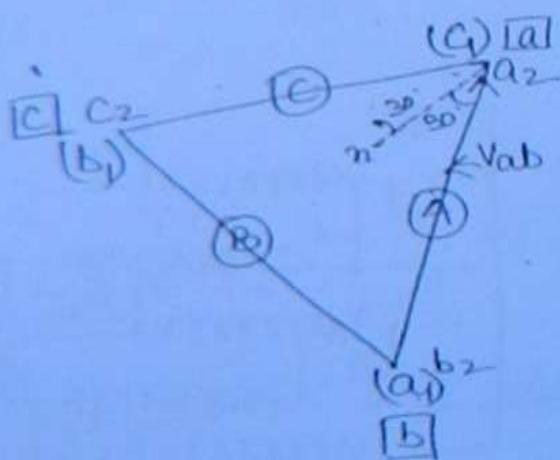

D/P taken from:
a₁, b₁, c₁

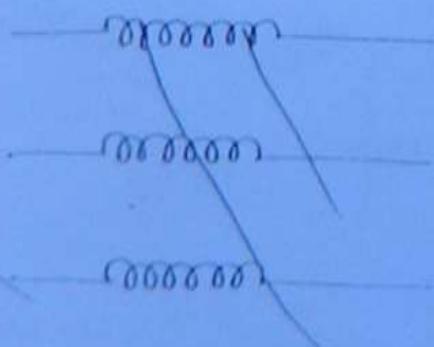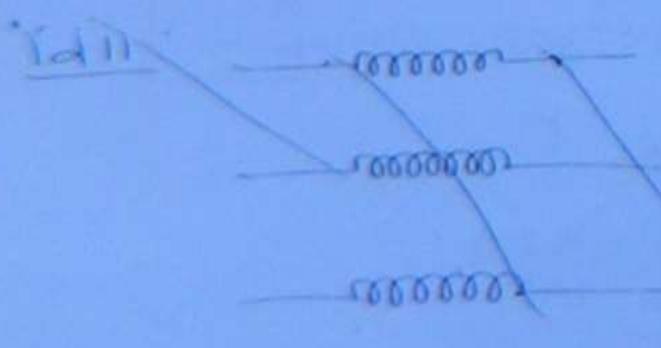




Phase voltage transformation ratio = $\frac{V}{\sqrt{3}} : \frac{V}{\sqrt{3}\alpha_t} = \alpha_t : 1$
 Line voltage transformation ratio = $V : \frac{V}{\sqrt{3}\alpha_t} = \sqrt{3}\alpha_t : 1$

$$S_{HV} = \sqrt{3} V I$$



(71)

$$\begin{aligned} S_{LV} &= \sqrt{3} \frac{V}{\sqrt{3}\alpha_t} \sqrt{3}\alpha_t I \\ &= \sqrt{3} V I \\ &= S_{HV} \end{aligned}$$

Yd11 →

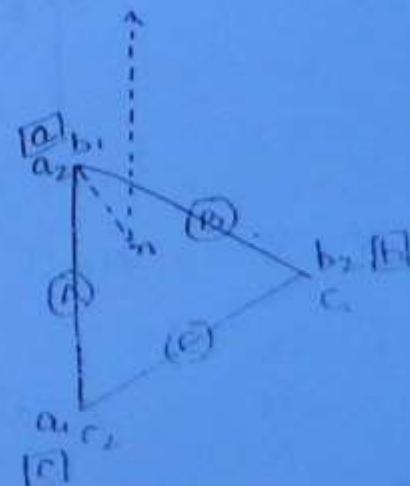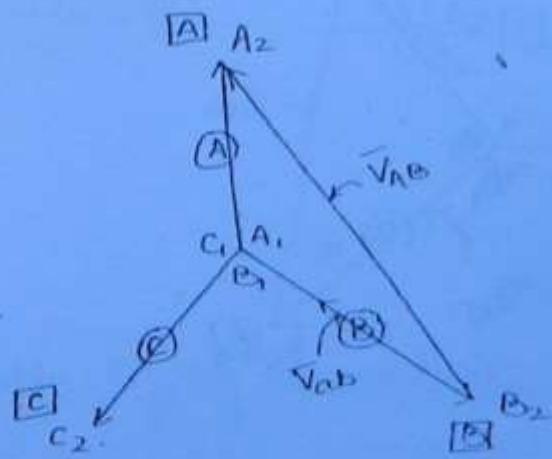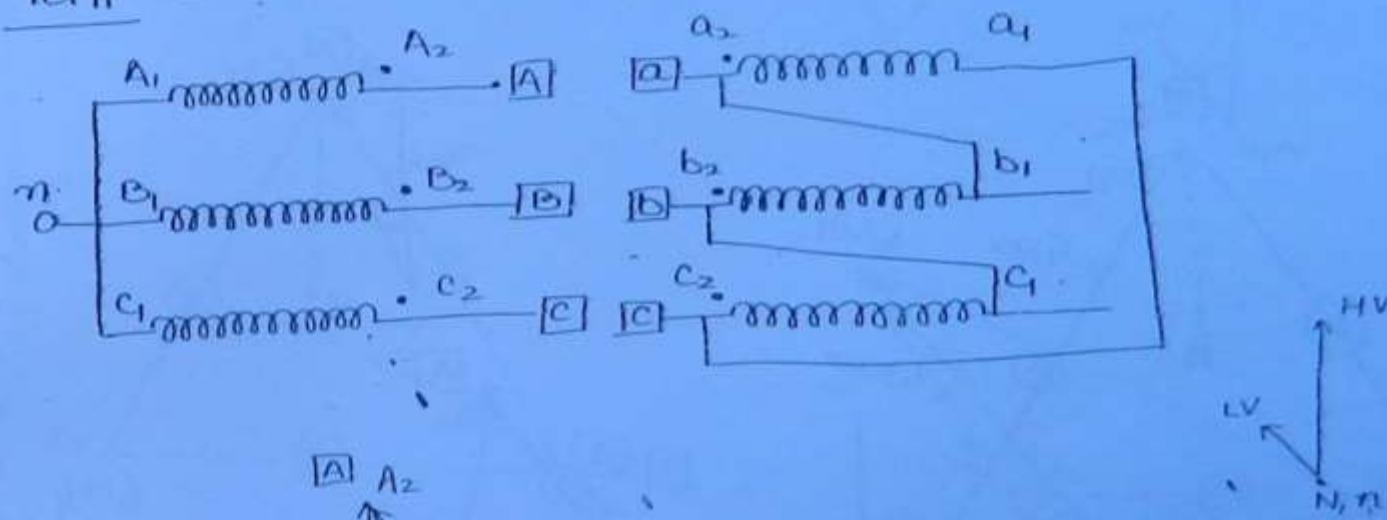

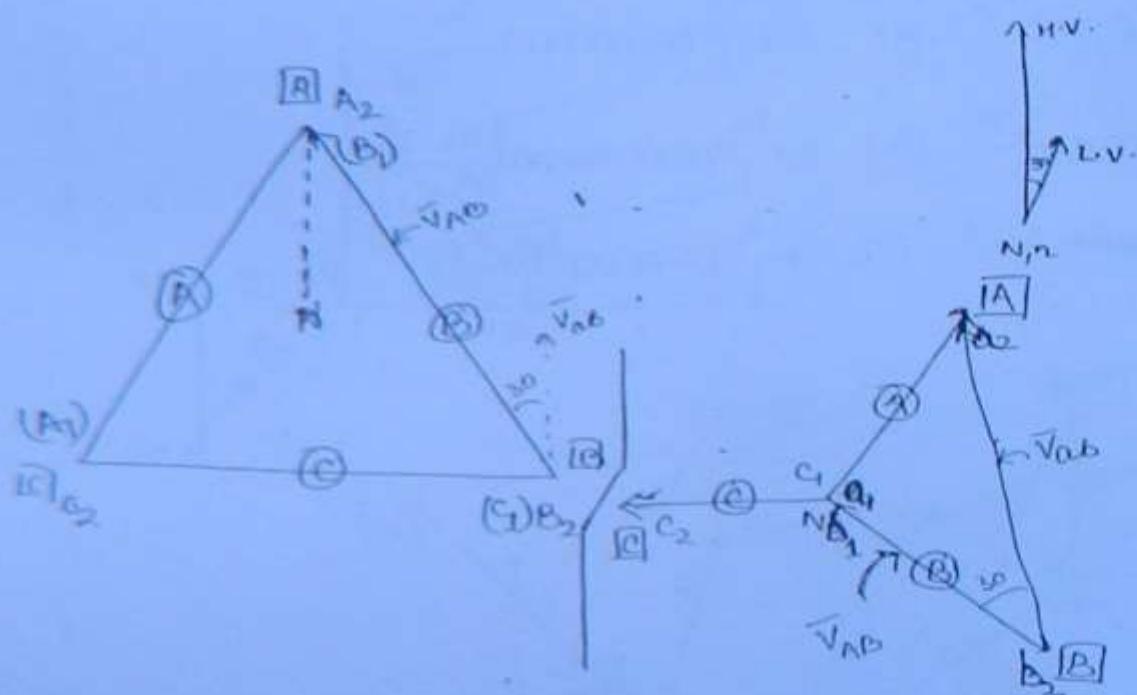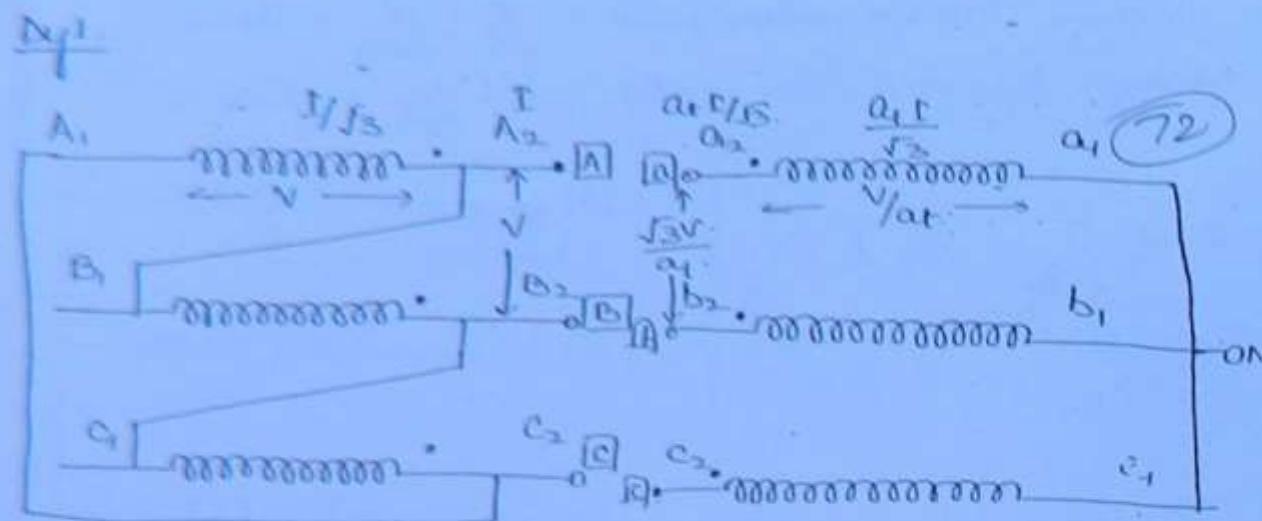$\text{Yd}11 \rightarrow \text{OP lower from } a_1, b_1, c_1$




$$FVTR = V : \frac{V}{\alpha_1} = \alpha_1 : 1$$

$$LVTR = V : \frac{V}{\alpha_1} = \frac{1}{f_3} : 1$$




$$S_{HV} = f_3 V I$$

$$S_{HV} = f_3 I \cdot \frac{f_3 V}{\alpha_1} \cdot \frac{\alpha_1 r}{f_3} = f_3 V I \\ S_{HV}$$

Dy III

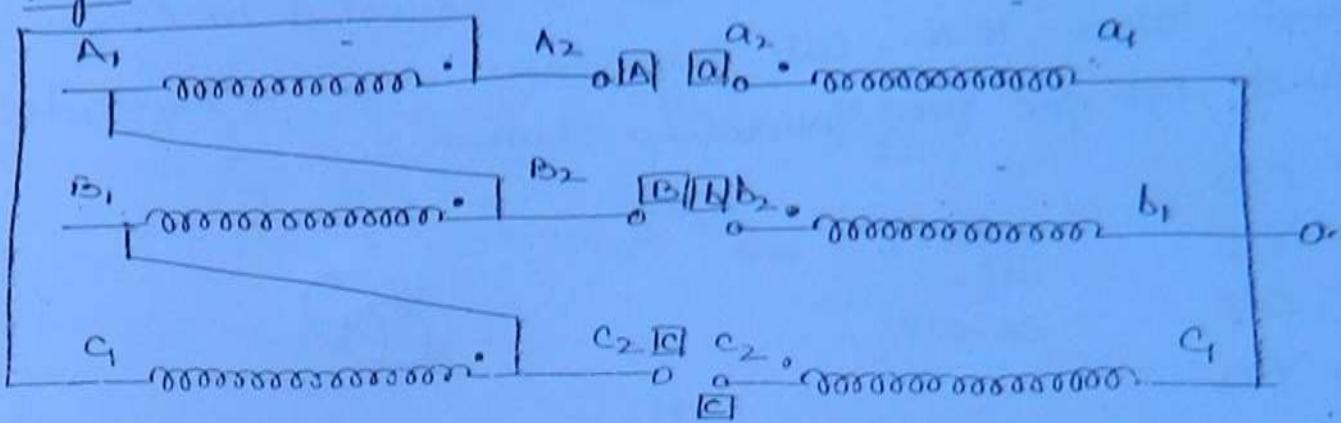

(73)

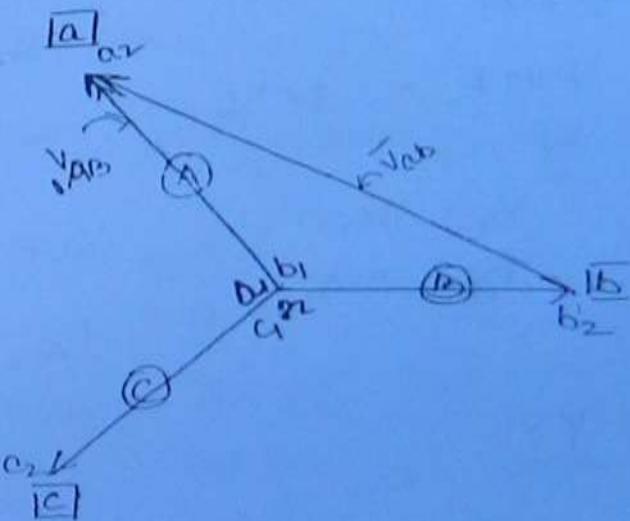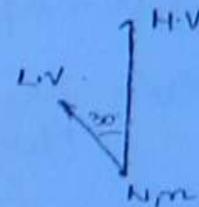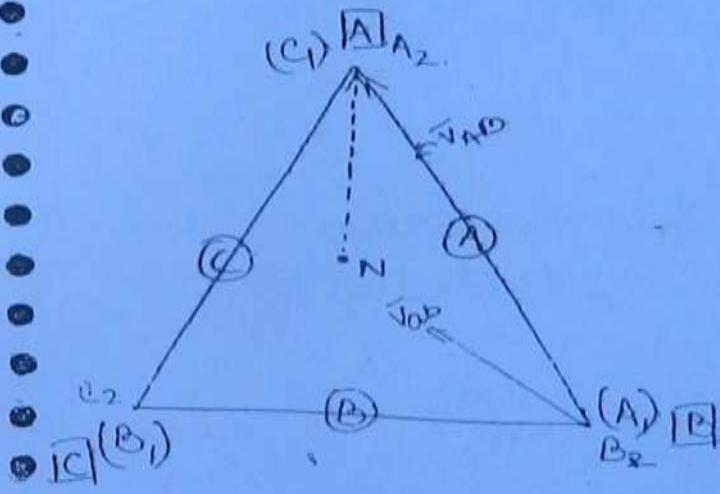

Possible zigzag connection. — [center star]

DZ 0

DZ 6

YZ 1

YZ 11

WVA 3-phase star drawn X-met is connected to 6600 V_{MA} and takes 10 A. Cal. Secondary line voltage, I_L and O/P for the following connection:-

- 1) $\Delta\Delta$
- 2) YY
- 3) ΔY
- 4) $Y\Delta$

(74) 3

The ratio of turns/pole is 12, neglect losses.

A/m: $\alpha_t = \frac{N_{HV}}{N_{LV}} = 12$.

- 1) $\Delta\Delta$.

$$S_{HV} = S_{LV} = \sqrt{3} \times 6600 \text{ VA}$$

$$\text{PVTR} = 12 : 1$$

$$= \sqrt{3} \times 66 \text{ kVA}$$

$$V_A = 6600$$

$$V_a = \frac{6600}{12} = 550$$

$$I_A = 10 \text{ A}$$

$$I_A = \frac{10 \times 6600}{10} = \cancel{6600} 120 \text{ A}$$

- 2) YY.

$$(V_A)_P = \frac{6600}{\sqrt{3}}$$

$$(V_a)_P = \frac{6600}{\sqrt{3} \times 12}$$

$$(V_a)_{\text{line}} = \frac{\sqrt{3} \times 6600}{12} = \frac{6600}{12}$$

$$(I_A)_P = 10$$

$$(I_A)_P = 10 \times 12 = 120 \text{ A}$$

3) ΔY

$$(V_a)_P = 6600 \quad \text{Ans}$$

$$(I_a)_P = \frac{10}{\sqrt{3}}$$

$$(V_a)_P = \frac{6600}{12}$$

$$(V_a)_{line} = \sqrt{3} \frac{6600}{12}$$

$$= 952.63$$

$$(I_a)_P = 12 \times \frac{10}{\sqrt{3}}$$

$$(I_a)_{line} = \frac{120}{\sqrt{3}}$$

4) $Y \Delta$ Y

$$(V_a)_P = \frac{6600}{\sqrt{3}}$$

$$(V_a)_P = \frac{6600}{\sqrt{3} \times 12} = 317.54 \quad \text{Ans}$$


$$(I_a)_P = 10 \text{ A}$$

$$(I_a)_P = a_t \times 10$$

$$= 120$$

$$(I_a)_{line} = 120 \sqrt{3}$$

$$= 207.85$$

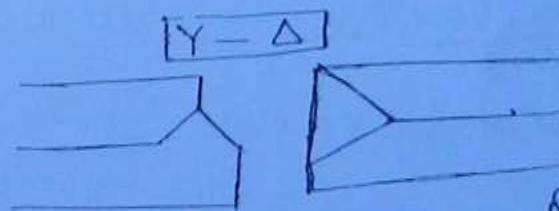

Q) On star line to neutral basis, we calculate all the values in power system

$$S_{HV} = S_{LV}$$

$$\sqrt{3} V_{HV} I_{HV} = \sqrt{3} V_{LV} I_{LV} \quad \text{After line to series impedance add}$$

$$\frac{I_{LV}}{I_{HV}} = \frac{V_{HV}}{V_{LV}}$$

include $\omega^2 Z$ from Star to Comp. & and then we calculate $\rightarrow 3\phi$ system




A \odot HP, 440 V, 3φ 1.M. with an off. of 0.9 and PF 0.85 on full load is supplied from 6600/410 V

ΔY connected motor. Ignoring the magnetising current, the current in the ~~high~~ and LV legs of Δ -motor, when the motor is running at F.L.


Line current or ph current

$$\eta = \frac{\text{Output}}{\text{O/P}}$$

(26)

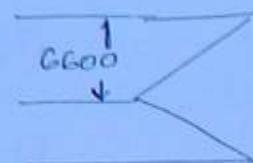

30
6600.

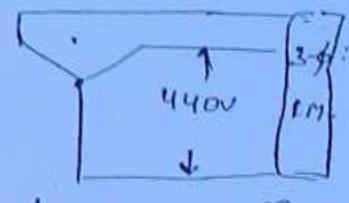

440V. $\eta = 0.6$
50HP

50HP

$$\text{Input} = \frac{\text{Output}}{0.9}$$

$$440 \times 0.9 = \text{O/P}$$

$$\text{O/P} = 396 \text{ V}$$

$$\sqrt{3} \times 440 \times I_L = 30 \times 746$$

$$I_L = 48.94$$

$$\sqrt{3} E_{\text{line}}(\text{line})_{\text{LV}} \times V_{\text{line(LV)}} \cos \phi = \frac{\text{Output}}{0.9}$$

$$= \frac{30 \times 746}{0.9}$$

$$\sqrt{3} E_{\text{line}} \times 440 \times 0.85 = \frac{30 \times 746}{0.9}$$

$$(E_{\text{line}})_{\text{LV}} = 63.98 \text{ V}$$

$$(E_{\text{line}})_{\text{LV}} = 63.98 \text{ V}$$

$$E_{\text{line}}(1\text{-ph})_{\text{LV}} = \frac{63.98}{\sqrt{3}} = 36.94 \text{ V}$$

$$(1\text{-ph})_{\text{UV}} = \left(\frac{36.94}{440} \right) = 2.463 \text{ A}$$

$$(I_{\text{line}})_{\text{V}} = 2.463 \text{ A}$$

Q. A star/star/delta with primary, secondary and tertiary voltages of 11000 V, 1000 V, and 400 V has a magnetising current of 3A. There is balanced load of 600 KVA at 0.8 pf lagging on the secondary wdg and a balance load of 150 kW on the tertiary wdg. Neglecting losses find the primary and tertiary phase current if the primary pf is 0.82 lagging.

(77)

Ans. $N_1 \quad N_2 \quad N_3$ $I_0 = 3A$

$$11000 \quad 1000 \quad 400$$

$$\begin{aligned} V_1 I_1^* &= V_2 I_2^* + V_3 I_3^* + V_1 I_0^* \\ \Rightarrow 11000 \times I_1^* &= -600 \times 0.8 + 150 + 11000 \times 3 \\ \Rightarrow I_1 &= 3.057 \angle -\cos^{-1} 0.82 \\ &= 3.057 \angle -54.32^\circ \end{aligned}$$

$$S_1 = \sqrt{3} \times 11000 \times I_1 \angle \cos^{-1}(0.82) \text{ KVA.}$$

$$S_2 = 600 \angle \cos^{-1}(0.8)$$

$$S_3 = \frac{150}{\cos \phi_3} \angle \phi_3$$

$$S_0 = \sqrt{3} \times 11 \times 3 \angle 90^\circ \text{ KVA.}$$

$$S_1 = 600 / \cos 10.8 + j 100 / \cos \phi_3 (\phi_3 + j \tan \phi_3 \times 3 \angle 90^\circ)$$

$$\begin{aligned} \sqrt{3} \times 11000 \times I_1^* \angle \cos^{-1} 0.82 &= 600 \{ 0.82 + j 0.6 \} + \frac{150}{\cos \phi_3} \{ \cos \phi_3 + j \sin \phi_3 \} \\ &\quad + j 100 \{ j \} \end{aligned}$$

$$\Rightarrow \sqrt{3} \times 11000 \times I_1 \{ 0.82 + j \sin \cos^{-1}(0.82) \} = 600 \{ 0.82 + j 0.6 \} + 100 + j 100 \tan \phi_3 + j 15 \times 33.3$$

$$I_1 = 40.325 \text{ A}$$

$$\phi_3 = 8.56 \text{ (lag)}$$

$$I_3 (\text{line}) = \frac{150 \times 10^3}{\sqrt{3} \times 400 \times \cos 8.56}$$

(78)

$$= 218.945 \text{ A}$$

Phase current in tertiary $\Delta = \frac{218.945}{\sqrt{3}}$

$$= 126.41 \text{ A}$$

$$S = \sqrt{3} V I$$
$$\Rightarrow I = \frac{S}{\sqrt{3} V}$$

→ High Voltage, low capacity Application →

$$\downarrow \downarrow I = \frac{\downarrow S}{\sqrt{3} V \downarrow}$$

I_o for star.

→ low voltage; high capacity application →

$$\uparrow \uparrow I = \frac{S \uparrow}{\sqrt{3} V \downarrow}$$

I is significant factor, I_o for delta.

conductor x-sec decreased, $I_L = \sqrt{3} I_P$.
preferable

→ ΔY → Step up

→ YΔ → Step down

Distribution transformer.

11 kV / 400 V → ΔY

3- ϕ X-mes connection :-

→ $\Delta-\Delta$ → $\Delta-\Delta$ X-mes is usually used at low volt. levels where high capacity loads to one to be supplied. Neutral loading is not possible because neutral is not available. However its chief advantage is that if a 3ϕ bar of single- ϕ transformer is used and one of the X-mes develops a fault after which it has to be removed, then also the remaining two X-mes can continue to feed 3ϕ loads but at reduced capacity of 57.7% using Vee (open delta) connection.

(79)

$Y-\Delta$:— (step down)

In accordance with general recommendation, the H.V. side is connected in Y and the low volt. side is connected in Δ . Therefore $Y-\Delta$ X-mes are suitable for step down applications in transmission and sub-transmission CTs.

$\Delta-Y$:— (step up)

$\Delta-Y$ X-mes are generally used in step up applicat. for transmission and sub transmission CTs. However in distribution CTs, these transformers are used for step down applications because a neutral connected is necessary for mix loading for 3ϕ load as well as 1ϕ load have to be supplied.


$Y-Y$


Though $Y-Y$ X-mes appear to be quite attractive for high voltage applications, they are not used w/o faulting delta in X-mes that have independent mag. core. Due to saturation associated with flux and

Oscillating neutral, magnetising I, harmonics and communication interference. However there is an increasing trend these days of using 3- ϕ -3 limb core type transformers for very high volt. application where the unbalance is not expected to exceed 10%.

"Vee" (or open Delta) connection : →

(80)

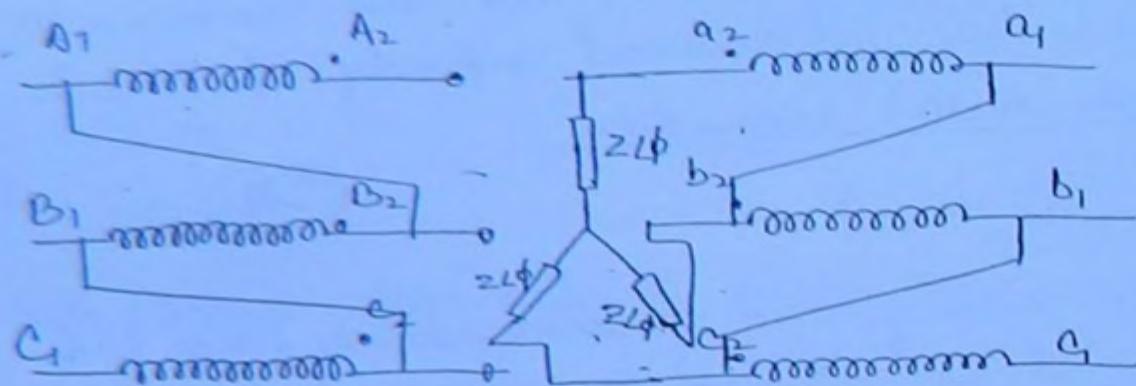

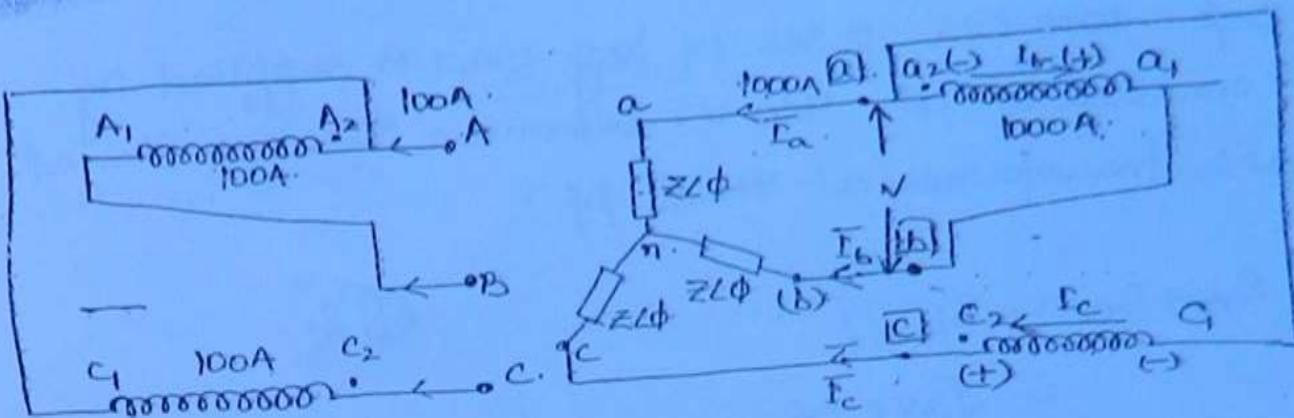

$$S_{\Delta-\Delta} = \sqrt{3} V_{L-L} I_L$$

(81)


$$S_{VEE} = \sqrt{3} V_{L-L} \left(\frac{P_L}{\sqrt{3}} \right)$$

$$= V_{L-L} I_L$$

$$\frac{S_{VEE}}{S_{\Delta-\Delta}} = \frac{V_{L-L} I_L}{\sqrt{3} V_{L-L} I_L}$$

$$= \frac{1}{\sqrt{3}} = 57.7\%$$

$$|I_a| = |I_b| = |I_c| = I$$

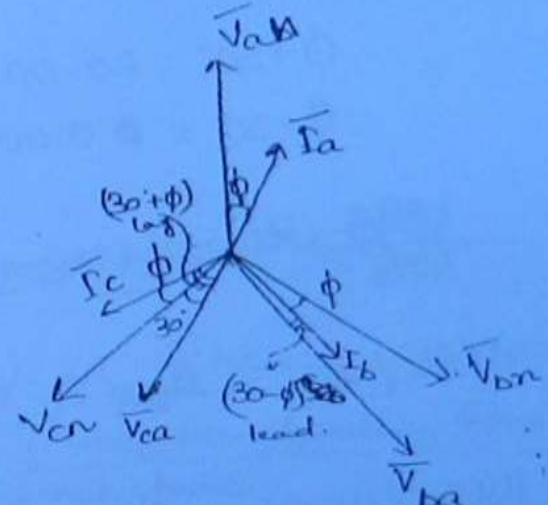

$$S_{load} = \sqrt{3} V L \cos \phi$$

$$S_A = V_L \angle (-30^\circ - \phi) = V_L \angle (\phi - 30^\circ) = \frac{S_L}{\sqrt{3}} \left[\cos(\phi - 30^\circ) + j \sin(\phi - 30^\circ) \right]$$

$$S_B = V_L \angle (30^\circ + \phi) = V_L \angle (\phi + 30^\circ) = \frac{S_L}{\sqrt{3}} \left[\cos(\phi + 30^\circ) + j \sin(\phi + 30^\circ) \right]$$

$$S_A + S_B = V_L \left[\cos(\phi - 30^\circ) + j \sin(\phi - 30^\circ) \right] + V_L \left[\cos(\phi + 30^\circ) + j \sin(\phi + 30^\circ) \right]$$

$$= V_L \left[2 \cos \phi \cos 30^\circ \right] + j V_L \left[2 \sin \phi \sin 30^\circ \right]$$

$$= 2 V_L \frac{\sqrt{3}}{2} \cos \phi + j V_L \cdot 2 \sin \phi \frac{1}{2}$$

$$= \sqrt{3} V L \cos \phi + j V L \sin \phi$$

$$= \sqrt{3} V L \left[\cos \phi + j \sin \phi \right] = \sqrt{3} V L \angle \phi = S_{load}$$

Q A 3- ϕ 1000 kVA 0.866 lag load is supplied by "Vee" connection at 400 V. Determine the kVA shared by each transformer at their pf.

(82)

Ans. $S_A + S_B = S_{\text{load}}$

$$= \sqrt{3} V I \angle \phi - 30^\circ$$


$$\phi + 30^\circ$$

$$\sqrt{3} V I \angle \phi = 1000$$


$$\phi = 30.00^\circ L$$

$$\phi + 30^\circ = 60.00^\circ$$

$$\phi - 30^\circ = 0.00^\circ L$$

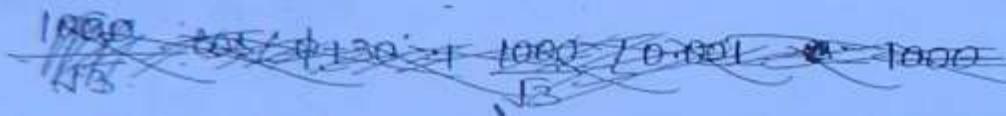
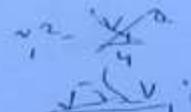
$$\frac{1000}{\sqrt{3}} \angle 60^\circ = S_C$$




$$\frac{1000}{\sqrt{3}} \angle 0.00^\circ L = S_A$$

$$S_A + S_B = \frac{1000}{\sqrt{3}} \angle 60^\circ + \frac{1000}{\sqrt{3}} \angle 0^\circ = 1000 \text{ kVA} \angle 30^\circ$$

Star connection \rightarrow

3 ϕ to 2 ϕ conversion \rightarrow

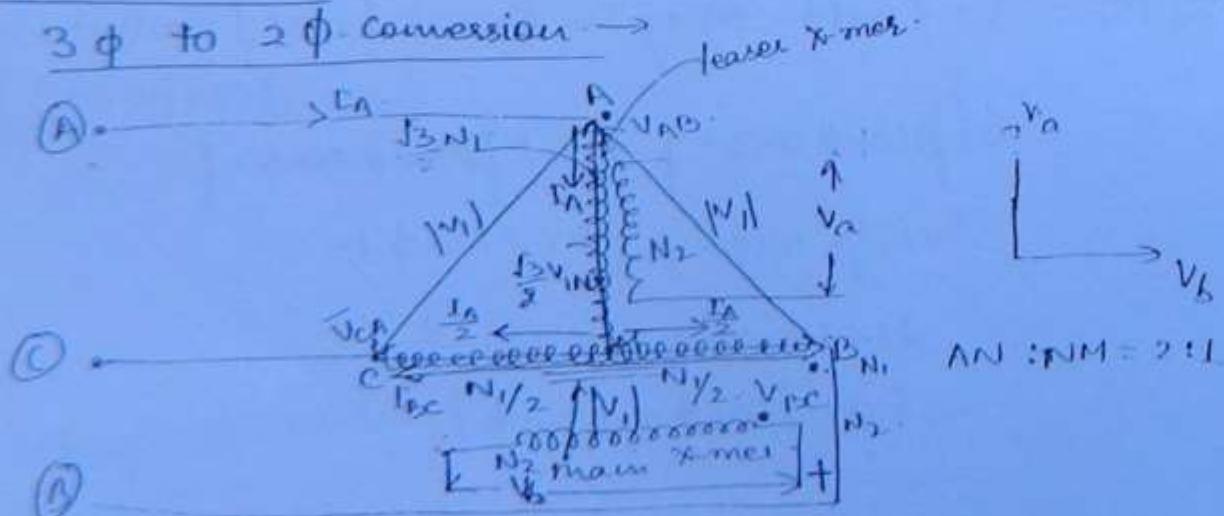

$$a_m = \frac{N_1}{N_2} \quad N_1 > N_2$$

$$a_1 = \frac{\sqrt{3} N_1 / 2}{N_2}$$

$$a_T = \frac{\sqrt{3} a_m}{2}$$

(63)

$$V_b = \frac{V_1}{a_m}$$


$$|V_a| = \frac{\sqrt{3} V_1 / 2}{a_T}$$

$$= \frac{\sqrt{3} V_1 / 2}{\sqrt{3} a_m / 2}$$

$$= \frac{V_1}{a_m}$$

$$= |V_b|$$

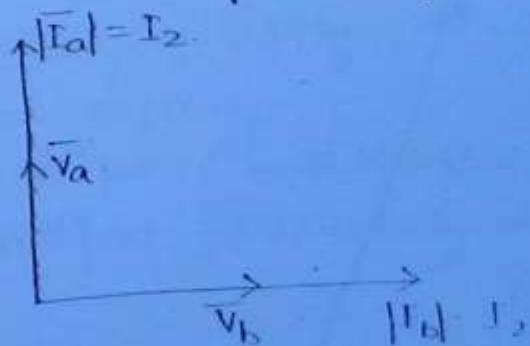* Five phase seq. heating is very high in Alternator. So, load must be balanced to avoid this. T-line transformation are also proposed. but it may or may not done.



Only if load is balanced,

$$P_A = \frac{P_2}{a_1} = \frac{2 P_2}{f_{1, \text{min}}}$$



$$\bar{I}_B = \bar{I}_{BC} - \frac{\bar{I}_A}{2}$$

$$\bar{I}_C = -\left(\bar{I}_{BC} + \frac{\bar{I}_A}{2}\right)$$

$$\frac{S_{min}}{S_{max}} = \frac{2}{\sqrt{3}} = 1.155$$

(84)

Q) two single phase furnaces A and B are supplied at 80V by means of Scott connected X-mes combination from a 3-Ø 6600 V system. The voltage of furnace A is leading. Cal. line current on 3-Ø side when furnaces take 500 kW and 800 kW respectively with furnace 'A' at unity pf and furnace B 0.7 pf lag.

Ans. let V_B be the ref. phasor

$$V_B = 80 \angle 0^\circ$$

$$V_A = 80 \angle 90^\circ$$

$$\bar{I}_A = |I_A| \angle 90^\circ$$

$$S_A = \frac{500}{1} = 500 = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi = \sqrt{3} \times 6600 \cdot I_A \times 1$$

$$S_B = \frac{800}{0.7} = 1142.86$$

$$I_A = \frac{500}{\sqrt{3} \times 6600} = 0.0443$$

$$I_A = 0.044 \angle 90^\circ$$

$$a_m = \frac{6600}{80} = 82.5$$

$$a_T = \frac{\sqrt{3}}{2} a_m \\ = 71.45$$

$$I_B = \frac{800 \times 10^3}{80 \times 0.7} \angle -\cos^{-1}(0.7)^\circ A$$

$$= 14285.71 \angle -45.57^\circ A$$

$$I_A = \frac{500}{80 \times 1.0} \angle 90^\circ = 62.50 \angle 90^\circ$$

$$I_{BC} = \frac{E_b}{a_n}$$

$$= 173.16 L - 45.57$$

$$E_A = \frac{E_a}{a_l}$$

$$= 87.47 L 90$$

(B)

$$\bar{I}_B : I_{BC} - \frac{E_A}{2}$$

$$= 206.67 L - 54.07 A$$

$$\bar{E}_c : -I_{BC} - \frac{E_A}{2}$$

$$= 145.19 L 146.6$$

Parallel operation of X-mes:

Need → when demand exceeds existing capacity.
 * In planning stage X-mes in pair may be planned
 to improve reliability of supply.

Advantage →

- 1) Improve reliability of supply.
- 2) Economic spare capacity.
- 3) Economic spare parts management.
- 4) Ease of transport (particularly in mines).


Disadv →

- 1) more costly
- 2) occupies more space and size
- 3) lower overall η.

conditions to be satisfied for parallel operation :-

1). Applicable to 1- ϕ and 3- ϕ A-mess.

1) Same polarity (MUST)

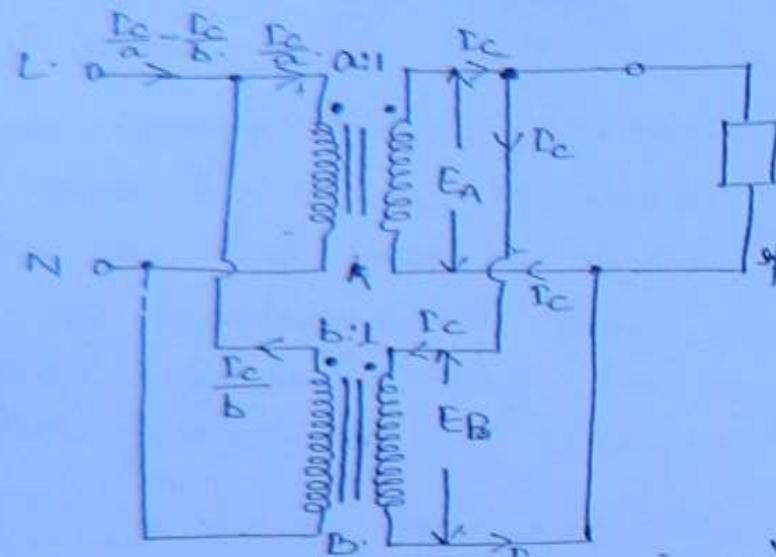

(86)

If $E_A > E_B$ at no load, the I_c will flow.

$$\Rightarrow \frac{V_L}{a} > \frac{V_L}{b} \\ b > a$$

2). Same Vout-ratio and Vout-rating (MUST)

Note - A small diff. in voltage ratio may be permitted if unavoidable.

3) $R_{ca} < R_{cb}$

$$\frac{R_c}{a} > \frac{R_c}{b}$$

when load is there, there is no $\leftrightarrow I_c$.

3) Same pu impedance for proportional load sharing.

[i.e. same name plate Z_{pu}]. [Desirable]

Same pu loading.


4) Same X_{min} for same pf operation (Desirable)

conditions applicable to 3- ϕ -A-mess only.


→ Same phase seq is must.

$\begin{matrix} R & Y & B \\ a & b & c \end{matrix}$


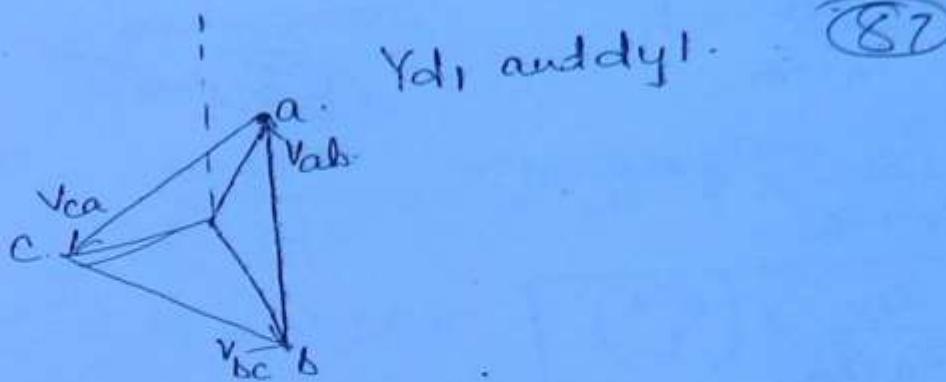
This means that \times -mers belonging to same phase of may alone be Nat.



→ Equal Volt. Ratio

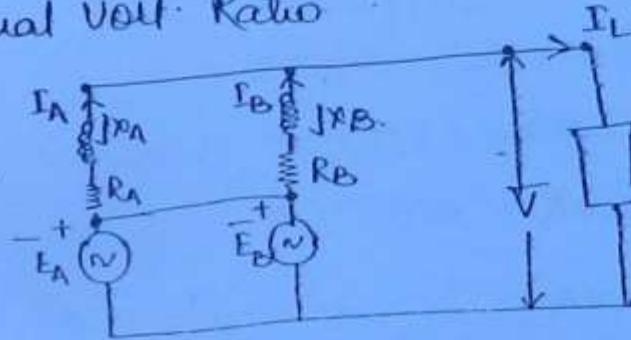

$$\bar{E}_A = \bar{E}_B$$

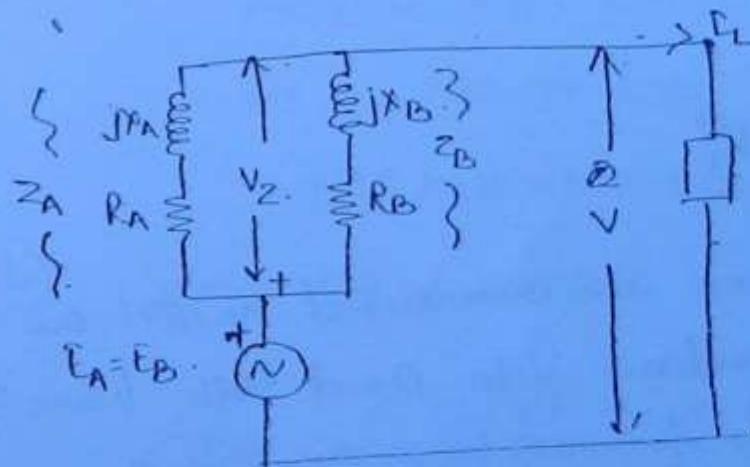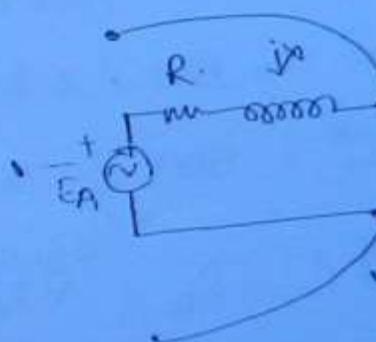

$$\bar{V}_Z \cdot \bar{r}_A \bar{z}_A = \bar{r}_B \bar{z}_B = \bar{I}_L \times (\bar{z}_A // \bar{z}_B)$$

$$= \bar{I}_L \times \left(\frac{\bar{z}_A \times \bar{z}_B}{\bar{z}_A + \bar{z}_B} \right)$$

$$r_A = \frac{z_B}{z_A + z_B} \times r_L, \quad r_B = \frac{z_A}{z_A + z_B} \times r_L$$

where r_A and r_B are the per unit resistances of the source impedances Z_A and Z_B respectively.

$$\begin{aligned}\vec{S}_A &= \bar{V} \vec{I}_A^* \\ \Rightarrow S_A^* &= \bar{V}^* \vec{I}_A \\ &= V^* \frac{\bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} \times \vec{I}_L \\ &= \frac{\bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} \times \bar{V}^* \vec{I}_L\end{aligned}$$

(88)

$$\boxed{\vec{S}_A^* = \frac{\bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} \times (\vec{S}_L^*)}$$

load \rightarrow 500 KVA, 0.8 pf lag.

$$\begin{aligned}\vec{S}_L &= 500 \angle \cos^{-1} 0.8 \text{ kVA} \\ &= 500 \angle 36.87 \text{ kVA}\end{aligned}$$

$$S_L^* = 500 \angle -36.87 \text{ kVA}$$

Similarly,

$$\begin{aligned}\vec{S}_B &= \bar{V} \vec{I}_B^* \\ S_B^* &= \frac{\bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} \times S_L^*\end{aligned}$$

Q. Two 150 KVA 1- ϕ X-mes are connected in $\pi\pi$ on both primary and secondary side and both have same V/A ratio. 1 transformer has an ohmic drop of 0.05% and resistive drop 21.6% of the load. On full load. Other has corresponding values of 0.75% and 4% respectively. Now will the following loads be shared.

- 180 KVA at 0.9 pf lagging
- 120 KVA at 0.6 pf lagging

c) 200 kW at unity PF

Ans. a) $S_L^* = 180 \angle -\cos^{-1} 0.9$

$$S_A^* = \frac{0.04 + j0.0075}{0.04 + 0}$$

(89)

$$S_A^* = \frac{0.5 + j0.8}{0.8 + j12} \times 180 \angle \cos^{-1} 0.9$$

$$S_A^* = 19.11 \angle 54.03^\circ$$

$$S_B^* = \frac{0.75 + j0.4}{0.8 + j12} \times 180 \angle \cos^{-1} 0.9$$

$$= 60.91 \angle -32.64^\circ$$

$$S_B^* = 60.91 \angle 32.64^\circ$$

= 60.91 KVA at 0.86 pf lag

$$S_A = S_L - S_B$$

$$= 180 \angle \cos^{-1} 0.9 + 60.91 \angle 32.64^\circ$$

$$= 119.73 \angle 23.47^\circ \text{ KVA}$$

= 119.58 KVA at 0.917 pf lag

b) $S_L^* = \frac{120}{0.6} \angle -\cos^{-1} 0.6$

$$S_B^* = \frac{0.75 + j4}{1.25 + j12} \times \frac{120}{0.6} \angle -\cos^{-1} 0.6$$

RE

$$S_A = S_L S_B$$

(c) At unity pf

$$S_i^* = \frac{200}{\sqrt{3}} \angle -\cos^{-1}(1)$$


$$\begin{aligned} S_A^* &= \frac{0.75 + j1}{1.25 + j12} \times 200 \angle -\cos^{-1}(1) \\ &= 67.464 \angle -4.67^\circ \end{aligned}$$

$$S_A = 67.464 \angle -4.67^\circ = 67.464 \text{ at } 0.9967 \text{ pf lag.}$$

$$\begin{aligned} S_B &= 132.8 \angle 2.37^\circ \text{ kVA i.e. } 0.999 \text{ pf lead.} \\ &= 132.8 \angle \cos^{-1}(0.9) - 67.464 \angle 4.67^\circ \end{aligned}$$

Phase diagram for →

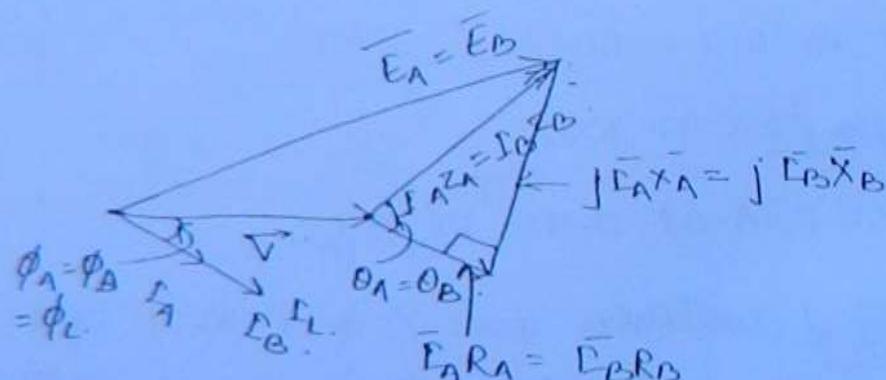$E_A = E_B$, lagging load., same $\frac{x}{R}$ ratio
i.e. $\theta_A = \theta_B$.




$$I_1 = I_A + I_B$$


Different $\frac{X}{R}$ ratio :-

$\theta_A > \theta_B$, $E_A = E_B$.

(91)

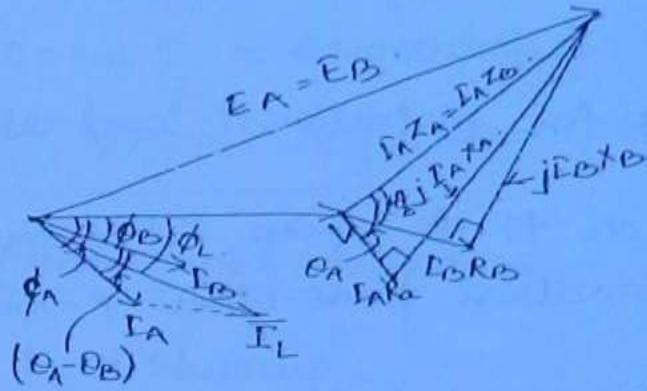

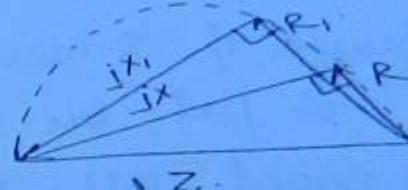$\frac{X}{R} \uparrow$, $P_f \downarrow$, $\phi \uparrow$



$$\underline{\underline{S}}_j^* \propto \frac{1}{\underline{\underline{Z}}_j(\omega)}$$

$$\underline{\underline{I}}_A \underline{\underline{Z}}_A(\omega) = \underline{\underline{I}}_B \underline{\underline{Z}}_B(\omega) = \underline{\underline{I}}_j \underline{\underline{Z}}_j(\omega) \\ = \text{const}$$

$$\frac{\underline{\underline{S}}_j^*}{S_j(\text{rated})} \propto \frac{1}{\underline{\underline{Z}}_j(\omega) \times S_j(\text{rated})} \Rightarrow \underline{\underline{I}}_j \propto \frac{1}{\underline{\underline{Z}}_j(\omega)}$$

$$\Rightarrow S_j^*(\text{pu}) \propto \frac{(V_{\text{rated}})^2}{\underline{\underline{Z}}_j(\omega) \times S_j(\text{rated})} \Rightarrow V_{\text{rated}} I_j \propto \frac{1}{\underline{\underline{Z}}_j(\omega)}$$

$$\Rightarrow S_j^*(\text{pu}) \propto \frac{V_{\text{rated}}^2 / S_j(\text{rated})}{\underline{\underline{Z}}_j(\omega)} \quad \underline{\underline{S}}_j^* \propto \frac{1}{\underline{\underline{Z}}_j(\omega)}$$

$$\propto \frac{\underline{\underline{Z}}_{\text{base}}(i)}{\underline{\underline{Z}}_j(\omega)}$$

$$\underline{\underline{S}}_j^* \propto \frac{1}{\underline{\underline{Z}}_j(\text{pu})} \quad \left| \begin{array}{l} \rightarrow \text{for proportional load change} \\ \underline{\underline{Z}}_j(\text{pu}) \text{ on its own base of} \\ \text{all } X-\text{mer must be same} \end{array} \right.$$

for proportional load sharing :—

$$S_j \propto S_j(\text{rated})$$

$$\Rightarrow \frac{S_j}{S_j(\text{rated})} = \text{const}$$

(93)

$$\Rightarrow S_j(\text{pu}) = \text{const}$$

thus $Z_j(\text{pu}) = \text{const}$ for proportional load sharing.

→ Which χ -mee will reach to its max. F.L. capacity?

where Z_{pu} is smallest from other χ -mee.

Q. Two single ϕ χ -mee rated 1000 KVA, 500 KVA resp. connected in π al on both H.V. and L.V. side.

They have equal volt. rating of 11 KV / 400 V. at their pu impedances are $0.02 + j0.07$ and $0.025 + j0.0875$ resp. What is the largest value of unity pf load that can be delivered by the π al combination at the rated voltage.

Ans. Trans A

1000 KVA

11 KV / 400

$0.02 + j0.07$

transformer B

500 KVA

11 KV / 400

$0.025 + j0.0875$

$$\frac{S_A^*}{S_B^*} = \frac{0.025 + j0.0875}{0.02 + j0.07}$$

$$= 1.25 \angle 0$$

$$= 1.25$$

$$S_A^* = S_B^* \times 1.25$$

Two X-mes \rightarrow same capacity
pu's same

$$\theta_A = 85^\circ$$

$$\theta_B = 80^\circ$$

(93)

$$= 1000 \text{ kVA} + 1000 \text{ kVA} \angle 5^\circ$$

$$= 2P \cos \frac{\delta}{2} \Rightarrow 2P \cos \frac{\delta}{2} = 2 \times 1000 \cos \left(\frac{\delta}{2} \right) = 1998 \cdot 1.$$

$$\boxed{\delta = \theta_A - \theta_B = 85^\circ - 80^\circ = 5^\circ}$$

$S \propto \frac{1}{Z}$ Classic old derivation \rightarrow

for proportional load sharing,

$$S \propto S_{\text{rated}}$$

$$\therefore \frac{S_A}{S_B} = \frac{S_A \text{ rated}}{S_B \text{ rated}}$$

$$\Rightarrow \frac{Z_B}{Z_A} = \frac{\sqrt[2]{S_A \text{ rated}}}{\sqrt[2]{S_B \text{ rated}}}$$

$$= \frac{\sqrt[2]{S_A \text{ rated}} / S_B \text{ rated}}{\sqrt[2]{S_B \text{ rated}} / S_A \text{ rated}}$$

$$= \frac{Z_{\text{base}}(B)}{Z_{\text{base}}(A)}$$

$$\frac{Z_A}{Z_{\text{base}}(A)} = \frac{Z_B}{Z_{\text{base}}(B)}$$

$$\Rightarrow \boxed{Z_A (\text{pu}) = Z_B (\text{pu}) \quad \text{pu if base}}$$

trans A will reach 1st at full load.

& trans A.

$$S_A = 1000$$

$$S_B = \frac{500}{1.25} = 400$$

(94)

$$S_A + S_B = 1400 \text{ kVA}$$

Since $S_j^* = \frac{1}{Z_j(\text{pu})}$

'A' would reach full load first

$$\therefore Z_A(\text{pu}) < Z_B(\text{pu}).$$

$$\frac{\bar{S}_B^*(\text{pu})}{\bar{S}_A^*(\text{pu})} = \frac{\bar{Z}_A(\text{pu})}{\bar{Z}_B(\text{pu})}$$
$$= 0.8$$

$$\frac{S_B^*(\text{pu})}{1 \angle -\phi_A} = 0.8 \angle \theta$$

$$S_B^* = 0.8 \angle -\phi_A$$

$$S_B = 0.8 \angle \phi_A$$

Thus $S_A = 1000 \angle \phi_A \text{ kVA}$

$$S_B = 0.8 \times 500 \angle \phi_A \text{ kVA}$$

$$S_L = 1000 \angle \phi_A + 400 \angle \phi_A$$

$$S_L \angle \theta = 1400 \angle \phi_A$$

$$1400 \text{ kVA}, \phi_A = 0^\circ$$

Unequal Voltage ratio \rightarrow

$$E_A > E_B$$


Step 1.

$$\begin{aligned}\bar{E}_A &= \bar{V} + \bar{I}_A \bar{Z}_A \\ &= \bar{I}_L \bar{Z}_L + \bar{I}_A \bar{Z}_A \\ &= (\bar{E}_A + \bar{E}_B) \bar{Z}_L + \bar{E}_A \bar{Z}_A\end{aligned}$$

$$\boxed{\bar{E}_A = (\bar{Z}_A + \bar{Z}_L) \bar{I}_A + \bar{Z}_L \bar{I}_B}$$

$$\text{Similarly } \bar{E}_B = \bar{V} + \bar{I}_B \bar{Z}_B$$
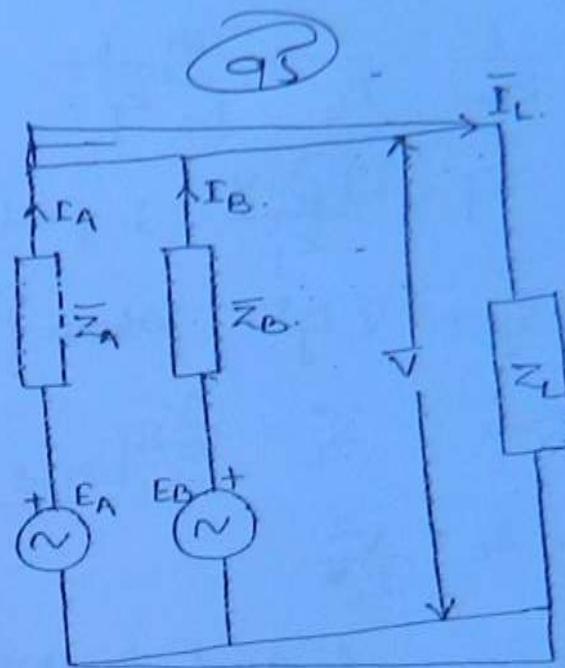
$$\Rightarrow \bar{E}_B = (\bar{Z}_B + \bar{Z}_L) \bar{I}_B + \bar{Z}_L \bar{I}_A$$



$$\begin{bmatrix} \bar{Z}_A + \bar{Z}_L & \bar{Z}_L \\ \bar{Z}_L & \bar{Z}_B + \bar{Z}_L \end{bmatrix} \begin{bmatrix} \bar{I}_A \\ \bar{I}_B \end{bmatrix} = \begin{bmatrix} \bar{E}_A \\ \bar{E}_B \end{bmatrix}$$

Solⁿ gives \$I_A\$ and \$I_B\$.

Step 2 $\bar{I}_L = \bar{I}_A + \bar{I}_B$

Step 3 $\bar{V} = \bar{I}_L \bar{Z}_L$

Step 4 $\bar{S}_A = \bar{V} \bar{I}_A^*$

$$\bar{S}_B = \bar{V} \bar{I}_B^*$$

Solⁿ by MILLMAN'S THEOREM or Nat generator method

Step 1 $V : I_{sc} > p$

Where $I_{sc} \geq 1$
for 25

marked notation form.

$$\frac{1}{Z_p} = \frac{1}{Z_L} + \sum_{j=1}^n \frac{1}{Z_j}$$

(96)

Step 2. $\Gamma_j = \frac{E_j - V}{Z_j} ; j = 1, 2, 3, \dots, n$

Step 3. $\bar{S}_j = \bar{V} \Gamma_j^*$, where $j = 1, 2, 3, \dots, n$.

Cat. Check $\rightarrow \bar{S}_L = \sum_{j=1}^n S_j$ $\boxed{\bar{V} \bar{V}^* = V^2}$

Also, $\bar{S}_L = \frac{V^2}{Z_L^*}$

Q two n-mems A and B are connected in parallel to a common load $\Delta + j 1.5 \Omega$. Their imp in second terms are. $Z_A = 0.15 + j 0.5 \Omega$ and $Z_B = (0.1 + j 0.6) \Omega$. Their no load terminal voltages are $E_A = 207 \angle 0^\circ$ and $E_B = 205 \angle 0^\circ$.

Find the power off and pf of each transformer.

Ans. $Z_L = \Delta + j 1.5 \Omega$

$Z_A = 0.15 + j 0.5 \Omega$

$Z_B = 0.1 + j 0.6 \Omega$

$E_A = 207 \angle 0^\circ$

$E_B = 205 \angle 0^\circ$

S_j and P_f

$S_j = V \Gamma_j^*$

$V = I_{sc} Z_p$

$$I_{sc} = \frac{E_A}{Z_A} + \frac{E_B}{Z_B} = \frac{207 \angle 0^\circ}{0.15 + j 0.5} + \frac{205 \angle 0^\circ}{0.1 + j 0.6}$$

$$= 732.105 \angle -76.63^\circ$$

$$\frac{1}{Z_P} = \frac{1}{Z_L} + \frac{1}{Z_A} + \frac{1}{Z_B}$$

$$Z_P = 0.2585 \angle 72.8498^\circ$$

(92)

$$V = E_{SC} Z_P$$

$$= 189.249 \angle -3.7802^\circ$$

$$E_A = \frac{E_A - V}{Z_A}$$

$$= \frac{207.10 - 189.249 \angle -3.7802^\circ}{(0.15 + 0.5j)}$$

$$= 42.2123 \angle -38.81^\circ$$

$$S_A = V E_A^*$$

$$= 8 \angle 35.03^\circ \text{ KVA}$$

$$S_B = V E_B^*$$

$$= 6.353 \angle 39.03^\circ \text{ KVA}$$

$$E_B = 38.57 \angle -42.87^\circ$$

Check →

$$S_A + S_B = S_L = 14.332 \angle 36.83^\circ \text{ KVA}$$


$$\text{Also, } \bar{S}_L = \frac{V^2}{Z_L} = 14.326 \angle 36.87^\circ \text{ KVA}$$

→ OKAY.

Phasor diagram → lagging pf

$$E_A > E_B$$

$$\theta_A = \theta_B$$

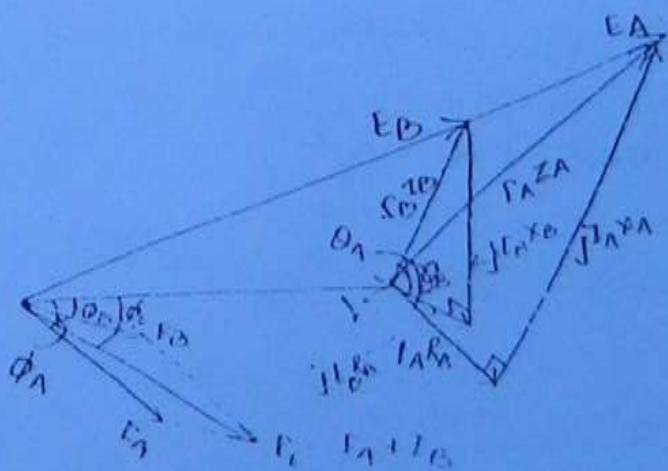

Q-38.

This is name plate rating of the load.

- Q. A 500 KVA, 1- ϕ x-mes A } having 0.015 pu resistance
 and 0.05 pu leakage reactance is to share a load of
 750 KVA at 400V and at 0.8 pf lagging with another
 250 KVA single- ϕ x-mes having 0.01 pu resistance
 and 0.05 pu leakage reactance. Their secondary no.
 load emfs are 405 V and 415 V respectively find
 a) circulating current at no load
 b) current supplied by each x-mes
 c) KVA, KW and pf of each x-mes.

(98)

Ans.

$$\text{pu} \quad Z_A = 0.015 + j0.05$$

$$Z_{\text{base}} (\text{A}) = \frac{400 \times 400}{500 \times 1000} = 0.32 \text{ ohms}$$

$$Z_A = 0.016725 \angle 73.30^\circ$$

$$Z_L = \frac{(400)^2}{750 \times 10^3} \angle 0.87(0.8)$$

$$= 0.21333 \angle 36.87^\circ \Omega$$


$$(Z_B)_{\text{actual}} = (0.01 + 0.05j) \times \frac{400^2}{250 \times 10^3}$$

$$= 0.03263 \angle 78.69^\circ \Omega$$

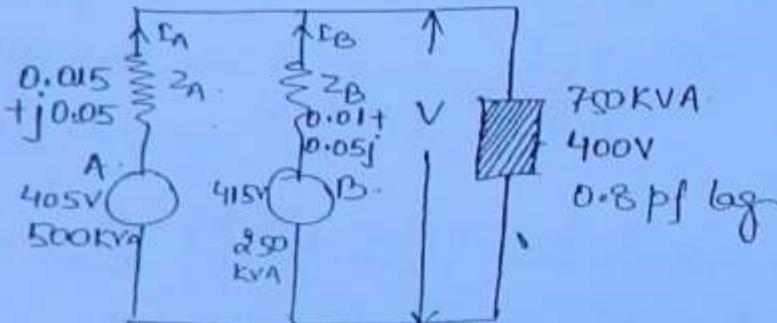Part A \rightarrow

$$I_c = \frac{415 \angle 0^\circ - 405 \angle 0^\circ}{Z_A + Z_B}$$

$$= 202.82 \angle -76.87^\circ \text{ i.e. at } \phi 0.2272 \text{ pf lag}$$



Part B →

$$I_{SC} = \frac{E_A}{Z_A} + \frac{E_B}{Z_B}$$

$$= 30932.35 \angle -75.15^\circ$$

$$Z_P = 0.01062 \angle 73.36^\circ$$

$$V = I_{SC} Z_P$$

$$= 392.23 \angle -1.79^\circ V.$$

$$I_A = \frac{E_A - V}{Z_A}$$

$$= \frac{405 - 392.23 \angle -1.79^\circ}{0.016725 \angle 73.301^\circ}$$

$$= 1066.3973 \angle -23.9131^\circ$$

$$I_B = \frac{E_B - V}{Z_B}$$

$$= \frac{415 - 392.23 \angle -1.79^\circ}{0.03263 \angle 78.69^\circ}$$

$$= 797.6 \angle -50.61^\circ$$

Part C

$$S_A = VI_A^*$$

$$= 418.902 \angle 28.12^\circ \text{ kVA i.e. } 363.46 \text{ kW at } 0.882 \text{ pf lag}$$

$$S_B = 312842 \angle 48.82^\circ \text{ VA}$$


$$= 312.842 \angle 48.82^\circ \text{ kVA}$$

i.e. 205.98 kW at 0.6584 pf lag.

Check

$$S_A + S_B = S_L = 720.09 \angle 36.95^\circ \text{ kVA}$$
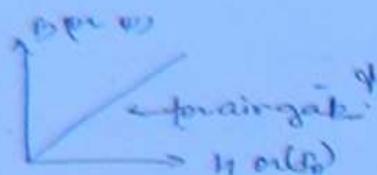
$$S_L = \frac{V^2}{Z_L} = 721.16 \angle 36.87^\circ \text{ kVA}$$





The ϕ will be sinusoidal with ϕ sinusoidal.

$\theta \quad \sin\theta$




| | | | |
|-----|------|---|----|
| 0 | 0 | } | 26 |
| 15° | 0.26 | | 24 |
| 30° | 0.50 | | 21 |
| 45° | 0.71 | | 16 |
| 60° | 0.87 | | 9 |
| 75° | 0.96 | | 4 |
| 90° | 1.00 | | |

(100)

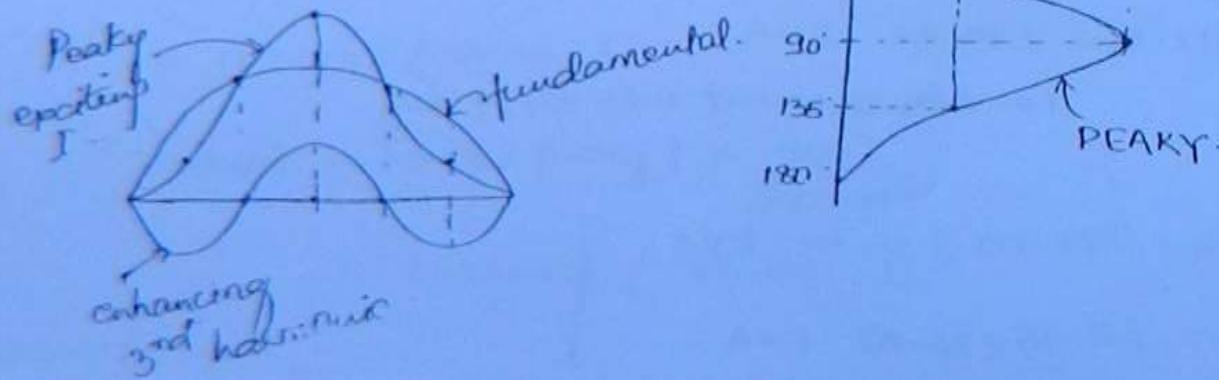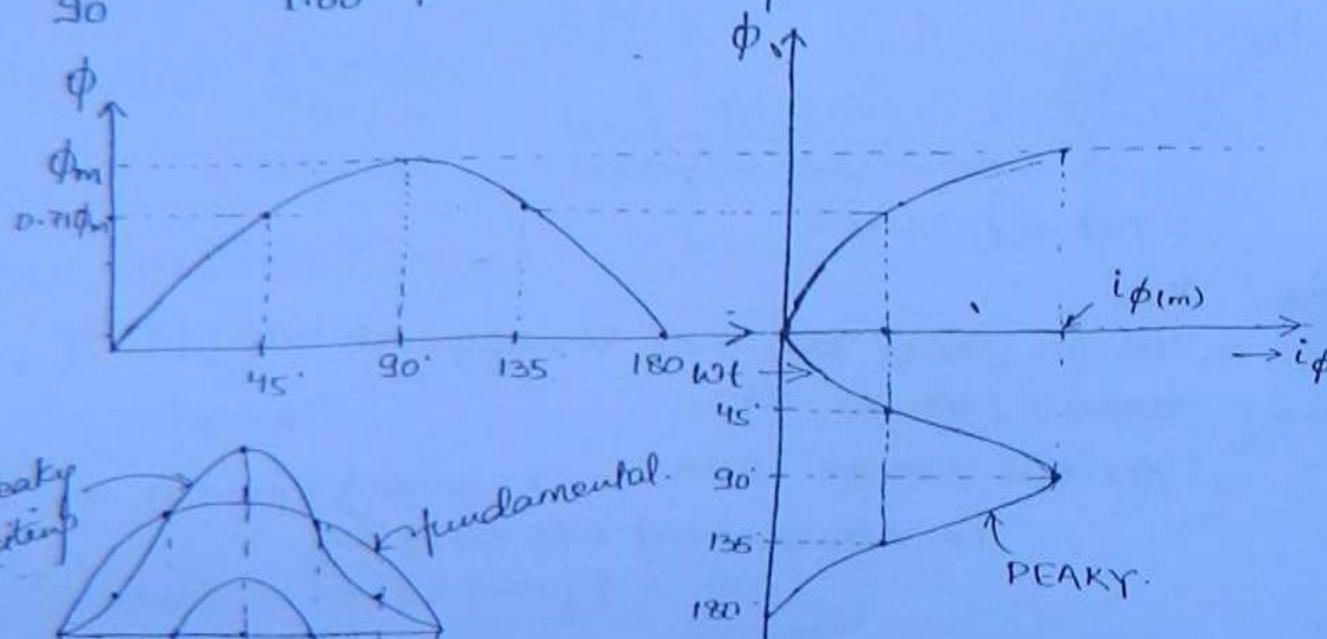

3rd harmonic $\rightarrow 3 \times 120^\circ = 360^\circ = 0^\circ$

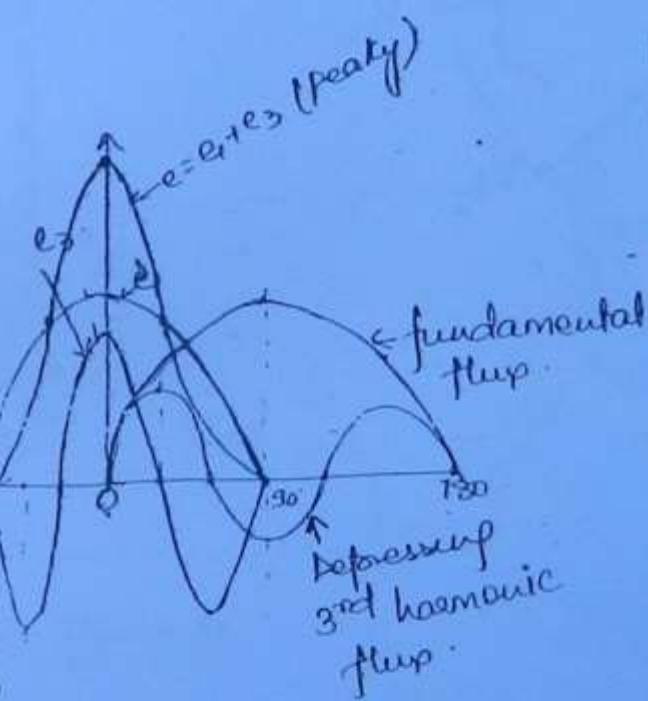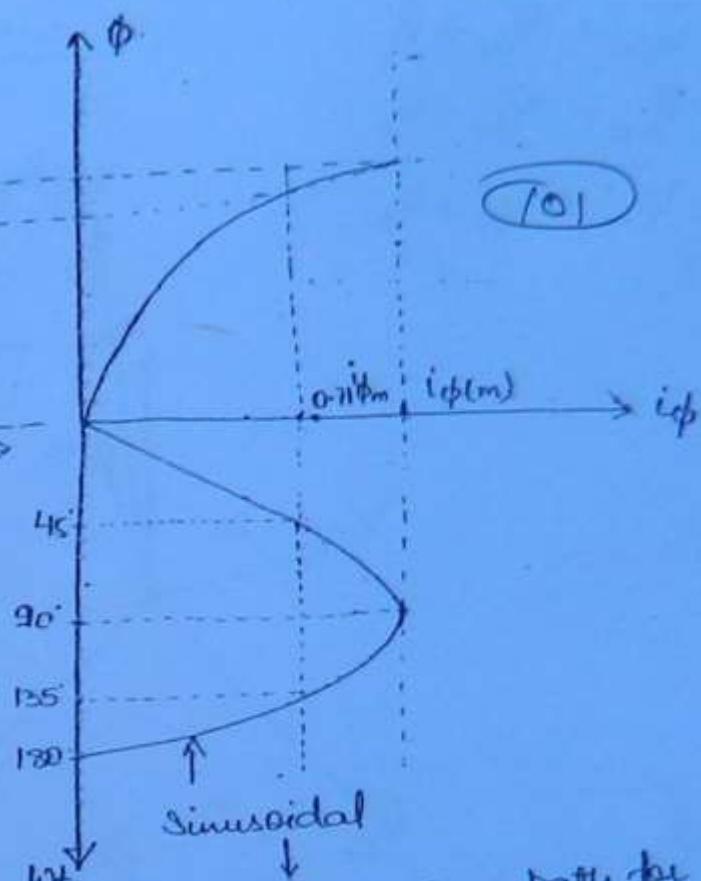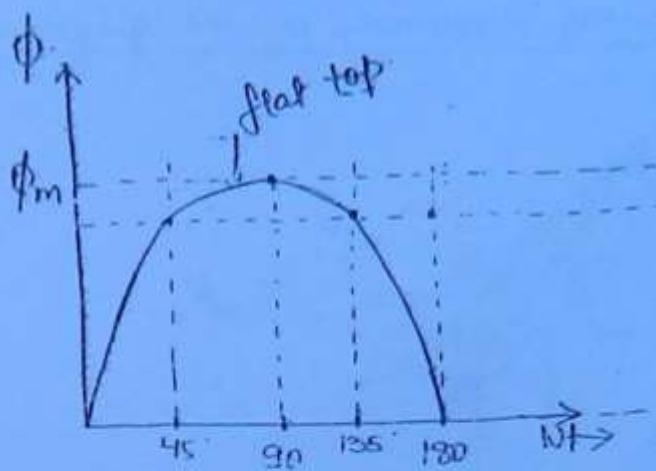
In phase \rightarrow zero seq. current. They would rise ^{together} together only through neutral of Y and inside A.



If there is no path for enhancing 3rd harmonic

$$E = \sqrt{2} N \phi_m \rightarrow E_{3\text{rd harmonic}} = 90\% \text{ of } E$$
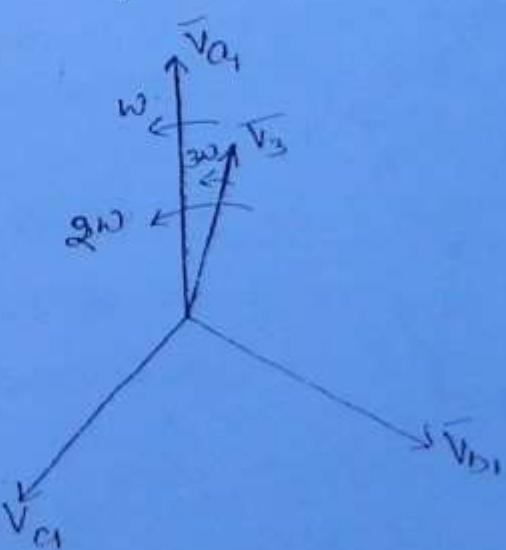
$$\begin{aligned} \omega &= 3\omega \\ &= \frac{\sqrt{2} N \times 3f \times 0.3 \phi_m \pi}{\pi} \\ &= 0.9 E \\ &= 90\% \text{ of } E \end{aligned}$$





$$\bar{V}_A, \bar{V}_B, \bar{V}_C = V_3$$

$$\bar{V}_{an} = \bar{V}_{a_1} + \bar{V}_3$$



$$\bar{V}_{bn} = -\bar{V}_{b_1} + \bar{V}_3$$

$$V_{cn} = \bar{V}_{c_1} + V_3$$

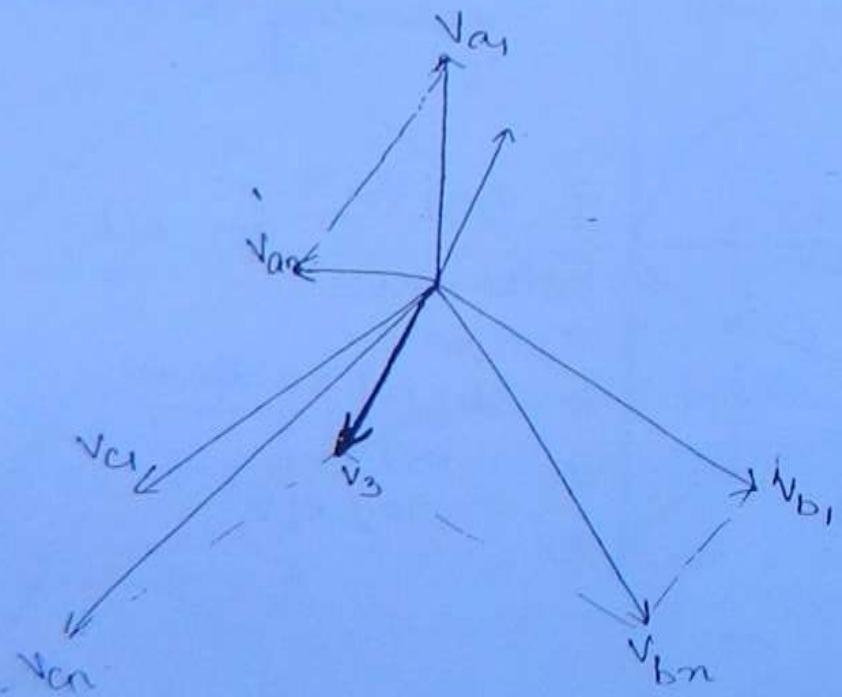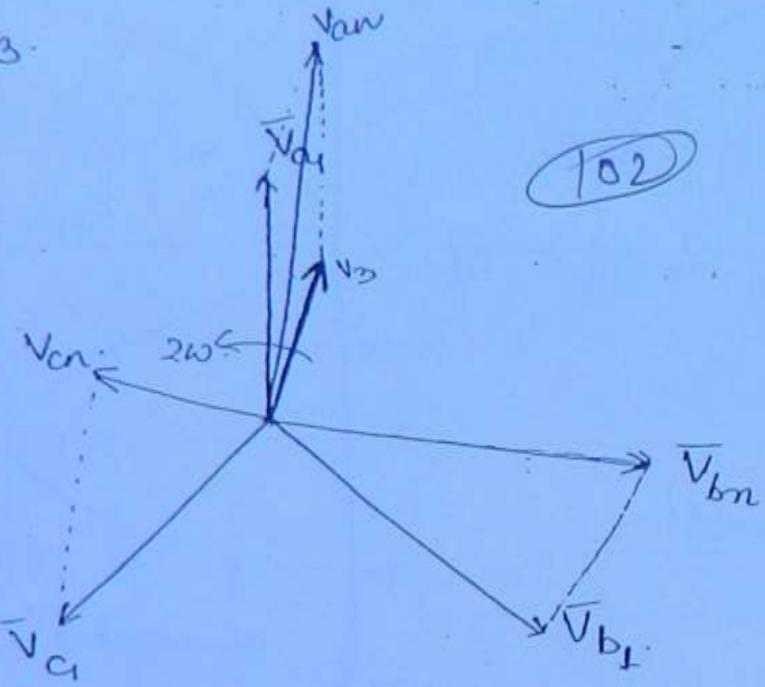


Oscillating neutral. at 2ω speed.

converging on a common point

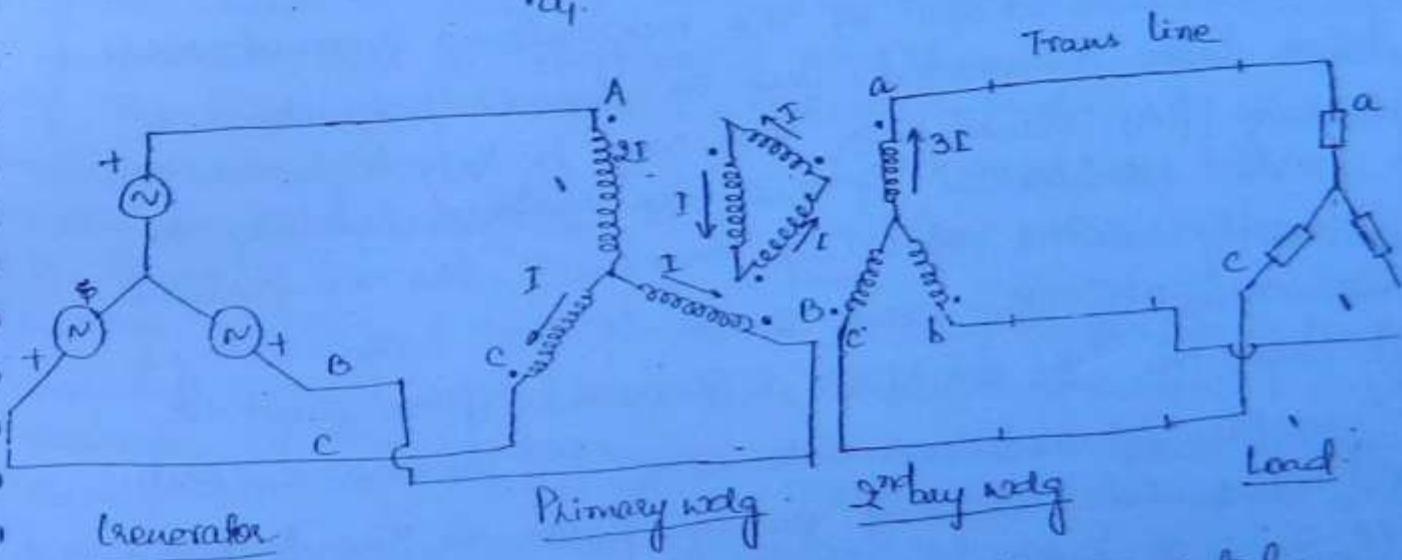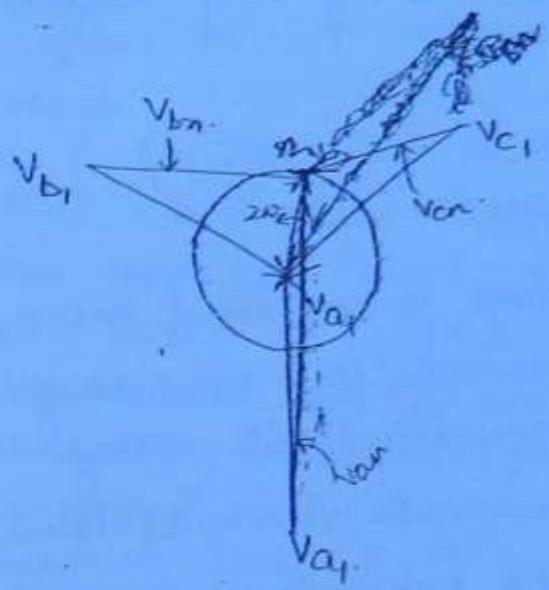

3rd harmonic is dominating or and invariably generated.
if Δ connection is either, it will circulate within the
if Y " " " , if 3rd harmonic is present then
also $V_L = V_{A\bar{B}} \bar{\oplus} V_{B\bar{C}} - V_{A\bar{B}} - V_{B\bar{C}}$
it will cancel out.

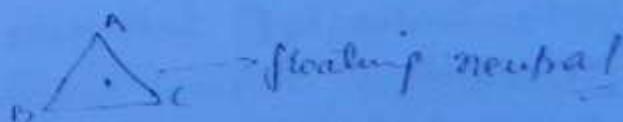3rd harmonic is due to ϕ flux is not pure sine



Δ - wind for flow of 3rd harmonic

In a λ -mer, any current which flows in only one leg is a magnetising current. Only mmf balance makes any current load current.

(104)

Magnetising current phenomenon:-

If magnetising sinusoidal voltage is impressed across the primary leg of a λ -mer, a sinusoidal flux must be established in the core to induce an equal & opposite voltage. If magnetisation curve of the core material would have been linear, the wave shape of the magnetising current would also have been sinusoidal. Due to economic consideration, the working flux density in the core is kept high and it causes partial saturation of the core material leading to non-linearity in the operating region of the magnetisation curve. Consequently the wave shape of the magnetising current required to establish a sinusoidal flux must be PEAKY containing dominant enhancing 3rd harmonic comp. This 3rd harmonic current easily flows in the primary leg of a 1- ϕ λ -mer in a single- ϕ CTF resulting in sinusoidal flux in the λ -mer core.

However, in a 3- ϕ λ -mer the 3rd harmonic components in the magnetising current of the 3- ϕ are all in phase. Obviously, unless they are provided with a path to flow, they would not move. The 3rd harmonic current would merely remain sinusoidal and with saturated and non-linear magnetisation curve would establish a non-sinusoidal flux which would be "FLAT TOP" and would contain depresso 3rd harmonic component in the ϕ wave in addition to the fundamental flux. The 3rd harmonic flux component would not establish in a λ -mer with independent cores.

path such as 3- ϕ shell type X-mas, 5 limbed core type X-mas and 3- ϕ bank of 1- ϕ X-mas. With this flat top flux, induced voltages in both the X-mas wedges would become 'PEAKY' containing enhancing 3rd harmonic components in all the 3- ϕ leading to problem of oscillating neutral that would cause stress to wedg insulation. However through the secondary line to neutral voltage would contain 3rd harmonic voltage in addition to the fundamental, line-to-line voltage would not contain 3rd harmonic component. If the secondary side of this star/star X-mas feeds a star connected load through a T-line and the neut. of the load is isolated, then unbalance load condition No problem will be experienced on the load side. However if the load itself become unbalanced, problem of floating neutral also known as neutral shift would crop up. It may be emphasised here that oscillating neutral phenomena is due to presence of 3rd harmonic components in induced voltage of phase wedge whereas floating neutral is a fundamental voltage comp. phenomena due to unbalanced load. However, if the load neutral is connected to secondary via T-line then presence of 3rd harmonic voltage would set up 3rd harmonics currents in the secondary coils and these current would flow through lines causing oblique wave communication interference. It is interesting note that these 3rd harmonic currents in the secondary wedge take the place of missing 5th harmonic components of primary current and restore harmonic variation to the flux making it almost sinusoidal with a very small component of 3rd harmonic flux sufficient enough to create the required 3rd harmonic current. A sinusoidal flux removes the problem of oscillating neutral but in this case at the cost of communication interference.

105

A star/star X-mas with isolated neutrals, while feeding unbalanced load, is unprincipled by the problem of

neutral is connected to the secondary neutral. The problem of neutral shift and choking can be addressed by connecting the load neutral to the secondary neutral and primary neutral to the source [generator] neutral. With this connection if the generated volt is sinusoidal 3rd harmonic currents would flow in the lines upto X-mos primary and may cause communication interference. Though flux would become and stabilize the X-mos oscillating neutral. However if the generated volt phase volt of the star connected generator itself contains 3rd harmonics, which invariably is the case, it would appear across the secondary to star line to neutral phase volt and create corresponding 3rd harmonic current that would flow through the T-line and cause communication interference.

(106)

Due to the above mentioned problem, a simple star-star connection for independent magnetic core X-mos is seldom used unless it is provided with a tertiary delta. The presence of tertiary delta in star/star connection, and of primary and/or secondary delta in other connections allows a closed path for the 3rd harmonic as well as for fundamental & freq to seq components. This prevents flow of 3rd harmonic currents through the T-line and thus the problem of communication interference is avoided. Also presence of delta wdg makes the flux sinusoidal resulting in elimination of the problem of oscillating neutral and hence tertiary delta wdg that is not designed to take load is also known as stabilizer wdg.


As mentioned earlier the above problem is applicable to 3φ X-mos with independent M CTs. However in a 3-limb core X-mos, magnetic CTs of the 3φ are interlinked. Therefore the 3rd harmonic flux finds very high reluctance path through the air outside the core. Therefore the flux leakages and therefore its magnitude will be

- negligible though it would cause heating of tank wall almost.
- Subsequently, core flux remains sinusoidal under all conditions. But the magnetising current in this case contain 5th and 7th harmonics and these can only be suppressed by using 5 limbed core χ -mer as this construction would allow setting up of 3rd harmonic flux. Despite the presence of 5th and 7th harmonic in magnetising current, 3-phase transformer units with 3 limbed core construction are finding increasing EHV applications even with star/star connection w/o tertiary delta. However, satisfactory operation requires balanced loads and if unbalance exceeds 10%, it would be prudent to include a tertiary.

X X

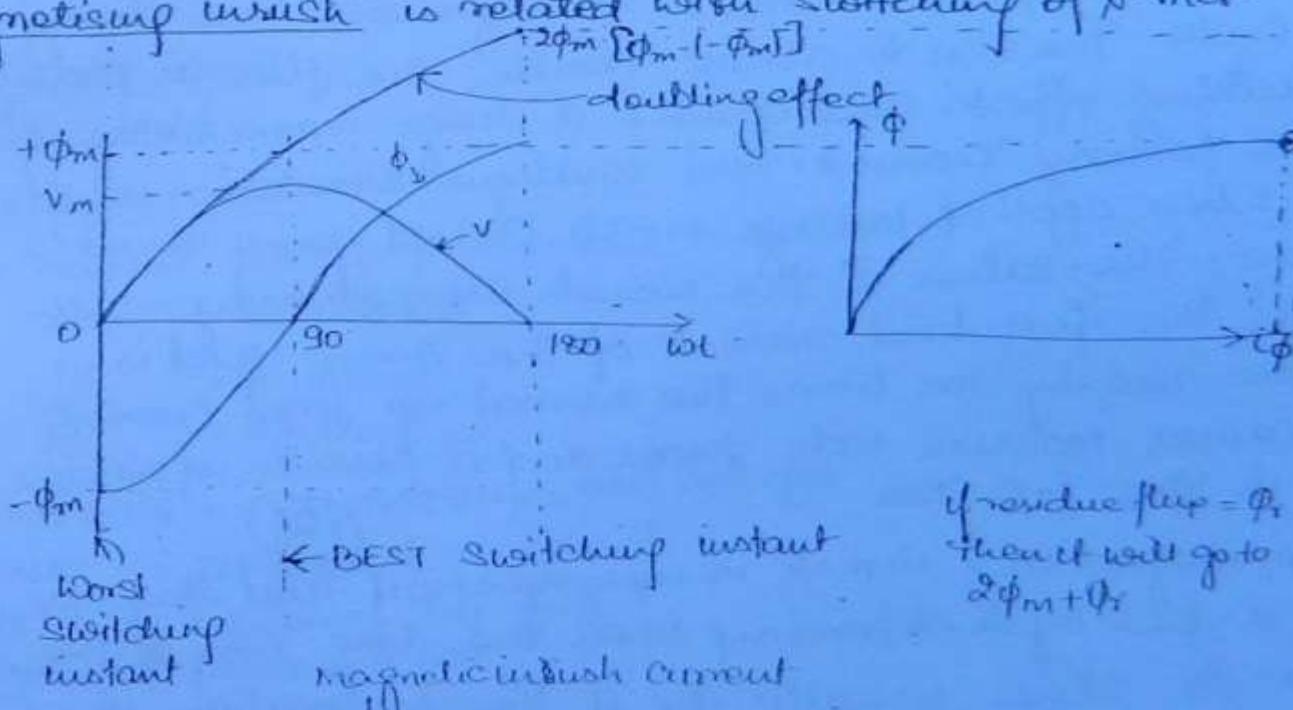
Q7

Magnetising inrush is related with switching of χ -mer.



If residue flux = Φ_r ,
then it will go to
 $2\Phi_m + \Phi_r$

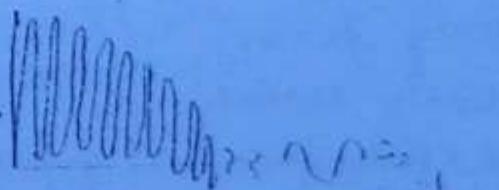→ To reach $2\Phi_m + \Phi_r$ will be root of times of normal full load current (or 5 times of full load current).



Under steady state condition, if the applied voltage is sinusoidal, the instantaneous value of common flux in the core with no residual flux changes from $-\phi_m$ to $+\phi_m$ in half cycle, to balance the applied voltage and lags its voltage wave by 90° . If the transformer is switched on at an instant when the applied voltage and is at its the peak then the flux rises for 0. and X-mer is switched on for with normal magnetising current. The same could happen when the applied voltage is at its negative at the switching instant. However, if the instant of switching, the applied volt. is at 0 and say going towards the, then the flux must change from 0 to ϕ_m in half cycle for a fluxless core and from residual flux ϕ_r to $\phi_r + \phi_m$ in a magnetised core during half cycle. The rise to almost double the flux is known as doubling effect. And causes a huge magnetising inrush in the primary current. And analogous situation would arise when applied voltage is at 0 and going towards negative. The value of the inrush current may reach 5 times the full load current of the X-mer. and is therefore nearly 100 times the normal no load current. This causes massive wedg forces and a possible short circuit in the p.s. The

(108)

The magnetising inrush is unsymmetrical and stage for quite a few cycle depending upon the time const of the system. It stays usually for a longer duration if switched on at no load. Since magnetising inrush is a primary wedg phenomena undesired tripping through X-mer differential protection may occur. In order to void such undesired tripping during switching, stage differential protection in large transformers is provided with a 2nd harmonic restrained feature.

"1 stepped core X-mer \rightarrow circular X-section should be less.

$$\frac{\text{Circum.}}{\text{Area.}} = \frac{d}{\pi r} = \frac{d \times \pi}{\pi r^2} = \underline{\text{mini for circle}}$$


Saving Cu and for the same I, Saving on η as copper loss.)

Yoke $=$ higher than 20% of core X-section limb.
X-sec.

core type and shell type

(copper) iron at outer iron sandwiched the wedg(copper).
(inner shield)

spiral wedg helix wedg

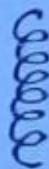

more strong.

to wedg where

I > 100A, spiral
wedg is used.

109

cooling methods \rightarrow

air Natural cooling for smallest X-mer

AN. \rightarrow Air Natural

AF \rightarrow Air forced

or AB \rightarrow Air Blast

'ONAN' or 'ON' \rightarrow Oil natural, air Natural

ONAF \rightarrow Oil natural air forced

OFAF \rightarrow Oil forced Air forced

mineral oil (Petroleum & C_{100})

and No of synthetic oils also used.

Bushing \rightarrow

Porcelain or hollow Cylinders in X-mer for wedg from $\frac{\text{perimeter}}{\text{diameter}}$ $\times 100$
highly polished Surface. $\left\{ \begin{array}{l} \text{shape} \\ \text{size} \end{array} \right\}$ \rightarrow perfect insulation & full

switches Relay \rightarrow cover coated with (Silicon oil) breather
pipe 50° inclination dry - blue - $\left\{ \begin{array}{l} \text{size} \\ \text{shape} \end{array} \right\}$ \rightarrow insulation

Explosion Vent (Diaphragm) \rightarrow



magnetostriiction \rightarrow

rapid fluctuation and variation of ϕ

Tap changer \rightarrow




(110)

\rightarrow tapping on HV side.


due to 1) low ω_L in HV side

2) due to smooth variation of voltage


Back to Back Submersible \rightarrow

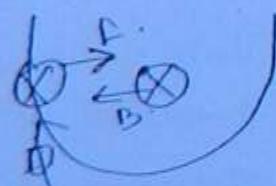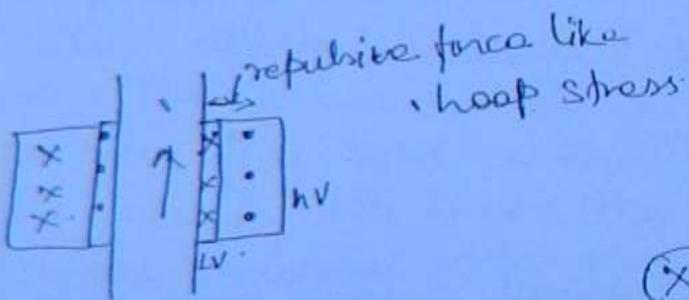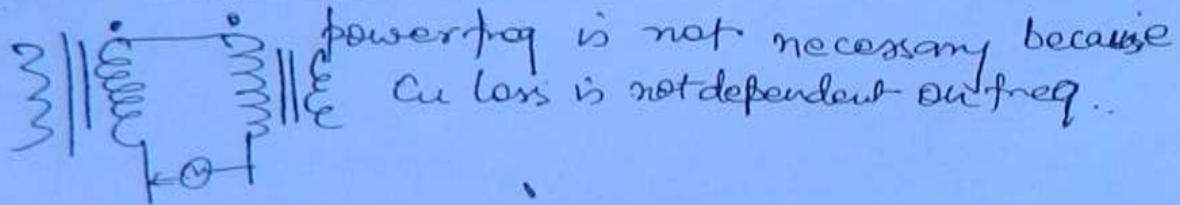


force
dirn
by Fleming's left
Hand rule

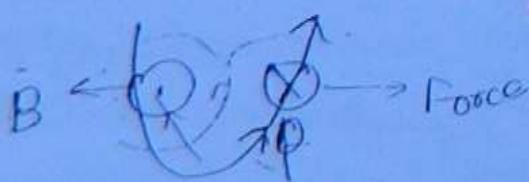

Fleming's left
hand rule
(motion)

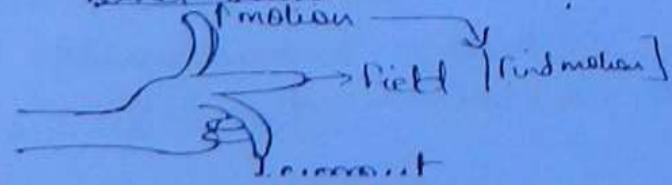


DC M/C

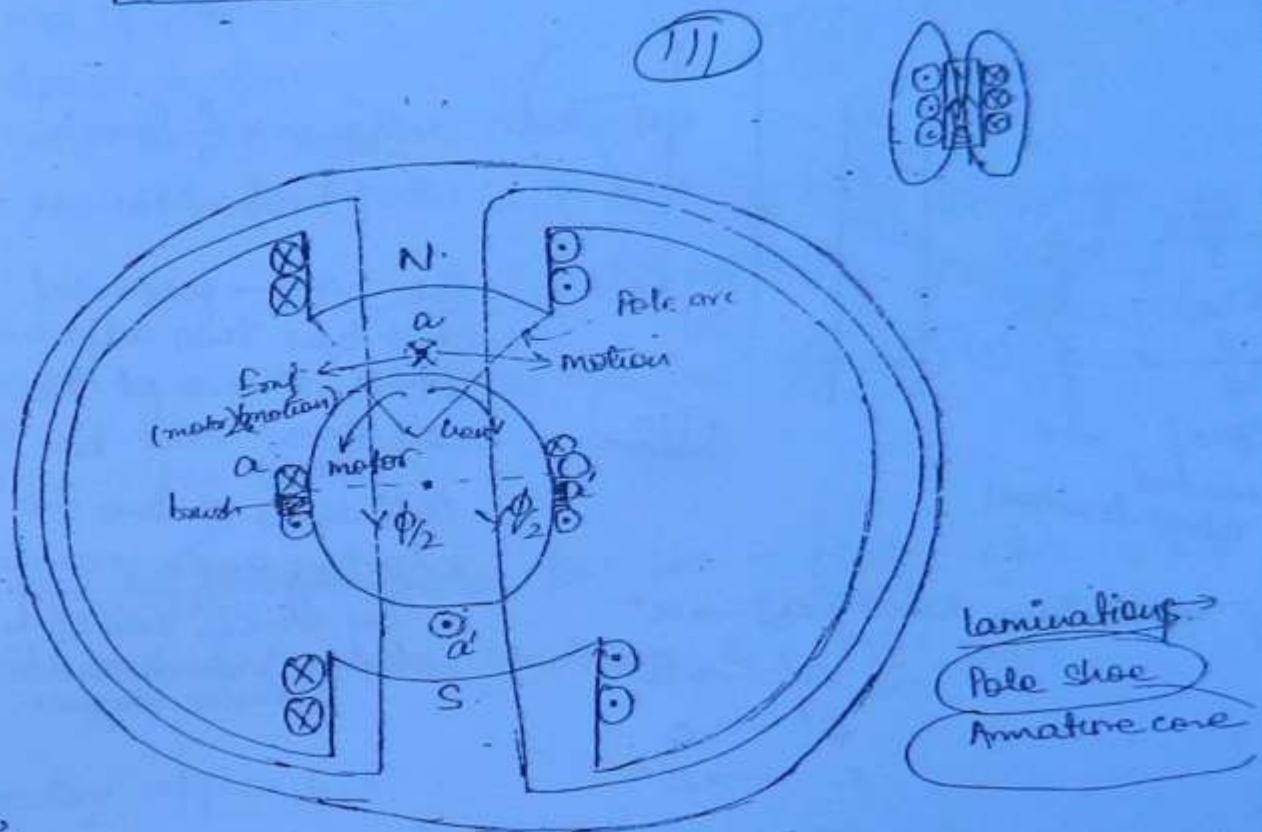

At aa' ,
 $\phi = \phi_{\text{max}}$.

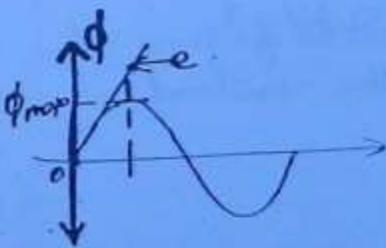
$$e = \frac{d\phi}{dt} = 0 \text{ for } \phi_{\text{max}}$$



at aa' ,

$$\text{flux} = 0.$$

$$e = m\omega \phi = \frac{d\phi}{dt}$$

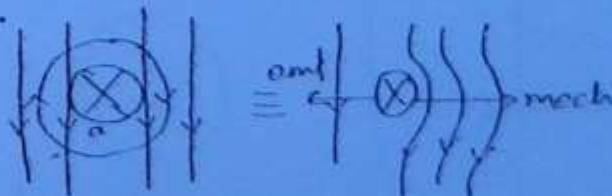


back emf \rightarrow max (0)

by Fleming's right hand rule \rightarrow for generated Emf (Generator Action)


Fleming's left hand rule for current carrying conductor \rightarrow motor Action experiences force.

Fleming's right hand rule

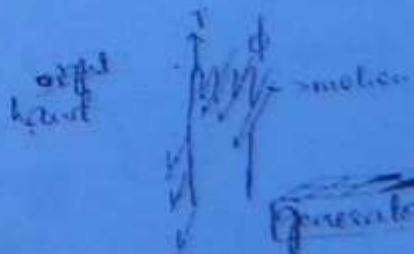motion of conductor
dir. of field
 \perp (current dir.)




for motor left hand

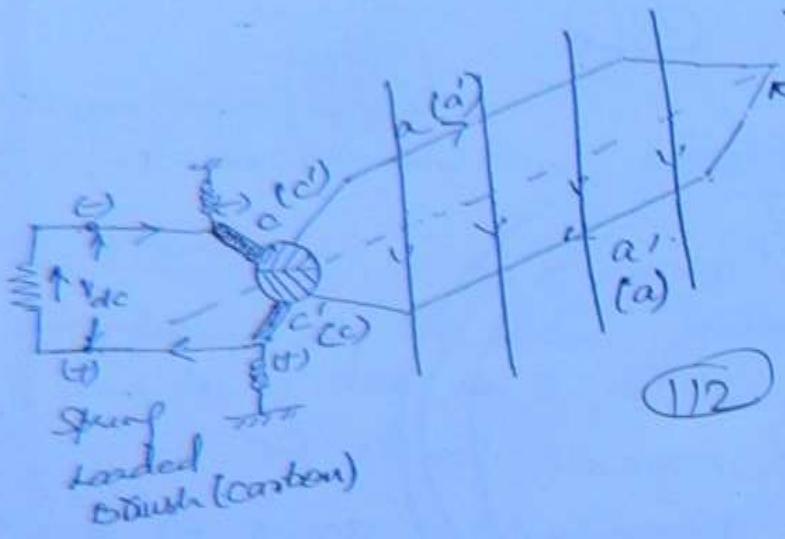


half revolution later $\{a\} \rightarrow a'$
 $a' \rightarrow a$
 $c' \rightarrow c$
 $c \rightarrow c'$

dc m/c → Armature wedges → on rotor

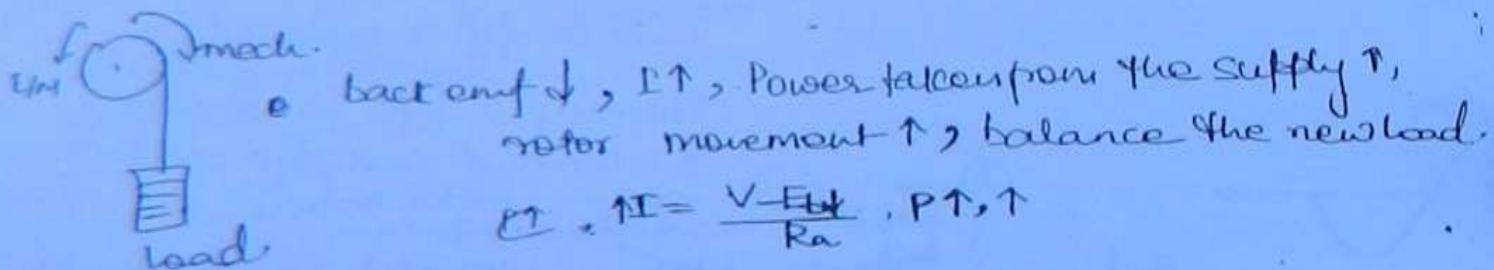

Induced Emf: →

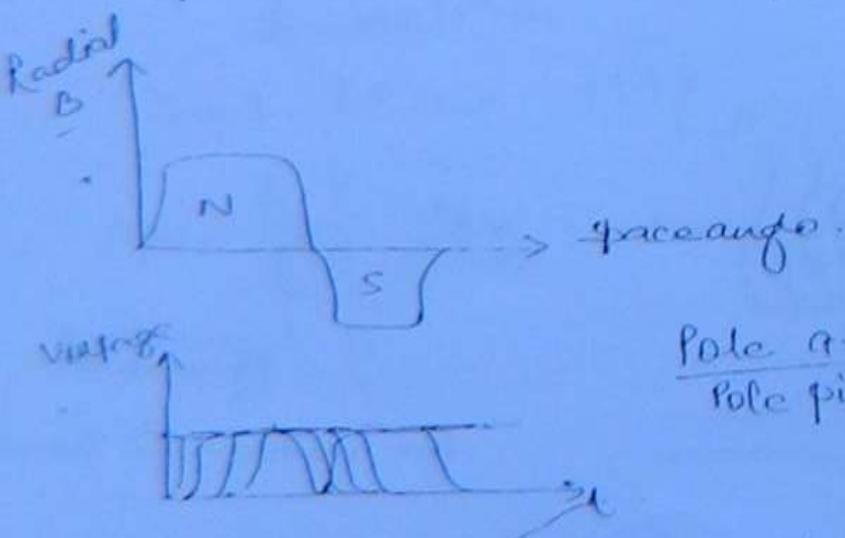

$$\frac{\text{Pole arc}}{\text{Pole pitch}} = 0.7$$

Flux per pole (wb) = ϕ \rightarrow magnetic lines entering or leaving the pole.

$P \rightarrow$ no. of poles.

$NR \rightarrow$ Speed in rpm.

$Z \rightarrow$ total no. of armature conductors.

(1/3)

$A \rightarrow$ No. of parallel paths = 2 for wave wdg (low capacity, high volt)
= P for lap wdg. (high capacity, low volt)

Flux cut by one conductor in one rev = $(P\phi)$ wb.

No. of rev. per sec = $\frac{N}{60}$

Flux cut by one conductor per sec. = $\frac{NP\phi}{60}$ wb/s i.e Volt

Av. induced emf in one conductor $e_c = \frac{P\phi N}{60}$ Volts.

Alternative approach \rightarrow

Flux cut by one conductor in 1 rev = $P\phi$ wb.

time taken in one rev = $\frac{60}{N}$.

Av. emf induced in one conductor = flux cut
time taken

$$e_c = \frac{P\phi}{60/N} = \frac{NP\phi}{60}$$

Blv approach \rightarrow




$$B = \frac{\phi}{A} = \frac{P\phi}{ADL}$$

$$V = \frac{RN\phi}{60} = \frac{RAN}{60}$$

$$BSV = \left(\frac{P\phi}{ADL} \right) \times (L) \times \frac{N}{60} \times 2 \times 8$$

$$\frac{P\phi N}{60}$$

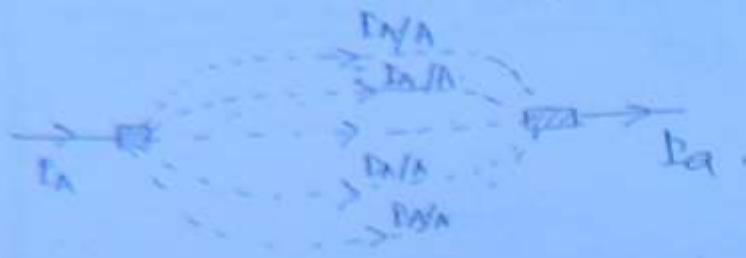

No. of conductors in series per parallel path = $\frac{Z}{A}$
 induced emf in the armature of a DC m/c,

$$E_a = \frac{e_c \times Z}{A}$$

$$E_a = \frac{P\phi N}{60} \times \frac{Z}{A} \times N$$

(1/4)

for 2 pole m/c $\rightarrow P=2$

$$\boxed{P/A = 1} \text{ for lap and wave wdg both.}$$

Alternative form for "E_a" \rightarrow

$$\text{since } N = \frac{60 \omega_m}{2\pi}$$

$$\boxed{\omega_m = \frac{2\pi N}{60}}$$

$$\therefore E_a = \frac{P\phi Z}{60 A} \times \frac{60 \omega_m}{2\pi}$$

$$= \left(\frac{PZ}{A\pi^2} \right) \times \phi \omega_m$$

$$\boxed{E_a = k \phi \omega_m}$$

ω_m \rightarrow mechanical angular
velo. in mech rad.

$$\text{where } k = \frac{PZ}{2\pi A}$$

$$\begin{array}{l} T_a \quad \text{- Armature force develops } P_a = E_a T_a \\ \text{Also } P_a = T \omega_m \end{array}$$

$$T \omega_m = E_a T_a$$

$$k \phi \omega_m T_a$$

$$\boxed{T_a = K \phi T_a} \quad \text{where } K = \frac{PZ}{2\pi A} \text{ - const}$$

mini possible value of $k = \frac{1}{2\pi}$

k value = very large.

BIL & Analogy

(115)

$$B = \frac{P\phi}{\kappa D L}$$

$$(cond) F = B I L = \frac{P\phi}{\kappa D L} \times \frac{I_a}{A} \times L$$

$$F = \frac{I_a}{A}$$

$$\frac{P\phi}{\kappa D L} \cancel{\times L}$$

$$= \frac{P\phi I_a}{\kappa D A}$$

$$\frac{P\phi}{\kappa D A}$$

$$T = Z \times T_{cond}$$

$$= Z \times F_{cond} \times \frac{D}{Z}$$

$$= Z \frac{D}{2} \times (B_{cond} L)$$

$$= \frac{Z D}{2} \times \frac{P\phi I_a}{\kappa D A}$$

$$= \left(\frac{PZ}{2\kappa A} \right) \phi I_a$$

$$\boxed{T = k \phi I_a}$$

Q. Find the Ampere turns/pole of std excitation required for single gap of a two pole dc gen. with the following particulars:-

200V on No load at 2000 rpm, Amature length 32cm
effective gap length 0.8 cm, pole circ = 30 cm, 200 amature conductors

Ans $\frac{A_t}{1} = 9$ N = 2000 rpm l = 32cm
Z = 200 P = 2 k = $\frac{PZ}{2\kappa A} = 31.83$

$$I_a = 200V$$

$$I_a = \frac{PZ}{2\kappa A} \phi_{wm} = 92$$

$$200 = \frac{\phi \times 200 \times 2000}{60} \times \frac{2}{2}$$

$$\rightarrow \phi = 0.03 \text{ wb/pole}$$

$$\begin{aligned}\text{Area per pole} &= \text{Pole Arc} \times \text{Pole length} \\ &= 0.3 \times 0.3^2 \\ &= 0.096 \text{ m}^2\end{aligned}$$

$$B = \frac{0.03}{0.096} \text{ Tesla}$$

(116)

$$= 0.3125 \text{ Tesla}$$

$$H = \frac{B}{\mu_0} \text{ At/m}$$

$$= \frac{0.3125}{\mu_0}$$

$$\begin{aligned}\text{MMF/pole} &= H \times \text{lgap} \\ &= \frac{B}{\mu_0} \times \text{lgap}\end{aligned}$$

$$\boxed{N = \frac{NI}{l}}$$

$$= \frac{0.3125}{4\pi \times 10^{-7}} \times 0.008 \text{ At/pole}$$

$$= 1989.44 \text{ At/pole}$$

Use of direct formula →

$$\text{mmf} = \phi \times \text{reluctance}$$

$$0.03 \times \frac{\text{lgap}}{\mu_0 \times \text{Area}}$$

$$\boxed{\phi = \frac{NI}{\text{reluctance}}}$$


$$NI = \phi \times \frac{l}{\mu_0 A}$$

$$= 0.03 \times 0.008$$

$$4\pi \times 10^{-7} \times 0.3 \times 0.32$$

$$1989.44 \text{ At/pole}$$

Power Balance in DC m/c:

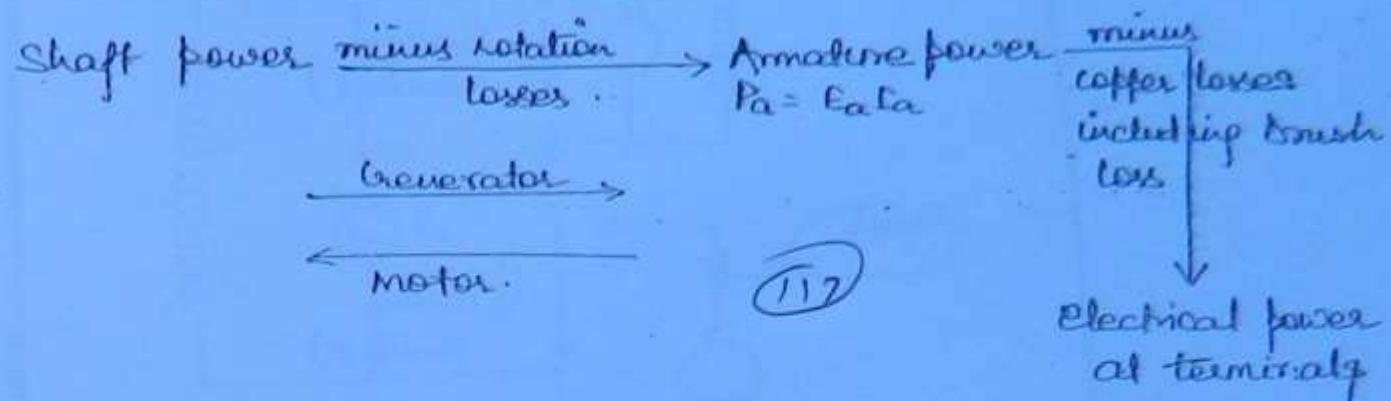

Generator →

Shaft power \rightarrow prime mover

Rotational losses $\rightarrow P_f + w + P_{mech} + P_{LL}$

\uparrow mech. losses
 bearing,
 brush contact,
 windage

\uparrow magnetic
 loss.
 (iron loss)
 or
 core loss

Stray
 load loss or
 unaccounted
 loss.

$$P_f + \frac{N}{2\pi m^2} I_a^2 + \frac{R_a}{2\pi m^2} I_a$$

Brush loss \rightarrow const


$$\text{as } R \propto \frac{1}{L} \quad L \rightarrow \text{temp}$$


$$I \uparrow, t \uparrow, R \uparrow; I^2 R = K.$$

$$I \downarrow, t \downarrow, R \downarrow; I^2 R = K.$$

NoData

Classification of DC M/C →

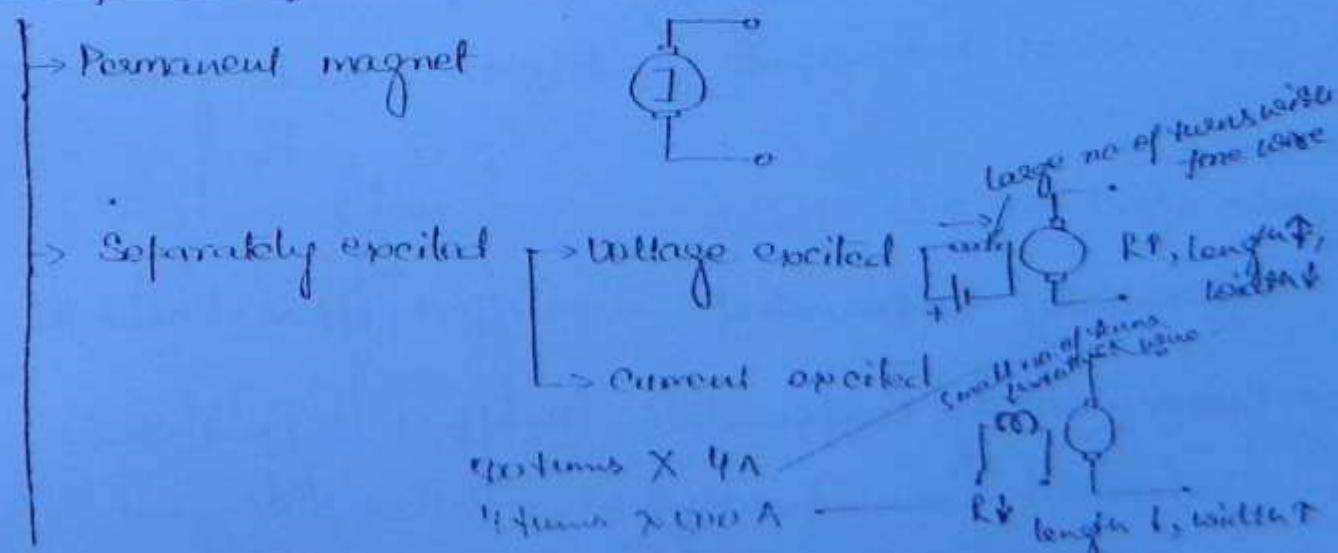

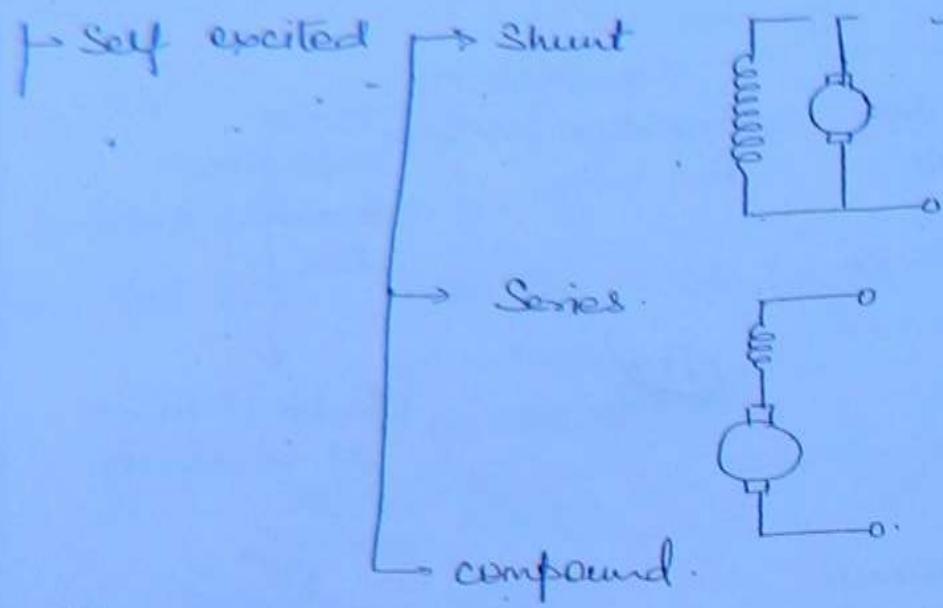

11B


18/iii

compound m/c →


Criterion 1 →

Electrical connection of Shunt m/c :-

long shunt

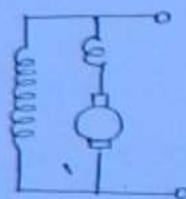

short shunt

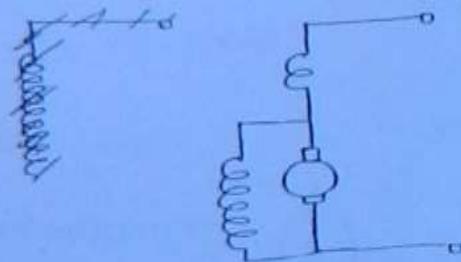


Criterion 2 →

magnetic effect of series f.t. on. 3. if. 1. 1.


→ differentially compounded → m.e.f. oppose shunt f.t.

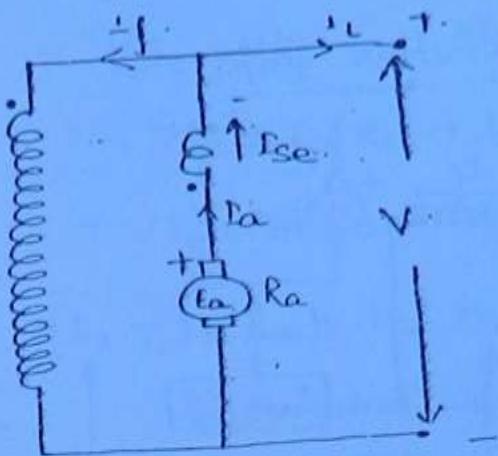→ cumulatively compounded → m.e.f. support shunt f.t.




719

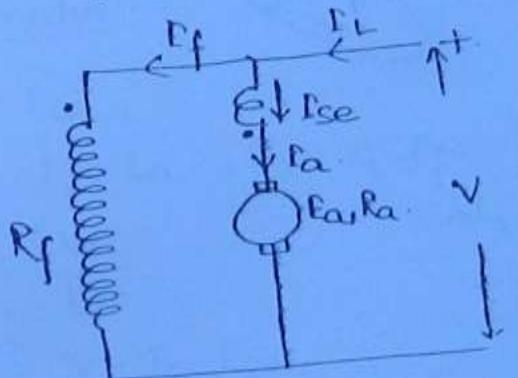
long shunt cumulatively compounded generator



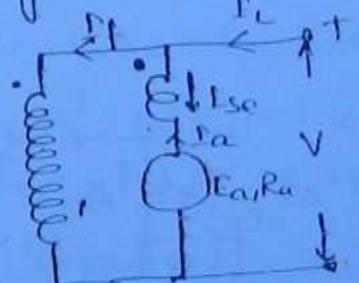long shunt differentially compounded motor.



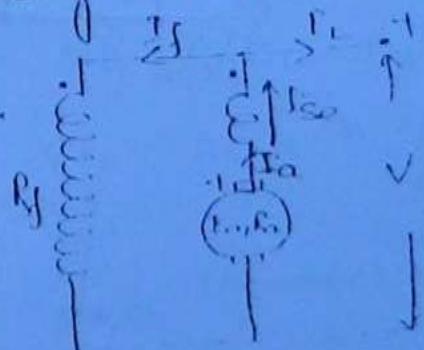long shunt cumulatively compounded motor.



long shunt differentially compounded generator

Power balance in separately excited m/c :-

For generator →


$$E_a = V + I_a R_a$$

multiplying by I_a .

$$E_a I_a = V I_a + I_a^2 R_a$$

$$\Rightarrow P_a = V I_L + I_a^2 R_a$$

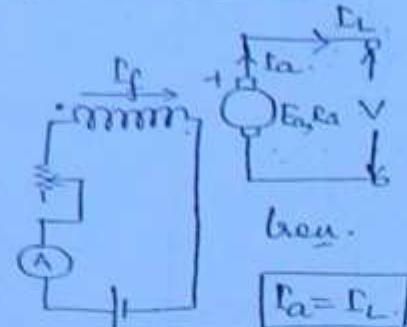↑ ↑ ↑
Amature o/p power Power Amature Cu loss.



(120)

for motor

$$E_a = V - I_a R_a$$

or

$$E_a I_a = V I_a - I_a^2 R_a \quad \leftarrow I_L, I_a$$

$$\Rightarrow P_a = V I_L - I_a^2 R_a$$

↑ ↑
Amature o/p power Amature Cu loss.

Power balance in short shunt m/c →

$$I_a = I_f + I_L$$

$$I_L = I_{se}$$

$$I_f = \frac{V_f}{R_f}$$

$$V_f = V + I_{se} R_{se}$$


$$= E_a - I_a R_a$$

$$E_a = V + I_a R_a + I_{se} R_{se}$$

multiply by I_a

$$E_a I_a = V I_a + I_a^2 R_a + I_{se} I_a R_{se}$$
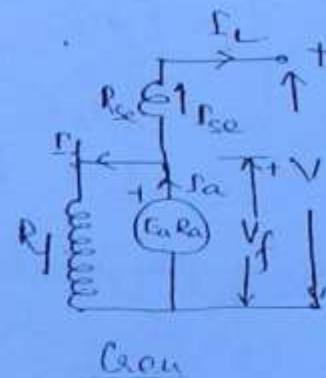
$$= V(I_a + I_f) + I_a^2 R_a + (I_{se} + I_f) I_{se} R_{se}$$



$$\begin{aligned}
 &= V I_L + V E_f + I_a^2 R_a + I_{se}^2 R_{se} + I_f I_{se} R_{se} \\
 &= V I_L + I_a^2 R_a + I_{se}^2 R_{se} + I_f (V + I_{se} R_{se}) \\
 &= V I_L + I_a^2 R_a + I_{se}^2 R_{se} + I_f V_f.
 \end{aligned}$$

for motor →

$$\mathbf{F}_L = \mathbf{F}_{se}$$

$$\mathbb{E}_L = \mathbb{E}_f + \mathbb{E}_{\alpha} \Rightarrow \mathbb{E}_{\alpha} = \mathbb{E}_L - \mathbb{E}_f$$

$$\Sigma_f = \frac{V_f}{R_f}$$

$$V_f = V - E_{se} R_{se}$$

= Eat LaRa

$$E_a = V - \Gamma_a R_a - \Gamma_{se} R_{se}$$

$$F_0 F_a = V F_a - F_a^2 R_a - F_{se} F_a R_{se}$$

$$= \sqrt{(T_i - T_f)} - R_a^2 Ra - (T_i - T_f) \ln e^{R_a}$$


$$= VI_L - VP_f = \frac{I}{2} \alpha^2 R_a - P_{air} \text{Rse} + P_f \text{Rse}$$

$$= V F_L - R_a^2 R_a - R_{Se}^2 R_{Se} - R_f (V - R_a R_a)$$

$$\therefore Vp_i - p_a^2 R_a - p_{se}^2 R_{se} = Vf(p_f)$$

$$\rightarrow P_a - Vr_1 = Pa^2 Ra - Pe^2 Reo = Pg^2 R_f$$

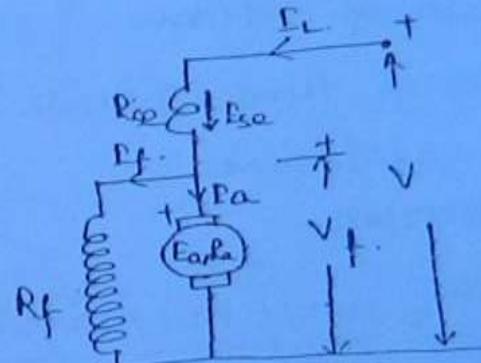↑
Signature D.P. (Signature) Paul Schmid
Power S.P. (Signature)
Power



Q. A 12 pole separately excited, DC generator has a wave wound armature containing 144 coils of 10 turns each. Resistance of each turn = 0.011 Ω. If ϕ / pole is 0.05 wb and it is turning at a speed of 200 rpm. If 1 kΩ resistor is connected to the terminals of this generator, what is the resulting induced counter EMF and torque on the shaft of the m/c?

Ans. P = 12 pole.

$$A = 2$$

144 coils of 10 turns.

R of each turn = 0.011 Ω


$$\phi = 0.05 \text{ wb/pole}$$

$$N = 200 \text{ rpm}$$

$$Z = (144 \times 10) \times 2 \\ = 2880.$$

$$E_a = \frac{\phi Z N P}{60 A} = \frac{0.05 \times 144 \times 10^2 \times 200 \times 12}{60 \times 2} \\ = 120 \cdot 2880 \text{ V.}$$

R

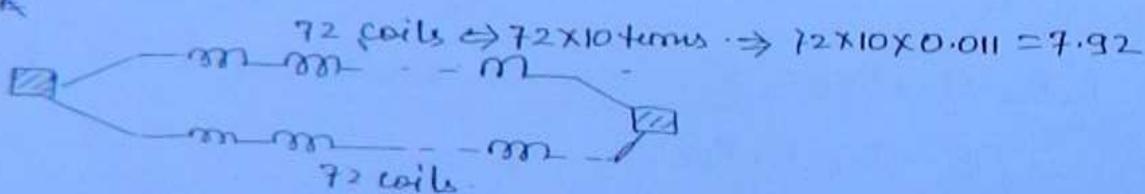

$$\text{for overall Res.} = \frac{7.92}{2} = 3.96.$$

$$R_a = \frac{1}{2} \left[\left(\frac{144}{2} \right) \times 10 \times 0.011 \right] \\ \approx 3.96.$$

↑ for wave wdg

$$I_a = \frac{E_a}{R_a + R_L} = \frac{2880}{3.96 + 1000} \\ = 2.87 \text{ A.}$$

$$\omega = \frac{2\pi \times 200}{60} \\ = \frac{2\pi \times 200}{3}$$

$$T = \frac{I_a E_a}{60 \times 1000} = \frac{2880 \times 2.87}{60 \times 1000} = 394.47 \text{ Nm.}$$

Q. A 100 kW belt driven dc shunt generator running on PL at 300 rpm and 220 V bus bars continues to run as a motor when the belt breaks then taking 10 kW. What will be its speed.

$$R_a = 0.025 \Omega$$

$$R_f = 60 \Omega$$

(123)

brush voltage drop = 2 V ignore armature reaction

B

$$\text{B.P.F} = \frac{E_f^2}{P_f}$$


$$100 = \frac{E_f^2}{100} \times 0.025$$

$$E_f = \sqrt{\frac{100}{0.025}} = 63.25$$

$$I_{a1} = E_f + E_L$$

$$= 63.25 + 300$$

$$= 363.25 \text{ A}$$

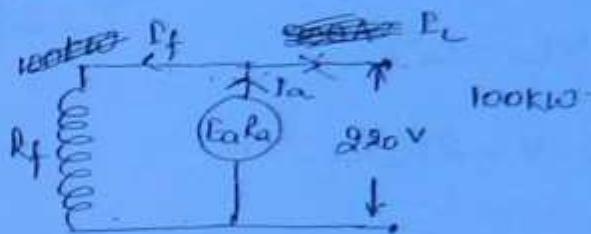

$$E_{a2} = 220 - 41.79 \times 0.025^2$$

$$= 216.96 \text{ V}$$

Since $E_a = k\phi \omega m$

$$E_a \propto N$$

$$\frac{E_{a2}}{E_{a1}} = \frac{N_2}{N_1}$$

$$\Rightarrow N_2 = \frac{300 \times 216.96}{233.46}$$

$$N_2 = 2788 \text{ rpm}$$

$$\begin{aligned} E_{a1} &= 220 + 454.55 + 3.67 \\ &= 678.2 \text{ V} \\ &= 458.2 \text{ A} \end{aligned}$$

$$E_{a1} = 220 + 458.2 \times 0.025 + 2 \\ = 235.46 \text{ V}$$

$$\text{As motor } E_{L2} = \frac{10 \times 10^3}{220} = 45.45 \text{ V}$$

$$\begin{aligned} I_{a2} &= E_{L2} - E_f \\ &= 45.45 - 3.67 \\ &= 41.78 \text{ A} \end{aligned}$$

1 V/mesh $\approx 2 \text{ V}$

$\frac{1}{2}$
total mesh
perf.

Maximum power O/P :-

$$\text{max Power} = P_a - P_{\text{lost}}$$

↓
max. count

$$P_a = E_a I_a$$

$$= (V - I_a R_a) I_a$$

$$= V I_a - I_a^2 R_a$$

$$\frac{dP_a}{dI_a} = V - 2 I_a R_a > 0$$

$$\Rightarrow I_a = \frac{V}{2R_a}$$

R_a is very low, V is applied voltage

$\therefore I_a \uparrow$ (abnormal condition). So, wedge insulation breaks and m/c gets oversteamed. burnt

$$E_a = V - I_a R_a$$

$$= V - \frac{V}{2R_a} R_a$$


$$E_a = \frac{V}{2}$$

$$\eta = \frac{P_a}{V I_a}$$

$$\approx \frac{E_a I_a}{V I_a}$$

$$= \frac{1}{2}$$

$$\eta = 50\%$$

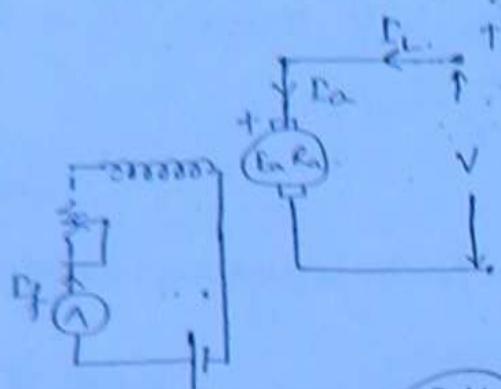

(T24)

HPT is applicable to electronic circs not in Power CK. electronic CKs deals with mW, few mW, few watts. Power CKs deals with MW.

Max power DIP of a separately excited gen:-

$$P_{\text{max}} = P_a + P_{\text{rot.}}$$

↓ ↓
Power. count


$$\begin{aligned} P_a &= E_a \times I_a \\ &= (V + I_a R_a) I_a \quad (125) \\ &= V I_a + I_a^2 R_a \\ \frac{dP_a}{dI_a} &= V + 2 I_a R_a = 0 \\ I_a &= -\frac{V}{2 R_a} \end{aligned}$$

High power rating in case of
SMR \rightarrow current consumed per
time is high and we can
not handle such high
current so if more matter.

$$P_{\text{out}} = V I_a \text{ if } V \text{ is const}$$

$$\begin{aligned} P_{\text{out}} &= V I_a \\ &= (E_a - I_a R_a) I_a \\ &= E_a I_a - I_a^2 R_a \end{aligned}$$
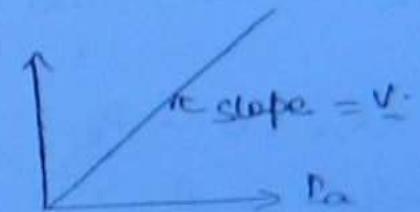
$$\frac{dP_a}{dI_a} = E_a - 2 I_a R_a = 0$$



$$\boxed{\frac{E_a}{2 R_a} = I_a}$$

then

$$\boxed{P_{\text{out}} = V I_a}$$

$$V = E_a - I_a R_a$$

$$\therefore \frac{E_a}{2}$$

$$\begin{aligned} \eta &= \frac{P_{\text{out}}}{P_a} \\ &= \frac{V I_a}{E_a I_a} \\ &= \frac{V}{E_a} = \frac{1}{2} = 50\% \end{aligned}$$

then →

$$\eta = \frac{V R_a}{V R_a + R_a^2 R_a + V_{BD} R_a + P_K}$$

where $P_K = \text{const}$ (ie fixed) losses.

(126)

Dividing by R_a :

$$\eta = \frac{V}{V + R_a R_a + V_{BD} + \frac{P_K}{R_a}}$$

emf →

- Statically (in pump)
- Induced "
- Dynamically " "
- (in generator)

η_{\max} when denom. is mini.

$$\frac{d}{d R_a} \left[V + R_a R_a + V_{BD} + \frac{P_K}{R_a} \right] = 0$$

$$\Rightarrow 0 + R_a + 0 - \frac{P_K}{R_a^2} = 0$$

$$\therefore R_a^2 = \frac{P_K}{R_a}$$

$$\boxed{R_a^2 R_a = P_K}$$

$$\boxed{\eta_{\max} = \sqrt{\frac{P_K}{R_a}}}$$

$$\text{losses} = ax^2 + bx + c$$

$$\text{For } \eta_{\max} \rightarrow \boxed{a^2 x^2 = c}$$

η of any system when the losses proportional to square of the variable are equal to const loss.

$$\eta_{\max} = \frac{\sqrt{R_a} \eta_{\max}}{V R_a \eta_{\max} + V_{BD} R_a \eta_{\max} + P_K}$$

Motors →

$$\eta = \frac{V_{Fa} - I_a^2 R_a - V_{BD} I_a - P_K}{V_{Fa}}$$

Dividing by I_a :

(127)

$$\Rightarrow \eta = \frac{V - I_a R_a - V_{BD} - P_K/I_a}{V}$$

η is max when η^2 is max.

$$\frac{d\eta^2}{dI_a} = \frac{d(V - I_a R_a - V_{BD} - P_K/I_a)}{dI_a} = 0$$


$$\Rightarrow 0 - R_a - 0 + \frac{P_K}{I_a^2} = 0$$

$$\Rightarrow I_a = \sqrt{\frac{P_K}{R_a}}$$

$$\Rightarrow \eta_{max} = \frac{V_{Fa(\text{max})} - I_{a(\text{max})}^2 R_a - V_{BD} - P_K}{V_{Fa(\text{max})}}$$

True: trailing pole
Mot: leading pole

Armature Reaction →

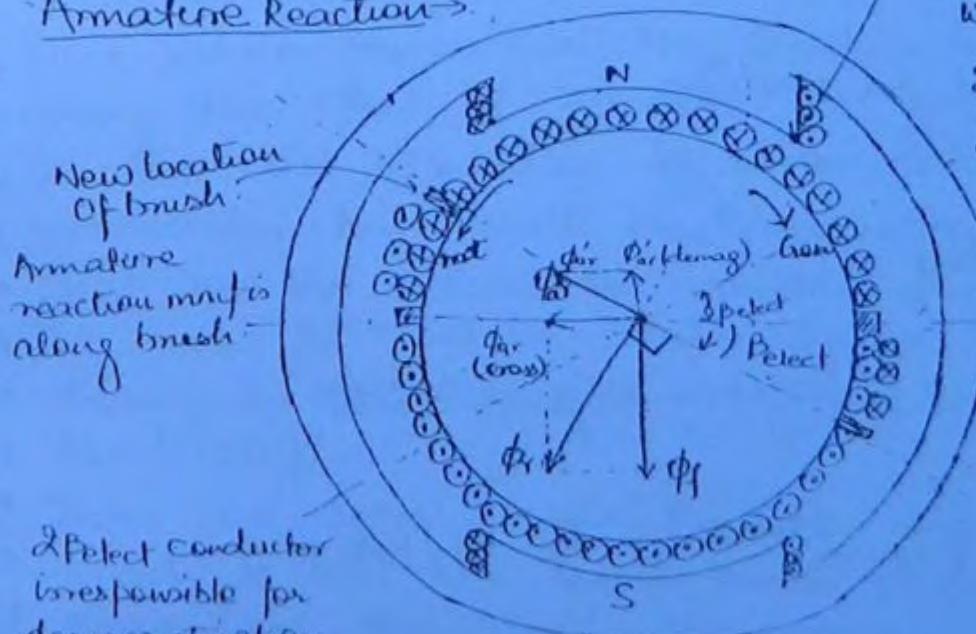


which pole comes first leading.
Sit on the D.P.P. part i.e. on rotor and move anti dir. of beam (if asked) for motors (if asked) then see which pole comes first Geometrical Neutral (G.N.A) & MNA

↓
our no lone long but narrow poles

Armature reaction →
 ϕ_{air} outwards

↑ MNA on land.

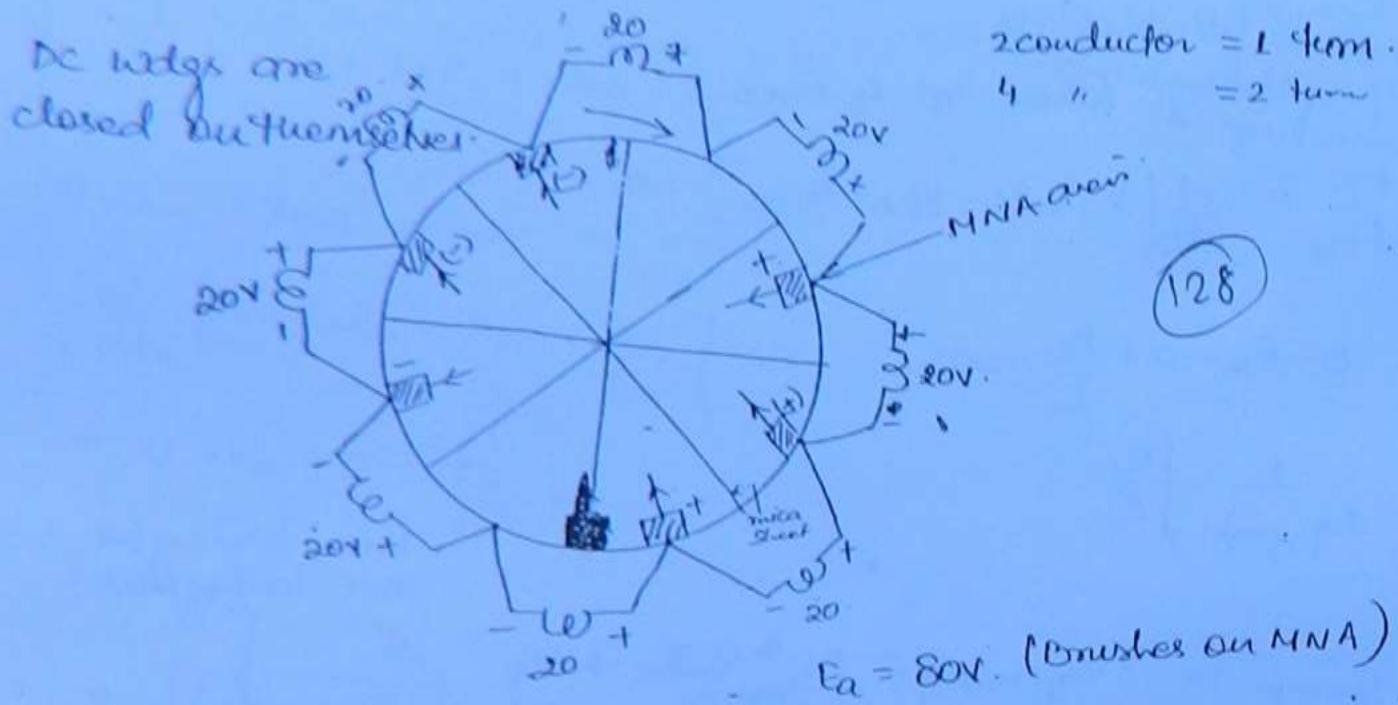- map voltage collected due when brush kept on the CNA and NNA axis.
- Map Voltage between commutator get short circuited for some time when reversal takes place. If so, if there will be an induced v. emf present in it, it will circulate cur. and damage the brush. So, it is kept on CNA axis so the $V=0$ as $\phi=0$.



Radial flux density = 0 at NNA.

$E_a = 40V. \text{ (Brushes not on NNA)}.$

$E_a = 0V.$

→ total no. of conductors

$$\text{For (Interpoles)} = \frac{(2/2)}{P} \times \left(\frac{\alpha \beta_{\text{rect}}}{180} \right) \times \frac{l_a}{A} \text{ At/pole.}$$

$$\text{For (cross)} = \frac{2/2}{P} \times \left(\frac{1 - \alpha \beta_{\text{rect}}}{180} \right) \times \frac{l_a}{A} \text{ At/pole.}$$

Armature reaction and brush shift:

The reaction of armature conductor flux on the main field is known as armature reaction. When the dc mfc is on no-load, its M.N.A. q coincides with BNA. However when the mfc is on load, armature reaction has cross magnetising effect with results in concentration of flux in the trailing pole tips in generator action and in the leading pole tip in the motor action. Consequently the dirⁿ of resultant flux remains no longer in the direct axis and left main M.N.A and therefore N.M.A shifts along the dirⁿ of rotation in gen. action and off to the dirⁿ of motion in motor action. It is well known that the brushes are placed in MNA to ensure connection of mag. induced emf and also to aid in a sparkless commutation, as the coil undergoing commutation would have 0 rotational emf when it is in the MNA. The effect of armature reaction results in the shift of magnetic neutral axis and consequently there is problem in commutation as well as in the reduction in available emf.

(129)


An obvious solⁿ appears to shift the brushes along the new MNA which means that the brushes have to be shifted along the dirⁿ of rotation in gen. action and off to the dirⁿ of rotation in motor action. This step improves commutation but results in demagnetisation of the main fd that in turn reduces the resultant flux. This means that the main fd must be made stronger to neutralise the demagnetisation effect of armature reaction caused by brush shift.

There are some serious limitations in brush shift, one of which is that the brush must be shifted to a new post every time the load changes. The other limitation is that if the ^{same} mfc operator in gen. as well as motor mode

The dirⁿ of brush shift has to be reversed everytime it happens.

In view of the above, brush shift is restricted to very small m/c and there too brushes are fed at a position corresponding to the normal load for the given mode of operation.

(T30)

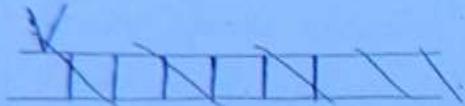

Q. A four pole generator supplied a current 143 A. Its has 492 armature cond.

- 1) wave connected
- 2) lap connected.

When delivering full load, brushes are given an actual load of 10° (mechanical). Cal the demagnetising AT per pole. The f/d wdg is shunt connected and takes 10 A. Find the no. of extra shunt f/d terms/pole necessary to neutralise this demagnetisation.

fun. wdg 492 → armature conductors

$$Z = 492$$

P = 4 pole

$$\frac{2/2}{P} = \frac{492/2}{4}$$

$$\beta_{\text{elec}} = 20. \quad I_A = 143$$

$$A = 4$$

$$\beta_{\text{mag}} = \frac{492}{8} \times \frac{2720}{130} \times \frac{112}{4} = 485.28$$

$$I_L = 143A \quad \& \quad I_f = 10A$$

$$I_a = I_L + I_f$$

$$\text{Pelect} = \frac{P}{2} \times B_{\text{mech}}$$

$$= \frac{4}{2} \times 10$$

$$= 20' \text{ elect}$$

(T3)

For wave:

$$\text{Far(demag)} = \frac{492/2}{4} \times \frac{2820'}{180} \times \frac{153}{2}$$

$$= 1045.5 \text{ At/pole}$$

$$\text{extra fld turns} = \frac{1045.5}{10} \approx 105 \text{ turns/pole}$$

Lap wound: —

$$A = 4$$

$$\text{Far(demag)} = 522.75 \text{ At/pole}$$

$$\text{extra fld turns} = \frac{522.75}{10} \approx 52 \text{ turns/pole}$$

Q. A separately excited dc gen. has the following data :-

$$\text{Armature } R_a = 0.04 \Omega$$

$$\text{fld resistance } R_f = 110 \Omega$$

Total core and mech. losses 960 W. Volt. across the fld 230 V. The gen. supplies a load at a terminal volt. is 230V. Calculate

A) Pa at which gen has max η due to R_a

B) max value of the gen overall η .

Ans.

a)

$$\frac{V_{T_{\text{max}}}}{R_a} = \frac{P_k}{P_a} = \frac{960}{0.04}$$

$$154.92$$

$$230 \times 154.92$$

$$230 \times 154.92 \times 0.04 = 154.92$$

b) η

$$P_K = 960 \times \frac{230^2}{110}$$

$$\approx 1440.91 \text{ W}$$


$$(I_a)_{\eta_{\max}} = \sqrt{\frac{1440.91}{0.04}}$$

$$= 189.8 \text{ A}$$

(132)

$$\begin{aligned}\eta_{\max} &= \frac{230 \times 189.8}{230 \times 189.8 + 2 \times 1440.91} \\ &= 0.938 \mu\text{u} \\ &\approx 93.8\%.\end{aligned}$$

Commutating poles and/or interpoles

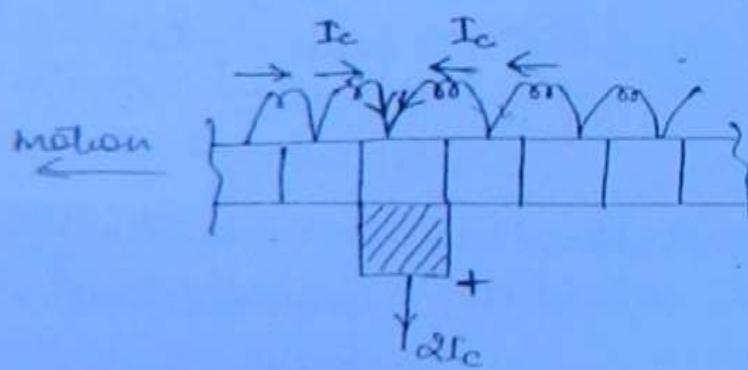

Impair loop:-

$$\phi H A I = N T \quad \text{for } \uparrow$$



$$\phi = \frac{N T}{\text{reluctance } H}$$

(Polar areas)
fixed -

Armature reaction \rightarrow density


triangular wave
shape of armature reaction

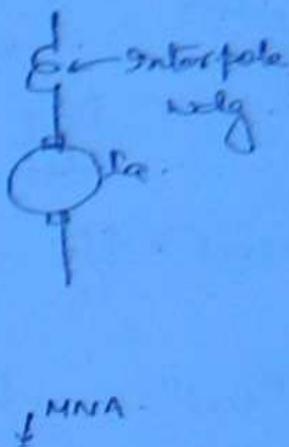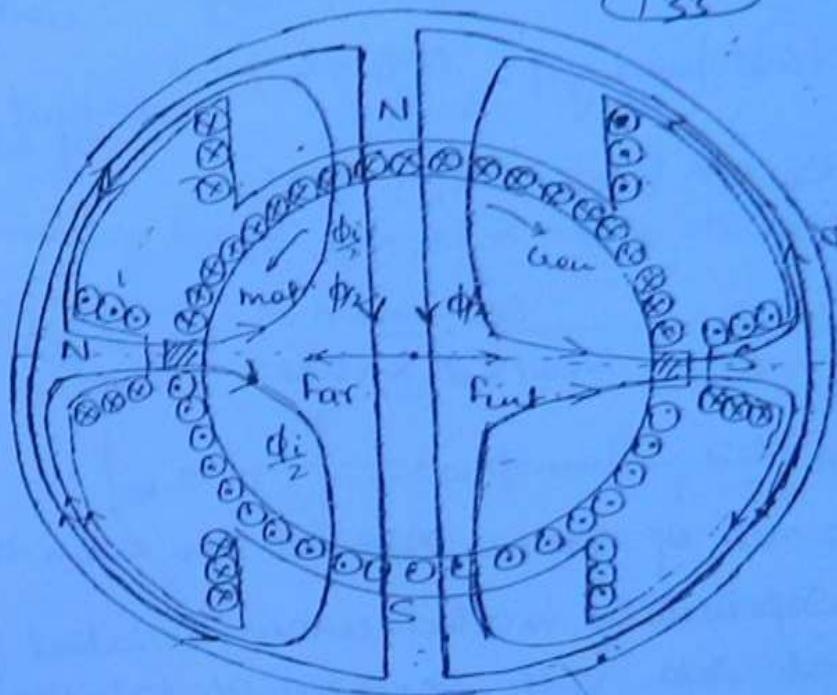1 dimension
 \rightarrow polar areas
space angle
1 slot per pole
2 slot per pole




It is mmf which decides the flux.


At $t = \frac{t_c}{2}$,

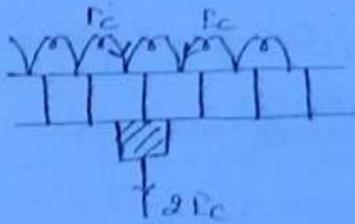

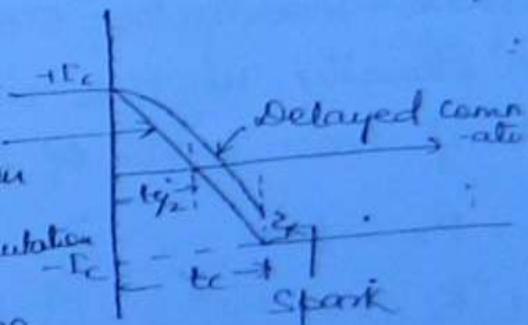ideal
commutation
or
linear commutation
or
straight line
commutation



at $t = t_c$,

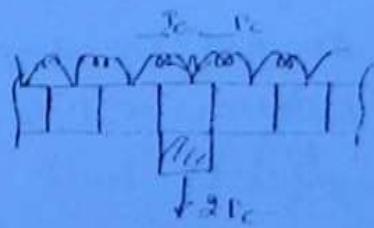

Reactance Voltage $\frac{2V_c}{t_c} \times t_{coil}$ t_c = commutation time
 $\frac{60}{N}$

Polarization voltage $\sum E_i$ Reactance Volt.

No. of commutator
segments

$$\text{W/o. flux} = \frac{\Sigma/2}{P} \times \frac{Pa}{A} \quad \text{At/pole}$$

~~compensating~~
~~airgap~~

$$\frac{B_{int}}{60} \times \text{interpole gap At/pole}$$

$$L_{coil} \times \frac{\partial L_c}{t_c} = B_{int} \times (N_{coil} \times \partial) \times L \times \frac{\pi D N}{60}$$

$$\frac{N_{coil}}{B} = \frac{B_{int}}{60} \times \frac{\pi D N}{60 \times 2 \times \frac{1}{\mu_m}}$$

↳ aerial length
of conductor

$$\Rightarrow B_{int} = L_{coil} \times \frac{\partial L_c}{t_c} \times \frac{60}{N_{coil} \times \partial L \times \pi D N}$$

(T34)

- Q: Estimate the no. of turns needed on each commutator pole of a 6 pole separately excited uncompensated gen. delivering 200 kW at 200 volt, given no. of lap connected armature conductor = 540, interpolar air gap = 1.2 cm, flux density in the interpolar air gap = 0.3 T. Ignore effect of iron parts of the core and leakage.

Ans: P = 6 pole

P


$$V = 200 = B_{int} \times N_{coil} \times \partial \times L \times \frac{\pi D N}{60}$$

= 0.32

$$\begin{aligned} B_{int} &= \frac{540/2}{6} \times \frac{1000}{6} + \frac{0.3 \times 10^3}{4 \pi \times 10^{-7}} \\ &= 9387.32 \text{ At/pole.} \end{aligned}$$

$I_a = \frac{200 \times 10^3}{200} = \frac{10^3}{10^3} A$


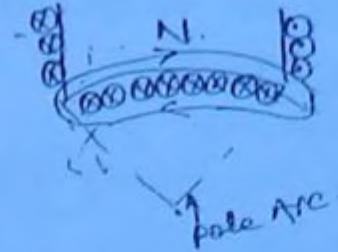
$$\text{No. of turns/pole} = \frac{9387.32}{1000} = 9.387 \approx 10$$



(135)

for decreasing load in gen, it is more dangerous.

for increasing " in motor, "

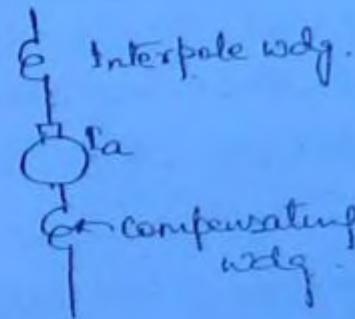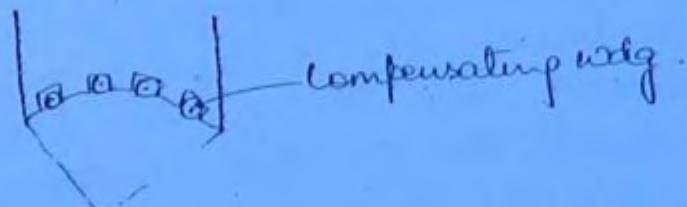

$$P_{\text{comp}} = \frac{2/2}{P} \times \frac{\text{Pole arc.}}{\text{Pole pitch}} \times \frac{I_a}{a}$$

$$= N_{\text{comp}} \times I_a. \quad \underline{\text{At 1/pole}}$$

M/Ic with compensating wedg :—

$$I_{\text{int}} = \frac{2/2}{P} \times \left(1 - \frac{\text{Pole Arc.}}{\text{Pole pitch}}\right) \times \frac{I_a}{A} + \frac{B_{\text{int}}}{H_0} \times \frac{\text{Interpol. gap}}{\text{gap}}$$

Q) A compensated generator has 12000 armature Amperes turn. The ratio of pole arc / pitch is 0.7. length of interpolar air gap = 0.12 cm and flux density of interpolar air gap is 0.3 T. find Amp turns/pole for compensating and interp. wedg.

$$\text{Ans: } P_{\text{comp}} = 12000 \times \frac{\text{Pole Arc.}}{\text{Pole pitch}}$$

$$= 12000 \times 0.7 = 8400 \text{ At 1/pole}$$

$$F_{int} = \frac{(12000 - 8400) + 0.3}{4\pi \times 10^{-7}} \times 1.25 \times 10^{-2}$$

→ 6584.16 N/pole

136

Interpoles

The coil undergoing commutation should ideally help low rotational voltage otherwise when the brush short circuit the brush, there would be a very heavy short circuit current causing massive sparking at the brush and commutator surfaces. Commutation therefore is carried out in the coil which lies in the interpolar axis where the radial flux density due to the main poles shown is supposed to be 0. Since the armature reaction effect shifts the magnetic neutral axis, commutation becomes problematic. Also, the reactance voltage in the coil undergoing commutation given by $\frac{L_{coil} \times \Delta I_c}{t_c}$ opposes the change in coil current resulting in delayed commutation and consequent sparking at trailing edge of brush and commutator segment. In this expression, L_{coil} includes self inductance of the coil undergoing commutation as well as mutual inductance due to neighbouring coils. The term ' ΔI_c ' is due to the change in coil current from $+I_c$ to $-I_c$ and ' t_c ' stands for commutation time. The problem of shift of MMNA as well as the difficulty faced in commutation due to reactance voltage is solved by a use of interpoles, also called commutating poles. Interpoles are long but narrow poles in the interpolar region and have polarity of the succeeding main field pole in generator action and of preceding (previous) main field pole in motor action. The interpole wedge is connected in series with the armature and carries full armature current. If M/L has compensating pole

Then the interpoles are responsible only for neutralising armature reaction effect in the interpolar region created by those armature conductors which lie outside the pole arc. However, if the mfc is not compensated then the interpole will be able to completely neutralise total armature reaction effect in the interpolar region. Additionally, in both cases, the interpole wedg must be designed to create a radial flux density in the interpolar air gap sufficient enough to create a rotational voltage in the coil undergoing commutation which would be equal and opposite to the resistance voltage. By these twin measures, commutation becomes problem free and is known as voltage commutation. The interpole is normally irrespective of the dirⁿ of rotation load on the mfc or lps mode of operation. The interpole face is kept narrow to prevent its influence on other coil. However its base is usually made wide so that saturation is prevent and required mmf of interpole pole is slightly reduced.

(137)

Compensating wedg:-

The cross magnetisation effect of the armature reaction on the main fd is caused mainly due to those armature conductors which are located ~~in~~ under the pole arc. This happens because armature mmf under the pole arc finds a low reluctance path through the air gap under the pole edges. The new conc. of flux in the trailing pole tip in generator action and in leading pole tip in motor action causes high rotational emf in the coil that are located under these pole tips. If the armature reaction is very strong due to heavy load and/or due to compensability weak fd's the induced voltage in these coils with in which incidently are physie close to the brushes may create high enough voltage b/w adjacent commutator segments resulting in brush


If there are some irregularities on the commutator surface, it might already be ionised due to heat in the commutation area. The process might become cumulative as it might spread to the neighbouring segments resulting in a fire from brush to brush over commutator segments. If the m/c. has rapidly fluctuating and decreasing load in generator action or increasing load in motor action, then the resulting $\frac{d\phi}{dt}$ voltage of the coil would add up to its rotational voltage and consequently the total coil voltage that appears across adjacent commutator segments may become high enough to start breakdown of air b/w these segments leading ultimately to similar fire over the commutator surface, as described above.

The problem can be addressed by the use of compensating wdg in the m/c. Compensating wdg is embedded in axial slots in the pole shoe and carries armature current in a dir² opposite to the dir² of current in the armature conductors & under the pole arc. By proper design of the compensating wdg, the armature mmf under the pole arc may be compensated. Once this happens, the main fd regains its original configuration in an under pole shoe. The compensating wdg fits normally and neutralises the effect of armature reaction of the conductors under the pole arc irrespective of the load, dir² of rotation, mode of operation of the m/c. Compensating wdg is needed where heavy loads, rapidly fluctuating loads or weak main fd during motor speed control are expected during operation.

(138)

Another method to reduce sparking near the pole arc :-

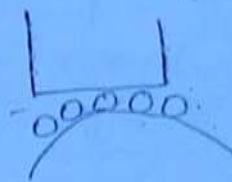1) Increase the air gap in the tip of pole.



139

2)



reluctance in ϕ -path

Q. Find the no. of poles of 1200 KW generator if the av. voltage b/w commutator segments is 15 V and Armature AT/pole is 10000. The generator has single term coil and lap connected and ignore all losses.

Ans. $P = 9$

$$P_{\text{int}} = 10000$$

$Z = \text{total cond.}$
 $A = \text{parallel path.}$

$$\frac{Z}{2A} \times 15 \rightarrow E_a = 7.5 \frac{Z}{A}$$

$$E_{Pa} = 12000 \times 10$$

$$E_{Pa} = 1200 \times 10^3$$

$$P_{\text{int}} = \frac{Z/2}{P} \times \frac{Pa}{A}$$

$$10000 = 1000 \frac{Z/2}{P} \times \frac{Pa}{A}$$

$$j_a = \frac{10000 \times 2P \times A}{Z}$$



$$\frac{7.5Z \times 10000 \times 2P \times A}{A} = 1200 \times 10^3$$
$$\Rightarrow \frac{7.5Z}{1P = 81} \times 2 = 1200 \times 10^3$$

open circ characteristics →

$V_{oc} \propto I_f$.

Magnetisation characteristics.

Saturation characteristics

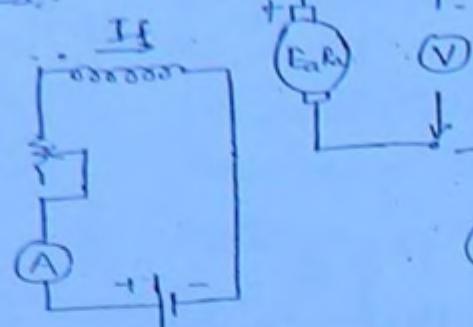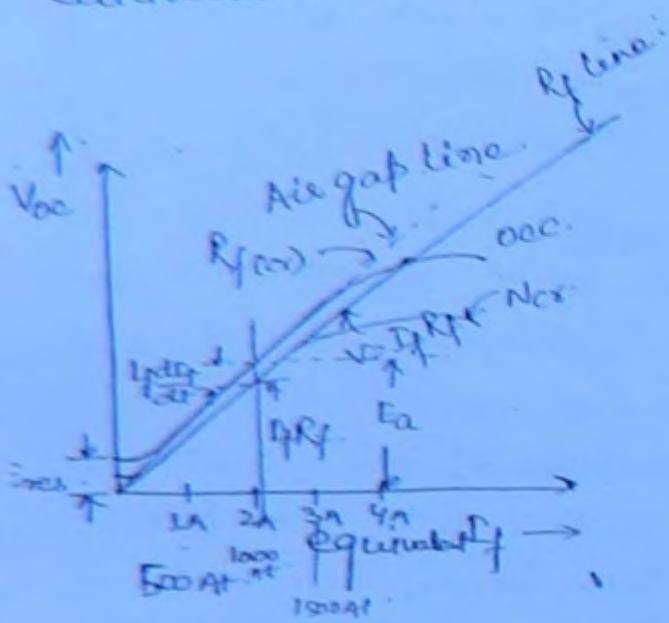

140

$$N_f I_f = 500 \text{ turns} \quad I_f = 1.6 \text{ A} \\ N_{se} = 4 \text{ turns} \quad E_{se} = 50 \text{ V}$$

$$N_f I_f (\text{eq.}) = N_f I_f + N_{se} I_{se}$$

$$I_f(\text{eq.}) = I_f + \frac{N_{se}}{N_f} I_{se}$$



$$= 1.6 + \frac{4}{500} \times 50$$

10

Irrespective of the type of MLC,
for plot of $V_{oc} \sim I_f$, excite the
MLC separately and plot the graph.

$V_{oc} \propto$ reading upto more than 25% of Brated voltage
Wdg insulation is no problem, as $I = 0.50$, no losses as $I^2 R$

$\frac{N_{se}}{N_f}$ Ratio →

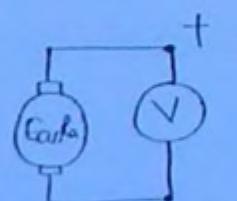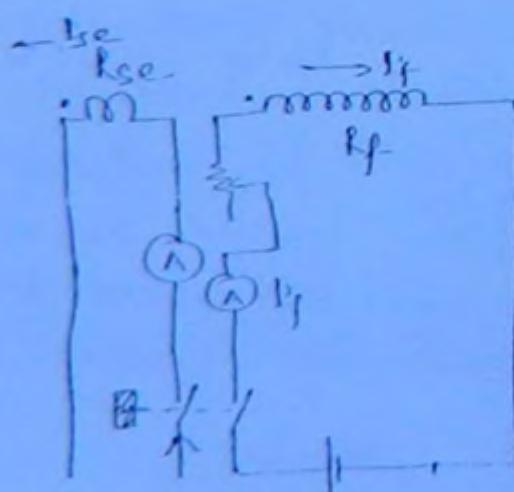

Simultaneous opening of two fild switches results in no change in voltmeter reading then it means that

$$N_f E_f - N_{se} E_{se} = 0$$

(74)

$$\frac{N_{se}}{N_f} = \frac{E_f}{E_{se}}$$


Voltage Build up in a Shunt generator :-

Condition to be satisfied for voltage build up in shunt generator.

1) Residual magnetism presence (H_{fr})

If residual magnetism is absent,
fld excitation is required.

Small current through ext. source

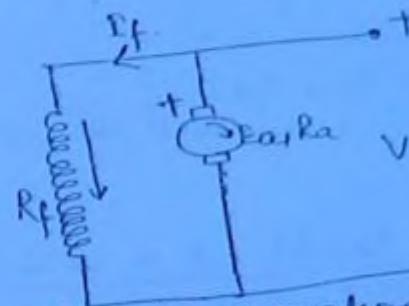

2) Connect polarity of fild wedg with respect to commutator wedg such that the fild flux is in the same dirⁿ as residual flux.

for the given dirⁿ of rot.

$$E_f = \frac{V}{R_f}$$

$$\Rightarrow V = E_f R_f$$


3) fild resistance should be less than critical value for the given speed of rotation.

$R_f(c)$ \propto Speed.

$R_f(c)$ is the slope of air gap line

on air gap line \rightarrow
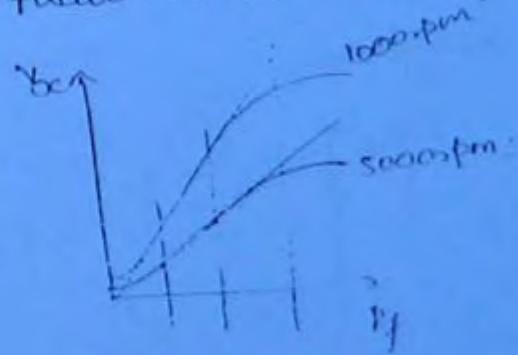
$$\begin{aligned} I_a &= K \phi \omega_m \\ &= K \sqrt{I_f / 2} \omega_m \\ &= [K \sqrt{I_f} / 2] \omega_m \\ &= R_f K \omega_m \end{aligned}$$



$$\begin{aligned} R_f(c) &= K \omega_m \\ \boxed{R_f(c) \propto K \omega_m} \end{aligned}$$

Q) speed should be more than critical value for the given field resistance.

neglecting armature resistance and inductance \rightarrow

$$E_a = I_f R_f + 4 \frac{dI_f}{dt}$$

$$\Rightarrow 4 \frac{dI_f}{dt} = (E_a - I_f R_f)$$


$$\Rightarrow \frac{dI_f}{dt} = \frac{1}{4f} (E_a - I_f R_f) = \text{five} \quad \text{then} \quad I_f \text{ increases with time.}$$

$$4 \frac{dI_f}{dt} \uparrow; E_a \uparrow$$

$= 0$ then I_f is const and volt. build up stops.


Voltage built up in a Seiling gen \rightarrow

1) same as shunt gen.

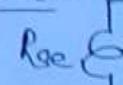


presence of residual magnetism

otherwise field flashing is required

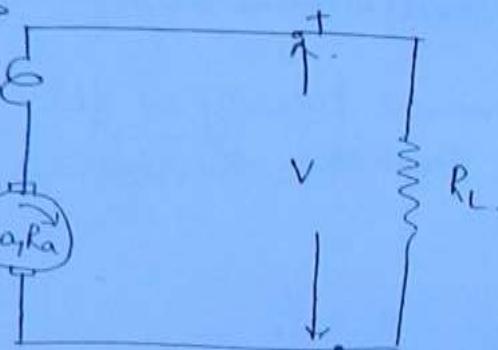

2) correct polarity of the series field (wdg) w.r.t. armature wdg so that the series field is in the same dirⁿ as the residual field for the given dirⁿ of rotation.

3)

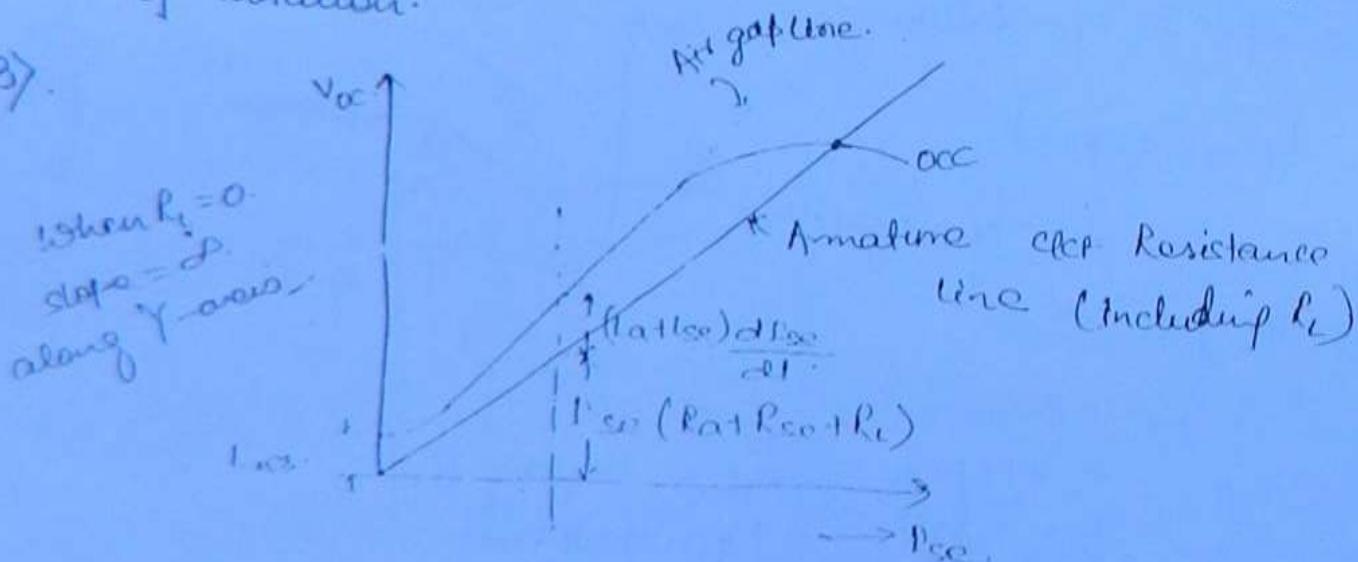

- 2) Armature C.R resistance including r_a should be less than the critical value for the given speed of rotation.
- 3) Speed should be more than critical value for the given value of armature C.R resistance including r_a .

$$E_a = E_a(R_a + r_a + R_L)$$

(143)

$$= I_a(E_a + R_a + R_L)$$

Generator characteristics →

External characteristics :-

$$V \propto I_L$$

[of interest to the user]

or O/P characteristics



or VI characteristics

$$\text{Voltage Regulation} = \frac{\text{No load Voltage} - \text{Full load Voltage}}{\text{F.L. Voltage}}$$

where, • F.L. Voltage = Rated Voltage



Internal characteristics → $E_a \propto I_a$

[of interest to designer]

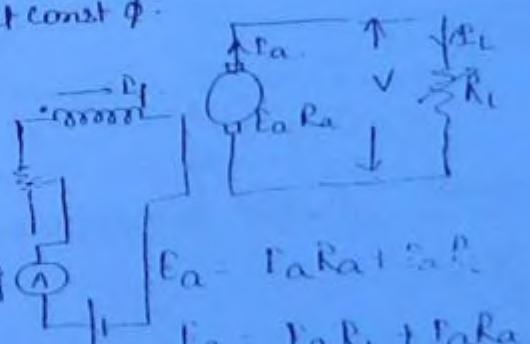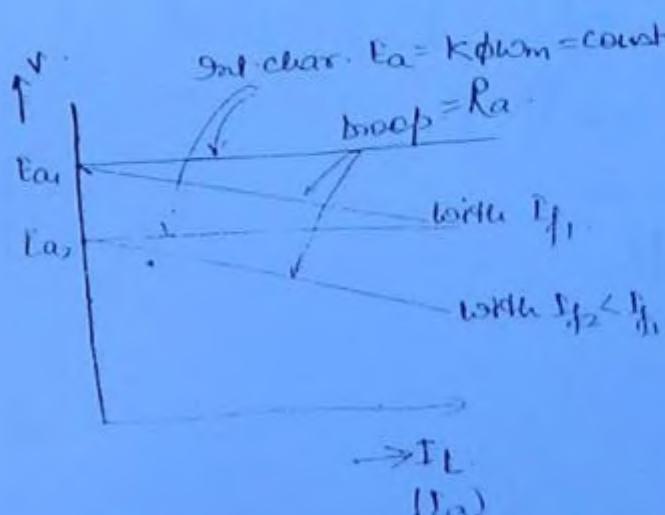

$$V = E_a - \frac{R_a}{R_a + R_L} E_a$$

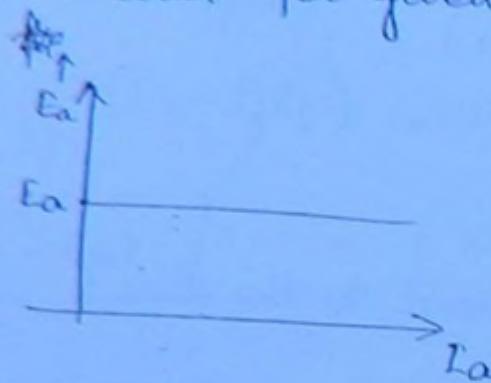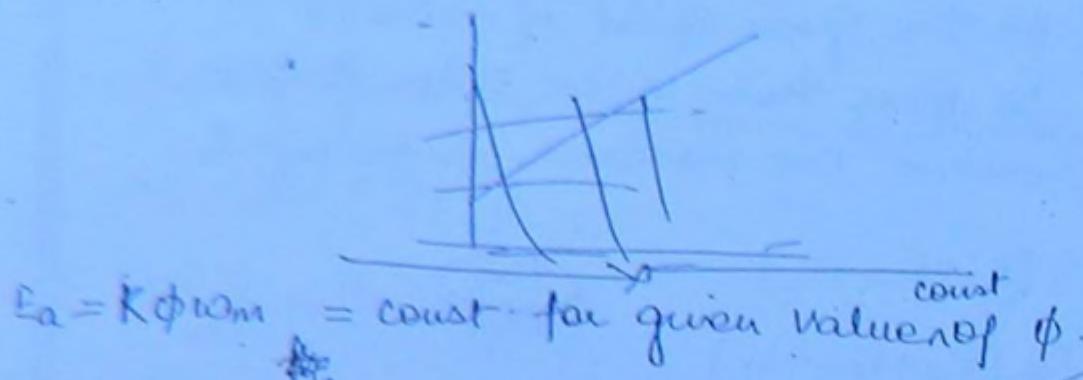R_a is very small, so small slope is small = E_a so, voltage profile is best and V.R. is best





144

$$E = k\phi \omega_m \\ \phi = f(I_a) \\ V = RI$$

solution

Characteristics of Shunt Generator:

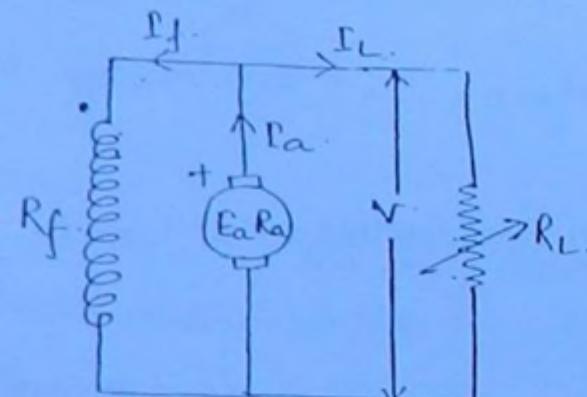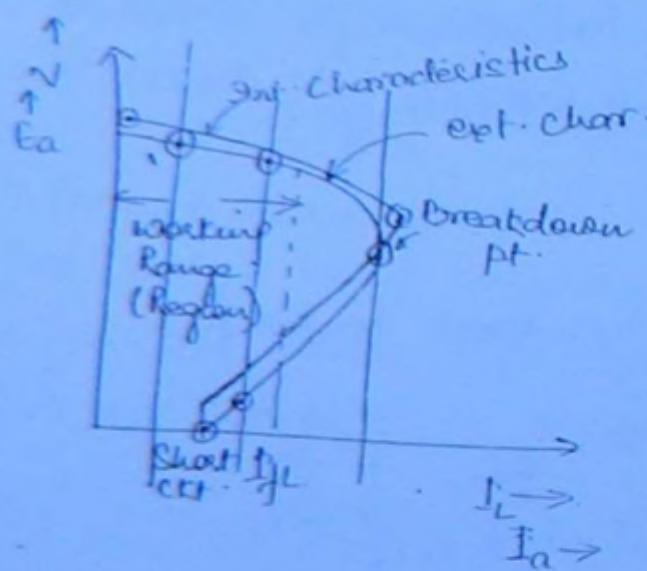

R_L decreases until breakdown pt.

$$1) I_L = \frac{V}{R_L}$$

$$2) I_a = I_L + I_f$$

$$3) V = E_a - I_a R_a$$

$$4) I_f = \frac{V}{R_f} \quad 5) \downarrow \phi = f(I_f)$$

$$e) \downarrow E_a = K(\phi) \omega_m$$


Ans to (3)

$$\downarrow V = E_a - I_a R_a$$

(145)

$$I_a = I_L = \frac{E_{no}}{R_a}$$

Condition at short circuit

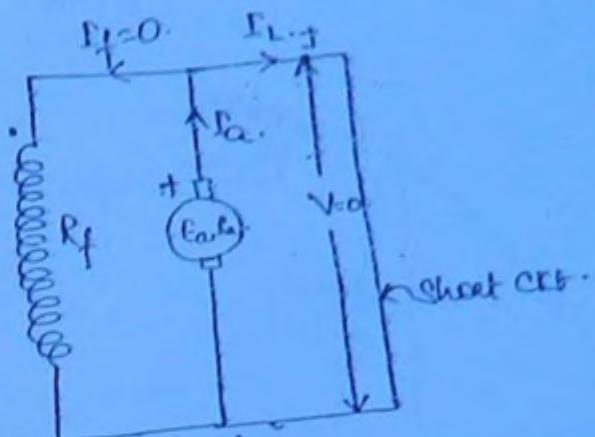

Beyond breakdown pt:

$$\downarrow I_L = \frac{V}{R_{a,i}}$$


external char. from OCC (or Armature char.) \rightarrow

$$E_a = V + I_a R_a$$


$$E_a = V + R_f I_f + I_a R_a$$

$$I_a = I_f + I_L$$


$$I_L = I_a - I_f$$

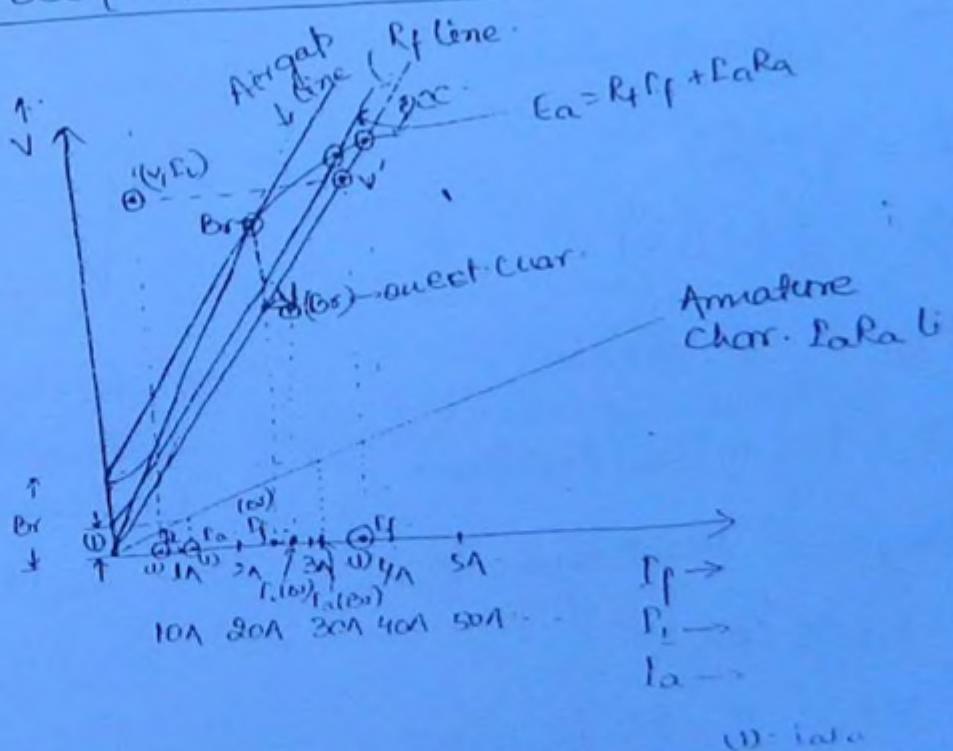

Series Generator →

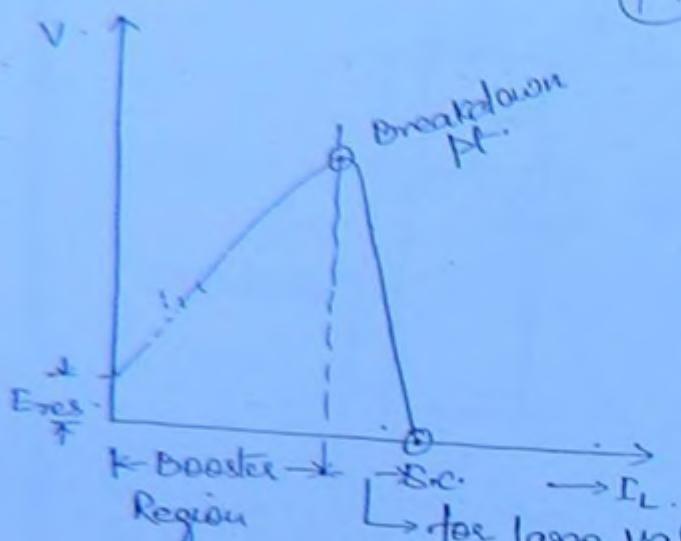

(146)

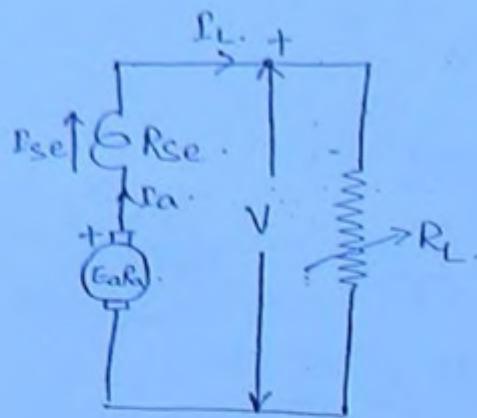

$$I_a = I_{se} = I_L$$

CONSTANT CURRENT REGION.
for large value of voltage change, current is
constant in this region used in arc welding

R_L decreases → (A) ^{untill} before breakdown pt : —

$$\Delta \uparrow I_L = \frac{V}{R_L}$$

$$\Rightarrow \phi = f(I_{se})$$

$$\uparrow \phi = f(I_L \uparrow)$$

$$3) \uparrow E_a = K(\phi) \omega_m$$

$$\uparrow V = \uparrow E_a - \uparrow I_a (R_{se} + R_L)$$


(B) Beyond breakdown pt ;

$E_a \approx \text{const}$

$$V \approx E_a - I_a (R_{se} + R_L)$$

booster region → (booster for line drop compensation)

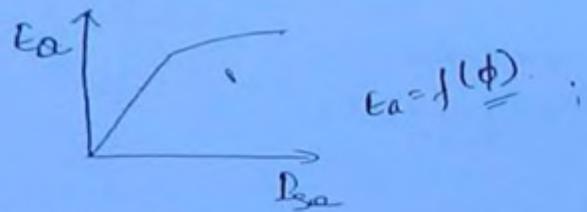
This is not suitable for home appliances as load increases
 $V \downarrow$ and $I \uparrow$ and $P^2 R$ losses \uparrow and bulb fuses.



As E_a becomes const after
certain time. As $I_{se} \uparrow$ but
 $E_a = \text{const}$

$I_a (R_{se} + R_L)$ dominant

∴ V rapidly decreases

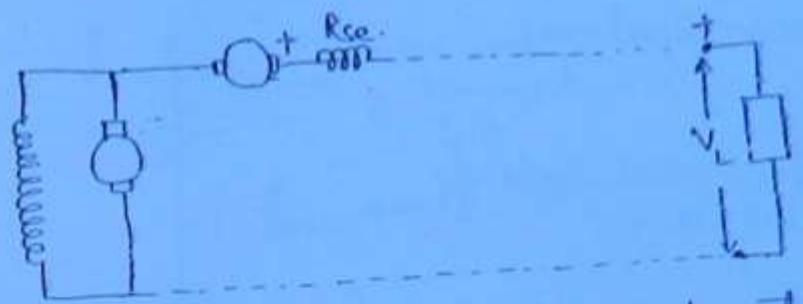

As Booster for line drop compensation

Internal char. →



$$E_a \sim I_a$$

$$\uparrow I_L = \frac{V}{R_L}$$

$$\uparrow I_{se} = I_L \uparrow$$

$$\uparrow E_a = K(\uparrow \phi) \omega_m$$

BB

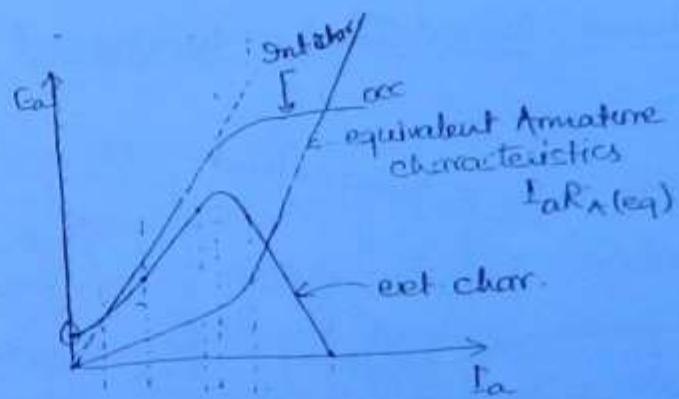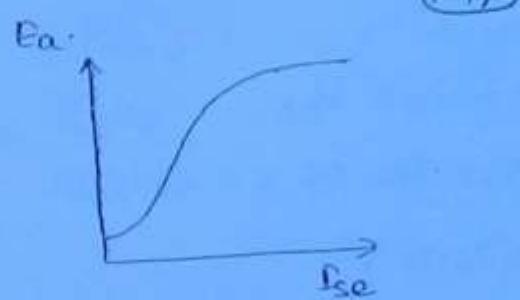

Q A 50 KW, 250V, short shunt compound generator has the following data.

$$R_a = 0.06 \Omega$$


$$R_{so} = 0.04 \Omega$$

$$R_f = 125 \Omega$$

Let the induced Amature Volt.

at loaded load and rated amature mechanical
voltage > volt - a, the total brush contact drop

$$I_a = I_{a0} + I_{k1} R_a + 250$$

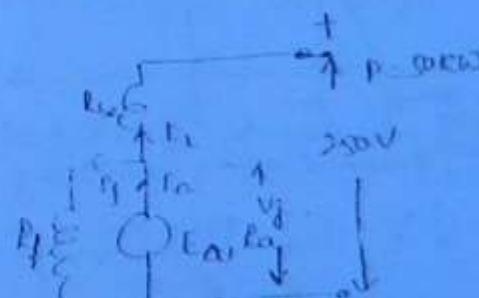

$$V_L = 250$$

$$V_L = 250 + I_a R_f$$

$$I_a = \frac{250}{R_f}$$

$$V_f = 250 + 200 \times 0.04 \\ = 258 V$$


$$I_f = \frac{258}{125} \\ = 2.06$$

$$I_a = I_a + I_f \\ = 200 + 2.06 \\ = 202.06$$

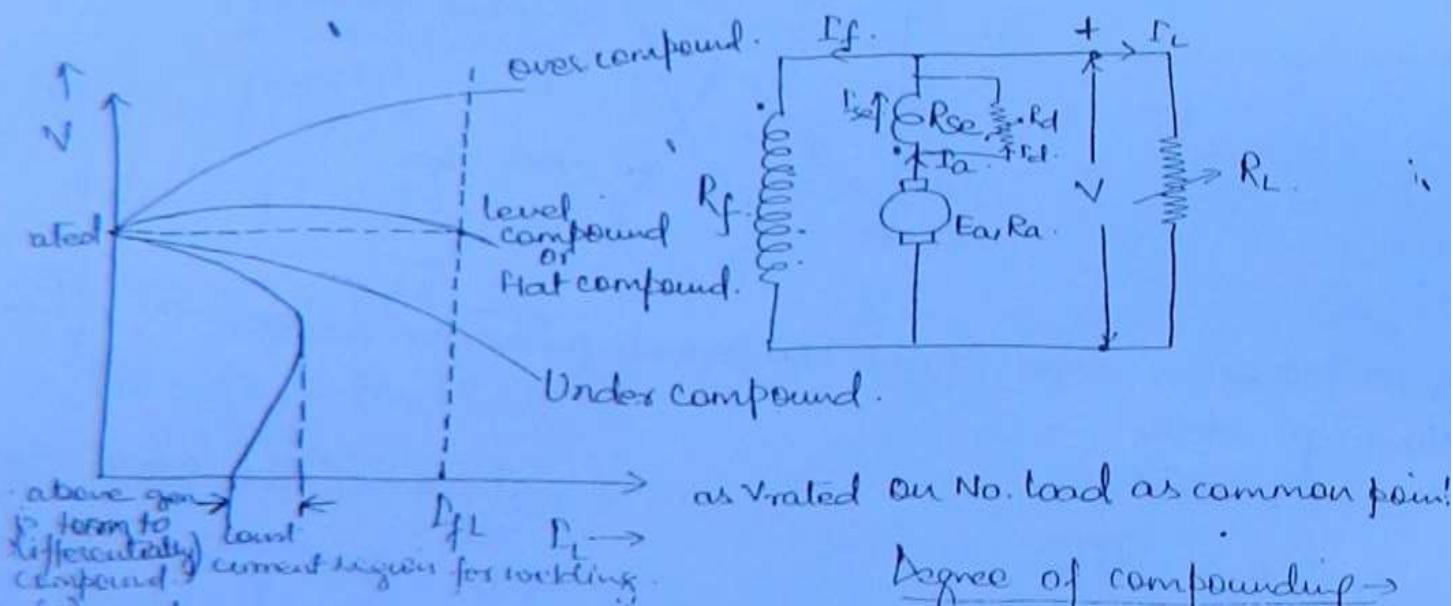(146)

$$E_a = V_f + I_a R_a + V_{BD} \\ = 258 + 202.06 \times 0.06 + 2 \\ = 272.12 V$$

long Shunt Cumulatively compounded Gen \rightarrow



$$(1) \Delta V = E_a - I_a R_a (R_a + R_{se})$$


$$\Delta \phi$$

$$(2) \phi = f(I_{se})$$

$$\Delta \phi = f(I_a)$$

$$(3) \Delta E_a = K(\phi \uparrow) \omega_m$$

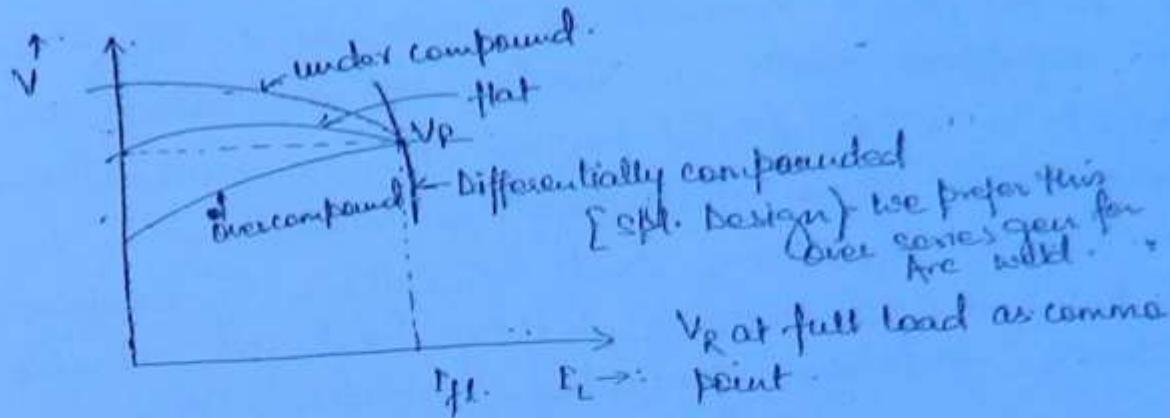to go \downarrow $n \downarrow$ $\omega_m \downarrow$



$$I_d R_d = I_{se} R_{ee} = I_a (R_d + R_{ee}) \\ = I_a \frac{R_d R_{ee}}{R_d + R_{ee}}$$

149

$$(N_f) N_f = N_{se} I_{se}$$

$$\Rightarrow I_{se} = \frac{N_f}{N_{se}} \times (N_f) \quad I_d = I_a - I_{se}, \quad R_d = \frac{I_{se} R_{ee}}{I_d}$$

Q. A long shunt compound gen. has a shunt fld wrdg of 1000 turns/pole. and a series fld wrdg of 4 turns/pole. In order to obtain same rated voltage at full load as at no. load, it is necessary to increase the shunt fld current by 0.2 A. When the m/k is operated as a shunt gen. with series fld wrdg unconnected. The full load armature current of the compound generator is 80 Amp. as the series fld resistance is 0.05 Ω. Cal. The directer resistance required for flat comp. operation.

$$\text{Ans: } N_f = 1000 \quad N_{se} = 4 \quad N_f = 6.2$$

$$I_{se} = \frac{1000}{4} \times 0.05 = 125 \quad I_a = 80 \text{ A}$$

$$125 - 80 = 45$$

~~$$I_d = 45 \quad \text{not pos} \\ \text{not pos} \quad 45 \quad 125 - 80 = 45$$~~

$$R_d = \frac{45 \times 0.05}{45 - 80}$$


A 50 KW, 500 V cumulatively compounded - long shunt gen equipped with a directer delivers rated load current to a load at rated voltage. The measured currents through the shunt fld windings and directer are 4A & 21A respectively. Amature and series fld wdg resistance are 0.1 Ω and 0.02 Ω respectively. Find the directer resistance and the generated amature volt.

Ans.

$$R_d = ?$$

$$E_a = ?$$
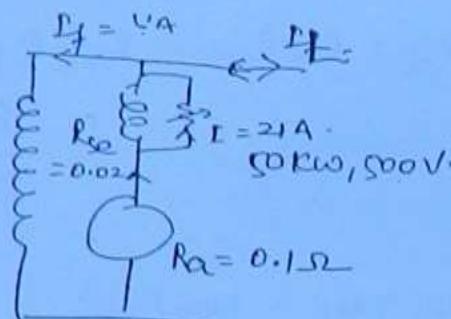
$$I_s = \frac{10}{50 \times 10^3} = 100 \text{ A}$$
150



$$I_A = I_f + I_L$$

$$= 100 + 4 = 104$$

$$I_{se} = 104 - 21$$

$$= 83 \text{ A}$$

$$I_{se} \times R_{se} = 83 \times 0.02$$

$$= 1.66$$

$$1.66 = E \times R$$

$$R_d = \frac{1.66}{21} = 0.079$$

$$E_a = \underline{I_A R_a} + 1.66 + 500 \rightarrow I_A R_a \Leftrightarrow 104 \times 0.1 \\ \Rightarrow 10.4$$

512.06 Ans.

$$E_a = V - I_a R_a \rightarrow \text{2nd dependent}$$

$$\omega_m = \frac{E_a}{K\phi} \rightarrow \text{last dependent}$$

(157)

KVL law \rightarrow based on law of conservation of energy.

Sequence of events

Generator:

- 1) ω_m is independent variable. 1) V is independent variable.
- 2) $E_a = K\phi \omega_m$ is 1st dependent $I_a = \frac{T_{load}}{K\phi}$ is 1st dependent variable.
- 3) $I_a = \frac{E_a}{R_a + R_L}$ is 2nd dependent $E_a = V - I_a R_a$ is 2nd dependent variable.
- 4) $V = E_a - I_a R_a$ is last dependent $\omega_m = \frac{E_a}{K\phi}$ is last dependent variable.

Motor



DC motor char.

Neglecting Ar. effect

$$E_a \sim I_a$$

$$\phi \sim I_a$$

$$T \sim I_a$$


$$\omega_m \sim I_a$$


$$\omega_m \sim T$$

Separately excited motor \rightarrow

$$E_a \sim I_a$$


$$E_a = V - I_a R_a$$

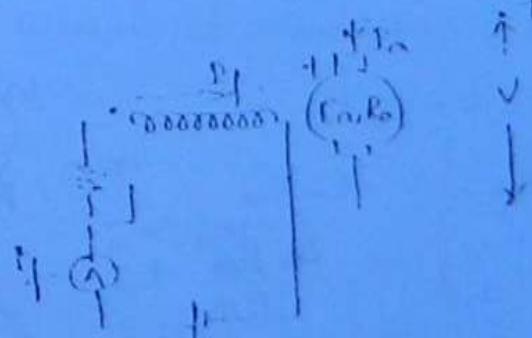

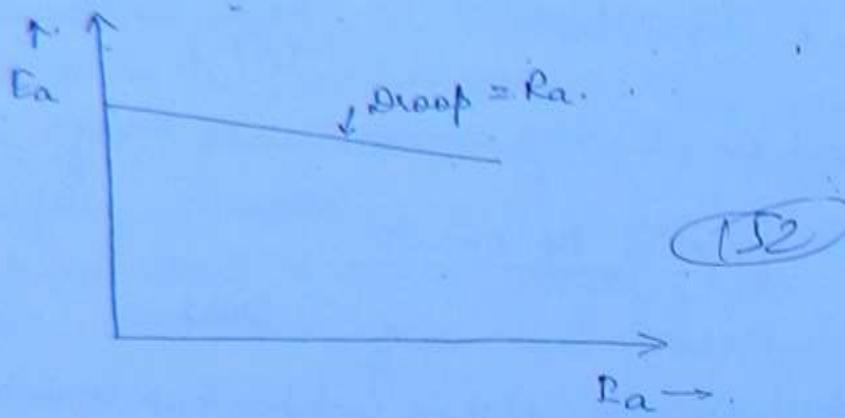


$$\psi \sim E_a$$
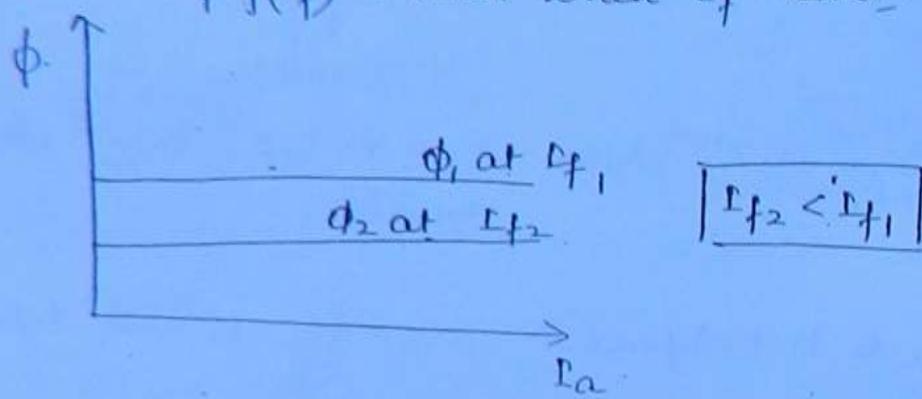
$$\phi = f(t_f) = \text{const when } E_f = \text{const}$$



$$T \sim I_a$$

$$T = k\phi E_a$$

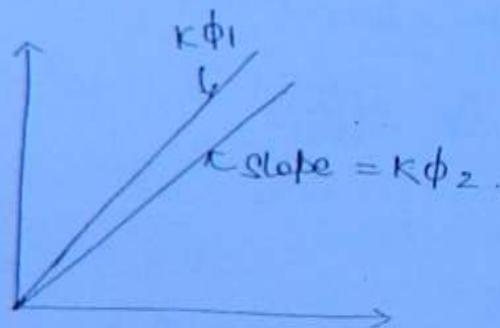



$$\omega_m \sim I_a \Rightarrow$$

$$E_a = V - E_a R_a$$

$$k\phi \omega_m = V - E_a R_a$$
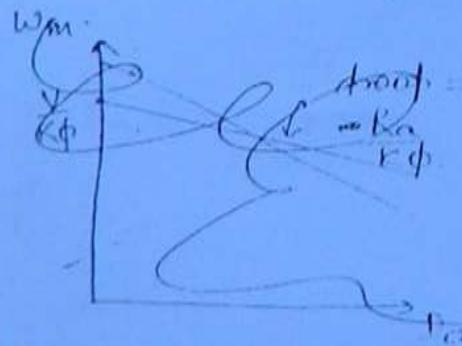
$$\omega_m = \frac{V}{k\phi} - \frac{E_a R_a}{k\phi} R_a$$



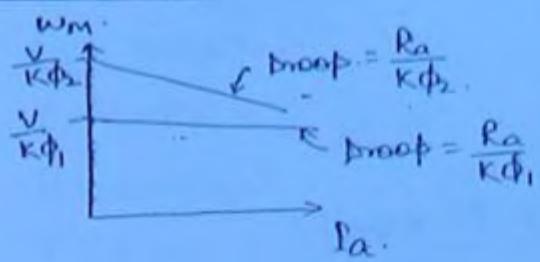



(TSB)

W_m N.T. →

$$W_m = \frac{V}{K\phi} - \frac{R_a}{K\phi} \times \frac{T_{load}}{K\phi} \quad [T = K\phi I_a]$$

$$W_m = \frac{V}{K\phi} - \frac{R_a}{(K\phi)^2} T_{load}$$

Kφ > 1

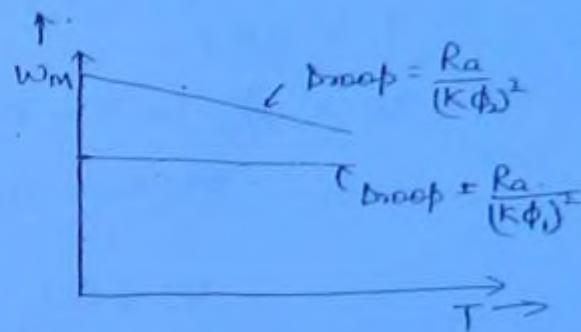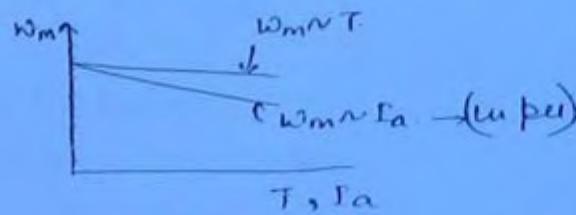



char. of Shunt Motor:

1) E_a ~ I_a Same as Separately excited motor.

2) φ ~ I_a, T_n I_a, W_m ~ I_a, W_m N.T similar as those respect in Separately excited motor except that only one each shall be obtained in a shunt motor instead of a family of such char. in separately excited motor.

Q. A DC Shunt motor is connected to 125 V dc supply line and is found to have back emf of 90 V at 1200 rpm. Find speed of this m/c, when it develops a torque of 30 N.m. R_a = 0.2 Ω.

Ans.

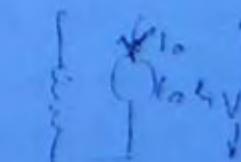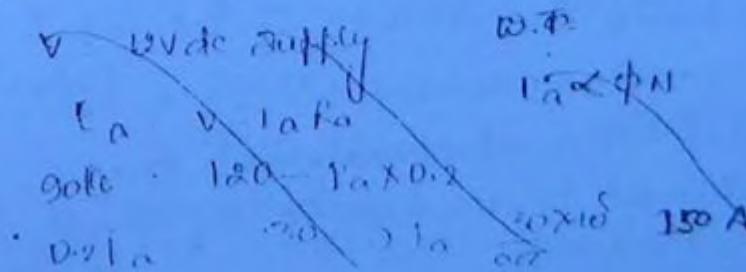

Ques -

~~Ques~~ at counter

$$\text{a) } E_b = K\phi w_m \quad w_m = \frac{2\pi \times 1200}{60} \\ \Rightarrow K\phi = \frac{E_b}{w_m} = \frac{90}{\frac{2\pi \times 1200}{60}} = 0.716.$$

$$T = k\phi I_a$$

$$30 = \frac{3}{40} I_a \times 0.716.$$

(154)

$$I_a = \frac{30 \times 40}{3} \approx 400 \times \frac{30}{0.716}$$

$$= 41.89 \text{ A}$$

$$E_{a_2} = V - E_{a_1} R_a \\ = 125 - 41.89 \times 0.2 \\ = 116.622 \text{ V}$$

$$E_a = K\phi w_m$$

$\propto N$

$$\frac{E_{a_2}}{E_{a_1}} = \frac{N_2}{N_1}$$

$$\frac{116.6}{90} = \frac{N_2}{1200}$$

$$\Rightarrow N_2 = 1555 \text{ rev/min}$$

- Q. A .40 HP, 230 V, 1150 rpm shunt motor has 4 poles, 4 parallel armature path and 882 armature conductors. Armature C.R. Resistance $R_a = 0.188 \Omega$ at rated speed and rated O.P. The armature current is 73 A. and d/d current is 1.6 A. Calculate (a) the electromagnetic torque, (b) the flux/pole (c) rotational losses, (d) η (e) shaft load torque.

$$R_a = 0.188 \Omega$$

$$P = 4 \text{ poles}$$

$$A = 4$$

$$P_e = 20 \times 746 \text{ W}$$

$$V = 230 \text{ V}$$

$$N = 1150 \text{ rpm}$$

$$\omega_m = \frac{2\pi N}{60}$$

$$Z = 882$$

$$I_a = 73 \text{ A}$$

$$I_f = 1.6 \text{ A}$$

$$E_b = \frac{\phi Z N P}{60 A}$$

$$E_L = \frac{P_o}{V} = \frac{20 \times 746}{230}$$

$$E_a = V - E_a R_a$$

$$= 230 - 73 \times 0.188$$

$$= 216.276$$

$$\frac{E_a}{60 \omega_m} = K \phi = \frac{216.276 \times 60}{230 \times 1150} = 1.79589$$

ϕ

$$(a) T = K \phi I_a$$

$$\phi = 1.79589 \times 73$$

$$= 131.101 \text{ N-m}$$

$$(b) \text{ flux/pole} = \phi$$

$$E_a = \frac{\phi Z N P}{60 A}$$

$$\Rightarrow 216.276 = \frac{\phi \times 882 \times 1150}{60} \times \frac{1}{4}$$


$$\therefore \phi = 0.0128 \text{ wb/pole}$$

$$(c) P_{output} = 20 \times 746 \text{ W}$$

$$= 14920 \text{ W}$$

$$P_{out} = P_a - P_{output}$$
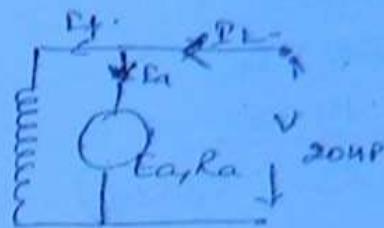
$$\therefore P_{out} = P_{a, ideal} - (216.276 \times 73) - 14920 \leq 870 \text{ W}$$



(SS)

$$\begin{aligned}
 (9) \quad \eta &= \frac{14920}{14920 \times 1.6} \\
 &= \frac{14920}{230(1.6 + 1.4)} \\
 &= \frac{14920}{230 \times (7.3 + 1.6)} \\
 &= 86.96\%
 \end{aligned}$$



(15b)

$$\begin{aligned}
 \text{(i) Shaft load torque} &= \frac{P_{out}}{\omega_m} \\
 &= \frac{14920}{120 \cdot 43} \\
 &= 124 \text{ NM.}
 \end{aligned}$$

DC Series motor : →


E_a vs I_a

$$E_a = V - I_a(R_a + R_{se})$$

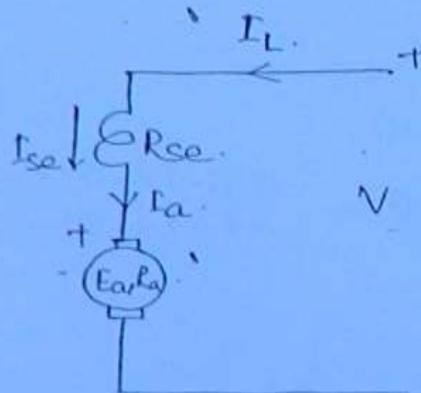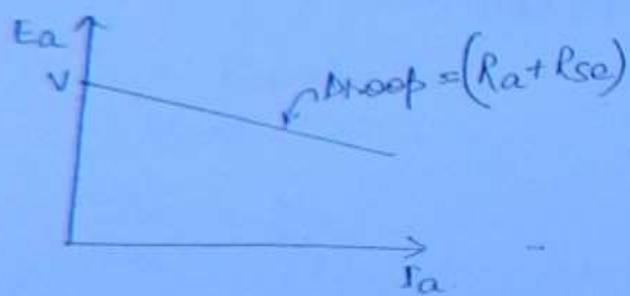


Φ vs I_a
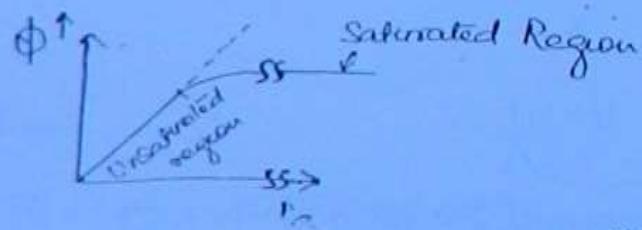
$$\begin{aligned}
 \Phi &= f(I_{se}) \\
 &= f(I_a)
 \end{aligned}$$



T vs I_a
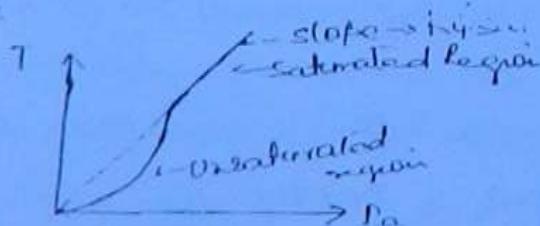
$$\begin{aligned}
 T &= K\phi I_a \\
 &= Kf(I_a) I_a
 \end{aligned}$$



$KI_a^2 \rightarrow$ Unsaturation region $\phi \propto I_a \Rightarrow \phi = k_{se} I_a$.

$K\phi I_a \rightarrow$ Saturated region $\phi = \phi_{sat} = \text{const}$

Starting torque is more high.

$$w_m \sim I_a$$

$$E_a = V - I_a(R_a + R_{se})$$

$$K\phi w_m = V - I_a(R_a + R_{se}) \rightarrow 0$$

Unsaturated Region \rightarrow

(157)


$$K \cdot I_a \cdot w_m = V - I_a(R_a + R_{se})$$

$$\Rightarrow w_m = \frac{V}{K \cdot I_a} - \frac{(R_a + R_{se})}{K \cdot I_a} \quad \phi = K_{se} I_a \text{ as } \phi \propto I_a$$

Saturated region \rightarrow $\frac{I_s}{I_a}$ $w_m \propto \frac{1}{I_a}$

$$K\phi w_m = V - I_a(R_a + R_{se})$$
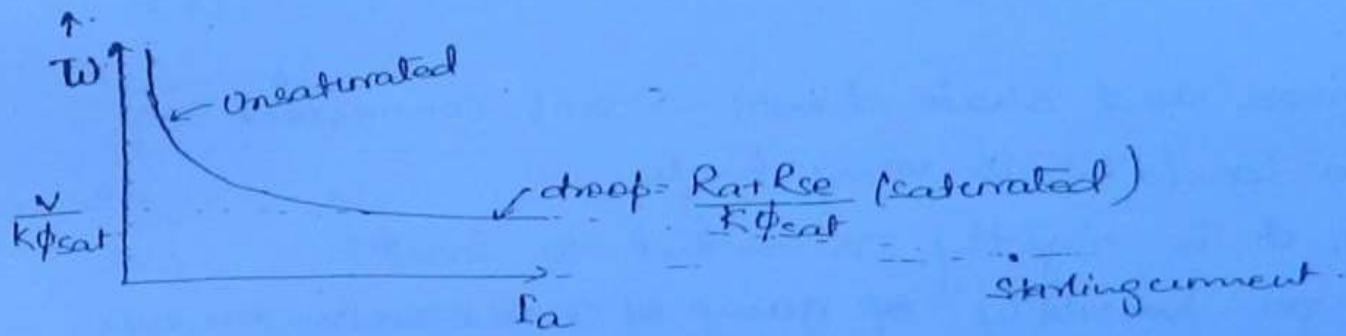
$$\Rightarrow w_m = \frac{V}{K\phi_{sat}} - \frac{I_a(R_a + R_{se})}{K\phi_{sat}} \quad \phi = \phi_{sat} = \text{constant}$$



$w_m \propto T$

$$\begin{aligned} w_m &= \frac{V}{K\phi} - \frac{I_a}{K\phi} (R_a + R_{se}) \\ &= \frac{V}{K\phi} - \frac{R_a + R_{se}}{K\phi} \frac{I_a T}{K\phi} \\ &= \frac{V}{K\phi} - \frac{R_a + R_{se}}{K^2} \frac{T}{\phi^2} \end{aligned}$$

$$I_a \approx T = K\phi I_a$$

$$I_a = \frac{T}{K\phi}$$

$$\phi \propto K_{se} T$$

Unsaturated Region

$$\phi = K_{se} I_a = K_{se} \times \frac{T}{K\phi} \rightarrow \phi = \sqrt{\frac{K_{se}}{K}} ST = K' ST$$

$$w_m = \frac{V}{K K' ST} - \frac{R_a + R_{se}}{K^2} \frac{T}{K_{se}^2 T^2}$$



$$= \frac{V}{K K' ST} - \frac{R_a + R_{se}}{K^2} \frac{T}{K' T} = \frac{V}{K K' ST} - \frac{R_a + R_{se}}{K^2}$$

Saturated Region \rightarrow

$$\phi = \phi_{sat} = \text{const}$$

$$\begin{aligned} W_m &= \frac{V}{K\phi_{sat}} - \frac{R + L \omega_e}{K^2} \frac{T}{\phi_{sat}^2} \\ &= \frac{V}{K\phi_{sat}} - \frac{R + L \omega_e}{(K\phi_{sat})^2} T \end{aligned}$$

(158)

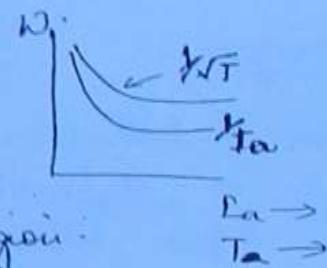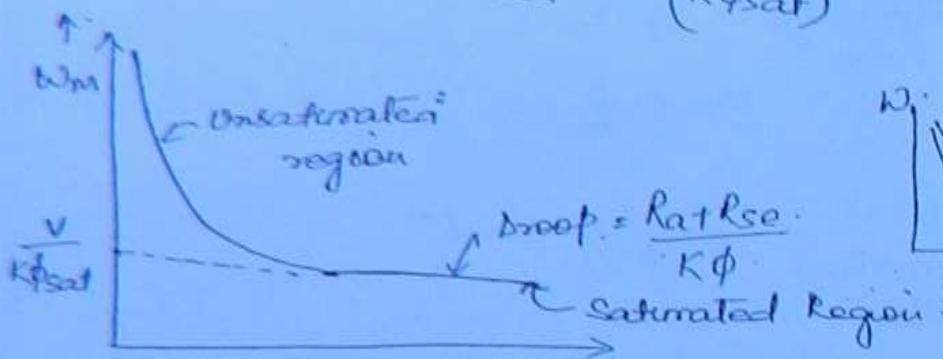

belt driven and chain driven \rightarrow not connected as on \Rightarrow no load ω is very high.
and so, it is rigidly connected to load.
There is no possibility of going of series motor on no load.

Q: A separately excited DC motor is operating at 1200 rpm. It draws 100 A from the line at a terminal voltage of 300 V. Armature resistance b/w terminals is 0.07 Ω .

- a) Find the torque being developed by this motor
b) find the speed and armature current in rpm when the torque is 300 Nm for the same excitation.

a) $T = \frac{i_a r_a}{\omega_m}$, $\therefore \frac{300 \times 100 \times 0.07}{2 \pi \times 1200} = 17.45$ N-m

$$T_a = 300 = \frac{V - i_a r_a}{r_a} \times 100$$

$$300 = \frac{300 - 100 \times 0.07}{0.07} \times 100$$

$$(b) T = K\phi I_a$$

$$T \propto I_a$$

$$\frac{T_2}{T_1} = \frac{I_{a2}}{I_{a1}}$$

$$\frac{300}{177.45} = \frac{I_{a2}}{100}$$

(154)

$$\Rightarrow I_{a2} = \frac{300 \times 100}{177.45} = 169A$$

$$E_{a2} = 230 - 169 \times 0.07 \\ = 218.17V$$

$$E_a = K\phi N$$

$$\propto N$$


$$\frac{E_{a2}}{E_{a1}} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{218.17}{223} = \frac{N_2}{1200}$$

$$\Rightarrow N_2 = \frac{1200 \times 218.17}{223} \\ = 1174 \text{ rpm.}$$

Q) A 230V shunt motor having an armature resistance of 0.05 Ω and a field resistance of 75 Ω draws a line current of 7A while running light 1120 rpm. Line current at a given load 46A. Determine the motor speed and η at given load.
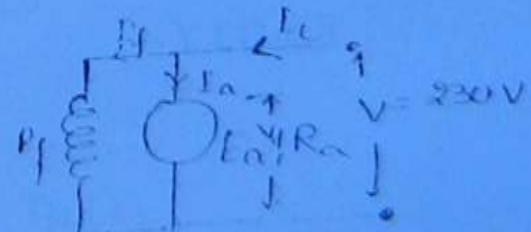
$$I_a = V - I_a R_a \\ = 230 - I_a \times 0.05$$



$$T = K\phi I_a \cdot I_f \quad \frac{V}{R_f} = \frac{230}{75} = 3.067$$

$$I_f = 7A \quad I_{a1} = 3.067 \quad \underline{\underline{223}}$$

$$I_{a1} = \frac{230 - 7 \times 0.05}{0.05} = 45.8$$

~~On light load (ie No load)~~

$$\begin{aligned} P_{\text{ext}} &= E_a I_a \\ &= 229.8 \times 3.933 \\ &= 903.8 \text{ N} \end{aligned}$$

At given load :-

(16)

$$\begin{aligned} I_{a_2} &= 46 - 3.067 \\ &= 42.933 \text{ A} \end{aligned}$$

$$\begin{aligned} E_{a_2} &= 230 - 42.933 \times 0.05 \\ &= 227.85 \end{aligned}$$

Since $E_a = K\phi w_m$
 $\propto w_m \propto N$


$$\frac{E_{a_2}}{E_{a_1}} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{227.85}{229.8} = \frac{N_2}{1120}$$



$$\Rightarrow N_2 = 1110.5 \text{ rpm}$$


$$\begin{aligned} \eta &= \frac{E_{a_2} I_{a_2} - P_{\text{ext}}}{V I_L} \\ &= \frac{227.85 \times 42.933 - 903.8}{230 \times 46} \\ &= 83.92\% \end{aligned}$$

Parallel operation of Generators:-

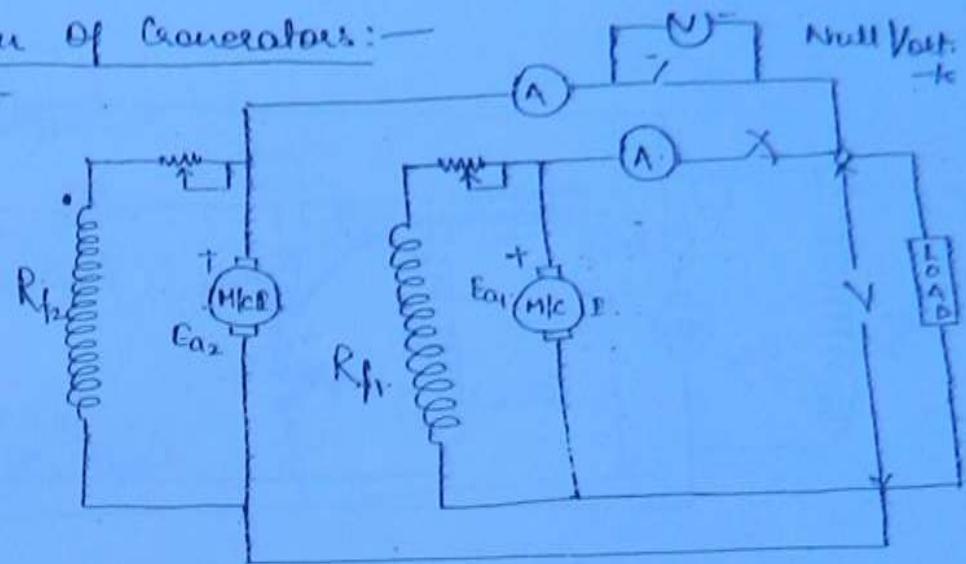

(161)

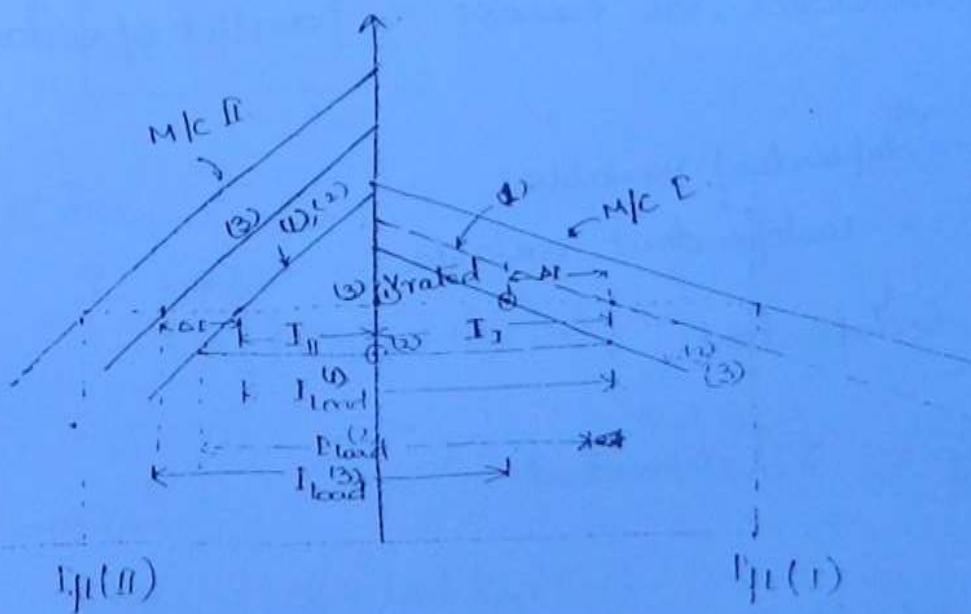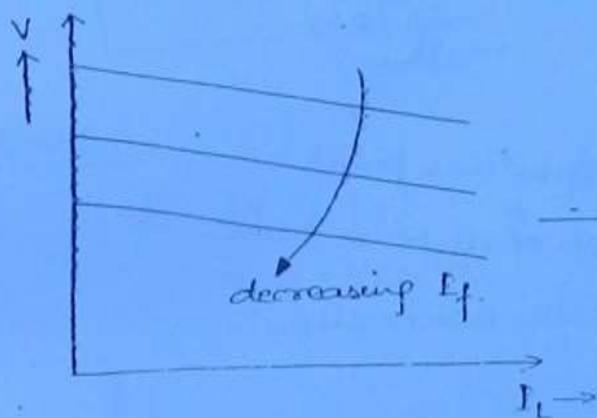

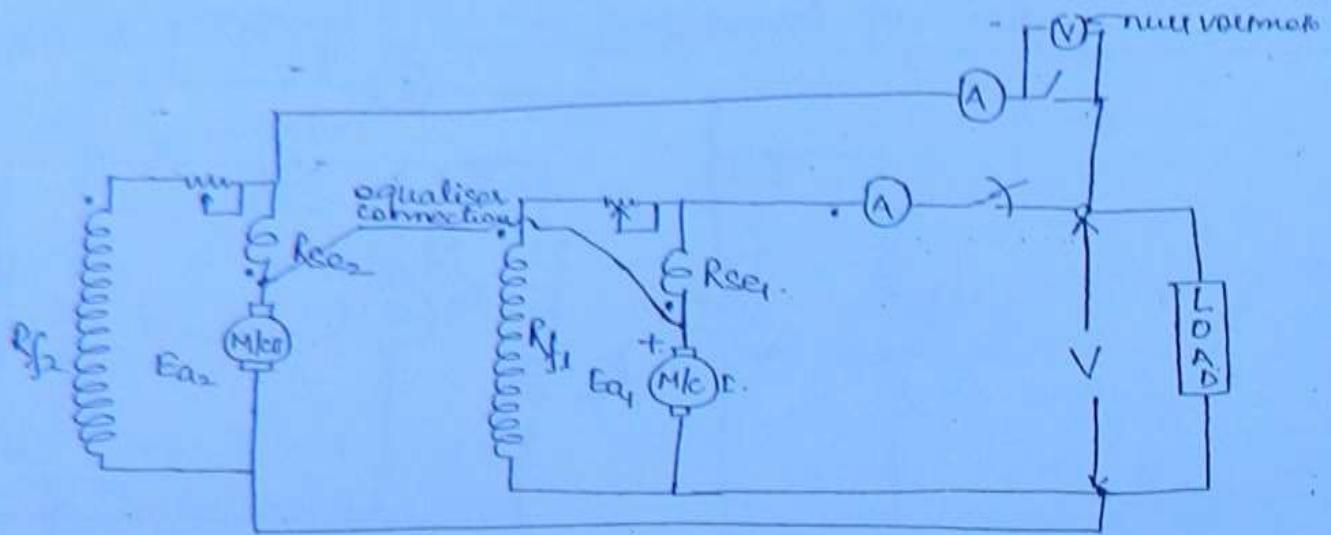

in lap wound m/c only.

(162)



equaliser ring \rightarrow connection of all equaliser points.
 pot. of all pt is same
 and connection is called equaliser connection.

For parallel operation, drooping characteristics is must.
 For rising characteristics, we cannot do parallel operation

Gen —

$$E_a = k\phi u_m \xrightarrow{1^{\text{st}}} \text{dependent variable}$$

Speed of m/c \rightarrow independent variable

$$I_a = \frac{E_a}{R_a + R_L} \xrightarrow{2^{\text{nd}}} \text{dependent}$$

$$\therefore E_a - I_a R_a \xrightarrow{3^{\text{rd}} \text{ or last}} \text{dependent}$$

motor \rightarrow

terminal V \rightarrow independent variable


$$i_a = \frac{V}{R_a + \frac{T_b}{k\phi}} \xrightarrow{1^{\text{st}}} \text{dependent variable}$$

DC motor char :-


Neglecting AR effect :-

$E_a \sim I_a$

$$E_a = V - I_a(R_a + R_{se})$$

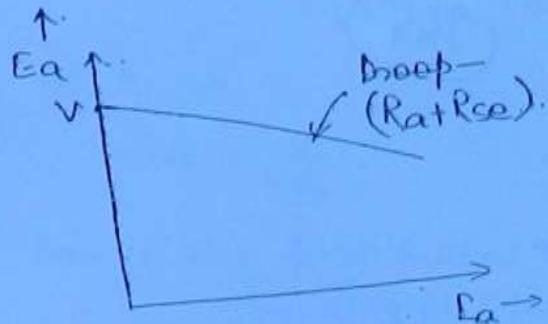



(163)

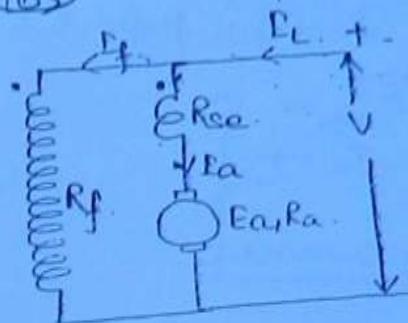

$\phi \sim I_a$

$$\phi = f(I_f, I_a)$$


$$= N_f I_f + N_{se} I_a$$

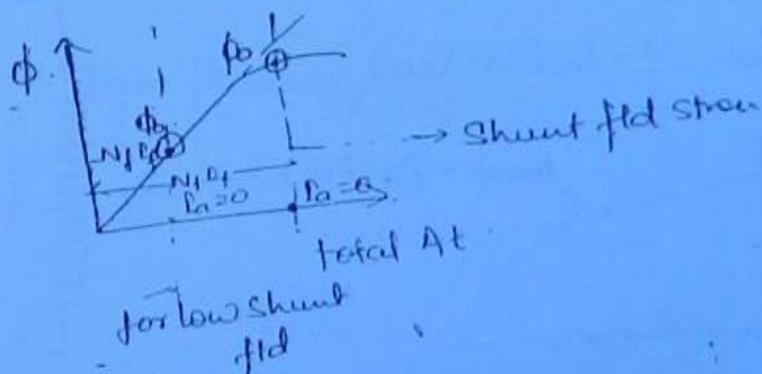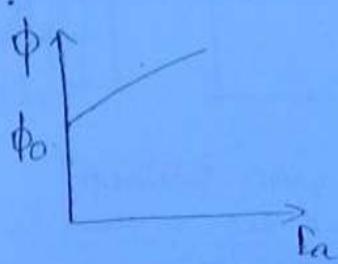

$T \sim I_a$

$$T = K\phi I_a$$

$$= K I_a [f(N_f I_f + N_{se} I_a)]$$

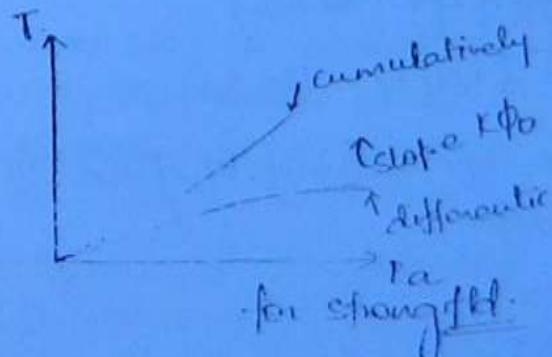


$\omega_m \sim I_a$

$$\omega_m = V - I_a(R_a + R_{se})$$

$$\approx K \omega_m \quad V = I_a(R_a + R_{se})$$

$$\Rightarrow \omega_m \approx \frac{V}{K \phi}$$
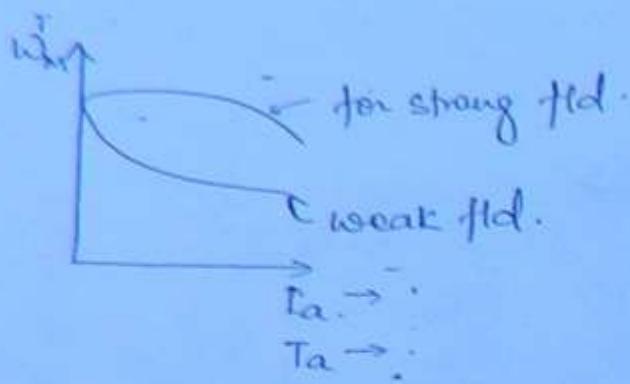
$$\frac{V}{K \phi} = \frac{V}{I_a(R_a + R_{se})} = \frac{V}{I_a \left(R_a + R_{se} \right)} = \frac{V}{K \left(N_f I_f + N_{se} I_a \right)}$$



164




Transformers...

Differentially compounded Motor:

E_a and I_a :

$$E_a = V - I_a(R_{se} + R_f)$$

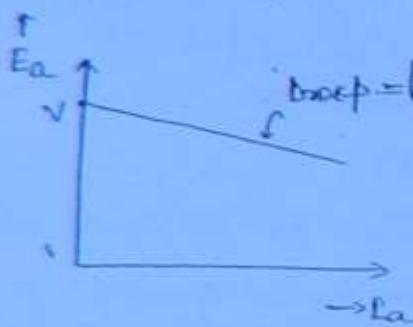


$\phi \sim I_a$



$$\phi = f(I_f, I_a)$$

$$= f(N_f I_f + N_{se} I_{se})$$

$$= f(N_f I_f - N_{se} I_a)$$

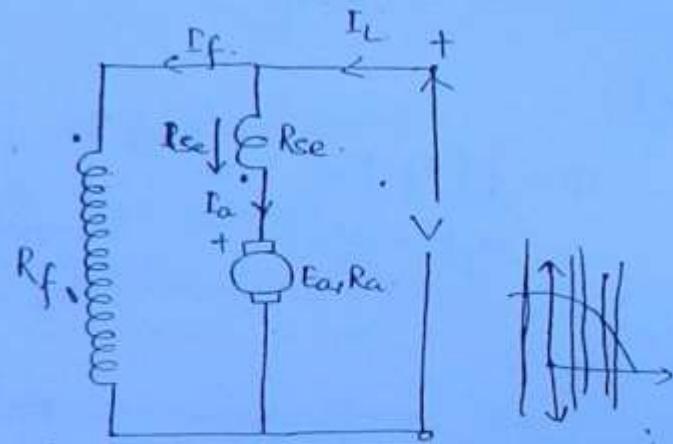

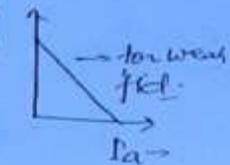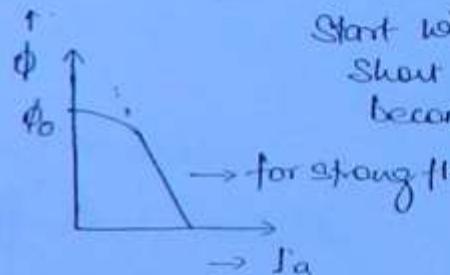Start with severest fld
short shrt so that I_a become low.




Process of unbuild of fld is the reverse of the process of build up.

$T \propto I_a$

$$T = K\phi I_a$$

$$= K I_a f(N_f I_f - N_{se} I_a)$$

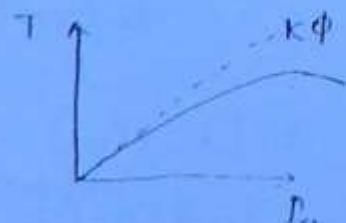

$\omega_m \propto I_a$

$$E = V - I_a R_a \text{ (at } \omega_m)$$


$$K\phi \omega_m = V - I_a R_a \text{ (at } \omega_m)$$

$$K_f (N_f f_f - N_s e_a) \omega_m = V - I_a R_a \text{ (at } \omega_m) \quad (165)$$


$$\therefore \omega_m = \frac{V - I_a R_a}{K_f (N_f f_f - N_s e_a)}$$

at $I_a = 0$,

$$\omega_{m0} = \frac{V}{K\phi_0}$$

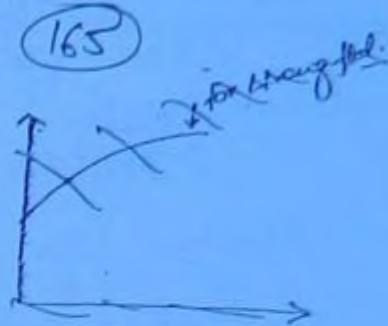

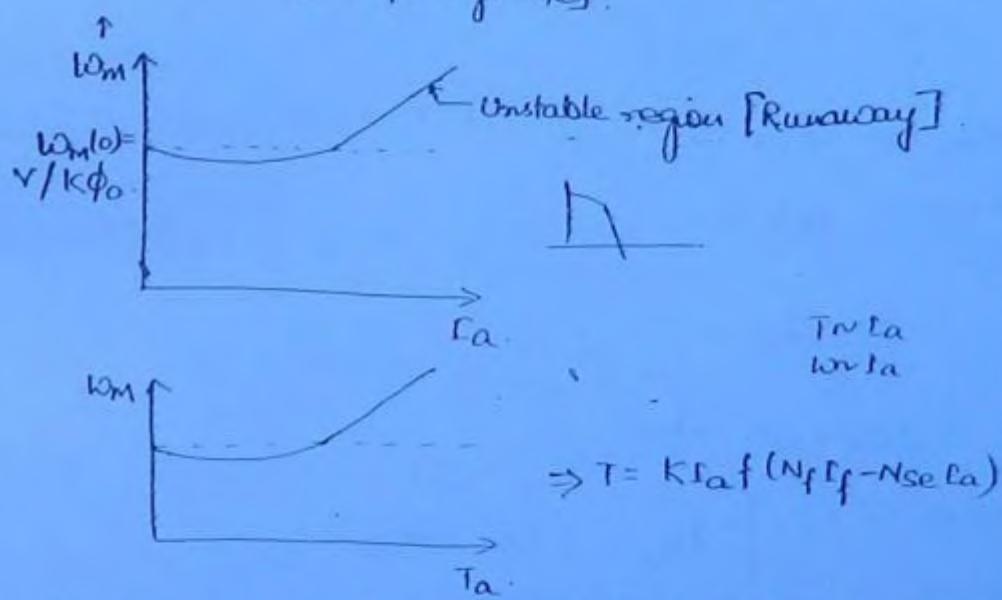This is the first motor which have speed regulation ≈ 0 .
[Except sym/m/c].



$$\Rightarrow T = K_f I_a f_f (N_f f_f - N_s e_a)$$


Q. A 100HP, 250V, 1200 rpm dc shunt motor has an armature resistance of 0.03Ω . The field current of the motor is 6A. and the motor is const. torque load with a line current of 126A and speed of 1103 rpm. Assuming linear magnetic curve of the motor, calc. the motor speed, if the field current is reduced to 5A. Neglect rotational losses and effect of armature reaction.

Ans $R_a = 0.03 \Omega$ $P = 100 \times 746$

$$I_a = \frac{250 \times 1200}{60} = 4600 \text{ A}$$

$$P_f = 6 \text{ A}$$
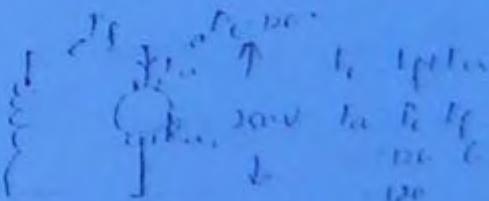
$$r = n_r / D \cdot 2 \pi = 1200 \text{ rev/min} / 60 \text{ sec} \cdot 2 \pi \cdot 0.03 = 846.4$$



$$E = K\phi \omega_m \quad , \quad I_f = 5A$$

$$\begin{aligned} E_{a_2} &= V - I_{a_2} R_a \\ &= 230 - (26-5) 0.03 \\ &= \frac{230}{226.37} \quad \downarrow \quad I_{a_2} = \text{wrong} \end{aligned}$$

$$\omega_m = \frac{E_{a_2}}{K\phi}$$

(16b)

$$\omega_{m0} = \frac{V}{K\phi_0}$$

$$\Rightarrow K\phi = \frac{V}{\omega_{m0}} = \frac{230 \times 60}{2 \times 1200} = 1.8303$$

$$\omega_m = 123.68$$

$$\Rightarrow \frac{2\pi N}{60} = 123.68$$

$$\Rightarrow N = \frac{123 \times 60}{2\pi} = 1181.06 \text{ rpm}$$

$$I_{a_1} = 126.6 = 120A$$

$$\begin{aligned} E_{a_1} &= 230 - 120 \times 0.03 \\ &= 246.4 \end{aligned}$$

$$T = K\phi I_a$$

$$\propto \phi I_a$$

$$\propto I_f^2 I_a$$

$$\Rightarrow I_f^2 I_{a_2} = I_f^2 \times 120$$

$$\Rightarrow 5 I_{a_2} = 6 \times 120$$

$$\Rightarrow I_{a_2} = 144A$$

$$\begin{aligned} E_{a_2} &= 230 - 144 \times 0.03 \\ &= 245.7V \end{aligned}$$

$$E_a = K\phi \omega_m$$

$$\propto \phi N$$

$$E_a \propto I_f N$$

$$\Rightarrow \frac{E_{a_2}}{E_{a_1}} = \frac{I_f^2 N_2}{I_f^2 N_1}$$

$$\Rightarrow \frac{245.7}{246.4} = \frac{5 \times N_2}{6 \times 1103}$$

$$\Rightarrow N_2 \approx 1320 \text{ rpm}$$

Speed control →

$$E_a = V - I_a R_a$$

(167)

$$K\phi \omega_m = V - I_a R_a$$

$$\Rightarrow \omega_m = \frac{V - I_a R_a}{K\phi} \quad \begin{matrix} \leftarrow \text{Armature} \\ \leftarrow \text{control} \end{matrix}$$

control — Armature resistance con
L Armature terminal Vol
control.


R_{adj} increases: 

$$\frac{d\omega_m}{dt} = T - T_{load}$$

= give for acc.

$$\uparrow T = K\phi I_a$$

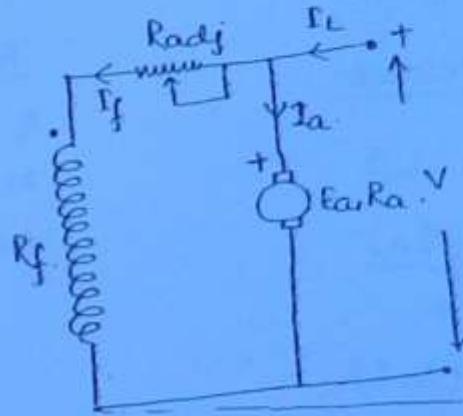$I_a \uparrow$ as compare to $\phi \downarrow$



CAUSE Effect behaviour : →

$$1) \downarrow I_f = \frac{V}{R_f + \uparrow R_{adj}}$$

$$2) \downarrow \phi = f(I_f)$$

$$3) \downarrow E_a = K\phi \downarrow \omega_m$$

$$4) \uparrow I_a = \frac{V - (\downarrow E_a)}{R_a}$$

$$5) T = \bar{R}(\phi)(I_a)$$

∴ Increase in I_a is much higher than reduction in ϕ .

Proof →

$$I_a = \frac{V - E_a}{R_a}$$

$$= \frac{V}{R_a} - \frac{K\phi \omega_m}{R_a}$$

$$\Rightarrow \frac{d\dot{\theta}_a}{d\phi} = 0 - \frac{Kw_m}{Ra} \rightarrow \text{very very high}$$

\emptyset

6) $T > T_{load}$

7) $\frac{dw_m}{dt} = \frac{1}{J} (T - T_{load})$

= five.

$\therefore w_m$ increase.

8) $\uparrow E_a = K\phi w_m \uparrow$

9) $\downarrow \dot{\theta}_a = \frac{v - (TE_a)}{Ra}$

10) $\downarrow T = K\phi (\dot{\theta}_a \downarrow)$

Until $T = T_{load}$ again at higher w_m .

$$f_f = \frac{V}{R_f}$$

$R_f \rightarrow$ constant, f_f is decreased only.


\Rightarrow Fld control for speed control above base, because f_{ld} can not be made any stronger.

for below speed (base)

$$w_m = \frac{V}{K\phi} - \frac{\dot{\theta}_a Ra}{K\phi}$$

$\propto \frac{1}{\phi}$

$$\partial \{ \phi \times f_f \}$$

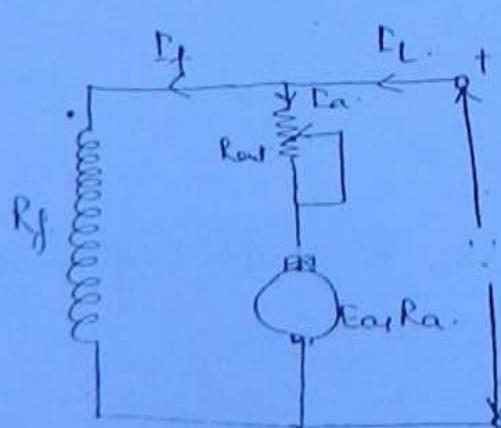

Ammature Resistance control

for speed control below base speed. \rightarrow

Rept increases \rightarrow

169

$$1) \downarrow I_a = \frac{V - E_a}{R_a + R_{ext}}$$

$$2) \downarrow T = K\phi I_a \downarrow$$

$$3) T < T_{load}$$

$$4) \frac{d\omega_m}{dt} = \frac{1}{J} (T - T_{load})$$

ω_m decreases.

$$5) \downarrow E_a = K\phi \omega \downarrow$$

$$6) \uparrow I_a = \frac{V - E_a}{R_a + R_{ext}}$$

$$7) \uparrow T = K\phi I_a \uparrow$$

until $T = T_{load}$ again
at reduced ω_m .

$$E_a = V - I_a (R_a + R_{ext})$$


$$\Rightarrow K\phi \omega_m = V - I_a (R_a + R_{ext})$$

$$2) \omega_m = \frac{V}{K\phi} - \frac{I_a (R_a + R_{ext})}{K\phi}$$

$$\eta \approx \frac{E_a I_a}{V I_a}$$

$$\approx \frac{I_a}{V}$$
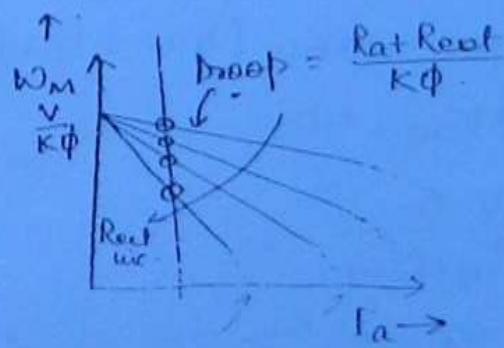
$$\approx \frac{K\phi \omega_m}{K\phi \omega_{m0}} \quad \frac{\omega_m}{\omega_{m0}}$$



Not recommended for
large m/c.

Q. A shunt motor operates at a flux $\phi = 25 \text{ mW/pole}$, is lap wound; and has two poles and 360 conductors. $R_a = 0.12 \Omega$ and motor is designed to operate at 115 V taking 60 A in armature current at full load.

A) Determine the value of R_{ext} to be inserted in the armature circuit so that armature current shall not exceed twice its full load value at starting.


$$\underline{\phi} = 25 \text{ mW/pole} \quad (170)$$

~~$$E_a = \frac{12N\phi}{60} \cdot 60A$$~~

$$= \frac{0.25 \times 360 \times 2 \times N}{60 \times 2}$$

$$= 1.5N$$

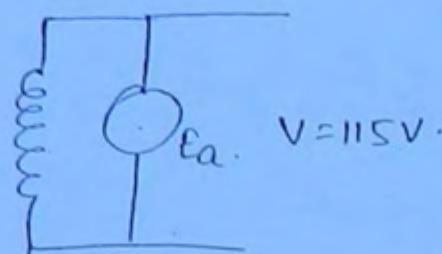~~$$E_a = 1.5N = 1.5 \times 120 \times \frac{50}{2}$$~~



$$N = \frac{120f}{P} = \frac{120 \times 50}{2}$$

~~$$E_a = V - I_a(R_a + R_{\text{ext}})$$~~

$$= 115 - 2 \times 60(0.12 + R_{\text{ext}})$$

$$4500 = 115 - 2 \times 60(0.12 + R_{\text{ext}})$$

~~$$E_a = K\phi W_m = 0$$~~

$$I_a = \frac{V - 0}{R_a + R_{\text{ext}}}$$

$$2 \times 60 = \frac{115 - 0}{0.12 + R_{\text{ext}}}$$

$$R_{\text{ext}} = 0.838 \Omega$$

(b) When motor reached at 400 rpm, the load resist is cut at 50Ω , what is armature current then at this speed

(T2)

$$\text{Ans: } E_a = \frac{1.5 \times 400}{800} = 0.75$$

$$E_a = \frac{0.15}{0.12} \times 400 = 60$$

$$V = 115 -$$

$$N = 400 \text{ rpm}$$

$$R_{aef} = \frac{0.838}{2} \Omega$$

$$I_a = \frac{V - E_a}{(R_{aef} + R_a)} = \frac{115 - 60}{(0.12 + \frac{0.838}{2})}$$

$$\Rightarrow 102.04 \text{ A.}$$

(c) Load res is completely cut out. When motor reaches its final speed. Armature current then is at its full load value, cat. motor speed.

$$\text{Ans: } I_a = \frac{V - E_a}{R_a} = \frac{115 - E_a}{0.12}$$

$$60 = \frac{115 - K \phi W_m \cdot E_a}{0.12}$$

$$\Rightarrow E_a = -60 \times 0.12 + 115$$

$$= 107.8$$

$$E_a = K \phi W_m$$

$I_a \propto N$

$$\frac{E_a_2}{E_a_1} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{107.8}{60} = \frac{N_2}{400} \Rightarrow N_2 = 718.67 \text{ rpm.}$$

d) compute the developed T in part-a,b,c.

at b

$$E = K\phi \omega_m$$

$$T = K\phi I_a$$

$$\frac{E}{\omega_m} = \frac{T}{I_a}$$

$$\Rightarrow T = \frac{E}{\omega_m} \times I_a$$

Ans.

$$T = K\phi I_a$$

$$= 172 \text{ Nm}$$

(172)

at b:

$$\frac{60 \times 60}{2\pi \times 400} = \frac{T}{102.4}$$

$$T = 146.68 \text{ Nm}$$

$$T = \frac{E_a I_a}{\omega_m} \text{ when } \omega_m \neq 0.$$

$$T = K\phi I_a$$

$$K = \frac{P_2}{2\pi A}$$

at c:

$$\frac{107.8 \times 60}{718.67 \times 2 \times \pi} = \frac{T}{60}$$

$$\Rightarrow T = 85.9432 \text{ Nm}$$

$$\omega_m \propto \frac{V}{\phi} \propto \frac{V}{V} \Rightarrow \text{const.}$$

When supply voltage changes, there will be no change in speed.

Ammature terminal Voltage Control $\rightarrow [\phi \rightarrow \text{const}]$
for $V_A \leq V_{\text{rated}}$

Speed control below base speed. because V cannot be exceed beyond V_{rated}
 V_A decrease.

D) $I_a = \frac{V_A - E_a}{R_a}$

$$2) T_b = K\phi I_a \downarrow$$

$$3) T < T_{load}$$

$$4) \frac{d\omega_m}{dt} = \frac{1}{J} [T - T_{load}]$$

= -ive.

(173)

ω_m decreases.

$$5) \downarrow E_a = K\phi \omega_m \downarrow$$

$$6) \uparrow I_a = \frac{V_A - E_A \downarrow}{R_a}$$


$$7) \uparrow T = K\phi I_a \uparrow$$

until $T = T_{load}$, again

at reduced ω_m

Q. A separately excited dc motor is initially running with $V = 250$ V DC, $I_a = 120$ A and $N = 1103$ rpm, by supplying const torque load, what will be speed of motor is V reduced to 200V. assume $R_a = 0.03 \Omega$.

Ans:

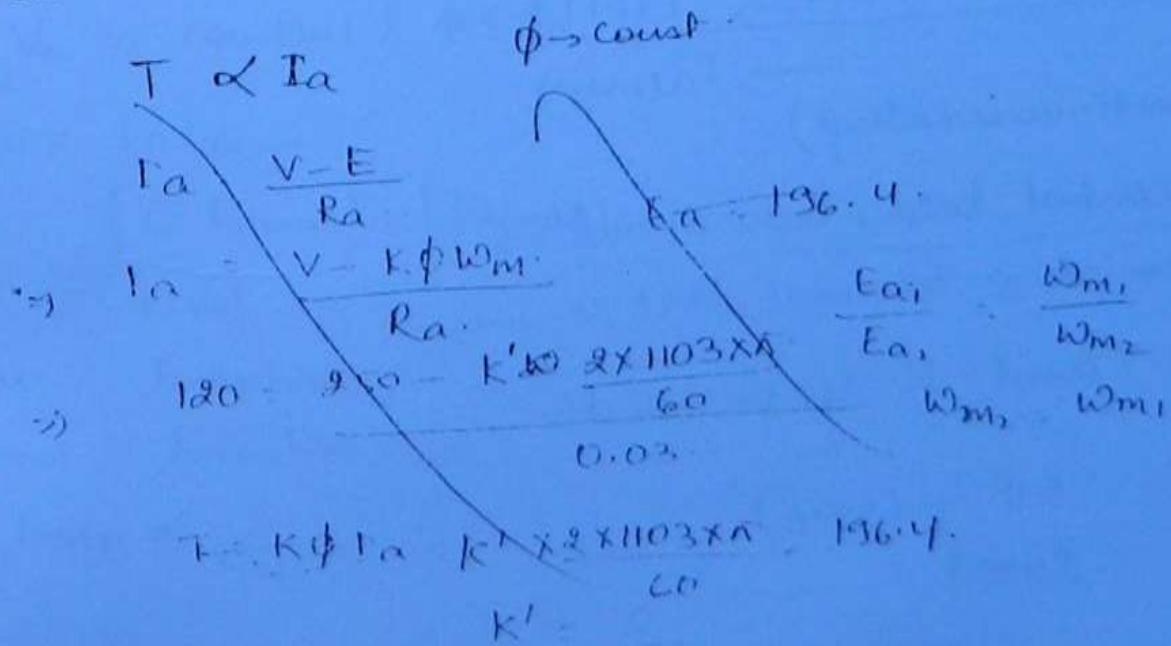

$$E_{a_1} = 200 - 120 \times 0.3 \\ = 184.4 \text{ V}$$

$T \propto I_a \rightarrow \text{const}$

$$I_{a_2} = I_{a_1} = 120 \text{ A}$$

(174)

$$E_{a_2} = 200 - 120 \times 0.03 \\ = 196.4 \text{ Volts}$$

$$E_a = K\phi \omega_m$$

$E_a \propto N$


$$\Rightarrow \frac{E_{a_2}}{E_{a_1}} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{196.4}{184.4} = \frac{N_2}{1103}$$

$$\Rightarrow N_2 = 879 \text{ rpm}$$

$$\omega_m \propto \frac{V}{\phi}$$

$$\omega_m \propto V$$

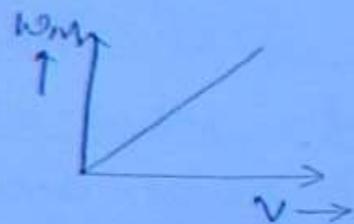

TORQUE AND POWER LIMIT →


MCR → $P_a(\text{max})$.
(max. continuous rating)

Speed control below base speed →

By → Commutator terminal Volt. control.


$\phi = \text{const}$ & V_a is variable.
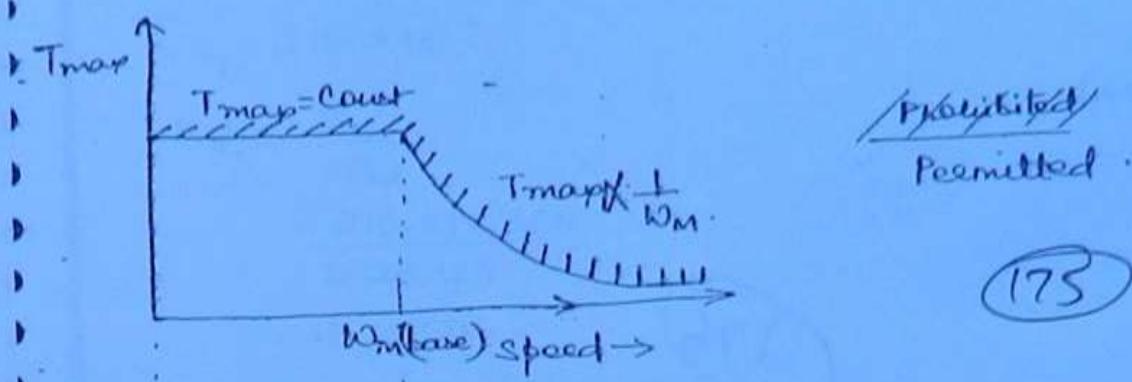
$$T_{\text{max}} = \frac{k\phi P_a(\text{max})}{\text{const}}$$



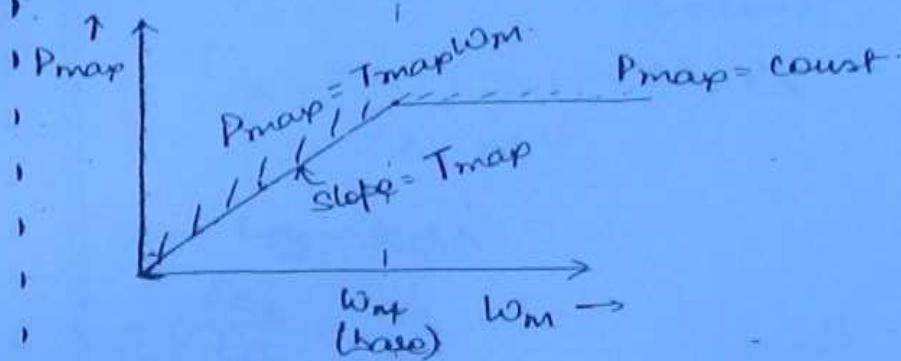(175)

$$Now P_{max} = T_{max} \times \omega_m \propto \omega_m$$



→ Armature \leftarrow ffd control
terminal VOLT for constant
control power (HP)
For Constant drive
torque drive

If Speed control above base speed \rightarrow

By ffd control

Here V_a is constant & $\phi \leq \phi_0$
Alternative

$$P_{max} = E_a I_{a(max)}$$

$$= [V_a - I_{a(max)} R_a] / I_{a(max)}$$

const

$$P_{max} = T_{max} \omega_m$$

$$\Rightarrow \text{const} = T_{max} \omega_m$$

$$\Rightarrow T_{max} \propto \frac{1}{\omega_m}$$

Alternate 2 →

$$T_{max} = K\phi P_{max}$$

$$\propto \phi$$

$$\propto \frac{E_a}{\omega_m}$$

$$\propto \frac{V - I_a R_a}{\omega_m}$$

$$\propto \frac{\text{const}}{\omega_m}$$

$$\propto \frac{1}{\omega_m}$$

(176)

$$T_{max} \omega_m \propto \text{const}$$

$$\propto P_{max} \rightarrow \text{const}$$

$$P_{max} = T_{max} \omega_m$$

$$= \text{const}$$

- Q A 20HP, 230V, 1150 rpm shunt motor equipped with a compensating wdg has a total Armature C.R. Resistance of 0.188Ω. At rated Q/P motor draws a line current of 74.6 A and I_f of 1.6 A

A) Find the speed when input line current 38.1 A


B) determine the speed regulation if motor draws line current 1.9 A at no load.

$$\therefore \omega_m \text{ at } I_i = 38.1 A$$

$$E_a = K\phi \omega_m$$

$$\frac{E_a}{\omega_m} = \frac{T}{I_a} \Rightarrow T = K\phi I_a$$
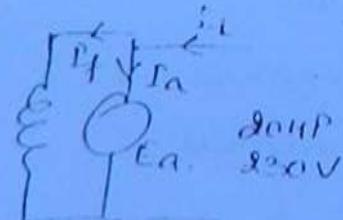
$$b) I_a = 230 - E_a R_a = 230 - (I_i - I_f) R_a = 230 - (74.6 - 1.6) 0.188$$



$$E_{a_1} = 216.276$$

$$\begin{aligned} K\phi &= \frac{E_{a_1}}{\omega_m} \\ &= \frac{216.276 \times 60}{1150 \times 2 \times \pi} \\ &= 1.7959. \end{aligned}$$

(77)

$$E_{a_2} = K\phi \omega_{m_2} \quad \phi \rightarrow \text{const.}$$

$\omega_f \rightarrow \text{const.}$

$$\begin{aligned} E_{a_2} &= 230 - (38.1 - 1.6) \times R_a \\ &= 223.14 \text{ V.} \end{aligned}$$

~~$E_{a_2} = K\phi \omega$~~

$$\frac{E_{a_2}}{E_{a_1}} = \frac{N_2}{N_1}$$

$$\Rightarrow N_2 = N_1 \times \frac{E_{a_2}}{E_{a_1}} = 1186.4 \text{ rpm.}$$

(b) Speed reg. $\rightarrow \frac{N_L - F.L.}{F.L.}$

$$P \propto \omega_m = \frac{K}{R_a}$$

On no load \rightarrow

$$\begin{aligned} E_{a_0} &= 230 - (1.9 - 1.6) \times 0.186 \\ &= 229.9 \text{ V.} \end{aligned}$$


$E_a \propto N.$

$$\frac{229.9}{216.3} = \frac{N_0}{110}$$

$$\Rightarrow N_0 = 1223.3$$

$$\begin{aligned} \text{Speed Reg.} &= \frac{1223.3 - 1}{1150} \\ &= 6.3 \%. \end{aligned}$$




WARD LEONARD SYSTEM →

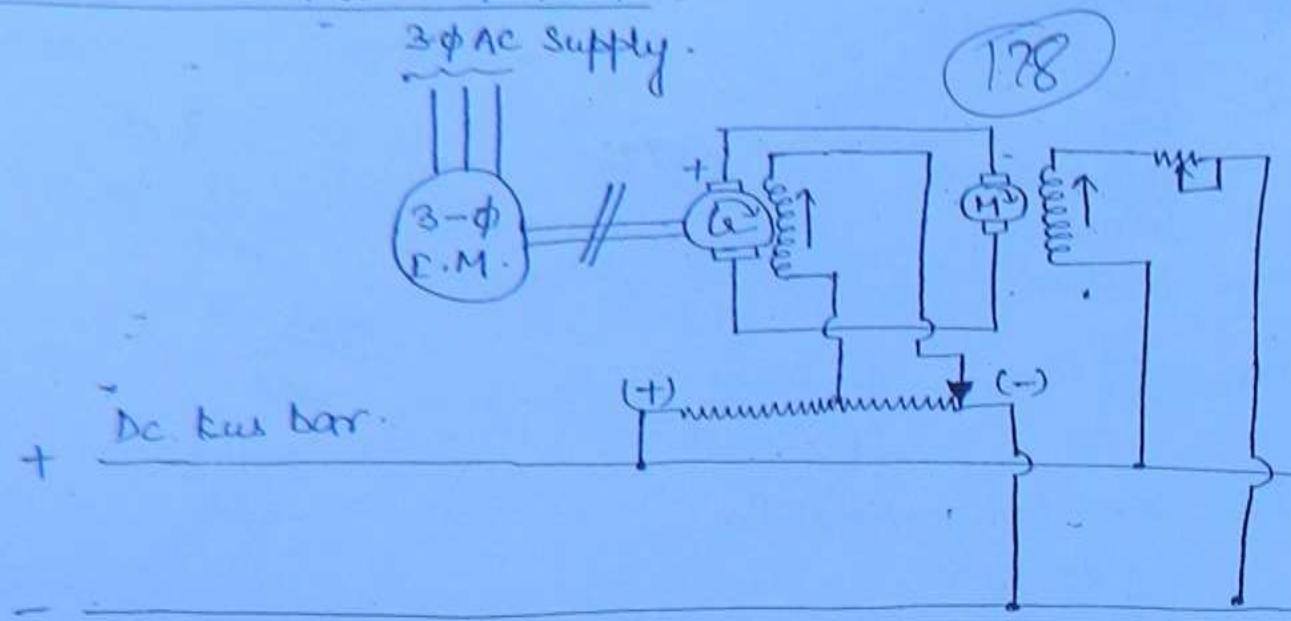


→ Works in both region.

Speed control of series motor →
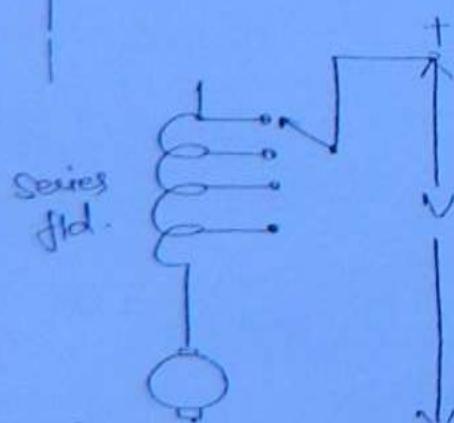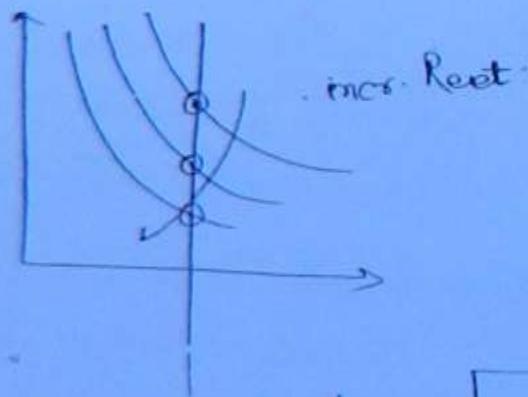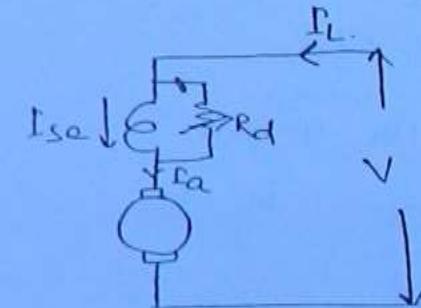
$$\omega_m = \frac{V}{KK_{ee}} \times \frac{1}{I_a} - \frac{R_a + R_{se}}{KK_{ee}}$$





Direrter Control

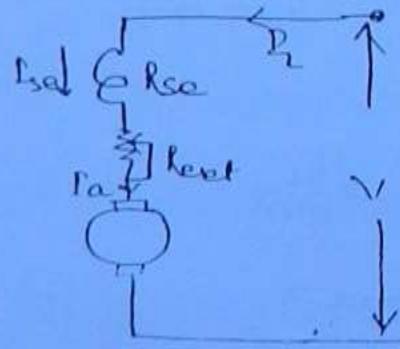

Armature Resistance Control

↑ → Field control.

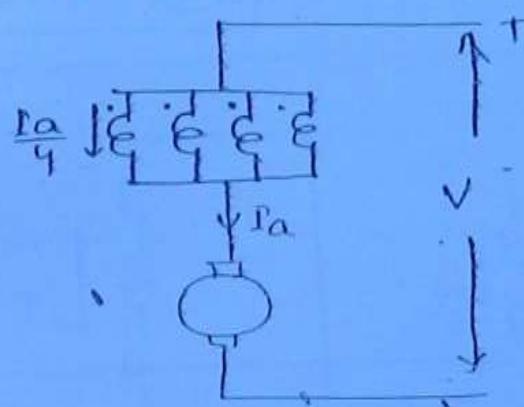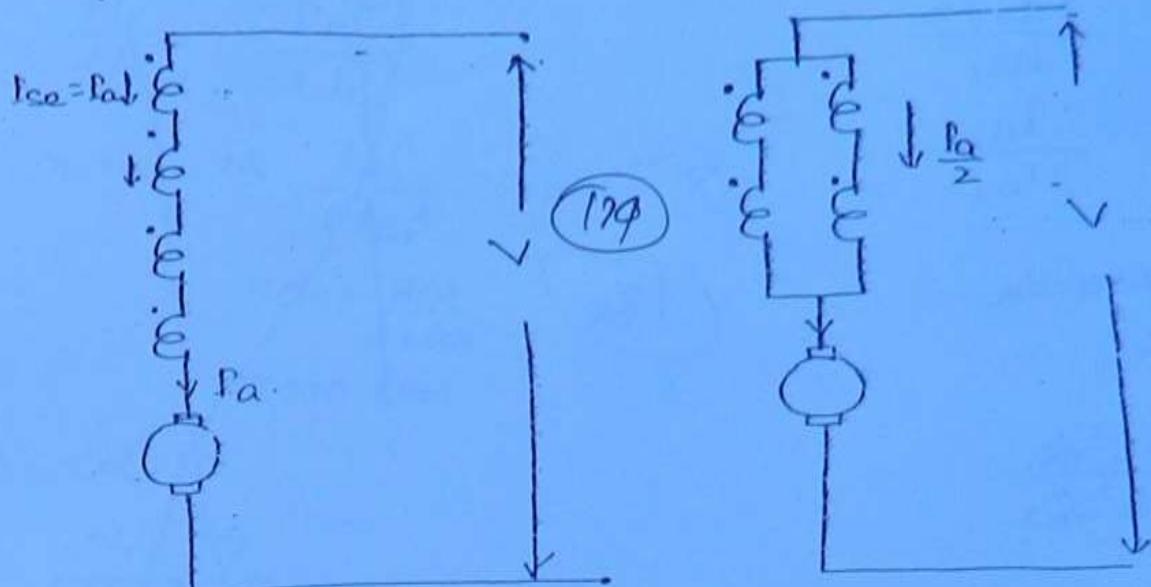

Q. A 4kW DC series motor has 4 fd coils. Motor runs at 900 rpm. and takes 20A from 230V DC source when fd coils are connected in series under normal operation. Estimate the speed and current taken by the motor if fd coils are reconnected into two 11fd gfs of two in series. Assume that flux is \propto to the current. all losses are neglected.

Ans: $T = K\phi I_a$

$$1) \text{ square of speed} \quad 2) \text{ speed. } 3) (\text{Speed})^0$$

Ans: $N_1 = 900 \text{ rpm. } I_a = 20 \text{ A. } V = 230 \text{ V.}$

$$\text{As } I_a \propto \phi_1 \propto I_a, \phi_2 \propto \frac{I_a}{2}$$

$$I_a = 4 \times 20 = 80 \text{ A}$$

$$\frac{\phi_2}{\phi_1} = \frac{\Gamma_{a_2}/2}{\Gamma_{a_1}}$$

$$\frac{\phi_2}{\phi_1} = \frac{\Gamma_{a_2}}{2\Gamma_{a_1}}$$

$$T = K \phi \omega_m \Gamma_a$$

$$T \propto N^2$$

186

~~$$\frac{T_1}{T_2} = \frac{N_1^2 \phi_1}{N_2^2 \phi_2}$$~~

$$\Gamma_a = V - L_a \Gamma_a$$

$$K \phi \omega_m = V$$

$$T = K \phi \Gamma_a \cdot \propto \phi \Gamma_a$$

$$\frac{T_2}{T_{a1}} = \frac{\phi_2 \Gamma_{a2}}{\phi_1 \Gamma_{a1}}$$

L7

$$\frac{N_2^2}{N_1^2} = \frac{\phi_2 \Gamma_{a2}}{\phi_1 \Gamma_{a1}}$$

$$= \frac{\Gamma_{a2}}{2\Gamma_{a1}} + \frac{\Gamma_{a2}}{\Gamma_{a1}} = \frac{\Gamma_{a2}^2}{2\Gamma_{a1}^2}$$

$$N_2^2 = \frac{900 \times 80^2}{2 \times 20^2}$$

$$N_2 = \sqrt{900 \times 20}$$

$$= 2545.6 \text{ RPM}$$

$$1070$$

$\tau \propto N^2$

(b) $\tau \propto N$

$$\frac{N_2}{N_1} = \frac{\phi_2 \Gamma_{a2}}{\phi_1 \Gamma_{a1}} = \frac{\Gamma_{a2}^2}{2\Gamma_{a1}^2} \propto$$

$$\frac{N_2}{N_1} = \frac{\frac{P_{a_2}}{2} \cdot \alpha^2}{\frac{P_{a_1}}{2} \cdot \alpha^2}$$

$$\Rightarrow N_2 = N_1 \cdot \frac{P_{a_2}}{P_{a_1}}$$

$$= 900 \times \frac{80^2}{\alpha \times 20^2}$$


$$= 7200 \text{ RPM}$$

(181)

c) $T \propto N^0$

$$N_1 = N_2$$

$$N_2 = 900 \text{ RPM}$$

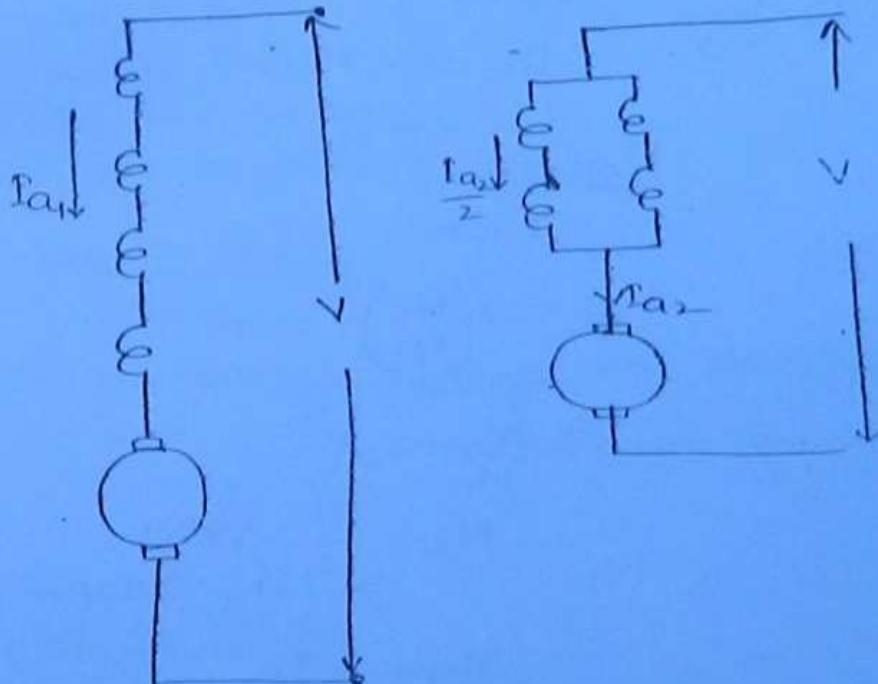

$$\phi_1 \propto l_{a_1}$$

$$\phi_2 \propto \frac{l_{a_2}}{2}$$

assuming losses \rightarrow

$$l_{a_1} = l_{a_2} = \text{const}$$

$$\frac{\phi_2}{\phi_1} = \frac{l_{a_2}}{2 l_{a_1}} = (\textcircled{A})$$

$$\kappa \phi \omega_m = \text{const}$$

$$\frac{\phi_2}{\phi_1} = \frac{N_1}{N_2} = (\textcircled{B})$$

$$\therefore \phi_1 N_1 = \phi_2 N_2$$

From (A) and (B) \Rightarrow

$$\frac{I_{a_2}}{I_{a_1}} = 2 \frac{\phi_2}{\phi_1}$$

$$\frac{I_{a_2}}{I_{a_1}} = \frac{2 N_1}{N_2}$$

$$T = k \phi I_a$$

$$\propto \phi I_a$$

$$\frac{T_2}{T_1} = \frac{\phi_2}{\phi_1} \times \frac{I_{a_2}}{I_{a_1}}$$

$$= \frac{N_1}{N_2} \times 2 \frac{N_1}{N_2}$$

$$\frac{T_2}{T_1} = 2 \left(\frac{N_1}{N_2} \right)^2 \rightarrow (\text{I}) \text{ Case}$$

Part b.

$$T \propto N$$

$$\frac{T_2}{T_1} = \frac{N_2}{N_1} \quad (182)$$

$$\frac{N_2}{N_1} = 2^{y_3}$$

$$N_2 = 2^{y_3} N_1$$

$$= 2^{y_3} \times 900$$

$$= 1133.93 \text{ rpm}$$

Hence \rightarrow

$$\frac{I_{a_2}}{I_{a_1}} = 2^{y_3}$$

$$I_{a_2} = 31.75 \text{ A}$$

Part a

$$\frac{T_2}{T_1} = 2 \left(\frac{N_2}{N_1} \right)^2$$

$$2 \left(\frac{N_1}{N_2} \right)^2 = \left(\frac{N_2}{N_1} \right)^2$$

$$\Rightarrow 2 \left(\frac{N_1}{N_2} \right)^4 = 1$$

$$\Rightarrow \left(\frac{N_2}{N_1} \right)^4 = 2$$

$$\Rightarrow N_2 = 2^{y_4} \times 900 > 1070.3 \text{ rpm}$$

Part c

$$T \propto N^0$$

$$1 = 2 \left(\frac{N_1}{N_2} \right)^2$$

$$\Rightarrow \frac{N_2}{N_1} = 2^{y_2}$$

$$N_2 = 2^{y_2} \times 900$$

$$= 1272.79 \text{ rpm}$$

$$\text{Thus } \frac{I_{a_2}}{I_{a_1}} = 2^{y_2}$$

$$\Rightarrow I_{a_2} = 28.28 \text{ A}$$

$$\text{Thus, } \frac{I_{a_2}}{I_{a_1}} = 2^{y_4} + \frac{2^{y_4} \times 900}{1070.3}$$

$$\begin{aligned} \frac{I_{a_2}}{I_{a_1}} &= 2^{y_4} \times 2^0 \\ &= 33.64 \text{ A} \end{aligned}$$

Applicable to this configuration only :-

If $T \propto N^x$

Then $\frac{N_2}{N_1} = 2^{\frac{1}{x+2}}$

(183)

$$\frac{P_{a2}}{P_{a1}} = 2^{\frac{2+x}{x+2}}$$

Braking →


To bring the m/c quickly to rest.

Motor →

Regenerative braking

Natural coasting →

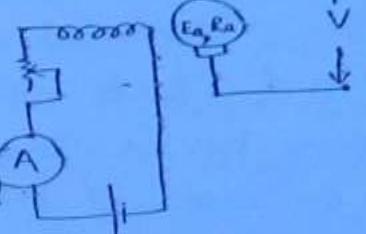When rotor is left
and it comes to rest
by friction and windage
loss, KE gets dissipated



when braking takes place

for changing torque,

$$T = K\phi I_a$$

ϕ or I_a change, change the polarity of V because $\frac{dI_a}{dt}$ is very high, so insulation gets damaged

Plugging


Both act as source

Electromagnetic and electrical source are absorbed by the m/c → massive heat take place.

$E_a + V \rightarrow$ Plugging voltage


$$I_a = \frac{E_a + V}{R + L_{tot}}$$

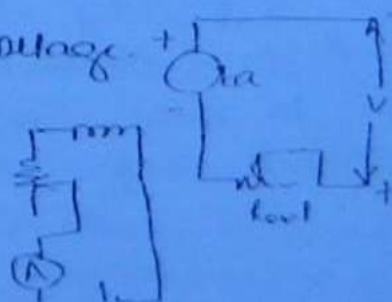all are dissipative
in R_{ext} and L_{ext}



Dynamic braking

Increase if output
decr. R.

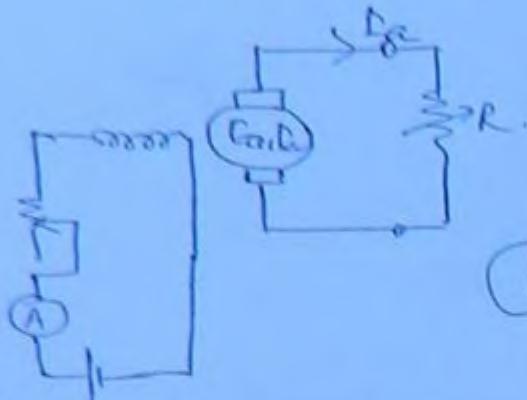

Braking of DC motors

Regenerative braking → when braking is desired fhd excitation is increased. As w/fd excitation increases, armature induced volt. and the moment more the terminal voltage, DC m/c becomes generator and starts delivering power to the supply system. Obviously under these conditions, the mechanical power is derived from the stored K.E of rotor and consequently speed reduces. This form of braking is known as regenerative braking. The fd current obviously can not be increased beyond its rated value and therefore when the forward power as gen becomes 0 with the max allowable fd current, the supply must be switched off. If desired, mechanical brakes may then be applied to bring the motor quickly to rest. In situations where it is possible to reduce the terminal volt, such action may prolong regeneration duration and consequently the time taken for the motor to come to rest shall reduce. Ofcourse protection must be taken to insure that the armature current does not exceed safe limit during braking.

(185)

2) Plugging →

In this method of braking, the polarity of the supply voltage to the armature is reversed. After polarity reversal, the armature induced emf and the terminal voltage add up to create an armature current in reverse dirⁿ. The sum of these two voltages is called plugging voltage. An external resistor in series with the armature ckt is therefore necessary to limit the armature current during plugging to safe value. Reversal in dirⁿ of armature current while flux dirⁿ remains unchanged produces an electromagnetic torque in a dirⁿ opp. to the present dirⁿ of rotation. Consequently rotor retards very quickly and comes to rest. At this stage, supply to the motor is switched off to prevent rotation in the reverse dirⁿ. It may be noted here that during the process of braking by plugging, electrical power is taken from the mains while mechanical power is also derived from the shaft and the sum of these two powers gets dissipated as loss in the motor and an external resistor.

Dynamic braking or Rheostatic braking :-

In it supply to the motor is switched off and a shunt resistor is connected across the terminals. Since the e.m.f. is still available, M/c becomes a generator delivering power to the resistor and at the terminals while drawing mechanical power from the stored k.e. of the rotor. Consequently the rotor slows down and ultimately comes to rest. The value of the resistor must be selected to insure that the armature current does not exceed its stat/saf value. The process of braking may be accelerated by maintaining the armature current at a high but safe value, this may be done by decreasing the load resistor and increasing the supply voltage.

reverses or course with in large limits, when the motor comes to rest field supply is switched off.

motor →


arm. & Hd.

Rheostate ↑ Rheostate ↓ at starting condition.


because flux & ↑ & for $T \propto \frac{1}{I}$, $E_b \propto I$ then $I \downarrow$ and rheostate is slowly cut off

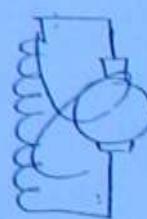(186)

State of the contact in deenergised state → No and NC
(A) (B)



3 pt. Starter & 4pt. starter

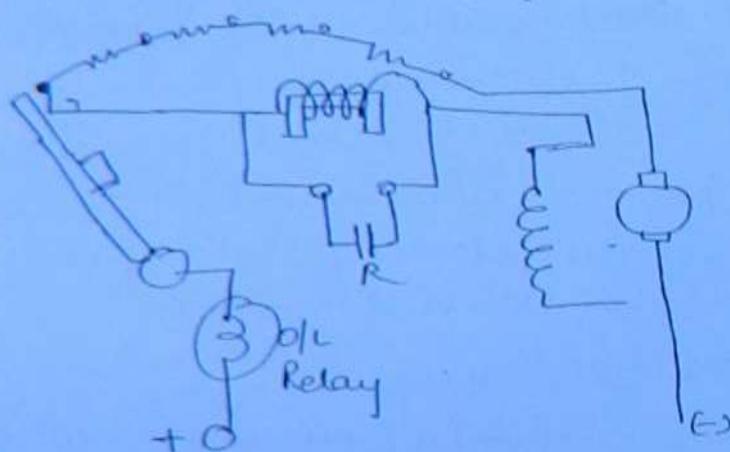

Hoffner's States →

Shorting & test (for shunt motor) (specially)

Series test is a no load test and can't be carried out in series motor test.

> Hd. test →

> Retardation or

Braking down test

$$K.E = \frac{1}{2} I^2 R$$

$$\frac{d}{dt}(K.E) = \frac{1}{2} \times 2 \times I^2 \frac{dR}{dt} - \left(\frac{dI}{dt} \right) R I^2$$

Dummy coil \rightarrow

for mechanical balancing outlet.

Brush positions

(787)



coil undergoing commutation \rightarrow DMMNA axis

radial force
 $= 0$

Physically on under pole

SYNCHRONOUS MFL

Actual speed = speed of rotating fld.

When 3- ϕ wdg carries 3- ϕ current wrt time then revolving fld produced

188

Revolving M-fld in 3- ϕ mfc:


When a 3- ϕ wdg balanced in space carries 3- ϕ current balance in time, a revolving M-fld is produced that rotates at synchronous speed given by $\frac{120f}{P}$ wrt the wdg structure in a dirⁿ from leading phase axis to lagging phase axis with a sinusoidal flux distribution in space having an amplitude $1.5 \Phi_m$ and resultant flux axis is coincident with the magnetic axis of that phase which carries peak current

$n_{\text{sync}} \rightarrow$

- B 3- ϕ wdg carries 3- ϕ current, if revolving fld produced
- n No, because wedges are ~~not~~ not 120° space distributed

dirⁿ of rotation change, change the seq. of supply

For wrt=0


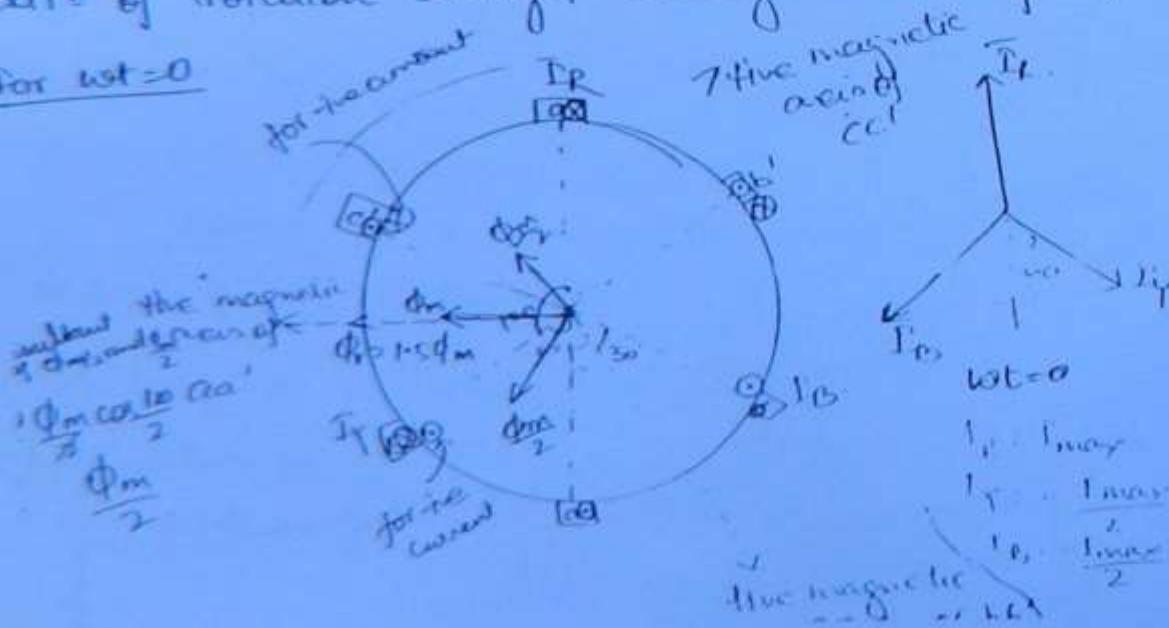


$$\omega_f = 120$$

$$F_R = -\frac{E_{max}}{2}$$

$$F_Y = E_{max}$$

$$F_B = -\frac{E_{max}}{2}$$

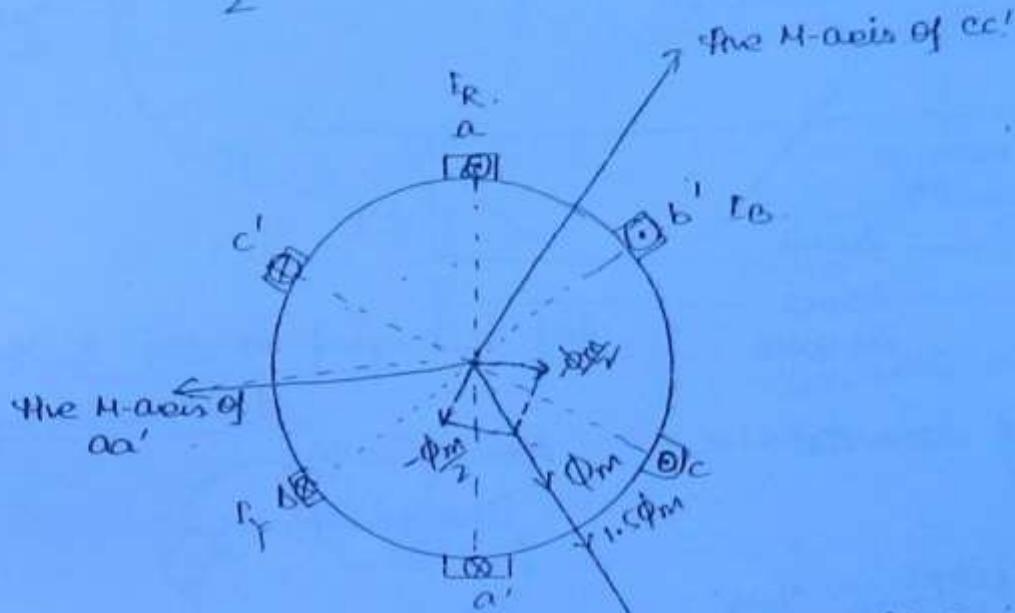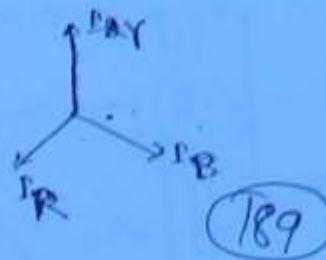


$$N_S = \frac{180f}{P} \text{ rpm}$$


Armature wrdg \rightarrow 3-ph A.C., 15.75 KV, 9050 A, Star connected to stator

Rld wrdg \rightarrow 2600 A DC at 310V \rightarrow Rotor

PITTING \rightarrow Small pits on slipping is 'pitting'.

void \rightarrow air gap.

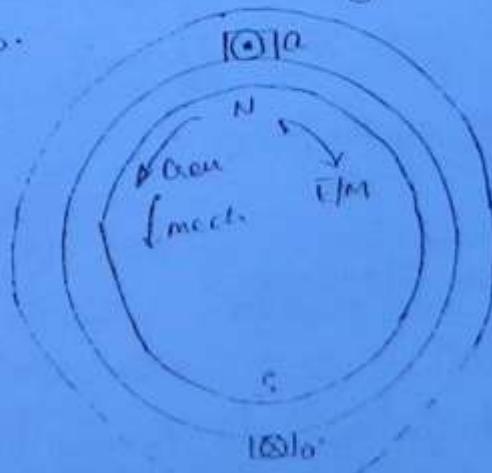

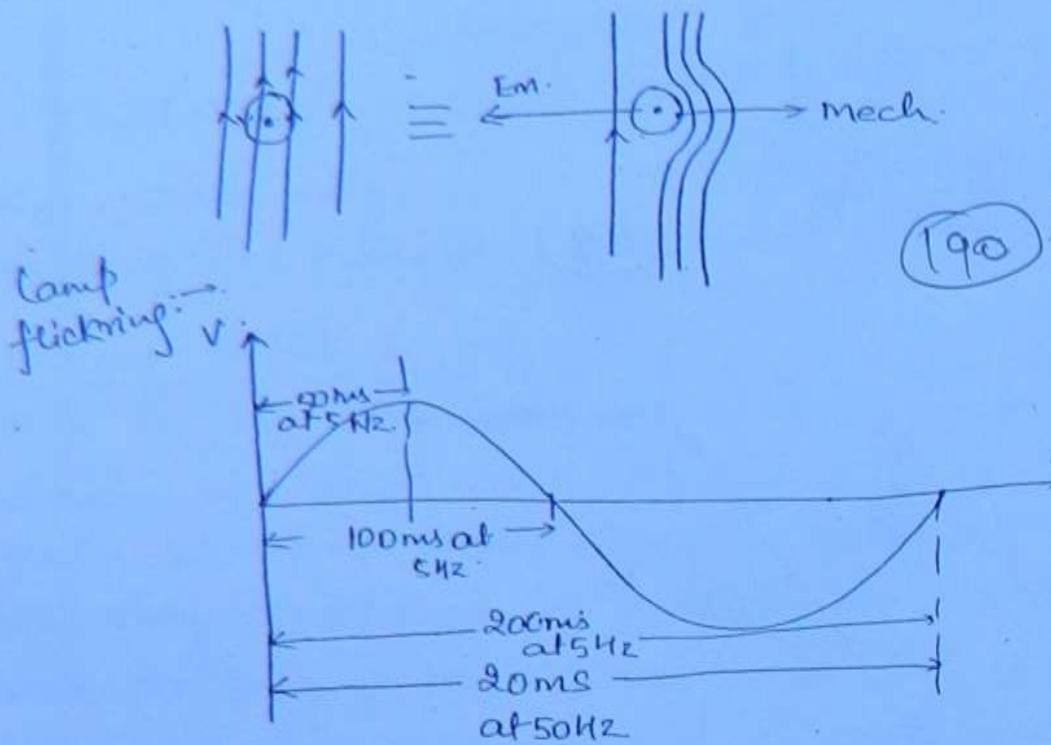

Flicker seen at 200ms at 50Hz
 $\propto D^2 LN$.

Around 30 Hz,
flicker disappears.

$$f_1, X_L = 2\pi f L \uparrow, f P_{max} = \frac{V_S V_R}{X \uparrow}$$

So, 50Hz is freezed when f further increased than 50Hz,
 $P_{max} \downarrow$.

$$f = \frac{PN}{120}$$

2 pole \rightarrow 1 cycle
6 pole \rightarrow 3 cycle

$$\Rightarrow PN = 120f$$

$$= 120 \times 50$$

$\frac{P}{2}$ cycle \rightarrow 1 revolution

$$PN = 6000$$

$\frac{P}{2} \times \frac{N}{60}$ cycle / s in $\frac{N}{60}$ rev/s

\downarrow
depends on prime-
motor chosen

$$f = \frac{PN}{120} \text{ cycles/sec}$$


$$(Hz)$$

Up to 4 poles \rightarrow cylindrical rotor structure.

$$P \neq 4$$

For greater than 4, slots made in the rotor become closer and thinner. Their area becomes less. So, due to centrifugal force they may

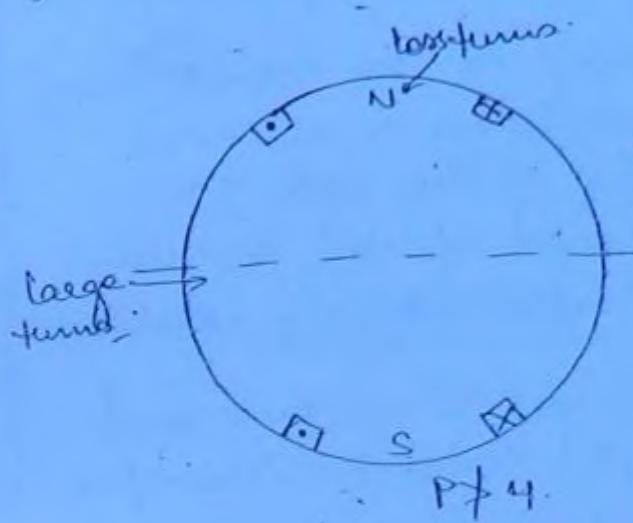Cylindrical Rotor OR Round Rotor or Non-salient pole Rotor



(19)

distributed wdg.


$$\Phi = \frac{mmf}{\text{Reluctance}} \rightarrow \text{change it}$$

count

} for Sin -
-datB.

for perfect sinusoidal $B_m \rightarrow$
infinite poles

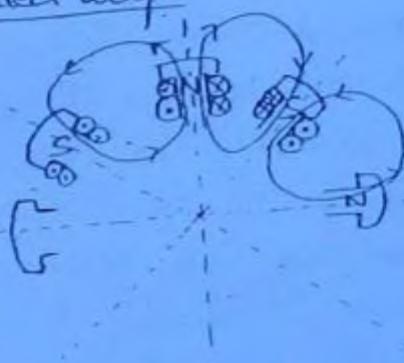Salient pole or projected pole \rightarrow
concentrated wdg.



Concentric Concentric



Sinusoidal is only
waveform which
provides inherently
revolving M-fld.

$$\Phi = \frac{mmf}{\text{Reluctance}} \cdot mmf \rightarrow \text{const as } NP$$

Reluctance change \rightarrow reluctance.

} for sinusoidal B


Sinusoidal distribution of air gap flux density in synchronous
MIC \rightarrow

↑ Sinusoidal AC voltage is obtained in a synchronous gen
if the flux density distribution in the air gap is sinusoidal
↑ Salient pole rotor has a conc. slot wdg and therefore
the slot mmf is const and is directed along the face
axis. A sinusoidal flux density distribution therefore

be reduced - i.e., the minimum of air gap. Accordingly, the air gap at the centre of the pole is minimum and goes on increasing as one moves away from the centre of the pole, and this is achieved by proper profiling that is shaping of the pole face. The variation in the air gap should of course be such as to result in a sinusoidal fld flux density distribution. In cylindrical rotor m/c, the air gap is uniform and the fld wdg is distributed but concentric. Therefore in this case the distributed fld mmf must approach a sinusoid so that a sinusoidal flux density distribution is obtained even with a const reluctance in gap. This is achieved by providing max. turns in the fld coils of those slots which are near the quadrature axis also called Interpolar axis. The no. of turns in the slots goes on decreasing in accordance with sinusoidal mmf distribution as one moves from the poles from the quadrature axis. Obviously the no. of turns in the slot nearest to the pole would be minimum and overall fld mmf distribution would be stepped that approaches a sinusoid. A perfect sinusoidal mmf distribution in the air gap of a cylindrical rotor m/c would be possible only when the no. of slots for fld wdg is infinite.

Induced emf →

Induced EMF

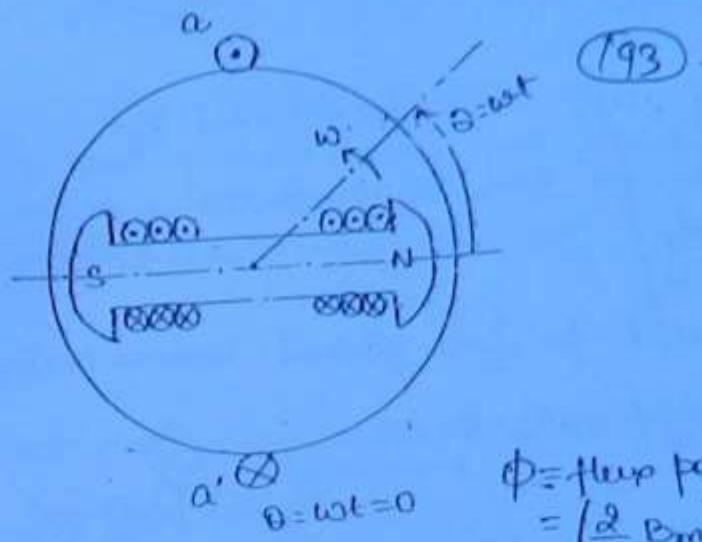


(193)


ϕ = flux per pole

$$= \left(\frac{d}{\pi} B_m \right) \left(\frac{\text{ADL}}{P} \right)$$

= Bar x Area per pole

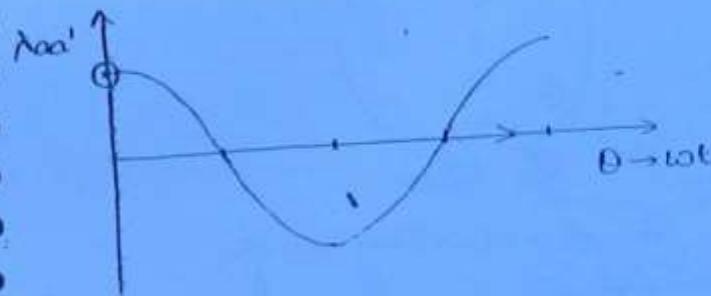
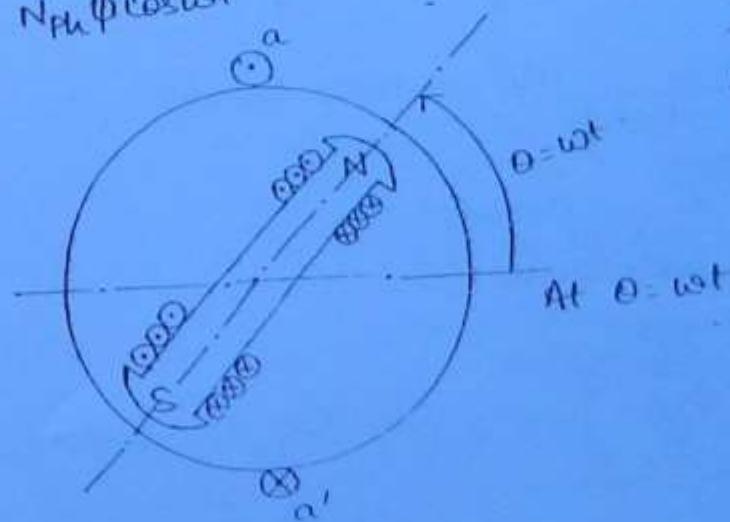
$$\lambda_{aad'} = N_{ph} \phi \cos \omega t$$



If AC is given in flat, then we get the emf with the freq other than original. So, freq will be not reach to S.C. and we don't get stability in m/c

$$e_{aad'} = - \frac{d}{dt} \lambda_{aad'}$$

$$= - \frac{d}{dt} (N_{ph} \phi \cos \omega t)$$

$$N_{ph} \phi \omega \sin \omega t \quad (\text{lags the } \phi \text{ by } 90^\circ)$$

$$e_{aad'} = \lambda_{aad'}$$

$$E_{ph} = \frac{N_{ph} \phi \omega}{\sqrt{2}}$$


$$= \frac{N_{ph} \phi 2\pi f}{\sqrt{2}}$$

$$= \sqrt{2} \pi f \phi N_{ph} \rightarrow \text{Induced emf eqn.}$$

Full pitched wedg \rightarrow coil span is 180°
concentrated wedg

chorded wedg \rightarrow Valid for full pitched concentrated wedg.

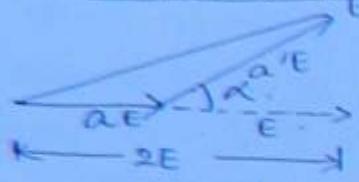
or Fractional pitched wedg or (short pitch wedg)



$$E_{ph} = 2E \cos \frac{\alpha}{2}$$

Chording factor, $k_c = \cos \frac{\alpha}{2}$

Pitch factor for fundamental comp.

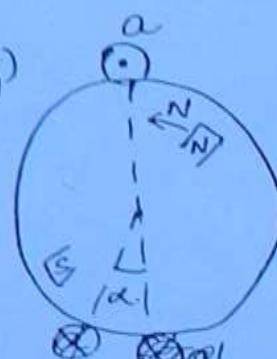

$\alpha \rightarrow$ chording angle

for n th harmonic,

$$k_c(n) = \cos \frac{n\alpha}{2}$$

To eliminate n th harmonic

$$\frac{n\alpha}{2} = 90^\circ$$

$$\alpha = \frac{180}{n}$$

Practical $\alpha = 30^\circ$

$$\alpha = 30^\circ$$

$k_c = 0.9659 \rightarrow$ fundamental is ~~not~~ reduced to very small value and can be tolerated

$$k_c(3) = 0.7071$$


$k_c(5) = 0.2588 \rightarrow$ 3rd and 5th harmonic is reduced.

$$E_{ph} = k_e \times \frac{1}{2} \pi f \phi N_{ph} \quad \text{Volts/phase}$$

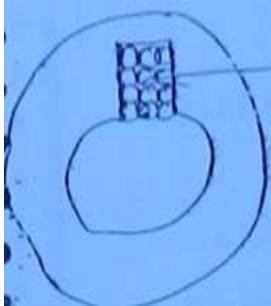(195)

Valid for short pitched concentrated wdg.

conc. wdg because is not used as area of stator inc, cond or near stator has nearly 0 induced emf. losses are more.
So, distributed wdg is used.



In 2 pole m/c →

if total slot = 60, slots per pole = 30.

slots per pole per phase = $\frac{30}{3} = 10$.

Distribution wdg →





$$\beta = \text{Angle b/w adjacent slots} = \frac{360^\circ}{\text{No. of slots}} \quad \text{mech.}$$

$$= \frac{P \times 360^\circ}{2 \times \text{No. of slots}} \quad \text{elec.}$$

$$= \frac{180^\circ}{\text{No. of slots per pole}} \quad \text{elect.}$$

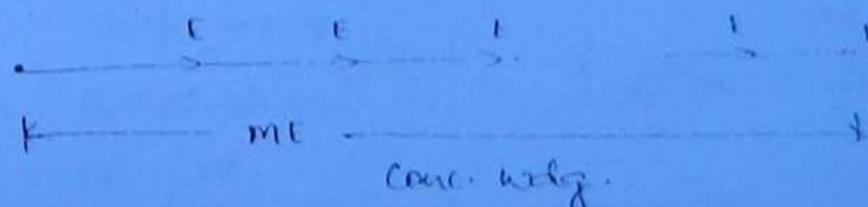$m \rightarrow$ no. of slots per pole per phase



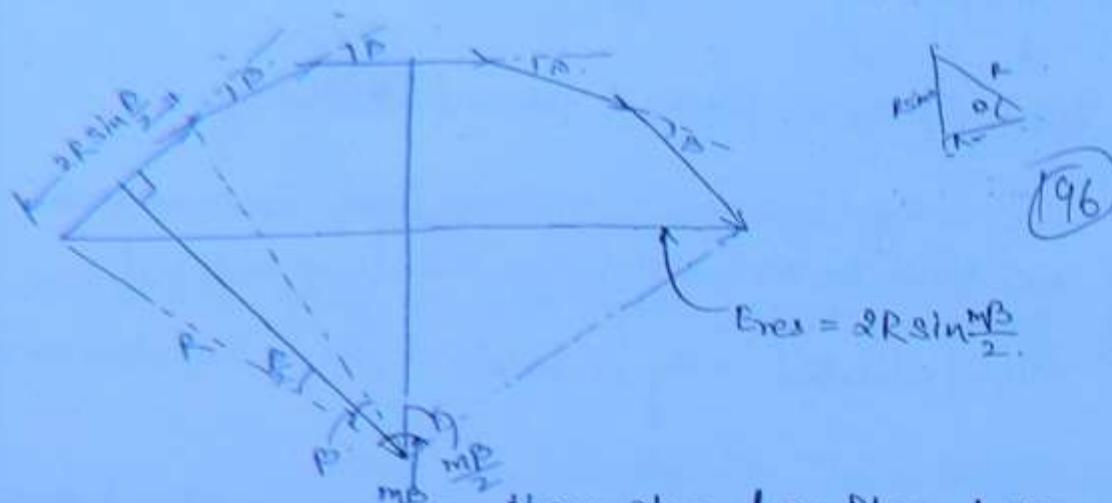

(96)

$$E_{res} = 2R \sin \frac{m\beta}{2}$$

Phase spread or Phase belt.

Distribution factor $k_d = \frac{2R \sin m\beta/2}{m \times 2R \sin \frac{\beta}{2}}$ $m\beta = 60^\circ$

Spread factor $\frac{k_d}{m}$ [normally]

Breadth factor $\frac{\sin \frac{m\beta}{2}}{m \times \sin \frac{\beta}{2}}$

$$\approx k_d \approx \frac{\sin \frac{m\beta}{2}}{\frac{m\beta}{2}} \quad \because \sin \frac{\beta}{2} \approx \frac{\beta}{2} \text{ rad as, } \beta \text{ is very very small}$$

$$\approx \frac{\sin \frac{\text{Phase spread}}{2}}{\frac{\text{Phase spread}}{2}}$$

For n^{th} harmonic \rightarrow

$$k_d^{(n)} = \frac{\sin n(\frac{m\beta}{2})}{m \times \sin \frac{(n\beta)}{2}}$$

P. 2, No. of slots = 60.

$$P = \frac{360}{60} = 6 \quad m = 10$$

$$k_d = \frac{\sin \frac{60}{2}}{\frac{\sin 60}{2}} = 0.3549 \quad k_d^{(6)} = \frac{\sin \frac{60 \times 3}{2}}{\frac{\sin 60 \times 3}{2}} = 0.6392$$

$$k_{d(5)} = \frac{\sin \frac{60 \times 5}{2}}{10 \sin \frac{30}{2}} = 0.1932.$$

(197)

$$E_{ph} = k_c k_d \sqrt{2} \pi f \phi N_{ph} \text{ Volts/phase}$$

Valid for short pitched distributed wdg.

$$= k_w \sqrt{2} \pi f \phi N_{ph} \text{ Volts/phase.}$$

where $k_w = k_c k_d = \text{wdg. factor.}$

$$k_w = 0.9227$$

$$k_w(3) = 0.4520$$

$$k_d(5) = 0.05$$

Q. A 3- ϕ , 2 pole 3000 rpm Y connected cylindrical rotor field generator has the following data.

Steam
prime

No. of slots = 60.

maximum flux density in the air gap = 1.32 T

mean air gap diameter = 1.12 m.

Axial length = 3 m.

No. of turns $\frac{1}{\text{slot}} = 10$.

Cal. Line to Line Voltage on no load if coil span is 150°.

Ans. $N_{ph} = 10$

$$B_m = 1.32 \text{ T} \quad \phi_m = B_m \times A \\ = B_m \times$$

$$E_{ph} = 0.9227 \times S_2 \times \lambda \times 50 \times \phi_m \times 10$$

$$\phi = \frac{2}{R} \frac{1.32 \times \pi \times 1.12 \times}{2} \\ = 0.4352$$

$$= 2049.724 \times \phi_m$$

$$= 9690.93 \text{ V.}$$


$$E_L = 15745.96 \text{ V}$$

$$f = \frac{P_N}{120} = \frac{2 \times 3000}{120} = 50 \text{ Hz.}$$


$$= 15.75 \text{ KV.}$$

Armature Reaction in Synchronous generators:

(198)

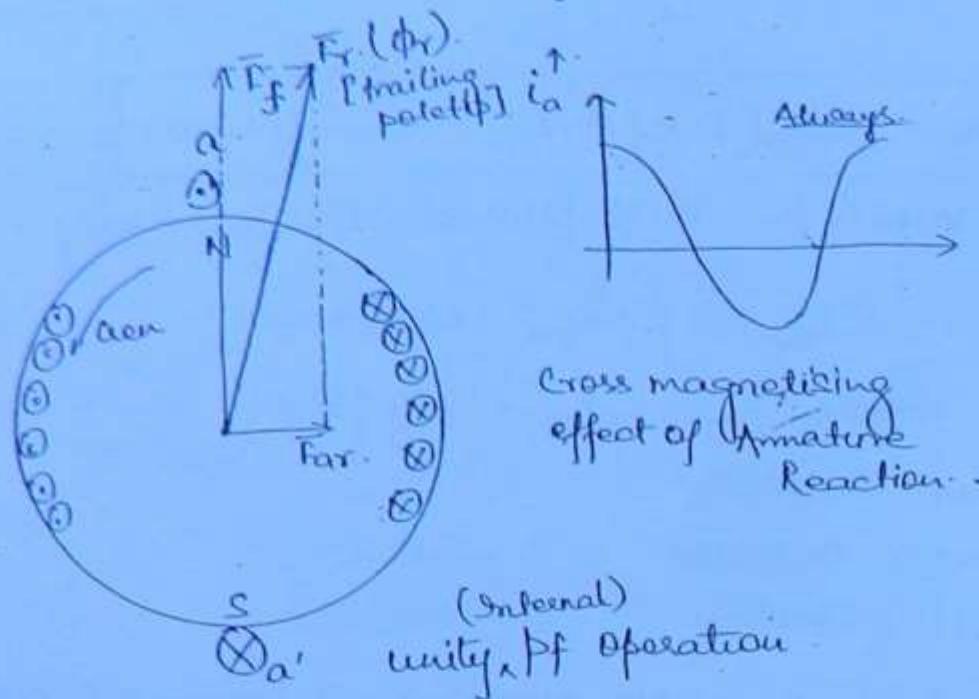

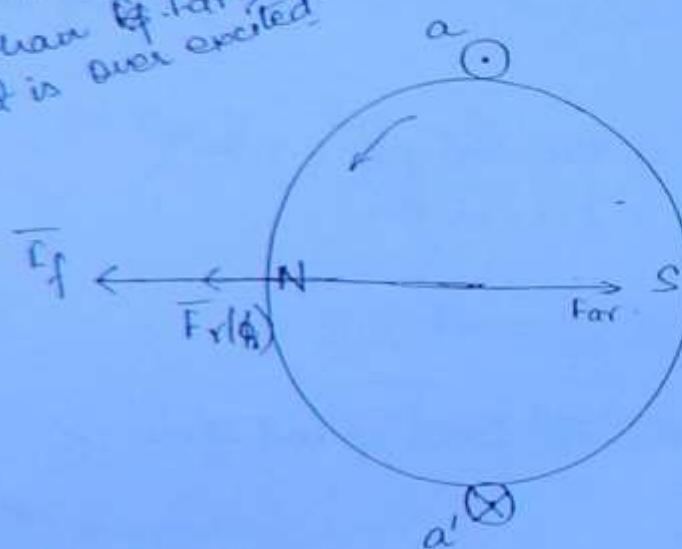If d mmf is higher
than B.F. mmf,
it is over excited.



zero pf $\rightarrow 90^\circ$ lag.

v [lag v by 90°

so, N moves
counter clockwise
dir.

zero pf lag.


Directly Demagnetizing Armature Reaction
Since $F_f > F_r$, if is an unexcited.

Armature on stator \rightarrow

high armature current

zero pf lead →


(799)

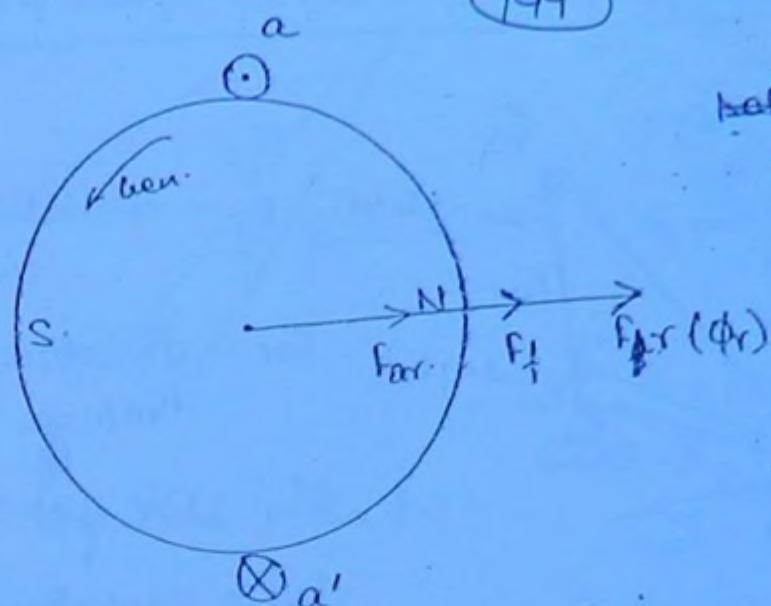


Directly magnetizing Armature Reaction

$F_f < F_r \rightarrow$ underexcited generator.

Intermediate Pf lag

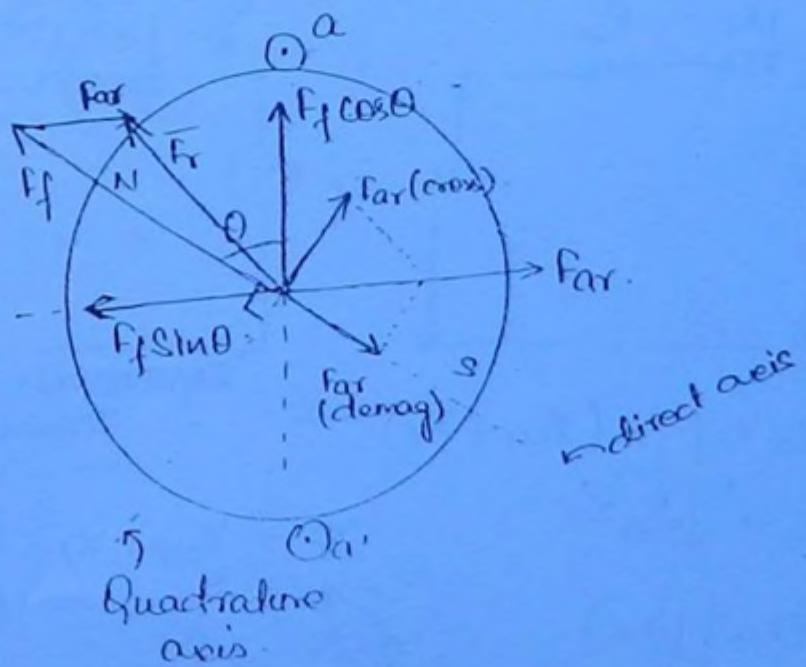

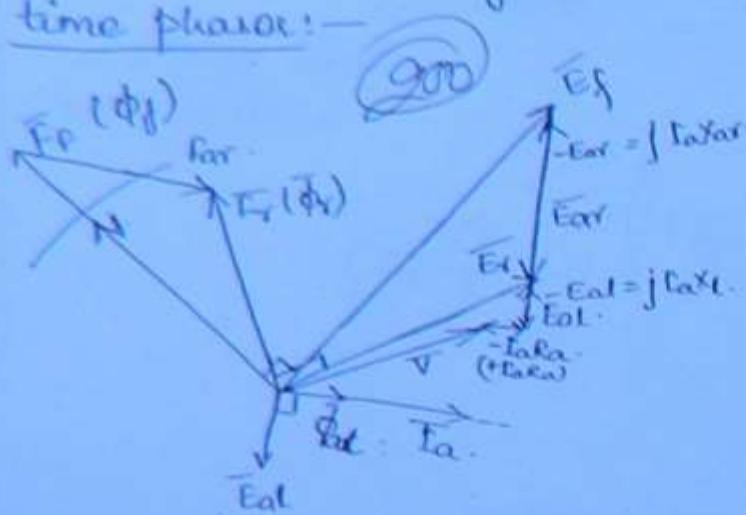General phasor diagram showing space phasors and time phasor:-



$E_f \rightarrow$ excitation Voltage or internal Voltage

$E_{ar} \rightarrow$ armature reaction Voltage

$E_aL \rightarrow$ air gap voltage


$X_{aL} \rightarrow$ armature leakage flux Voltage

$X_{ar} \rightarrow$ Armature reaction Reactance

$X_{ar} \rightarrow$ Armature Reaction Reactance

$$\bar{V} = \bar{E}_f + \bar{E}_{ar} + \bar{E}_{aL} - I_a R_a$$
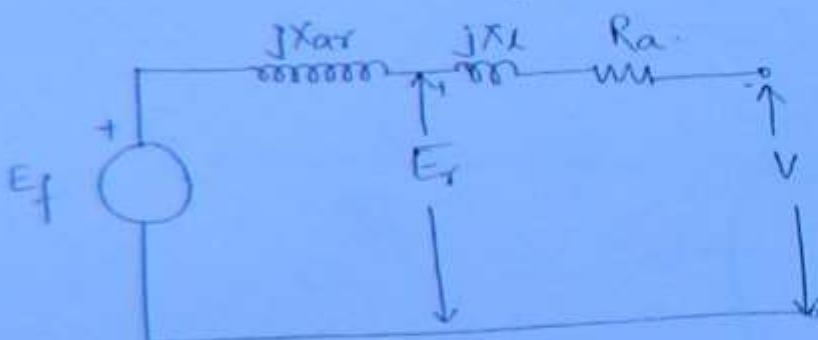
$$\begin{aligned}\bar{E}_f &= \bar{V} + I_a R_a - \bar{E}_{aL} - \bar{E}_{ar} \\ &= \bar{V} + I_a R_a + j I_a X_{aL} + j I_a X_{ar}\end{aligned}$$




$$\bar{E}_f = \bar{V} + I_a R_a + j I_a (X_{ar} + X_L)$$

$$\bar{E}_f = \bar{V} + I_a R_a + j I_a X_S$$

$$= \bar{V} + I_a (R_a + j X_S)$$

$$= \bar{V} + I_a Z_S$$

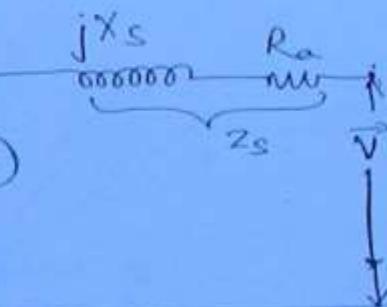


EQUIVALENT CIRCUIT OF SYNCHRO GEN.

$X_S \rightarrow X_{ar} + X_L \rightarrow$ Synchronous Reactance

$Z_S \rightarrow R_a + j X_S \rightarrow$ Synchronous Impedance

$R_a \rightarrow 1\%, X_S \approx 200\%$

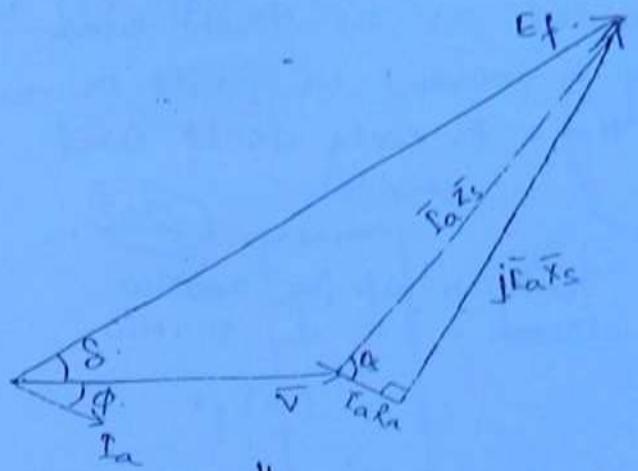as ω_0, I_a give no effect on the calculation. So,
as R_a very small and can be ignored



Lagging pf operation $R_a \neq 0$

$S = P_f$ and I_a (almost)


$\delta \rightarrow$ Power angle
or

Rotor angle
or



load angle
or

torque angle.

For $R_a = 0$

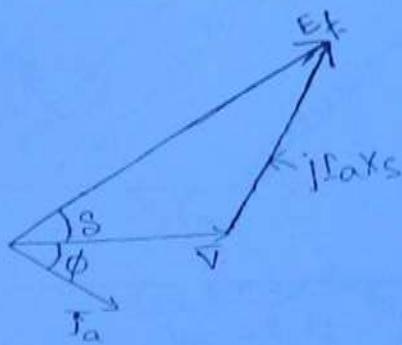


For leading pf \rightarrow

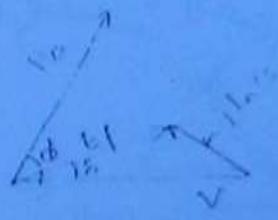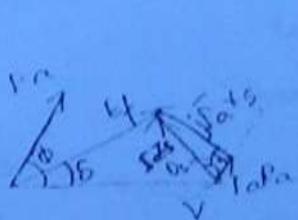

|| Power transfer even if the load is $\phi = 0^\circ$ for pf.

lag and lead pf operation of load.

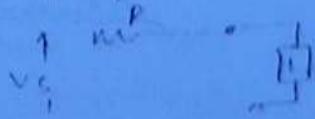

" Core are never Δ connected as in fault case
 3rd harmonic is dominately present in fault current
 and it will circulate in the Δ way itself and
 cause massive heating.

(202)


Open circuit test :

if air gap increases,



the air gap line will decrease.

$$\downarrow \phi = \frac{mnf}{\text{reluctance}} \uparrow$$

for same flux, IT,
and same volt

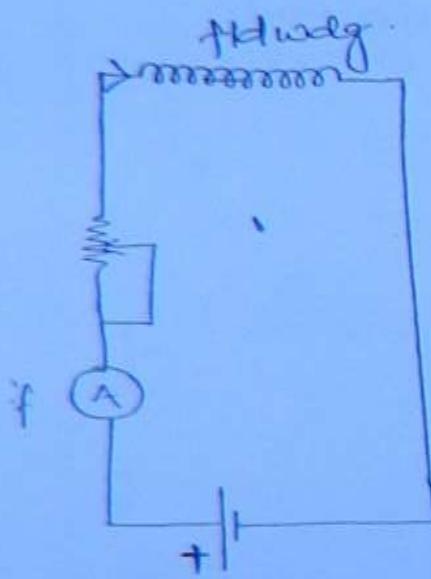

7cm airgap for 200MW
 130mm " " 500MW

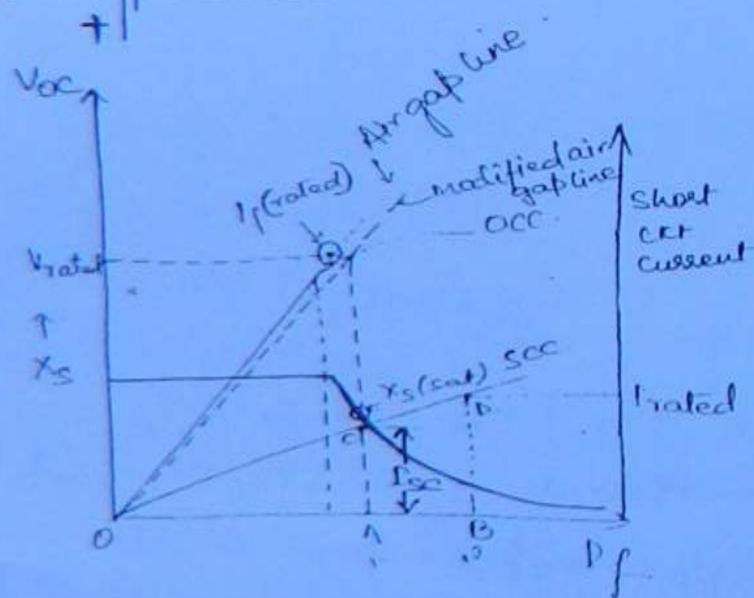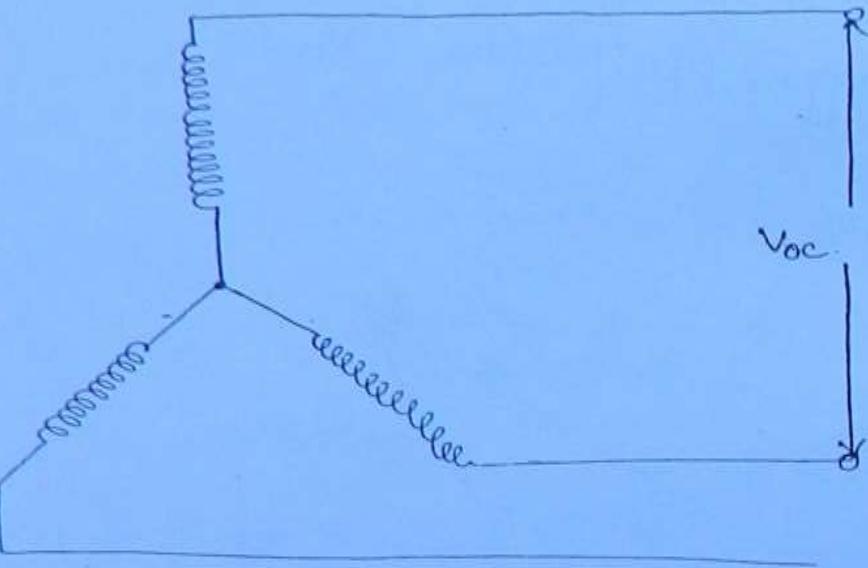

$I_f(\text{rated}) = 1 \text{ pu}$
 1 pu fld current gives rated
 voltage on the air gap line





$$X_s(\text{sat}) = \frac{V_{\text{rated}}}{I_{\text{sc}}}$$

Saturated syn. reactance
 or

Adjusted syn. Reactance

Short CCR Test →

(203)

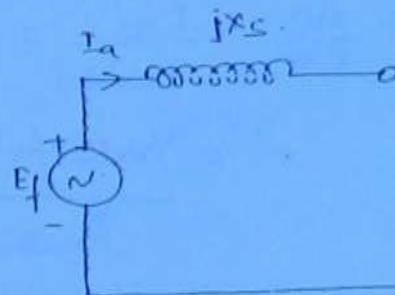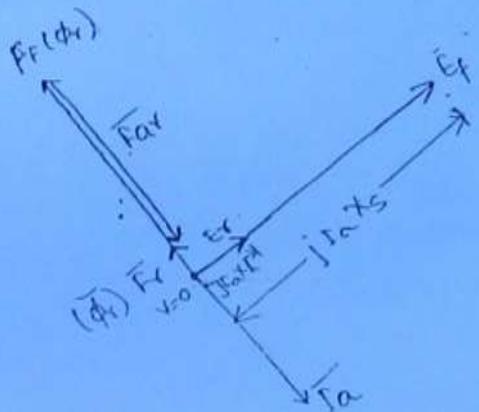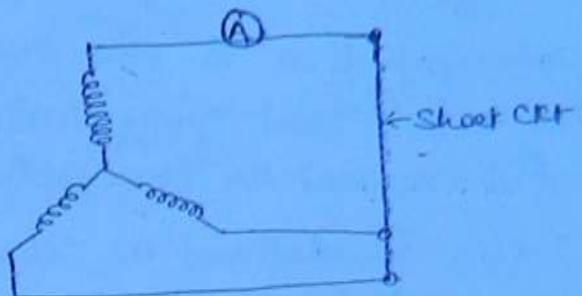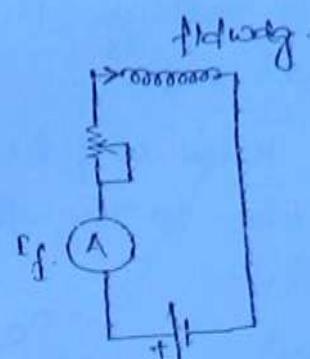

$$E_f = jI_a X_s$$

OPF lagging

$$e^{-j\frac{d\phi}{dt}} \phi = 1$$

$$\frac{dI}{dt}$$

$$\frac{V_{oc}}{I_{sc}} = X_s$$

$$\begin{aligned} \text{for Linear Region, } & \frac{V_{oc}}{I_{sc}} = K_1 P_f & a \propto x & b \propto x \\ & V_{oc} = K_1 P_f & & = K_2 x \\ & I_{sc} = K_2 P_f & \frac{a}{b} = \frac{K_1}{K_2} = \text{const} & ; \\ & \frac{V_{oc}}{I_{sc}} = \frac{K_1}{K_2} = X_s = \text{const} & & \end{aligned}$$



For Saturated Region of CCC

$$V_{oc} = \text{const}$$

$$I_{sc} = K_2 P_f$$

$$\frac{V_{oc}}{I_{sc}} = \frac{\text{const}}{K_2 P_f} \propto \frac{1}{P_f}$$

from OCC,

$$\frac{V_{rated}}{I_{sc}} = X_s (\text{saturation})$$

Pcc by definition is that value of short CCR current which is obtained at that value of Net current which give

at rated voltage on open C.R.

- Modified air gap line is the occ of an equivalent unsaturated m/c that gives rated voltage that gives the same fd current as the actual m/c
- Short C.R. Ratio is defined as the ratio of fd current required to give rated volt. on open C.R to the fd current required to give rated current on S.C.

$$SCR \triangleq \frac{OA}{OB} = \frac{AC}{BD} = \frac{E_{sc}}{I_{rated}} = E_{sc} (\text{pu})$$

204

$$= \frac{V_{rated}/X_{s(\text{sat})}}{I_{rated}}$$

$$\begin{aligned} SCR &= \frac{V_{rated}/I_{rated}}{X_{s(\text{sat})}} \\ &= \frac{\text{Base impedance}}{X_{s(\text{sat})}} \\ &= \frac{1}{X_{s(\text{sat})}/Z_{\text{base}}} \end{aligned}$$

$$SCR = \frac{1}{X_{s(\text{sat})} \text{ pu}}$$



12/11

$$SCR = \frac{OA}{OB} \propto \frac{\text{Air gap}}{\text{No. of turns / t}}$$

Now a trend, generators are designed to have low value of SCR. but stability decreases. If SCR \downarrow , M of induction, $\propto 1$, $P_{max} \downarrow$. ($0.5, 0.45, 0.35$) $\propto SCR$

In turbo generator, 1.2 dia of rotor \rightarrow max as they are high speed m/c
Hydro m/c are more stable than all m/c far away from

Potier characteristics or ZPFC :-

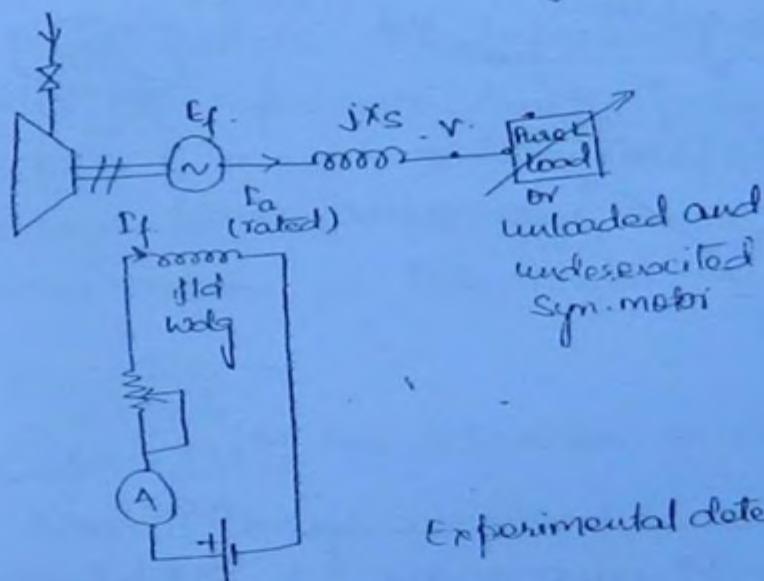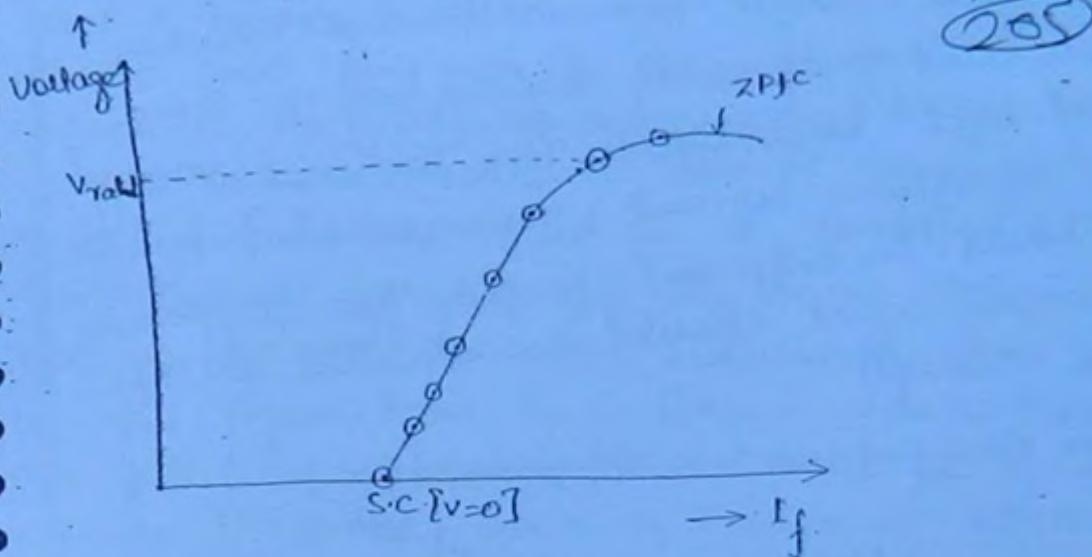

Experimental determination

Experimental determination of ZPFC :-


ZPFC also called Potier characteristics is the plot of lemaire voltage against fld current when rated armature current is maintained at zero pf lag.

Syn. motor is driven by syn. speed by prime mover. The D.P terminals of the gen. are short circuited and field current is increased until the L.C. armature current equals its rated value. This is the 1st pt on ZPFC.


Subsequently, the SC is removed and a pure induct or underevolved and unloaded syn. motor is connected.

and the pair of readings that is terminal voltage versus fd current for rated armature current is plotted. The step is repeated until terminal voltage reaches its rated value and preferably slightly higher. Since fd current and load both affect the terminal voltage as well as the armature current, recommended practice is fd current should be adjusted keeping the starting voltage in view and load should be adjusted for the rated armature current.

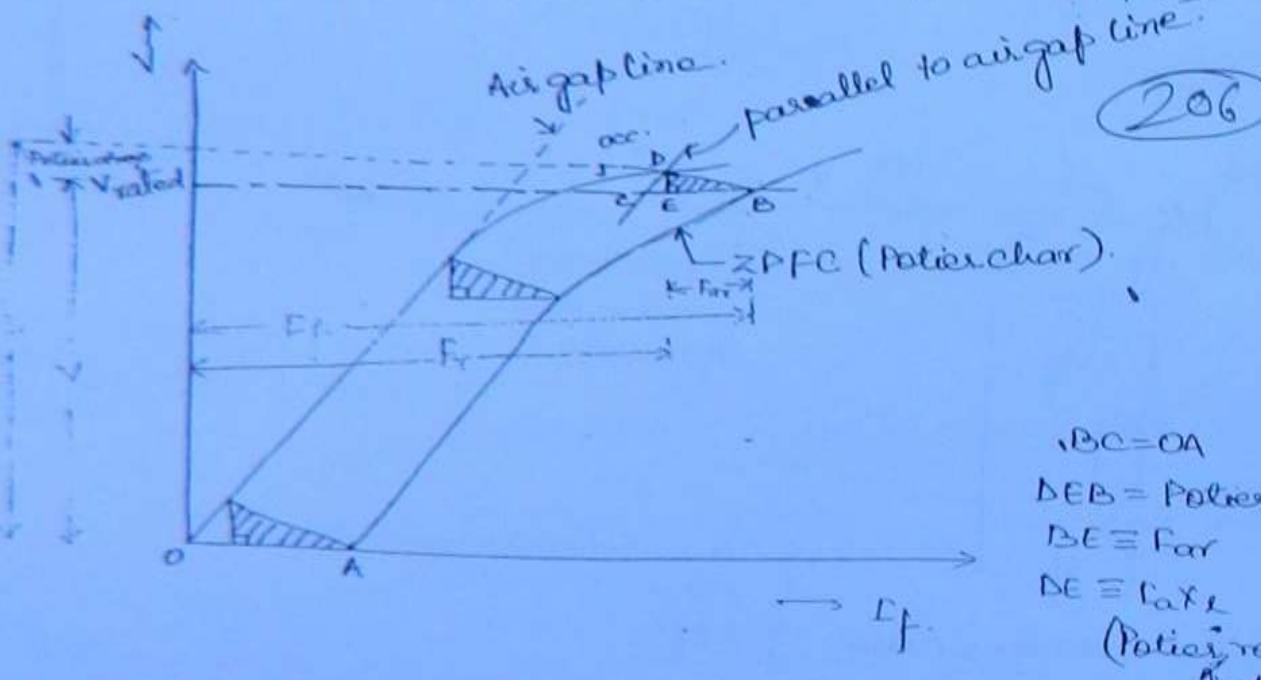Potier char from OCC \rightarrow [And two experimental pts.]



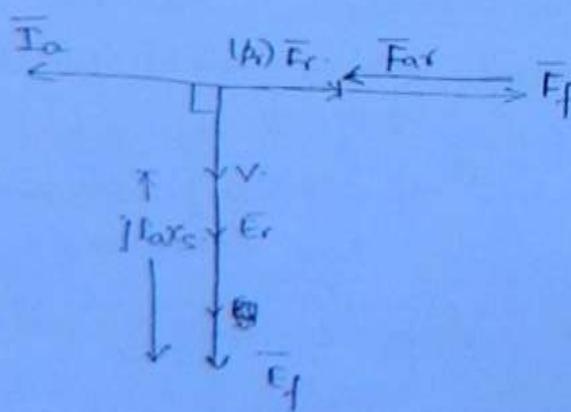$BC = OA$
 $DEB = \text{Potier triangle}$
 $EAO = \text{Far}$
 $DOB = \text{Far}$
 $(\text{Potier reactance drop})$




The o.c.c is plotted and two pts A and B are already obtained & experimental data are located on the same graph.
 Point A represents f.t current required to give rated current at S.C. and this can be obtained from S.C. char. Pt B represents the f.t current required to give rated voltage at the terminals while a zero pf lagging load draws rated current i.e. that is if corresponds to rated armature current at zero pf lag being delivered at rated voltage. $I_{sc} = 0A$ is taken horizontally from pt B as shown in the figure. From C, a line is drawn parallel to the air gap line intersecting the o.c.c at pt 'D'. From D, DE is drawn \perp to BC. ΔDEB is known as 'POTIER TRIANGLE'
 In the potier triangle, DE represents the potier reaction drops while BE represents armature reaction mmf. The potier Δ DEB is moved \parallel to itself while keeping its vertex always on the o.c.c. The locus of pt 'B' is the 'ZPF', also known as Potier char.

207

Voltage Regulation →

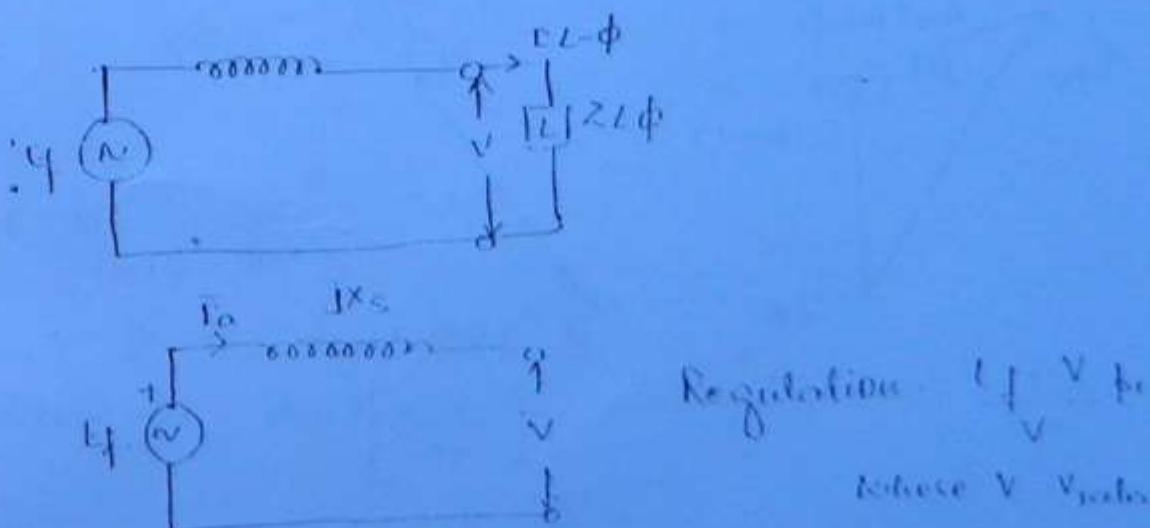Voltage Regulation of an alternator is defined as the rise in terminal voltage expressed as a fraction of the F.T. rated voltage when E.L. at a given pf is thrown off keeping the excitation const.



$$\text{Regulation} = \frac{E_f - V}{V} \text{ pu} \quad \text{where } V = V_{\text{rated}}$$

$$= \frac{E_f}{V} - 1 \text{ pu.}$$

$$= E_f (\text{pu}) - 1.$$


(D08)

Enf method or Synchronous reactance method :—

For lag :—


$$\text{Reg}^n \rightarrow \frac{\text{DQ-OP}}{\text{OP}} \text{ pu.}$$

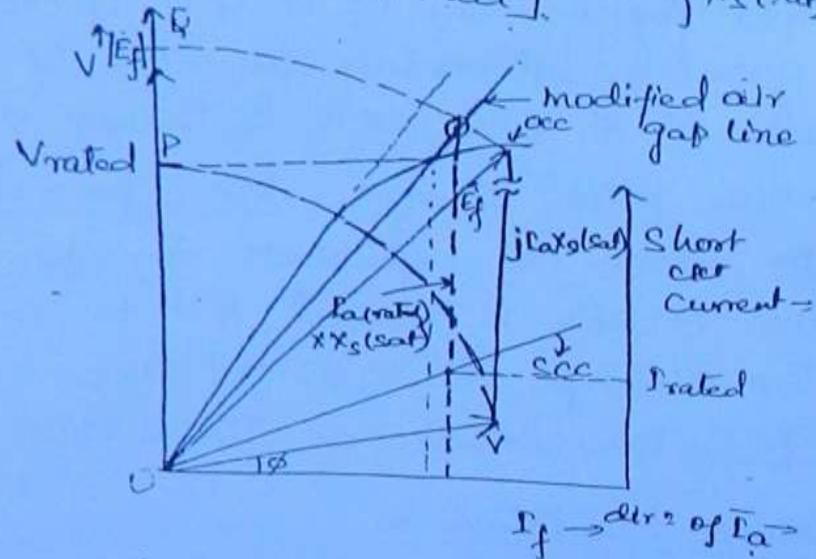[Pessimistic method] using $X_s(\text{sat})$




MMF method or Ampere turn method :—
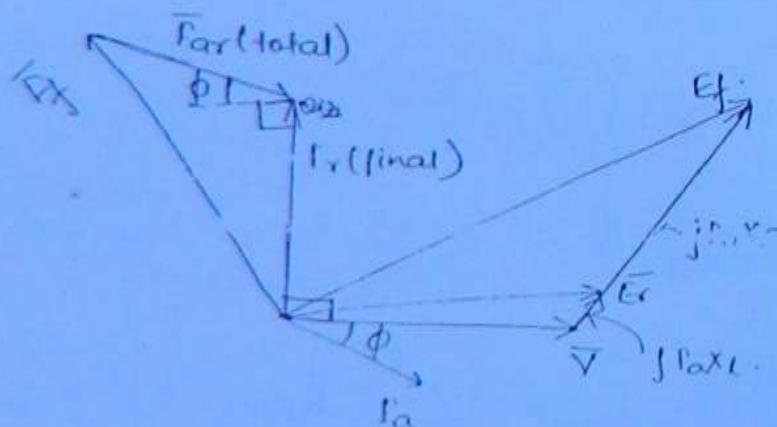
$$\text{Far(total)} = \text{Far} + \text{far}$$



Zero Reg^n → (Emf method)

(209)

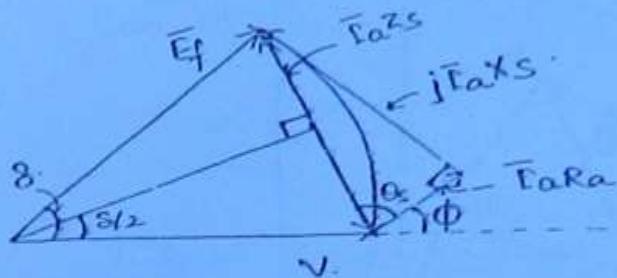

For zero Reg^n →

$$E_f = V$$


From phasor diagram,

$$\theta_s + \phi = 90^\circ + \frac{\delta}{2}$$

$$\Rightarrow \phi = (90 - \theta_s) + \frac{\delta}{2} \text{ leading}$$

$$\text{where } \frac{\delta}{2} = \sin^{-1} \left[\frac{Ra z_s}{2V} \right]$$

for $R_a = 0$

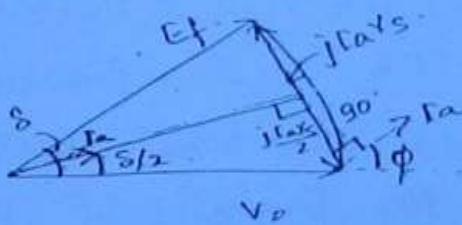

$$E_f = V$$

$$\theta_s + \phi = 90^\circ$$



$$\theta_s + \phi = 90 + \delta_2$$

$$\Rightarrow \phi = \delta_2 \text{ leading}$$


$$\text{where } \frac{\delta}{2} = \sin^{-1} \left[\frac{Ra x_s}{2V} \right]$$

Polar method or ZPfc method:

211

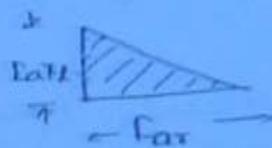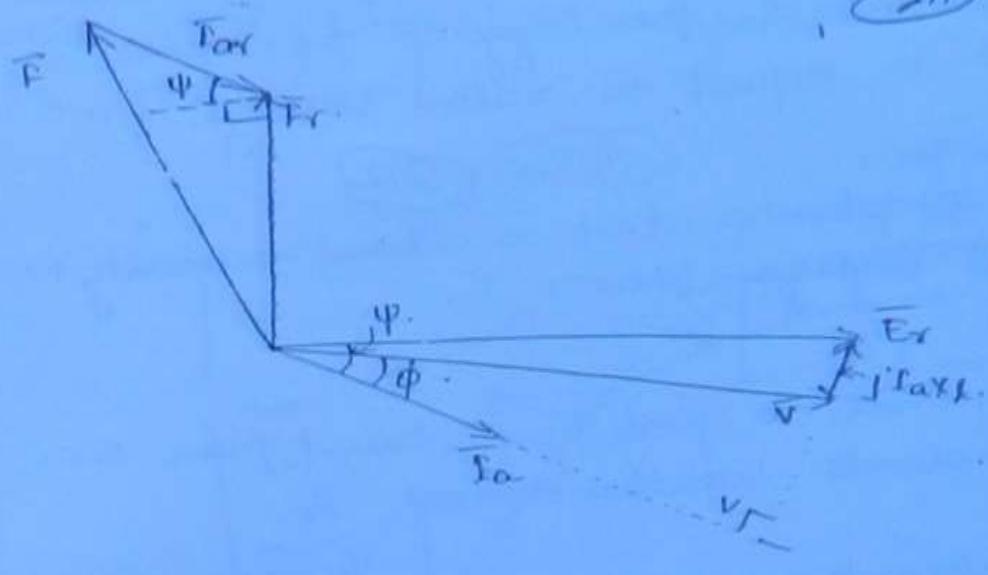

Potier △

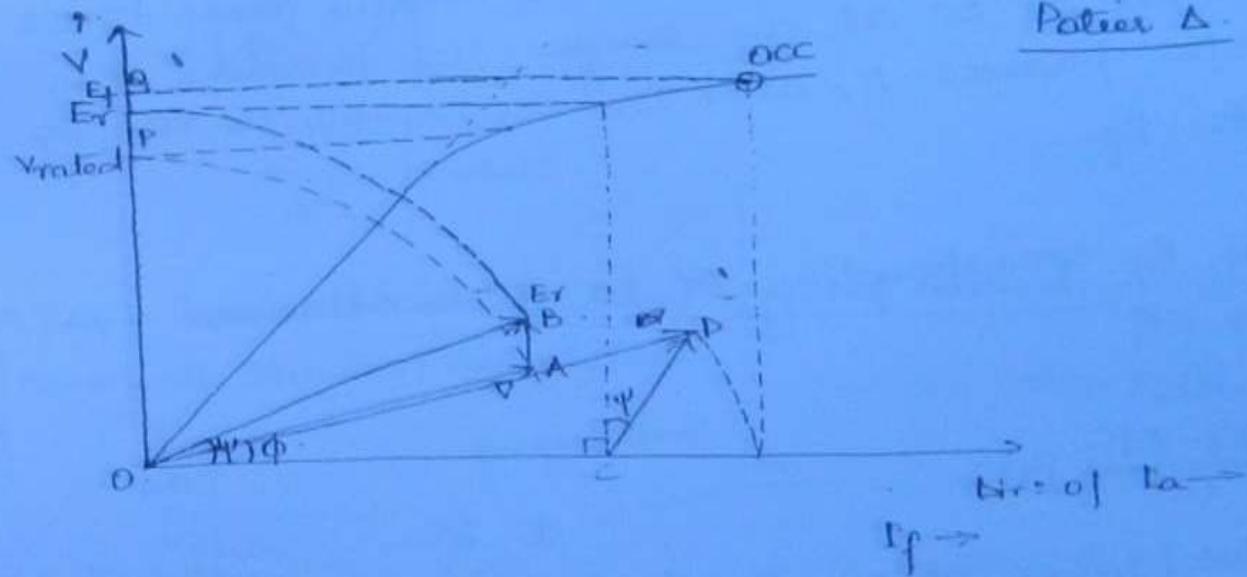

OA&EV

PB = Poles Arof Maxe)

$$DB = E_T$$

$$\alpha = \beta_\epsilon$$



CD: See § from Policy.)

015 = 1


$$\text{Req} = \frac{\partial Q - \partial P}{\partial V}$$

Polaris method or ZPFc method:

(211)

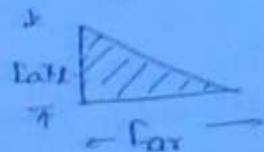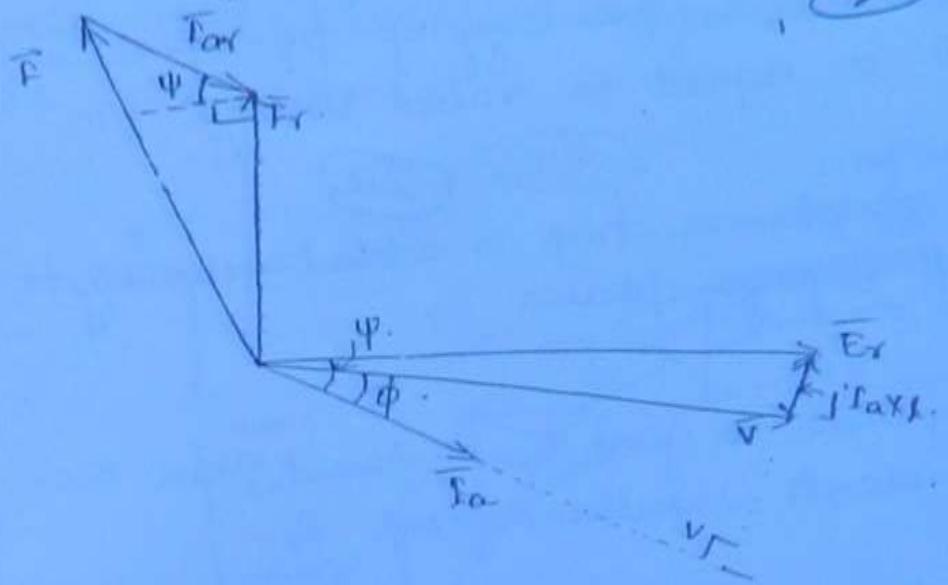

Polaris Δ

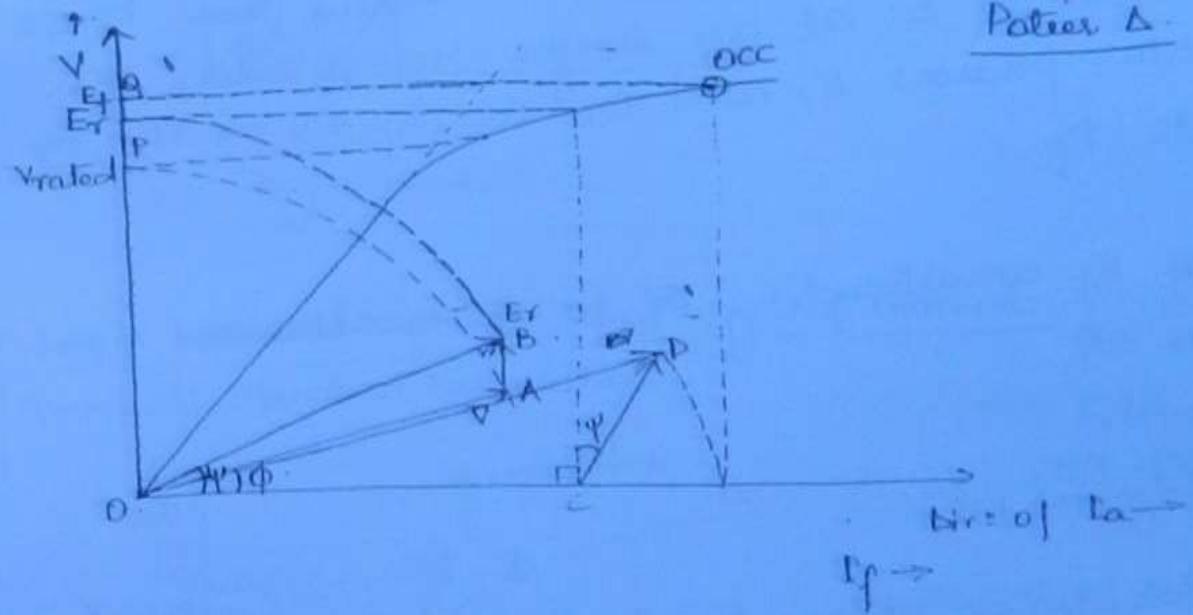

$$OA \equiv V$$

AB = Polaris drop (Max.)

$$DB \perp E_r$$

$$OC \equiv F_x$$

CD = Far from Polaris

$$OD \equiv F_y$$

$$\text{Req'd } \frac{OD}{OP} = \frac{OC - OB}{OP}$$

steps 1 ->

The terminal voltage phasor \bar{V} represented by OA is drawn leading armature current I_a for lagging pf operation. The magnitude of \bar{V} is equal to rated voltage 'OP'.

steps 2 ->

AB equal to pole reactance drop is added vertically to OA. OB gives air gap voltage phasor E_r . (212)

steps 3 ->

The fd current required to give E_r is found from $\frac{out}{occ}$. This is OC and represents resultant mmf F_r .

steps 4 ->

CD representing Amature Reaction is obtained from POISSON triangle is added to OC at an angle $90^\circ + \psi$ where ψ is the angle b/w phasors E_r and I_a as shown in the fig. OD represents F_f .

steps 5 ->

Magnitude of E_f corresponding to F_f is obtained from occ. This is OQ.


steps 6 ->

$$V.R. = P \frac{OQ - OP}{OP} \text{ pu.}$$

Comment -> Regulation obtain by Emf method where even relevant quantity was represented by an equivalent voltage was found to be much higher than actual. In mmf method where all quantities are represented by equivalent mmf give the best value of voltage regulation lower than actual.


The pole method treats the quantities as they are and therefore give quite acceptable value of V.R..

- Comparison of the three methods →
 - Rated armature current at 2 pf lag is maintained while field current is vary. Locus of $|V|$ is plotted for comparison

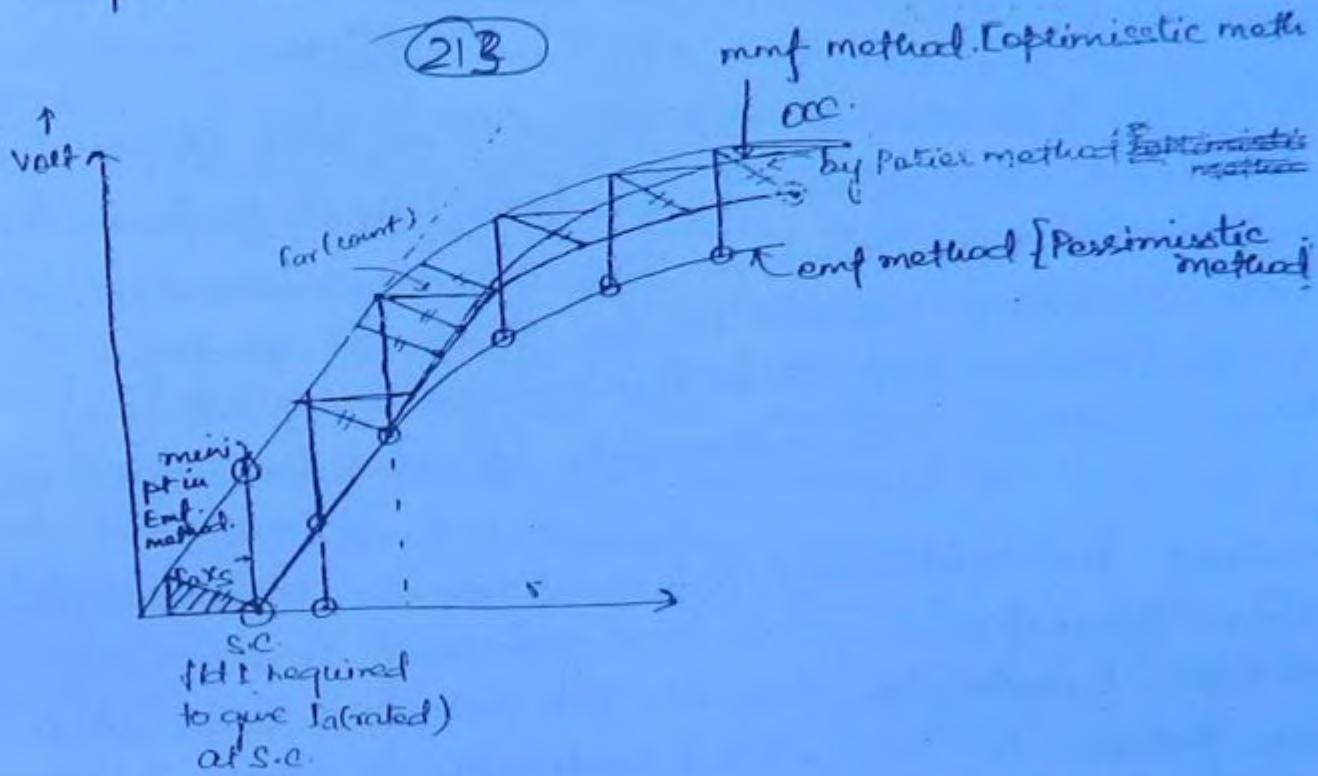

ASA's ~~method~~ modification of monte carlo method:-

American Standard Association

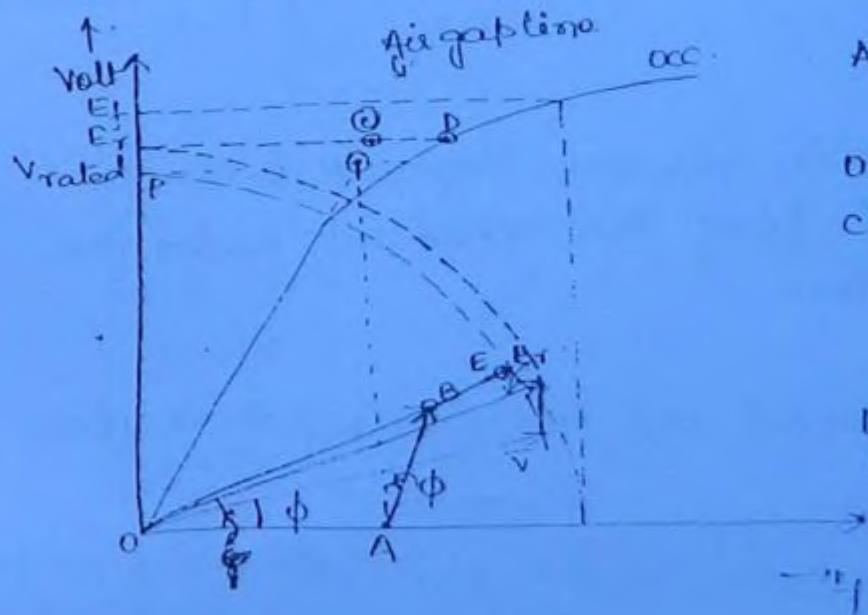

$\text{ON} \equiv F_s(\mu_{\text{real}})$ of unsat
ted ml

A_{SE} = $\frac{\text{Par (total) obtained}}{\text{Par}}$

DB = f_f of unsaturated

ΔP = Additional head required to overcome saturation
(Under the actual operating conditions)

$$\mathbf{B}\epsilon = \mathbf{C}\mathbf{D}$$

$\text{OC} = \sum_{j=1}^n \text{of actual intc}$

Biology

Step 1 :-

Alt current OA corresponding to rated voltage OP is obtained from air gap line. OA represents fr (final) of unsaturated m/c.

(214)

Step 2 :-

At $90 + \phi$ to A is drawn AB equal to far total obtained from SOC data. AB represents far (Total) and pertain to a unsaturated m/c because the m/c remains unsaturated & rated armature current under short ckt condition in the wake (presence) of directly demagnetizing effect of armature reaction. OB represents ff of unsaturated m/c.

Step 3 :-

for finding the additional fd mmf require to overcome saturation corresponding to air gap mmf fr, the air gap voltage Er has to be found. The potier reactance drop on the potier Δ is added vertically to terminal Voltage / to get Er. Corresponding to the magnitude of Er, the additional fd mmf require to overcome saturation is read from horizontal intercept b/w the air gap line and x. This is CD.

Step 4 :-

BE = CD is added as a collinear segment to OB. DE represent the fd mmf ff of the actual m/c under the dual operating condition.

Step 5 :-

Magnitude of E_f is found out corresponding to OC from x. This is OQ.

Step 6 :-

$$i.R. = \frac{OQ - OP}{OP} \text{ pu.}$$

Comment-

The ASA method acknowledge the fact the degree of saturation in m/c depends upon the value of air gap mmf Φ under the operating conditions. In this method therefore, the Φ required for an unsaturated m/c is determined by the use mmf method. The additional fld mmf required to overcome saturation is found out corresponding to the airgap voltage E_f under the operating condition. This additional magnitude of fld current is directly added to the fld current obtained by mmf method of an unsaturated m/c. The sum of these two fld mmfs therefore truly represent fld mmf of actual M/c. The ASA method has been found to give satisfactory results for cylindrical as well as salient pole m/c and is therefore recommended method for determination of V.R. of syn. gen. of all types.

Power Angle eqⁿ ->

(215)


$$\bar{V} = V \angle 0^\circ$$

$$\bar{E}_f = E_f \angle 8^\circ$$

$$\bar{Z}_S = Z_S \angle 0^\circ$$

$$\bar{I}_a = \frac{\bar{E}_f - \bar{V}}{\bar{Z}_S}$$
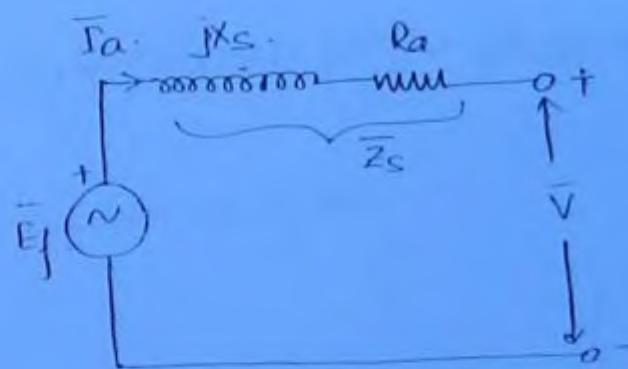
$$\frac{I_f \angle 8^\circ - V \angle 0^\circ}{Z_S \angle 0^\circ}$$



$$\frac{I_f \angle 8^\circ - V \angle 0^\circ}{Z_S \angle 0^\circ}$$

$$\text{complex power off. sent} = \frac{P_{\text{out}} + jQ_{\text{out}}}{V \angle \alpha}$$

$$\rightarrow S_{out} = VLO \left[\frac{E_f}{Z_s} \angle \theta_s - \frac{V}{Z_s} \angle \theta_s \right]$$

$$= \frac{VE_f}{Z_s} \angle \theta_s - \frac{V^2}{Z_s} \angle \theta_s \quad \text{--- (1)} \quad (216)$$

$P_{out} = \frac{VE_f}{Z_s} \cos(\theta_s - \delta) - \frac{V^2}{Z_s} \cos \theta_s$

→ Power angle eqⁿ.

$P_{out} = \text{max. when}$

$$\delta = \theta_s$$

$$\bar{S}_{\text{developed}} = \bar{E}_f \bar{E}_a^*$$

$$= \bar{E}_f \angle \delta \left[\frac{E_f}{Z_s} \angle \theta_s - \frac{V}{Z_s} \angle \theta_s + 90^\circ \right].$$

$$S_{dev} = \frac{E_f^2}{Z_s} \angle \theta_s - \frac{VE_f}{Z_s} \angle \theta_s + 90^\circ$$

$$P_{dev} = \frac{E_f^2}{Z_s} \text{ cos } \theta_s - \frac{VE_f}{Z_s} \cos(\theta_s + 90^\circ)$$

$P_{dev} = \text{max.}$

$$\theta_s + 90^\circ = 180^\circ$$

$$\Rightarrow \boxed{\delta = 180^\circ - \theta_s}$$

& This decides Stability.


✓ 12/11

Sure $P_a \geq 0$


$$Z_s = X_s, \theta_s = 90^\circ$$

$$P_{out} = P_{dev} - P \cdot V = \frac{VE_f}{X_s} \sin \delta$$
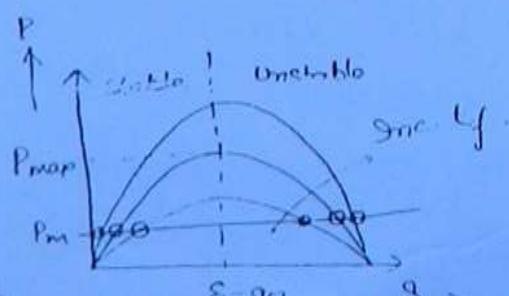
$$P_{max} = \frac{VE_f}{X_s} \sin 90^\circ$$



Power angle curve
of Power angle char

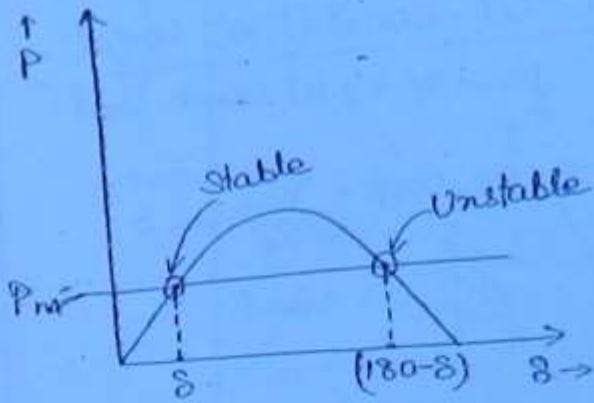

(217)

$$Q_{out} = \frac{V E_f \cos \delta}{X_s} - \frac{V^2}{X_s}$$

$$Q_{out} = \frac{V}{X_s} (E_f \cos \delta - V)$$

Case 1. →

$E_f \cos \delta = V$ i.e. Normally excited Gen.

Then $Q_{out} = 0$.

$$\tan^{-1}\left(\frac{Q}{P}\right) = 0 = \phi$$

$\cos \phi = \cos 0^\circ$ = unity pf operation

Case 2. →

$E_f \cos \delta < V$ i.e. underexcited Gen.

$$F_f < F_r$$

Then $Q_{out} = -\text{ive}$

Gen is supplying leading VARs and operating at leading

This means that it is receiving lagging VARs.


Case 3. →

$E_f \cos \delta > V$ i.e. overexcited Gen.

Then $Q_{out} = +\text{ive}$

is supplying lagging VARs and operating at lag.


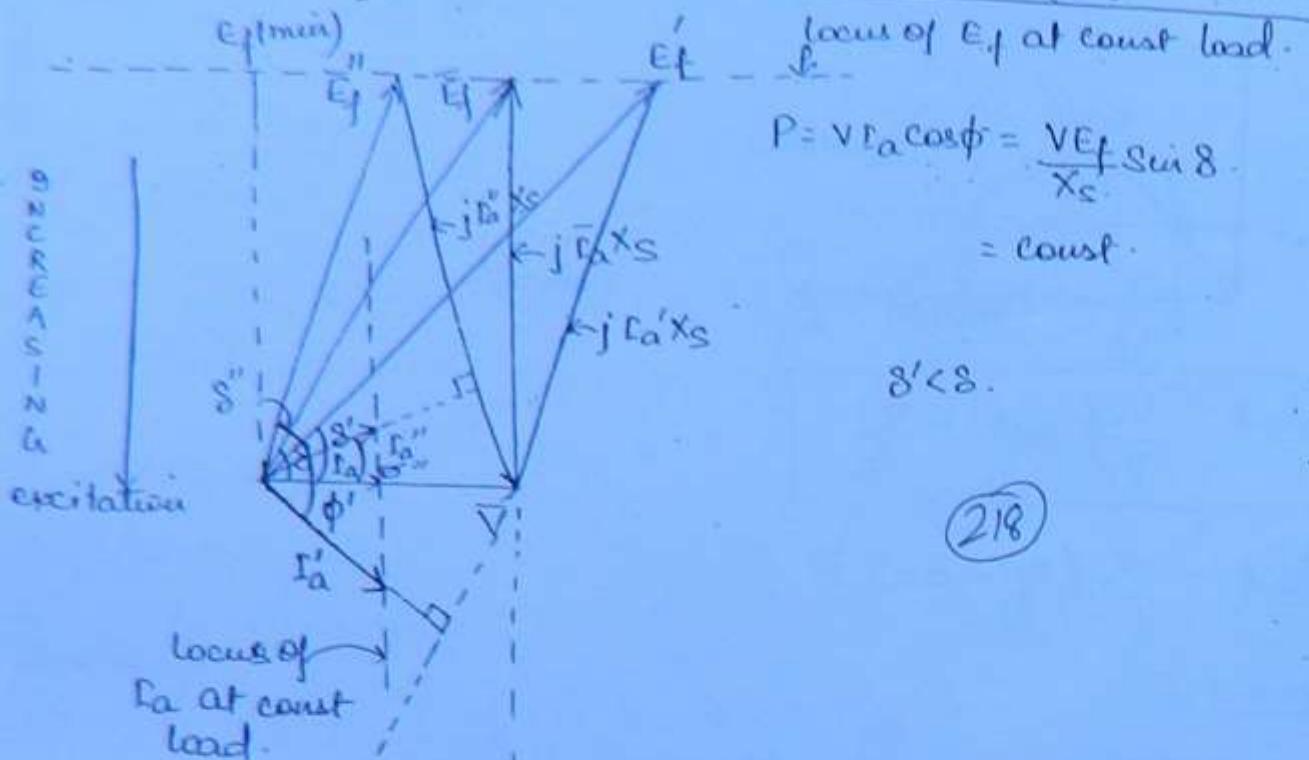
Effect of change in excitation at const (K_f) load:-



$$\delta' < \delta.$$

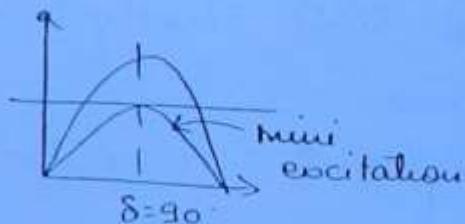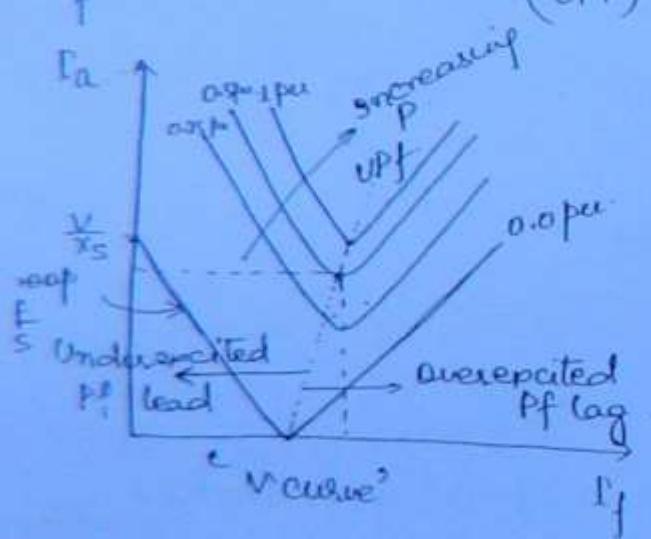(218)

Underexcited Pf lead. Normally excited (UPF) Over excited (Pf lag)



No load $\delta = 0$,

Underexcited Region,


$$I_a = \frac{V - E_f}{X_s}$$

$$= \frac{V}{X_s} - \frac{E_f}{X_s} = \frac{V}{X_s} - K_f I_f$$

Overexcited,

$$I_a = \frac{V}{X_s}$$

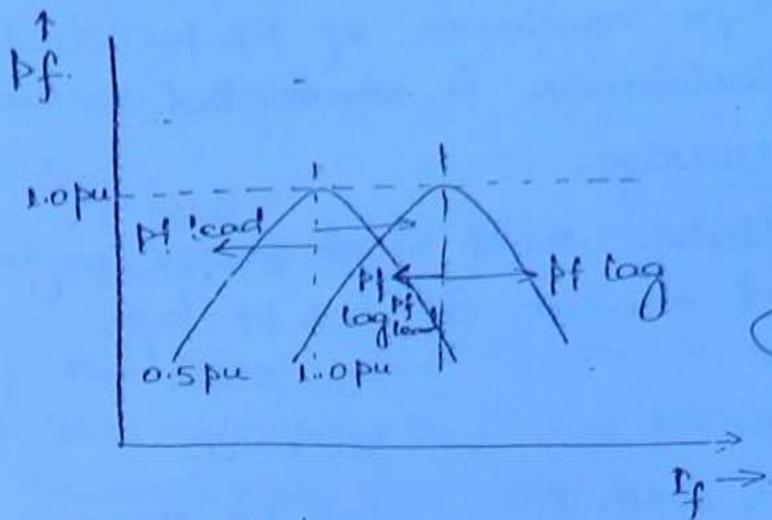
$$I_a = \frac{K_f}{X_s} I_f - \frac{V}{X_s}$$



219

Inverted 'V' curves.


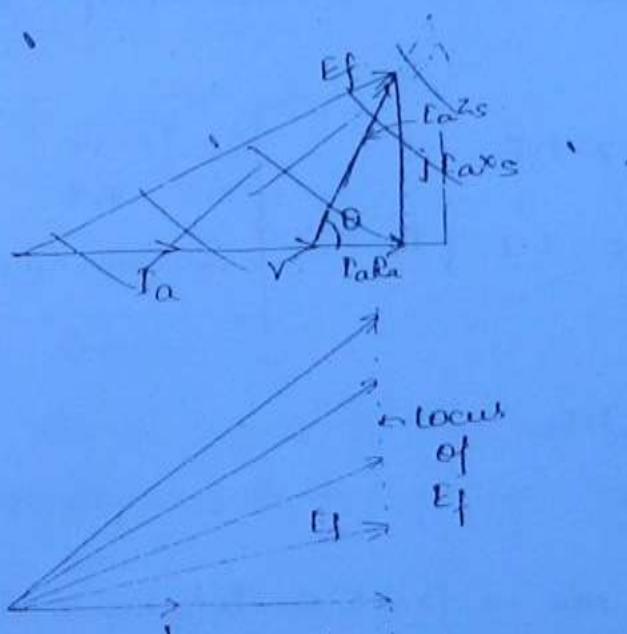
- Compounding curve of syn. gen. is the plot of field current vs armature current required to maintain const terminal voltage when a const pf load is varied.
- vary $\frac{R}{R_a}$ keeping their ratio const for same pf but load v



Unity pf

219

0.8 pf load

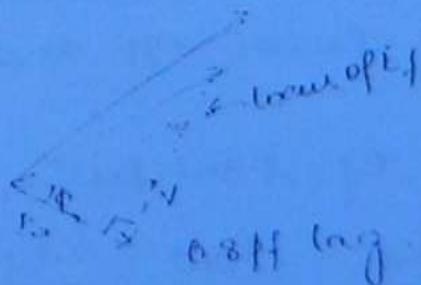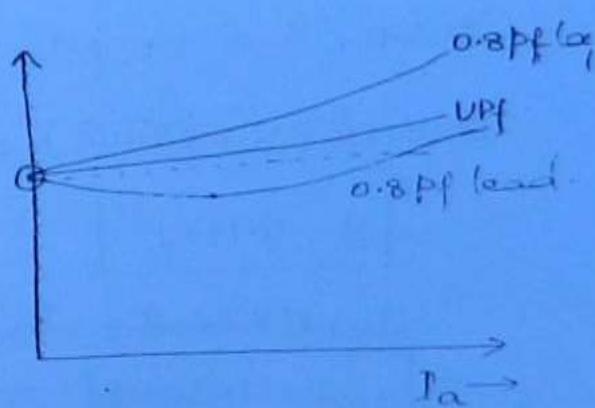

Q A syn. gen. with syn. reactance of 1.6 pu and negligible armature resistance is connected to an infinite bus at rated voltage

a) Determine the excitation emf and power angle when its full load current at 0.8 pf lag.

$$\text{Ans} \quad \bar{E}_f = V + j I_a x_s \\ = 1 + j \times 1 \times 1.6 \angle -\cos^{-1} 0.8 \\ = 2.341 \angle 33.15^\circ$$

V = 1 LO'
 $I_a = 1 L - \cos^{-1} 0.8$
 $x_s = 1.6 \text{ pu} = j 1.6$

$$E_f = 2.341 \text{ pu}$$

$$\delta = 33.15^\circ$$

(220)

b) with the excitation in part a, the gen is made to operate at UPF. Calc. the corresponding I_a and δ .

$$2.341 \angle \delta = 1 + j I_a x 1.6$$

$$2.341(\cos \delta + j \sin \delta) = 1 + j I_a 1.6$$

$$\boxed{\delta = 64.7^\circ}$$

$$\boxed{I_a = \frac{\sqrt{2.341^2 - 1^2}}{1.6}} \\ \boxed{\delta = \tan^{-1}(1.6 I_a)}$$

$$2.341 \times \sin \delta = I_a 1.6$$

$$\Rightarrow \boxed{I_a = 1.323 \text{ kA}}$$

c) With the excitation as in part a, determine the max. power output and the corresponding I_a and P_f .

$$E_f = 2.341 \text{ pu}$$

$[At P_{max}, \delta = 90^\circ]$

$$P_{out} = \frac{V \cdot E_f}{X_s}$$

$$= \frac{1 \times 2.341}{j 1.6} = 1.462$$

$$I_a = \frac{V - 1}{j X_s}$$

$$= \frac{2.341 \angle 90^\circ - 1 \angle 0}{j 1.6}$$

$$\text{pf} = \cos 23.13$$

= 0.9196 leading

Cat. check \rightarrow

$$P = VI \cos \phi$$

$$= 1 \times 1.591 \times 0.9196$$

(22)

- d) If the steam input of part A remains unchanged,
Cat. the excitation emf and power angle at which
pf becomes unity.

$$VI_a \cos \phi = V$$

$$\frac{V \cdot E_f \sin \theta}{X}$$

$$E_f = 1 + j \times 0.8 \times 1.6 \\ = 1.6243 / 52.0013 \\ = 1.6243 / 52.$$

P is same

$$VI_a \cos \phi = \text{const}$$

$$\Rightarrow I_a \cos \phi = \text{const}$$

$$\Rightarrow I_{a_2} \times 1 = I_{a_1} \times \cos \phi_1$$

$$\Rightarrow I_{a_2} = 1.0 \times 0.8$$

$$\Rightarrow I_{a_2} = 0.8 \text{ pu}$$

$$I_{a_2} = 0.8 / 0$$

- e) If the steam input of Part A remains unchanged

Cat. the emf and θ at which pf becomes 0.8 leading

$$I_{a_2} \cdot \cos \theta / 1 / \cos^{-1} 0.8$$

$$E_f = 1 + j \times 0.8 \times 1 / \cos^{-1} 0.8$$

$$= 1.2806 / 88.21 \text{ Am}$$

f) Cal. the min. excitation for the same steam input as in part a determine the corresponding I_a and P_f

$$E_f = j I_a X_S$$

$$I_a \cos \phi_1 = I_a \cos \phi_2$$

(222)

$$\Rightarrow I_a \cos \phi_2 = 1 \times 0.8$$

$$\delta = 90^\circ$$

$$0.8 = \frac{1.0 \times E_f^{(\min)}}{|1.6|} \sin \delta$$

$$\delta = 90^\circ$$

$$E_f \sin \delta = \text{const}$$

$$\Rightarrow 2.341 \sin 38.15^\circ = E_f (\min)$$

$$\Rightarrow E_f (\min) = 1.28 \text{ pu.}$$

$$I_a = \frac{1.28 \angle 90^\circ - 1.10^\circ}{|1.6|}$$

$$= 1.0152 \angle 37.99^\circ$$

$$P_f = 0.788 \text{ leading}$$

g) A steam input of part a remains unchanged but excitation is increased by 50% cal. new I_a and P_f .

$$E_f \sin \delta = \text{const}$$

$$1.28 = \pm 2.341 \angle (140.3) \sin \delta$$

$$\Rightarrow \delta = 24.87^\circ$$

$$2.341(1.3) / 24.87^\circ = 1.10^\circ + j \times 1.6 \times I_a / + \cancel{\phi}$$

$$\Rightarrow I_a = \frac{2.341 \times 1.3 \angle 24.87^\circ - 1.10^\circ}{|1.6|}$$

Now $E_f 2 = 1.3 E_f 1$.

$$I_a = \frac{1.3 \times 2.341}{24.88 - j1.6}$$

$$P = \frac{V E_f \sin \delta}{X_s}$$

(223)

$P \propto E_f \sin \delta$.

~~$E_f \cdot E_f \sin \delta = \text{const}$~~

$$\cos \phi = P_f = \cos 53.93^\circ$$

$$E_f 2 \sin \delta_2 = E_f 1 \sin \delta_1$$

$$\sin \delta_2 = \frac{\sin 33.15^\circ}{1.3}$$

$$\delta_2 = 24.88^\circ$$

- h) For a power angle of 20° , cal. the two possible val. of excitation conf, if gen. delivers 30% of P_{FL} . determine corresponding P_f .

Ans. $\delta = 20^\circ$


$$I_a 2 = 30\% \text{ of } I_a 1 \\ = 0.3 \times 1$$

~~$E_f 2 \sin \delta = \text{const}$~~

~~$E_f 1 \propto E_f 2$~~

$$I_a 2 / 0.3 \times I_a 1 = 1$$
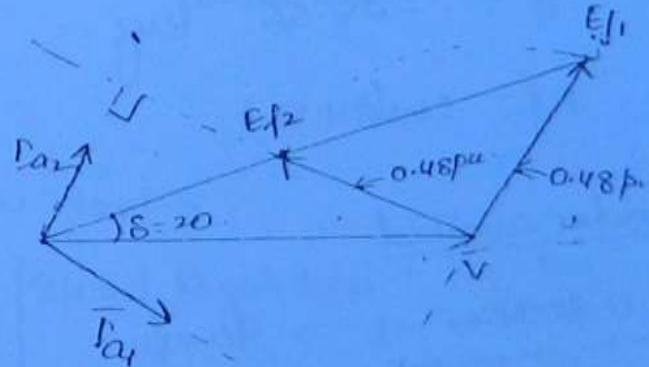
$$P_f = 0.16 \times 1.6 \times 0.3 + j1.6 \times 0.3 + 0.3 \times 0.48 \cos \phi \\ = 0.48 \angle 30^\circ$$



$$U_f \angle 20^\circ = 1.6 \angle 0^\circ + j0.3 \angle \phi + 1.6$$

$$U_f \angle 20^\circ = 1 + 0.48 \angle 90 + \phi$$

$$\therefore 0.48 \angle 30 + \phi = U_f \angle 20^\circ - 1$$

$$\Rightarrow 0.48 \angle 90 + \phi = E_f \angle 20^\circ - 1$$

$$\Rightarrow 0.48 \angle 90 + \phi = (E_f \cos 20^\circ - 1) + j(E_f \sin 20^\circ)$$

$$\Rightarrow 0.48 \cos(90 + \phi) + j 0.48 \sin(90 + \phi) = (E_f \cos 20^\circ - 1) + j(E_f \sin 20^\circ)$$

$$\therefore 0.48^2 = (E_f \cos 20^\circ - 1)^2 + (E_f \sin 20^\circ)^2$$

$$= E_f^2 + 1 - 2 \cos 20^\circ E_f$$

(224)

$$\therefore E_f^2 - 2 \cos 20^\circ E_f + 1 - 0.48^2 = 0$$

$$E_f = 1.2765 \rightarrow \text{overexcited}$$

$$= 0.603 \rightarrow \text{under excited}$$

Overexcited \rightarrow

$$90 + \phi = \text{Arg} [1.2765 \angle 20^\circ - 1]$$

$$90 + \phi = 65.44$$

$$\phi = -24.56^\circ \text{ lag}$$

$$P_f = \cos(24.56)$$

=

Under excited

$$\underline{1.603 \angle 20^\circ - 1} = 90 + \phi$$

$$\Rightarrow 1154.55 = 90 + \phi$$

$$\Rightarrow \phi = 64.56^\circ \text{ lagging}$$


$$P_f = \cos 64.56^\circ = 0.4296 \text{ leading}$$

map n of steam turbine at $n_L \rightarrow 35^{\circ}$

The needs and advantages of parallel operation of syn. generators are similar to those discussed under Time with an additional factor as follows:-

- 1) With more no. of generators available for PEL operation, it would be possible to switch off subgenerators and operate the remaining generators near their full load cap. as operation of a large unit at partial load is inefficient. This may be required when the system demand become low.

Q25

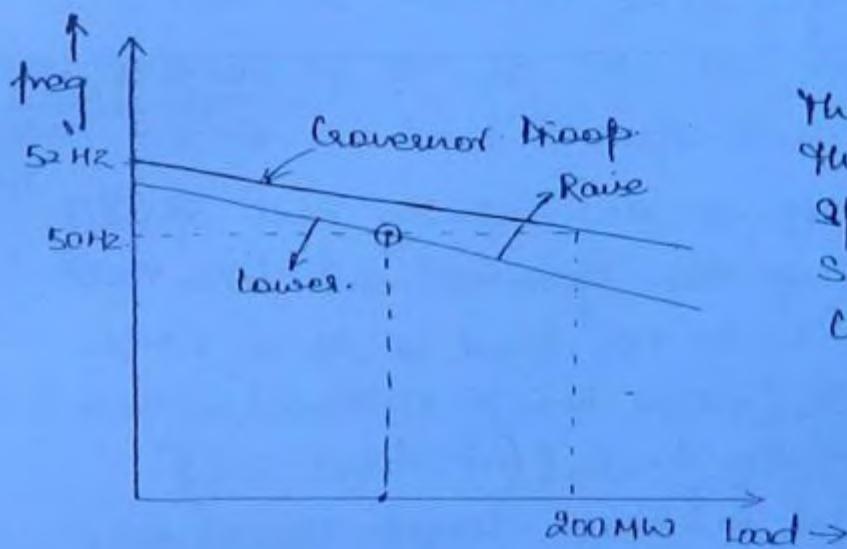

The device which changes the droop is called speed changer or Speeder gear or Control gear

Governor Regulation (or Droop)

$$= \frac{(52 - 50) \text{ Hz}}{200 \text{ MW}} = \frac{1.0 \text{ rpm}}{1 \text{ pu}} = \frac{2 \text{ Hz}}{200 \text{ MW}} = 0.01 \text{ Hz/MW}$$

Speed Regulation = $\frac{52 - 50}{50 \text{ Hz}}$


$$= 0.04 \text{ pu.}$$

OR $\frac{3120 \text{ rpm} - 3000}{3000 \text{ rpm}}$

$$= 0.04 \text{ pu.}$$


OR $\frac{1.0 \text{ pu} - 1.0 \text{ pu}}{1.0 \text{ pu}} = 1.09 \text{ pu.}$

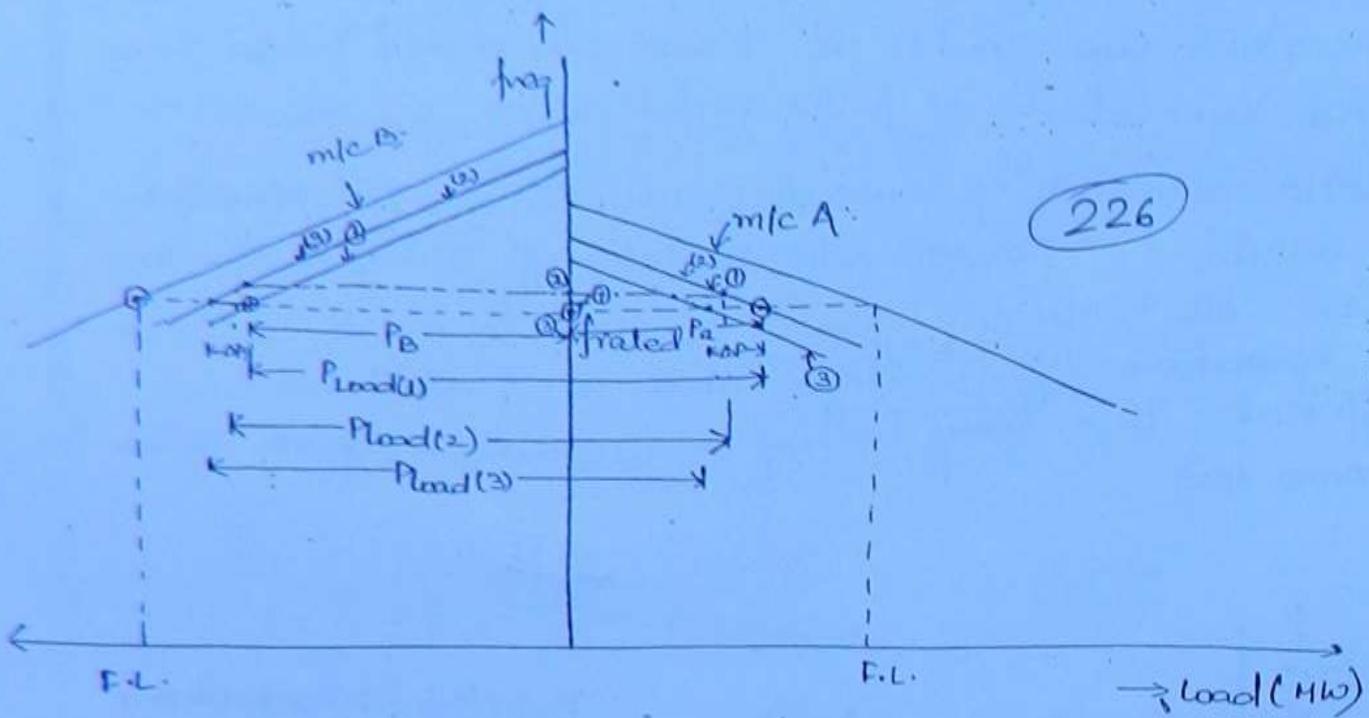Effect of change in steam input :—
with const. load demand.




Q. Two 3- ϕ alternators of 50 MW capacity each operate in parallel. The settings of the governor are such that rise in speed from F.L. to no. load is 2% in 1st m/c and 3% in 2nd m/c. The char. being st. line in both cases. If each m/c is fully loaded (at rated freq). When the total load is 100 MW. What would be the load on each m/c when the total load is 60 MW.

A.m.

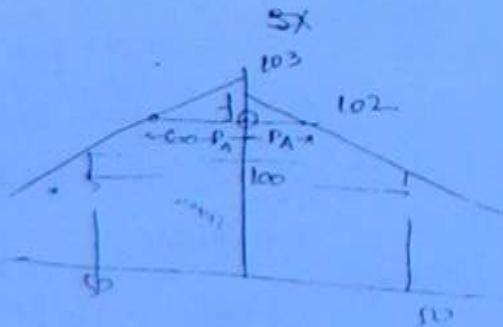
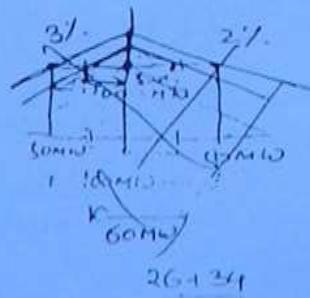
$$\begin{aligned} \text{M/c A} &\Rightarrow 120 - \frac{100}{P_A} = \frac{102 - 100}{50} \\ \text{M/c B} &\Rightarrow 100 - \frac{103}{60 - P_A} = \frac{103 - 100}{50} \end{aligned}$$



$$\frac{102-f}{P_A} = \frac{2}{50-25} = \frac{1}{25} \Rightarrow 25 \times 102 - 25f = P_A$$

$$\Rightarrow P_A + 25f = 25 \times 102$$

$$\frac{103-f}{60-P_A} = \frac{3}{50} \Rightarrow 50 \times 103 - 50f = 3 \times 60 - 3P_A$$

$$\Rightarrow 3P_A - 50f = 3 \times 60 - 50 \times 103$$

$$P_A = 26 \text{ MW}$$

$$f = 100.96\%$$

(227)

$$P_B = 60 - 26$$

$$= 34 \text{ MW}$$

Q. Two identical 2000 kW, 50 Hz alt. operate in parallel.


The governor of the 1st m/c has regulation of 4% and from F.L to No load corresponding speed regulation of 2nd m/c is 5%.

a) How will the two m/c share a load of 3000 kW

b)

$$\text{MICA}) \quad \frac{104-f}{P_A} = \frac{104-100}{2}$$

$$2(104-f) = 4P_A$$

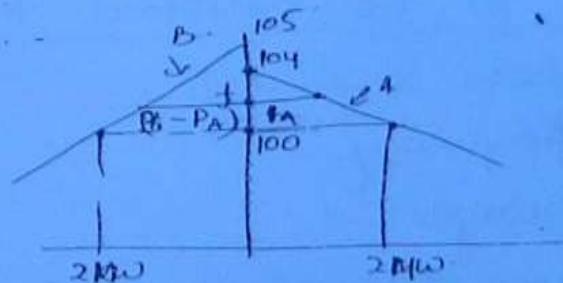

$$\frac{105-f}{60-P_A} = \frac{105-100}{2} = \frac{5}{2}$$

$$\Rightarrow 2 \times 105 - 2f = 15 - 5P_A$$

$$\Rightarrow 5P_A - 2f = 15 - 2 \times 105$$

$$\Rightarrow 4P_A + 2f = 2 \times 104$$


$$\therefore P_A = 1444.4 \text{ MW}$$

$$P_B = 3000 - 1444.4$$

$$= 1555.56 \text{ kW}$$

$$f = 101.11 \text{ Hz} \approx 1\%$$

at 50.5 Hz

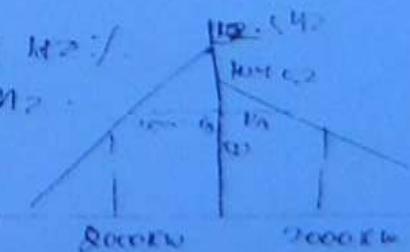

Q) what is max load that can be delivered w/o overloading either the m/c


Ans 4000 kW or 4 MN. ($2000+2000$)

(228)

2) Cat max load at which one of the m/c would become unloaded.

$$\frac{52.5 - 52}{P_L} = \frac{52.5 - 50}{2000}$$

$$P_L = 400 \text{ kW}$$

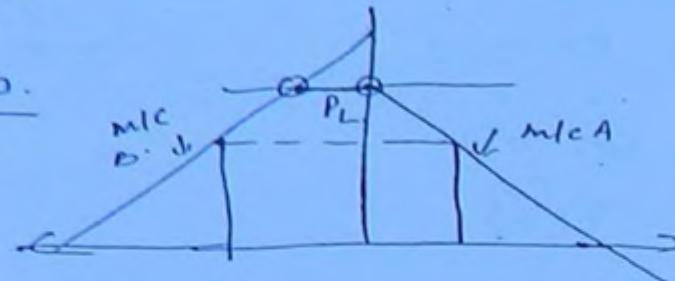

Parallel Generator theorem by millman's theorem

Synchronisation →

It is the process of connecting electrically an incoming m/c to a running m/c.

Conditions to be satisfied for Synchronisation —


- 1) Same phase sequence
- 2) Same frequency
- 3) Same voltage
- 4) Zero phase diff. at the instant of Synchronisation
- 5) Same waveform.

4/27/11

Synchronisation by Dark lamp method :-

Synchronisation by dark lamp method:-


229

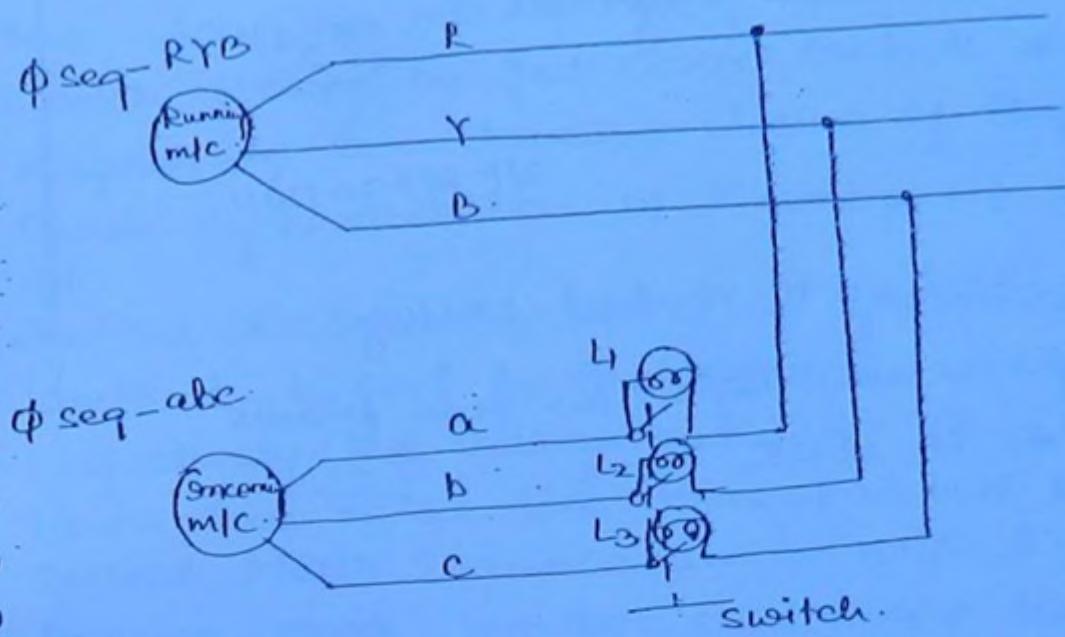

a-R: L_1


b-Y: L_2

c-B: L_3

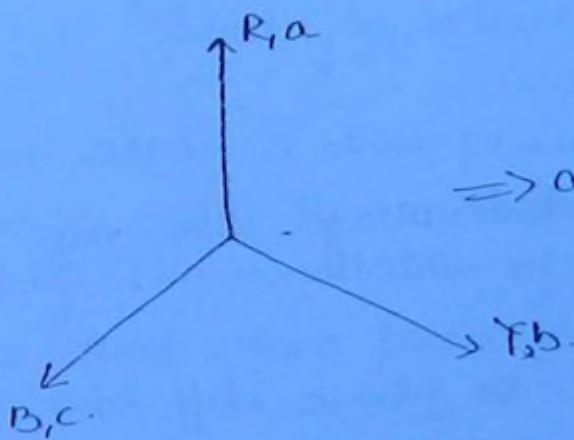


\Rightarrow all lamps dark together

\rightarrow all bright or dark together

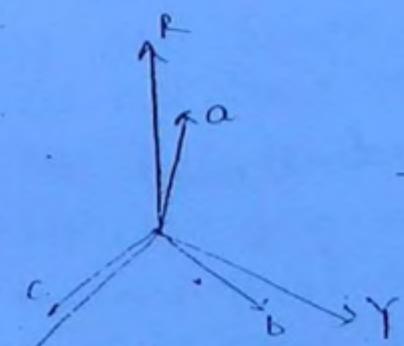

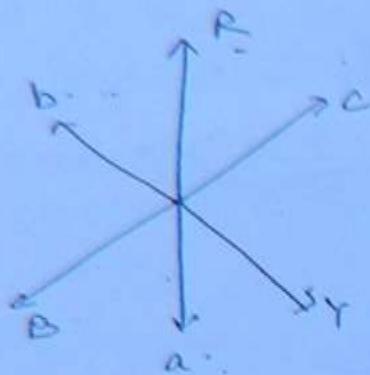\rightarrow Some are bright, one is less bright
One is dark.




→ maxⁿ brightness.

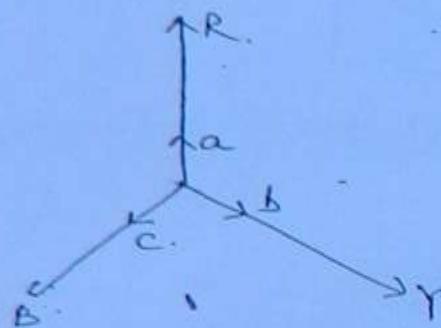(23)


O/P of P.T = 110V.

- rating of bulb = $2 \times$ line to neutral voltage.
- if phase diff mag. diff is very high b/w two phases then lamp will not be dark.



→ At mini 30% of rated voltage, we can just see the brightness of lamp.

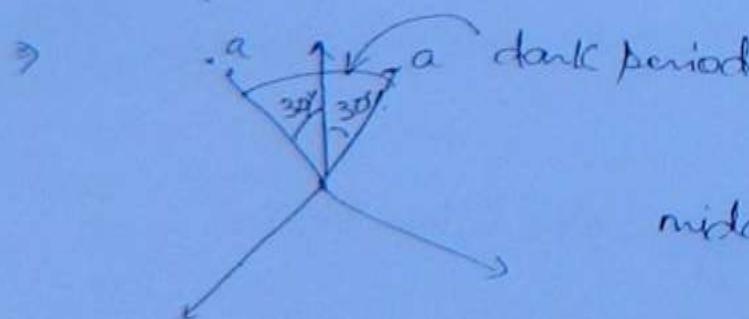- At 100% freq equal or phase diff b/w phases is same then the we const. brightness of bulb.
- for incommg m/c, interval b/w successive dark must be max.




middle of dark period →

if breaker close and
Synchronisation
possible,

- By dark lamp method : —
- If the phase seq. of incoming m/c is R-Y-B and if the incoming m/c is A-B-C, then the synchronisation switch would be put across contacts at A-R, B-Y, C-B respectively. Simultaneous closure of these switches would cause synchronisation of incoming m/c with the running m/c.
- (231)
- In the dark lamp method of synchronisation, 3 identical lamps L_1 , L_2 and L_3 are connected across A-B-R, B-Y, C-I respectively. The voltage rating of these lamps should be twice the rated line to neutral volt of the m/c to. Correct phase sequence can be verified if all the 3 lamp become dark together and bright together with the same intensity of brightness. If not so, any two terminals of the incoming m/c should be interchanged to correct the phase seq.
- If the lamps never attain a dark phase but intensity of brightness changes with time. Then if measured the volt. diff is too high. The excitation of the incoming m/c must be varied so that dark phase of all the lamps is obtained.
- If the lamps are dark or glow with the same intensity at all time then it means that the freq. of incoming m/c has become exactly equal to the freq. of running m/c. The freq. of incoming m/c should be adjusted in a manner that the interval b/w successive dark phases is maximised. This would insure that freq. diff has become very low. Under these conditions, duration of the dark period would become long enough to correctly anticipate the middle of the dark period at which the synchronisation switch should be closed to insure proper synchronisation of the incoming m/c with the running m/c.

232

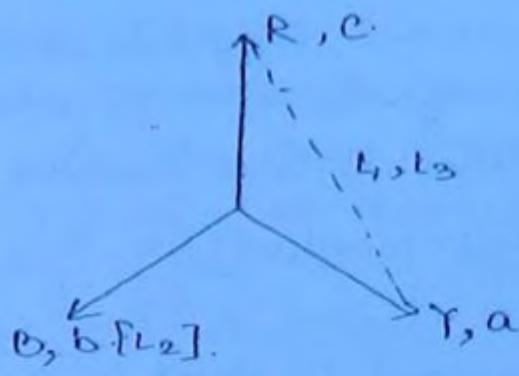


(233)

$l_2 \rightarrow$ dark.

l_1 and $l_3 \rightarrow$ equally bright.

Synchronise \rightarrow No.

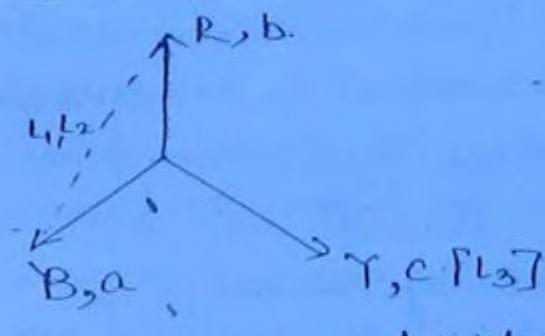Synchronisation Only at l_1 [dark], $[l_2$ and $l_3]$ \rightarrow equally bright.]



$l_1, l_2 \rightarrow$ equally bright


$l_3 \rightarrow$ dark

Synchronise \rightarrow No.

If Seq. of Dark lamp \rightarrow

$l_1, l_3, l_{22} \rightarrow$ incoming m/c is faster

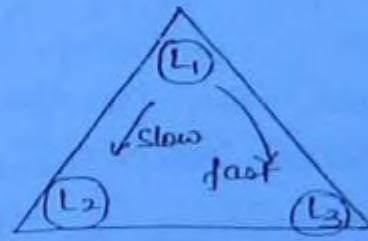$l_1, l_2, l_3 \rightarrow$.. " .. Slower



By Rotating lamp method \rightarrow

In the dark lamp method, an operator can misjudge the middle of the dark point because of contraction and expansion of the pupil of his eyes due to change in brightness of the lamps. This error judgement would lead to synchronisation at the wrong instant.

which obviously would be premature synchronisation. This drawback may be overcome by the use of dark amp method also called Siemens and Halske method or one dark and two bright lamp method. In this method L_1 remains connected b/w 'A' and 'R' but connection of L_2 and L_3 are interchanged so that L_2 is now b/w 'B-B' and L_3 is b/w 'C-Y'. With this arrangement, the voltage and frequency of the incoming m/c is adjusted according to similar procedure as in dark amp method. But the synchronisation switch is closed when L_1 is dark and L_2 and L_3 are equally bright. The operator can sense equal brightness correctly and therefore error in the instant of synchronisation is unlikely. This method offers a further advantage that the freq. of a incoming m/c ~~with~~ whether a lower or higher as compared to running m/c may be found out by the seq. in which the 3 lamps become successively dark. So if seq. of darkening is L_1, L_3, L_2 then the incoming m/c is fast. However the seq. of darkening is L_1, L_2, L_3 then the incoming m/c is slow. Corrective action can therefore be taken accordingly.


Synchronoscope method \rightarrow

At 12 o'clock, freq. diff = 0.

At 6 o'clock, freq diff = 120.

At 3 o'clock, 30° leading of incoming m/c.

234

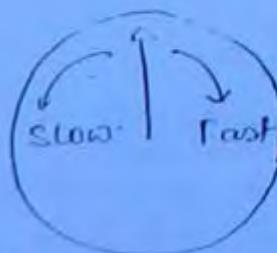

incoming m/c must have higher freq and voltage for generation action.

Synchroscope method:-


- 1) Using the speeder gear match the freq. of the incoming m/c with the freq. of the running m/c. It is recommended that the freq. of the incoming m/c be kept very slightly higher than that of the running m/c.
- 2) Using the excitation control switch, match the voltage of the incoming m/c with the voltage of the incoming m/c. Again, it is recommended that the incoming voltage be kept slightly higher than the running m/c voltage.
- 3) Switch on the synchroscope and also check the synchronism relay if available. Switch off the anti-motoring protection if provided. 235
- 4) Find control the freq. of incoming m/c such that the pointer of synchroscope rotates very slowly in the fast dirⁿ. When the pointer reaches 11 o'clock position, give a command to the circuit breaker switch to close the breaker. By this action, it is expected that the circuit breaker contacts would actually close at 12 o'clock position, a position that represents 0 phase displacement b/w the voltages of the incoming and running m/c.
- 5) Take initial load on the m/c with the help of speed gear and adjust fd excitation for desired power factor.
- 6) Switch off the synchroscope and check synchronism relay. Switch on the Autostarting protection scheme after a mini load has been taken on the m/c.

Q. A syn. m/c is synchronised with an infinite bus at rated voltage. Now the steam input to prime mover is inc. till syn. m/c starts operating at rated kva. The m/c has syn. impedance $Z_s = (0.02 + j 0.8) \text{ pu}$. Determine the operating power factor of alternator and its load angle.

$$\frac{\delta}{2} = \sin^{-1} \left(\frac{P_d Z_s}{2 \times V} \right)$$

$$= \sin^{-1} \frac{1 \times 0.80025}{2 \times 1}$$

$$\delta = 47.172$$

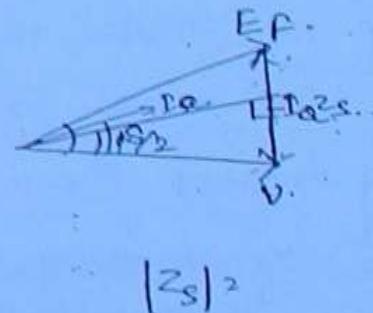

$$\phi = 90 - \theta_s + \frac{\delta}{2} \text{ leading}$$

$$= 90 - \tan^{-1} \frac{0.8}{0.02} + \frac{3}{2}$$

$$= 25.02 \text{ leading}$$

(23c)

$$\cos \phi = 0.906 \text{ leading}$$

Q) A 3MVA, 50 Hz, 11KV, 3φ star connected alt.

Supplies 100 Amp at 0 pf leading. When the load is removed, terminal volt. falls down to 9.63 KV. Calc. regulation of alternator when supply full load at 0.8 pf lagging. Assume an $R_s = 0.4 \Omega$ per phase.

$$V_m = 11 \sqrt{3} \text{ KV}$$

$$P = 100 \angle 90^\circ$$

$$E_f = \frac{9.63 \times 1000 \angle 0^\circ}{\sqrt{3}}$$

$$R_s + j X_s = (0.4 + j X_s) = R_s \angle \tan^{-1} \frac{X_s}{R_s}$$

$$\frac{9.63 \times 1000}{\sqrt{3}} \angle 8^\circ = \frac{11}{\sqrt{3}} \times 1000 \angle 0^\circ + 100 \angle 90^\circ \sqrt{0.4^2 + X_S^2} \angle 0^\circ$$

$$\left(\frac{9630}{\sqrt{3}}\right)^2 = \left(\frac{11000}{\sqrt{3}}\right)^2 + 100^2(0.4^2 + X_S^2)$$

$$X_S = 7.91 \Omega$$

237

$$\begin{aligned} \text{Vout. Reg} &= \frac{E_f - V}{V} \times 100\% \\ &= \frac{E_f - \frac{11000}{\sqrt{3}}}{\frac{11000}{\sqrt{3}}} \times 100\% \end{aligned}$$

$$E_f = \frac{11}{\sqrt{3}} \times 1000 \angle 0^\circ + I_a (0.4 + j7.91)$$

$$= \frac{11 \times 1000 \angle 0^\circ + 157.459}{\sqrt{3}} (0.4 + j7.91)$$

$$= \frac{11000 \angle 0^\circ + 157.459}{\sqrt{3}}$$

$$= 7212.53 \angle 7.6377^\circ$$

$$\boxed{\text{Vout. Reg}^2 = 13.56\%}$$

~~$$\begin{aligned} I_a &= \frac{18 \times 10}{11 \sqrt{3} \times 10^3} \\ &= \frac{9}{\sqrt{3}} \\ &= 1.412 \\ &= 1.4125 \\ P &= \sqrt{3} \times 11 \times 10^3 \\ &= 3300 \text{ W} \\ P_m &= \frac{1}{3} \times \frac{1}{\sqrt{3}} \times 100 \\ &= 19.6782 \\ \frac{3}{2} \times 10 &= 15 \\ \frac{3}{2} \times 10 &= 15 \\ 11 &= 11 \end{aligned}$$~~


$$S = I_a V_L S_C$$

$$\eta = \frac{S}{\sqrt{3} V_L} = S_C$$

$$= S_C \times 11.459\%$$

288

Generator connected to isolated load →

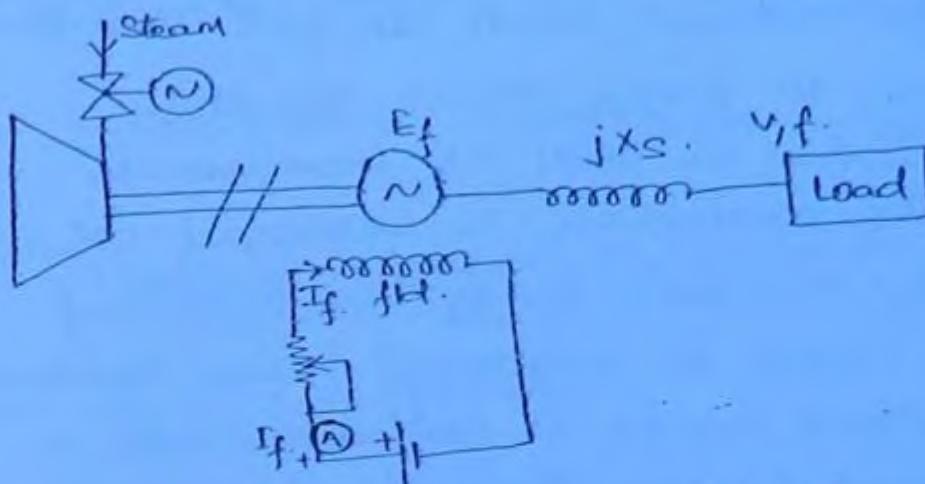

Q39

→ What is total current & electrical load?

Any device capable of drawing electrical power is an electrical load.

Static load $\rightarrow P \propto V^2$

Steam E/P increases \rightarrow
Speed \uparrow , f \uparrow (always), v \uparrow , static load P \uparrow

Rotating loads \rightarrow f \uparrow , speed of loads \uparrow , syn. m/c speed \uparrow
induction m/c slip S \uparrow ; demand \uparrow .

Overall unit loading and freq \uparrow .

Operation →

When prime mover E/P is increased while excitation remains const, it results in an increase in freq. The increase in freq increases the terminal voltage for the same excitation. The inc. in terminal voltage causes the static loads to inc. their respective demands. As their power consumption is proportional to the square of the voltage. The rotating loads have their respective speeds increased because of the inc. in freq. that inc. their syn. speed. The inc. in voltage to results in inc. their developed torque and consequently power drawn.

may increase particularly if when they are during
unit torque load, the load factors result in an increased
power demand by the rotating loads as well. The final
conclusion is increase in prime mover D/P alone
results in increase in freq as well as increase in
unit loading. If the excitation is increased while
the prime mover input remains const, the terminal
volt increases. This results in increased power consump-
tion by the connected loads as explained above.
Since this increased power demand is not met
by the prime mover, it is fed from the stored K.E.
of the rotating mass resulting in reduction of freq.
To restore the freq. to its previous value, the prime-
mover input must be increased.

(240)

04
3.20

Q. A 20 MVA, 3-φ Y-connected alt. with an impedance
of $5\ \Omega$ and a resistance of $0.5\ \Omega$ is operating in
parallel with const voltage 11 KV bus bars. If its field
current is adjusted to give an excitation voltage of
12 KV then Cal.

- 1) Max power o/p from the alt.
- 2) Amature current and pf under max power
condition

$$\text{P}_{\text{max}} = \frac{E_1 V}{X} = \frac{N \times 12}{5^2}$$

$$\begin{aligned} Z_s' &= R^2 + X_s^2 \\ X_s^2 &= Z_s^2 - R^2 \\ &> 5^2 - 0.5^2 \\ &= 24.75 \Omega \\ X_C &= 4.975 \Omega \end{aligned}$$

$$E_f = V + I_a Z_s$$

$$\theta_s = 84.26^\circ$$

$$\Rightarrow \frac{12000}{\sqrt{3}} \angle 8^\circ = \frac{11000}{\sqrt{3}} \angle 0^\circ + I_a I_a L - \cos \phi \times p \left[0.5 + j 4.975 \right]$$

$$8 = 90 - \theta_s$$

$$\Rightarrow \frac{12000}{\sqrt{3}} \angle 84.26^\circ = \frac{11000}{\sqrt{3}} \angle 0^\circ + I_a I_a L - \phi \times 5 \angle 84.26^\circ$$

$$\Rightarrow \left(\frac{12000}{\sqrt{3}} \right)^2 = \left(\frac{11000}{\sqrt{3}} \right)^2 + (5 I_a)^2$$

241

$$\Rightarrow I_a = 553.775 \text{ A}$$

$$\theta = \theta_s$$

$$I_a = \frac{\bar{E}_f - \bar{V}}{Z_s}$$

for max power

$$= \frac{\frac{12000}{\sqrt{3}} \angle 84.26^\circ - \frac{11000}{\sqrt{3}} \angle 0^\circ}{5 \angle 84.26^\circ}$$

$$= 1783.61 \angle 45.12^\circ$$

~~$$P_{max} = \frac{12000 \times 11000}{\sqrt{3} \times \sqrt{3}} - \left(\frac{11000}{\sqrt{3}} \right)^2 \cos 84.26^\circ$$~~


~~$$= 8 \times \sqrt{3} \text{ MW}$$~~

$$= \sqrt{3} V E \cos \phi$$

$$= \sqrt{3} \times 11 \times 10^3 \times 1783.6 \times 0.7056$$


$$= 23.978 \text{ MW}$$

check: P_{max} →

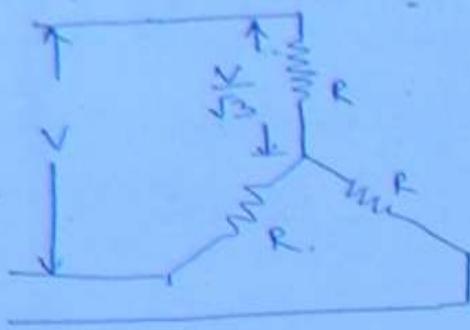

$$P_{1-\phi} = \frac{(V/\sqrt{3})^2}{R}$$
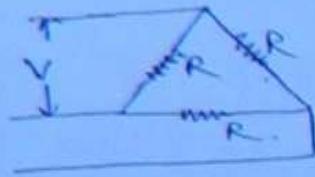
$$\begin{aligned} P_{3-\phi} &= 3 \times P_{1-\phi} \\ &= 3 \times \frac{V^2}{3R} \\ &= \frac{V^2}{R} \end{aligned}$$





$$P_{1-\phi} = \frac{V^2}{R}$$


$$P_{3-\phi} = 3 \times \frac{V^2}{R}$$

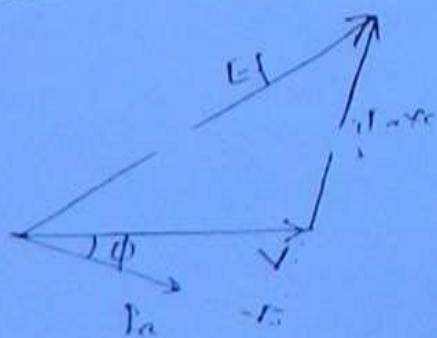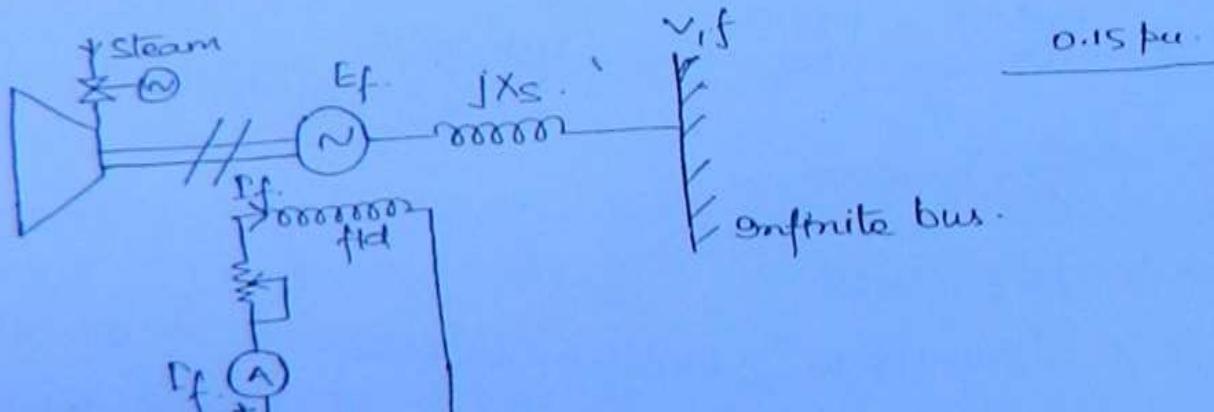(242)

Generator connected to infinite bus \rightarrow

$$\begin{aligned} Z_s &= 0 \\ I &= \text{infinite} \end{aligned}$$



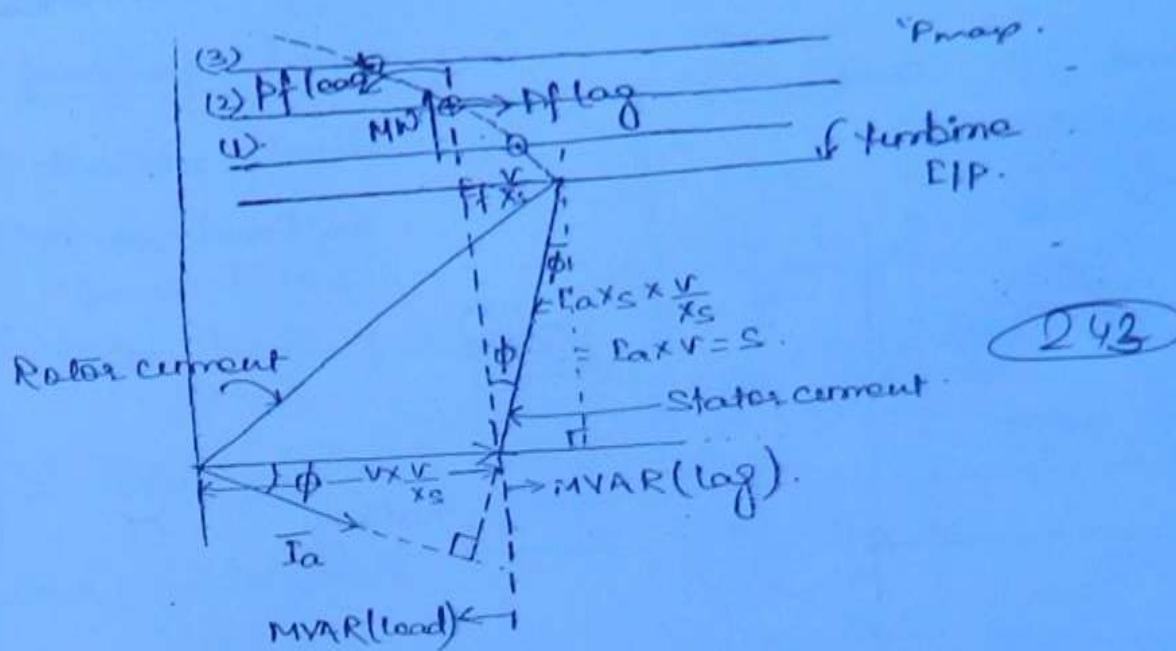

Initial operation :-

Lagging Pf →

(a) Prime mover i/p increases
Excitation is const.

i) MVAR (↓) → decreases.
Pf (↑) → improves, less lagging
Stator current → increase
power angle ↑ → increase

→ Prime mover I/P ↑, α m/c acc², δ ↑



2) Becomes 0 → MVAR.

Pf → unity

Stator current → increase


power angle → increase

3) MVAR → increases becomes leading
Pf → deteriorate but now on leading side.
Stator current → increases
 δ → inc.

Sept m/c → overexcited
generator → lagging Pf
motor → leading Pf

if in question if nothing
is given

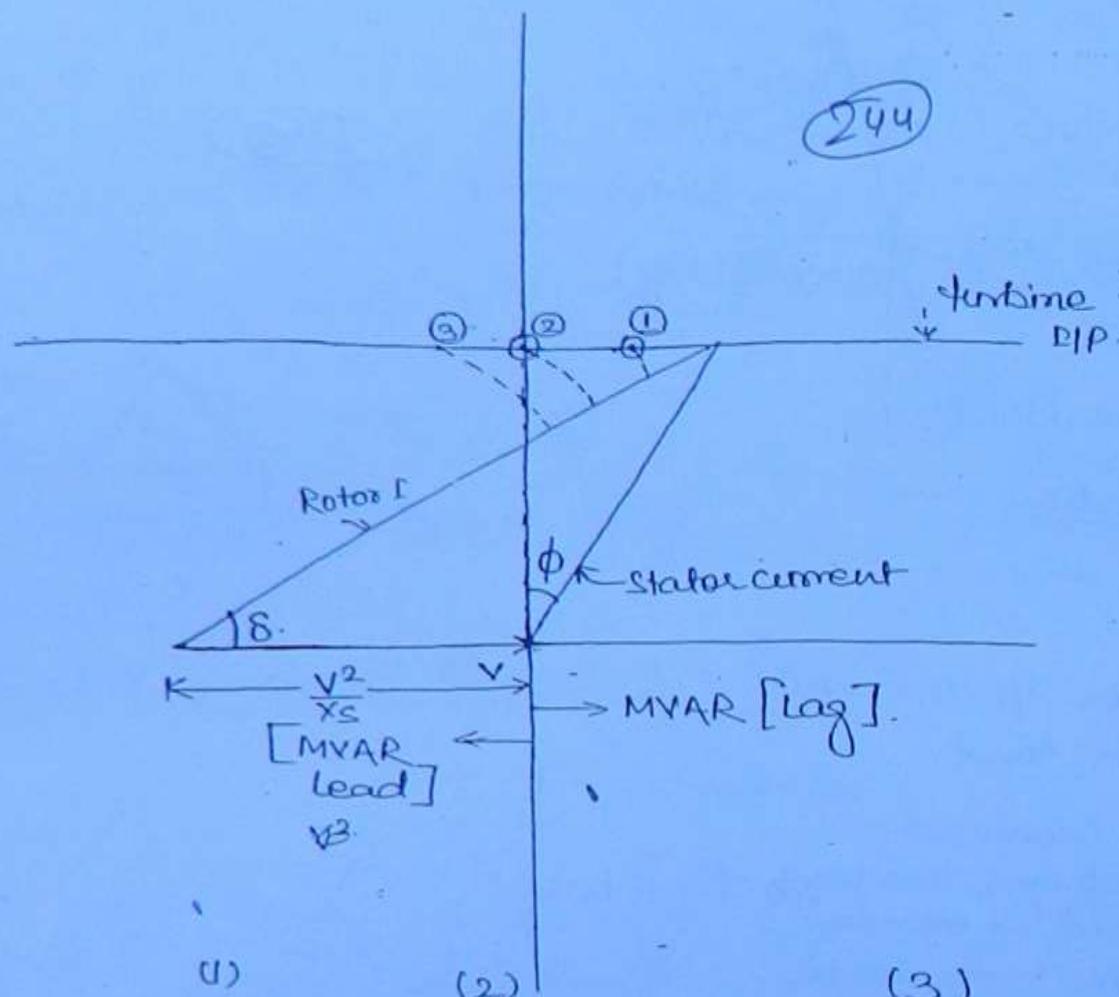⇒ Prime mover E/P const,
excitation varies.



MVAR : Decreases

Becomes 0

Pf : Improves

Becomes unity

Stator current : Decreases

Becomes mini

Power angle : Increases

Increases

(3)

Inc. but leading side
deteriorate on lead
side
increases again on
lead side

Increases

$$\delta = \frac{v}{X_s} [r_f n - \theta - v]$$

$$= \frac{V^2}{X_s} \text{ when either } S=0 \text{ or } \alpha_f = 0$$

\downarrow leading \rightarrow line charging capacity = $V^2 \times \text{scr}$

line charging capacity of hydro is more compared to

Operating limits :-

1) turbine limits.


2) stator heating limit. [SHL]

3) Rotor heating limit. [RHL]

4) Stability limit

The max limit of S

$$= 70 \text{ [in India]}$$

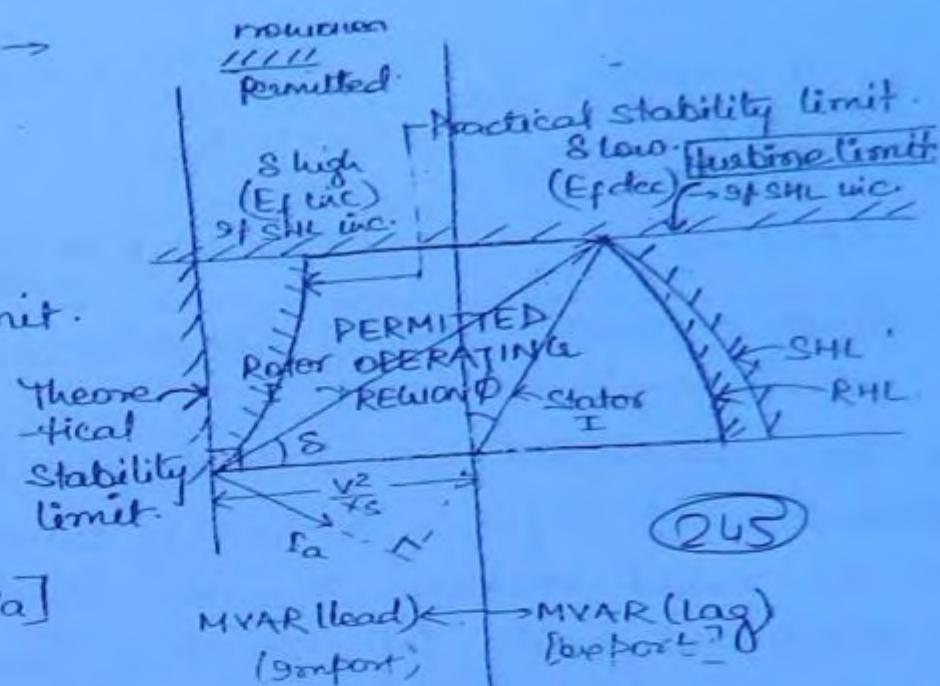

GENERATOR CAPABILITY CURVE
[At rated condition only].

5.98

5.14 An alternator with sym. reactance 0.18 pu is connected to an infinite bus at rated voltage. When its excitation emf adjusted to 1.3 pu , alt. delivers an o/p of 0.5 pu real power if not given neglect all losses.

i) determine S, Amature current in pu. and pf of the alternator.

ii) It is now made to operate at another value of E_f of which results in the same values of power o/p and current. Under these condition E_f, S and H.

$$\text{Ans (1)} P = \frac{1.3 \times 1}{0.8} \sin S$$

$$\Rightarrow 0.5 \times 0.8 = \sin S$$

$$\Rightarrow S = 17.32^\circ$$

$$(2) E_f P = \frac{1 \times 1}{0.8} \sin S, 1 \sin S = 0.8 \times 0.5 = 0.4$$

$$E_f = 0.5811 L - 50.64$$

$$\frac{1.3 / 8 = 1.60}{10.9} = I_a \text{ amp}$$

$$\frac{E_f L S - 120^\circ}{j 0.8} = \bar{I}_a$$

$$E_f L S - 90^\circ = 0.5811 [30.64 \times 0.8] + 120^\circ$$

$$E_f L S = 0.8615 [27.662]$$

A star connected 11 KV turbogenerator with syn. impedance of $(1+j10) \Omega/\phi$ is connected to infinite bus at rated voltage. The alt. delivers an I_a of 100 A. at unity pf. to the bus bar.

a) with the alt. o/p remaining const, alt. excitation is inc. by 15%. Find the new values of I_a , load angle and pf.

b) with the excitation of part A, discuss how alt. can made to operate at unity pf.

Under this condition, find I_a , load angle, power delivered to the bus.

Ans:

$$V = \frac{11000}{\sqrt{3}} L O^\circ$$

246

$$Z_s = (1+j10) \Omega/\phi$$

$$I_a = 100 L O^\circ$$

$$E_f = V + I_a Z_s$$

$$= 652 + 902 L O^\circ \cdot 0 i^\circ$$

$$E_f = 7507 \cdot 0873 L S^\circ$$

$$\frac{E_f - 7507 \cdot 0873 L S^\circ - \frac{11000}{\sqrt{3}} L O^\circ \phi}{(1+j10)} = I_a$$

$$P_{out} = \frac{V E_f \cdot \cos(\theta_s - \delta) - \frac{V^2}{Z_s} \cos \theta_s}{Z_s}$$

≈ 11000

$$Z_s = 10.0499 \angle 84.29^\circ$$

(247)

$$E_f \cos(\theta_s - \delta) = \text{const}$$

$$6527.902 \cos(84.29^\circ - \delta \cdot 812) = 7507.0873 \cos(84.29^\circ - \delta)$$

$$\Rightarrow \boxed{\delta = 6.884^\circ}$$

$$I_a = 141.57 \angle -45^\circ$$

$$\boxed{P_f = 0.707 \text{ lagging}}$$

(b) $E_{f2} = 7507.0873$

$$P_f = \text{unity}$$

$$\phi = 0^\circ$$

$$qf_{1+0.15}$$

But

$$7507.0873 \angle \delta = \frac{11000}{\sqrt{3}} \angle 0^\circ - I_a \angle 0^\circ 10.0499 \angle 84.29^\circ$$

$$\Rightarrow I_a \angle 0^\circ = \frac{7507.0873 \angle \delta - \frac{11000}{\sqrt{3}} \angle 0^\circ}{10.0499 \angle 84.29^\circ}$$

$$= -598.398 \angle 298^\circ$$

$$\delta = 3 - 84.29^\circ$$

$$\boxed{\delta = 84.29^\circ}$$

$$7507.07 / 85 \times (6350.85 + I_{a2}) + I_a \angle 10^\circ$$

$$\therefore (7507.07)^2 + (6350.85 + I_{a2})^2 + 100 I_{a2}^2$$

$$\therefore 100 I_{a2}^2 + 2 \times 6350.85 I_{a2} + \left[(6350.85)^2 + (7507.07)^2 \right] = 0$$

$$I_{A3} = 340.35 \text{ A}$$


$$\delta_3 = \tan^{-1} \frac{10 \times 340.35}{6350.85 + 310.35} \\ = 26.36^\circ$$

O/P power = $\sqrt{3} \times I_{A3} \cos \phi_3$

248

Synchronising power : →


Two identical m/cq on No-load : →

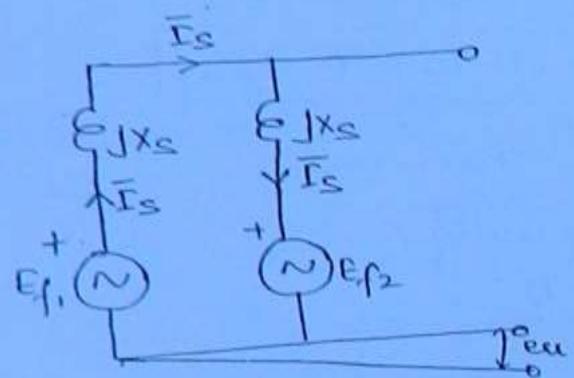

$$\bar{E}_f_1 = \bar{E}_f_2$$

Before disturbance.

After disturbance →

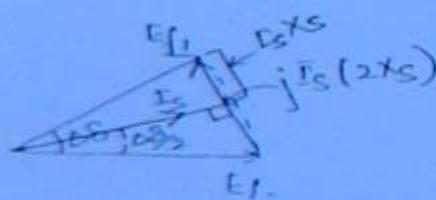

$I_s \rightarrow$ Synchronising current

$$\frac{\sin \Delta S}{2} = \frac{I_s X_s}{E_f} \Rightarrow I_s = \frac{E_f \sin \Delta S}{2 X_s}$$

$$|E_f_1'| = |E_f_2'| = |E_f|$$

Synchronising power $P_s = \Delta P = E_f I_s \cos \frac{\Delta S}{2}$

$$= E_f \left[\frac{E_f \sin(\Delta S)}{2 X_s} \right] \cos \frac{\Delta S}{2}$$

| |
|--|
| $P_s = \Delta P = \frac{E_f^2 \sin \Delta S}{2 X_s}$ |
|--|

$\sin \Delta\delta$ is very small,
 $[\sin \Delta\delta \approx \Delta\delta]$ in elec. rad.

$$\Rightarrow P_S = \Delta P = \frac{E_f^2 (\Delta\delta \text{ in rad})}{2X_S} \text{ watts.}$$


(249)

Synchronising power coefficient or stiffness coefficient,

$$Sp = \frac{P_S}{\Delta\delta} = \frac{\Delta P}{\Delta\delta} \text{ watts per elec. rad.}$$

$$Sp = \frac{E_f^2}{2X_S} \text{ watts per elec. rad.}$$


when X_S is replaced by R_a →

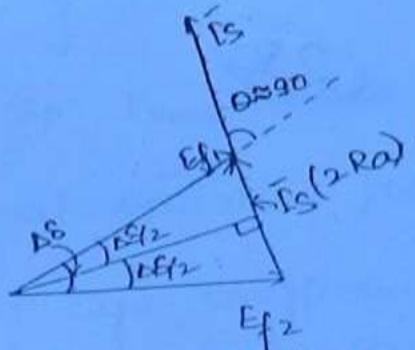

Synchronising power $= E_f, E_{f\text{const}}$
 \therefore mfc will never go to synchronous after the disturbance and synchronism is lost. So, Reactance is important for synchronism.


After the disturbance

MIC connected to infinite bus →

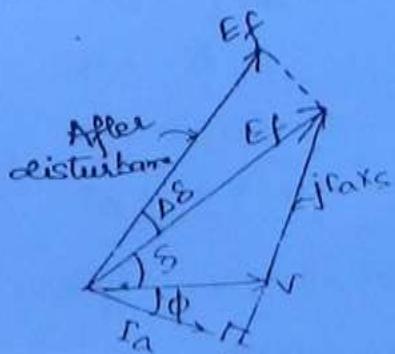

Before disturbance,

$$P = \frac{V E_f \sin \delta}{X_S}$$

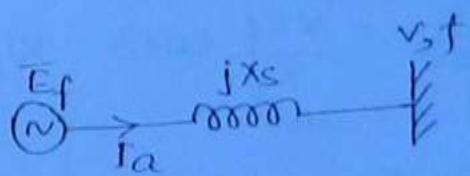

After the disturbance,

$$P_{IND} = \frac{V E_f \sin (\delta + \Delta\delta)}{X_S}$$

Synchronising Power = $\Delta P = (P + \Delta P) - (P)$

$$P_S = \frac{V_E f}{X_S} [\sin(\delta + \Delta\delta) - \sin \delta] \text{ watts}$$

$$= \frac{V_E f}{X_S} [\sin \delta \cos \Delta\delta + \sin \Delta\delta \cos \delta - \sin \delta]$$

$$= \frac{V_E f}{X_S} [\sin \Delta\delta \cos \delta - \sin \delta \{ 1 - \cos \Delta\delta \}]$$

$$= \frac{V_E f}{X_S} \left[\sin \Delta\delta \cos \delta - \sin \delta \times 2 \sin^2 \frac{\Delta\delta}{2} \right]$$

Since $\sin \frac{\Delta\delta}{2}$ is very small

(250)

$$\sin^2 \frac{\Delta\delta}{2} \approx 0$$

$$\therefore P_S = \Delta P = \frac{V_E f}{X_S} \cos \delta \sin \Delta\delta \text{ watts}$$

Since $\Delta\delta = \text{Small}$, $\sin \Delta\delta = \Delta\delta \text{ in elect. rad.}$


$$P_S = \frac{V_E f}{X_S} \cos \delta (\Delta\delta) \text{ watts.}$$

$$S_p = \frac{P_S}{\Delta\delta} = \frac{V_E f}{X_S} \cos \delta \text{ W/elect. rad.}$$

$$P = P_{max} \sin \delta$$

$$\frac{dP}{d\delta} = P_{max} \cos \delta$$

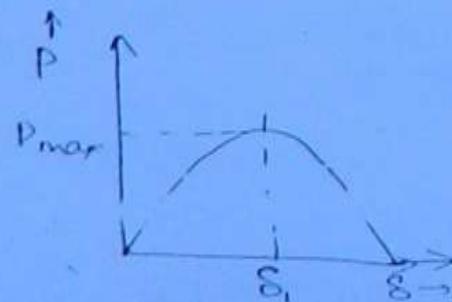↑
slope of power angle curve
at operating angle δ .



$$S_p = \frac{V_E f}{X_S} \cos \delta = P_{max} \cos \delta = \frac{dP}{d\delta} |_{\delta}$$


Linearised Analysis

$P = P_{max} \sin \delta$:
in the range

$$-30^\circ \leq \delta \leq 30^\circ$$

$\sin \delta \approx \delta$ in elect. rad.

$$P = P_{max} \times \delta$$

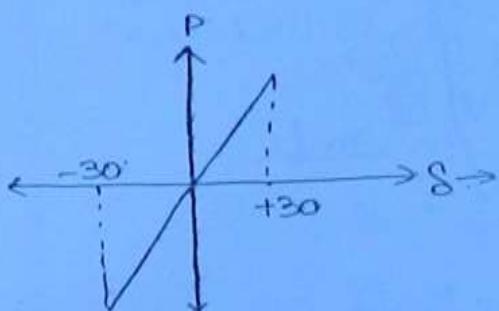


-30 to +30

$$\sin \delta \approx \delta$$

δ → electric rad.

(25)

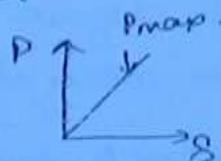

$$S_p = P_{max} \text{ in the range } -30^\circ \leq \delta \leq 30^\circ$$

⇒ Normal operating power angle is less than 30° .

Q. Cal. Sym. coefficient in kW and N-m per mech degree
at full load. for 50 Hz., 1000 KVA, 0.8 pf lag, 6.6 KV,
8 Pole Y-connected generator of negligible resistance
and sym. Reactance of 0.8 pu.

$$\text{Ans. } X_s = j 0.8$$

$$P = \delta$$

$$V = 110$$

$$I_a = 1 / -\cos^{-1} 0.8$$

$$E_f = V + I_a X_s$$

$$= 110 + 1 / -\cos^{-1} 0.8 \times j 0.8$$

$$= 1.6125 L 23.38^\circ$$

$$\theta_{elec} = \frac{\delta}{2} \text{ mech}$$

$$180^\circ - \theta_{elec}$$

$$23.38^\circ - \frac{\pi}{180}$$

$$\begin{aligned} S_p &= \frac{V E_f \cos \delta}{X_s} \Big|_{\delta=23.38^\circ} = \frac{1 \times 1.6125 \cos 23.38^\circ}{0.8} \\ &= 1.85013 \text{ Watt / elect. degree} \times \frac{1.6125 \times 2 \pi}{0.8} \\ &\approx 10.62 \text{ W / rev.} \end{aligned}$$

$$S_f = 1.847 \text{ pu per elect. rad.}$$

$$= 1847 \text{ kW per elect. degree.}$$

~~= 32.236~~

$$= 1847 \times \frac{\pi}{180} \text{ kW per elect. degree.}$$

$$= 32.236 \text{ kw per elect. degree}$$

$$= 32.236 \times \frac{P}{2} \text{ kW per mech degree}$$

$$= 32.236 \times \frac{8}{2} \text{ kW per mech degree}$$

$$= 128.94 \text{ kW per mech degree.} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{ } \begin{array}{l} 5 \text{ s/mm}^2 \\ e_{cu} \\ 1 \text{ kN/mm} \\ = 12 \text{ / km} \\ 1 \text{ rad} = 57.3^\circ \end{array}$$

ω_m &

$$\omega_e = 2\pi f$$

$$\omega_m = \frac{8\pi f}{2}$$

$$\omega_m = \frac{2}{P} \times 2\pi f$$

$$= \frac{2}{8} \times 2\pi f$$

$$= \frac{\pi f}{2}$$

(252)

$$\text{El Synchronising torque co-eff} = \frac{128.94 \times 10^3}{78.54} \text{ Nm per mech degree}$$



$$= 1640 \text{ Nm per mech degree}$$

Q A 4 pole Star connected 50 Hz, 11 KV, 40 MVA turbo generator with Sgn reactance 0.8 pu. is connected to a power net. This power net can be represented by 11KV in junc bus with series reactance of $j0.5 \Omega$. Voltage regulator adjust the fd current such that all terminal volt remains const at 11 KV. The gen deliver an pf of 0.8

1) draw the phasor diagram under the condition Specified above.

2) ~~Draw~~ Δ ϕ vs θ

$$|V_E| = |V_f| \quad (253)$$

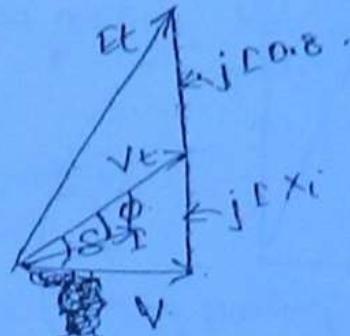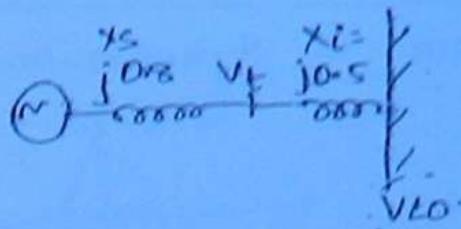

$$Z_b = \frac{11^2}{40}$$

$$= 3.025$$

$$X_t = \frac{0.5}{3.025}$$

$$= 0.1653j$$

$$\Delta \frac{\theta}{2} = \sin^{-1} \frac{1 \times X_t}{2V}$$

$$= \sin^{-1} \frac{1 \times 0.1653}{2 \times 1}$$

$$S = 9.482$$

$$\phi = \frac{\theta}{2} = 4.74 \text{ lag}$$

$$\text{Alternator Pf} = \cos 4.74 \text{ lag}$$

$$= 0.9966 \text{ lagging}$$

$$\bar{E}_f = \bar{V}_f + j E_a x_s$$

$$\bar{E}_f = 110 + j 1L - \cancel{4.74 \times 0.8}$$


$$= 1.3312 \angle 36.79^\circ$$

$$= 1.3312 \times 11 \text{ KV} [L-L]$$

$$= 14.643 \text{ KV} [L-L]$$

SYNCHRONOUS MOTOR

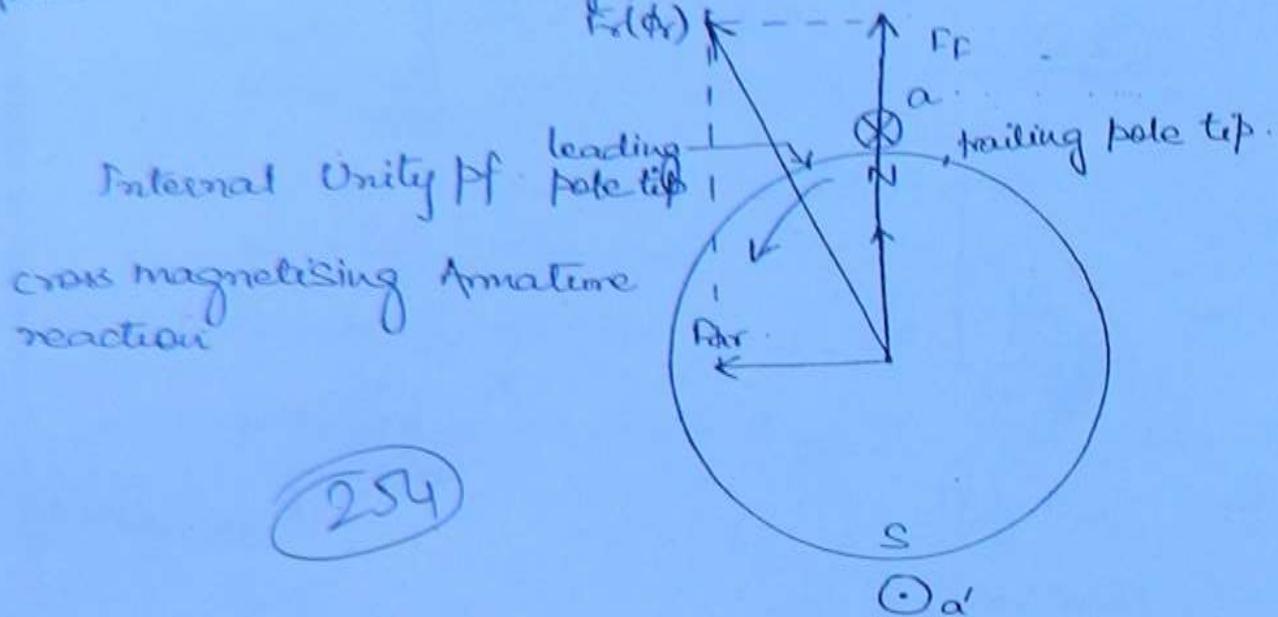
Armature Reaction in Synchronous motor :→



zpf lag →

Directly Do magnetising
Armature Reaction


$F_f < F_r$, under-excited
motor

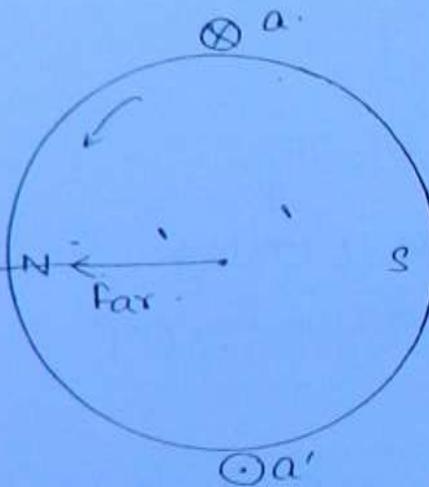


zpf lead →

Inverter driven zpf
Armature Reaction

$F_f > F_r$, over-excited
motor.

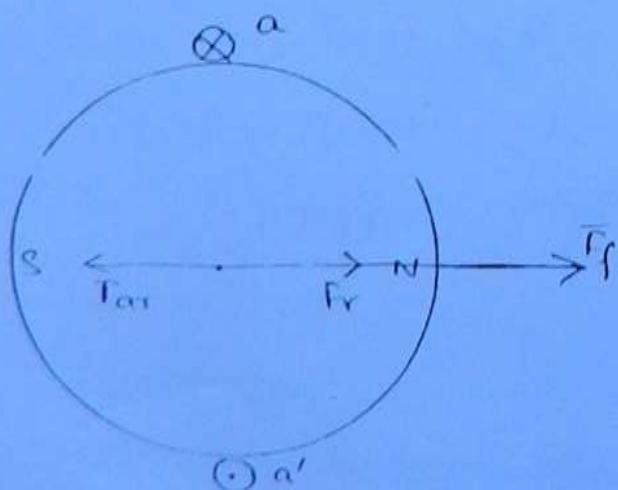


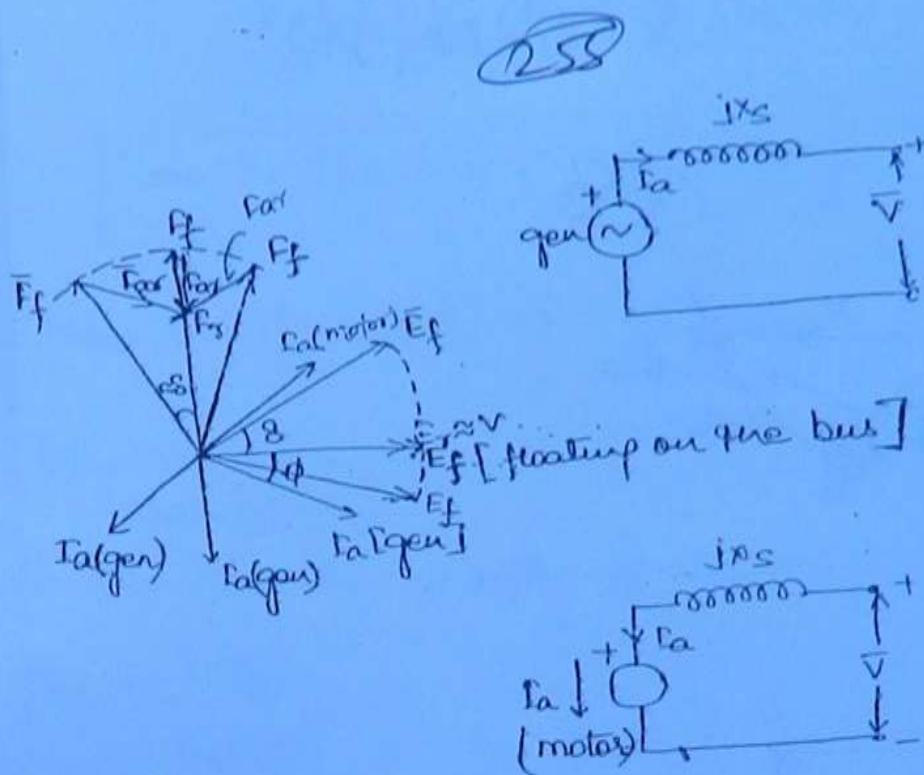Transition from generator action to motor action →





Overexcited →
(leading P_f)

$$\bar{V} = \bar{E}_f + j\bar{I}_a X_s$$

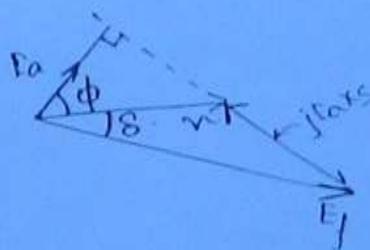

$R_a = 0$

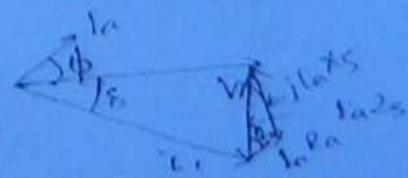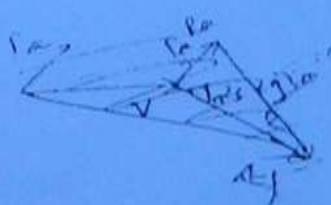


Under excited \rightarrow


$$V = E_f + R_a(R_a + jX_s)$$

$R_a \neq 0$,

(25b)

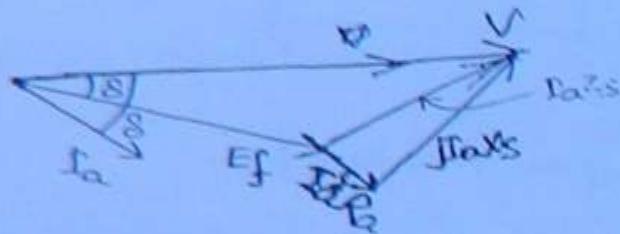

$R_a = 0$,

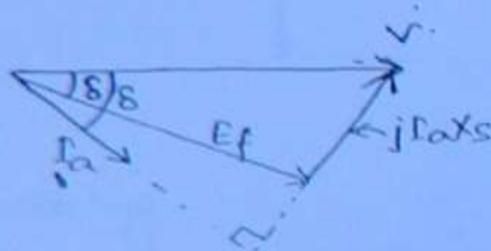

Power angle equation:

Here, $\bar{V} = V \angle 0^\circ$

$$\bar{E}_f = E_f \angle -\delta$$

$$\bar{Z}_s = Z_s \angle 0^\circ$$

$$\begin{aligned}\bar{I}_a &= \frac{\bar{V} - \bar{E}_f}{\bar{Z}_s} \\ &= \frac{1}{Z_s \angle 0^\circ}\end{aligned}$$

$$= \frac{V}{Z_s} \angle 0^\circ - \frac{E_f}{Z_s} \angle (\theta + \delta)$$

$$S_{dev} = \bar{E}_f \bar{I}_a$$

$$= -\bar{E}_f L \delta \left[\frac{V}{Z_s} \theta_s - \frac{\bar{E}_f}{Z_s} \theta_s + \delta \right]$$

(257)

$$\boxed{S_{dev} = \frac{V \bar{E}_f}{Z_s} \theta_s - \frac{\bar{E}_f^2}{Z_s} \theta_s}$$

$$P_{dev} = \frac{V \bar{E}_f}{Z_s} \cos(\theta_s - \delta) - \frac{\bar{E}_f^2}{Z_s} \cos \theta_s$$

$$P_{dev} = \max^m,$$

when $\boxed{\delta = \theta_s}$

& This decides stability of motor.

$$S_{in} = \bar{V} \bar{I}_a$$

$$= V L O' \left[\frac{V}{Z_s} \theta_s - \frac{\bar{E}_f}{Z_s} \theta_s + \delta \right]$$

$$\boxed{\bar{S}_{in} = \frac{V^2}{Z_s} \theta_s - \frac{V \bar{E}_f}{Z_s} \theta_s + \delta}$$


$$P_{in} = \frac{V^2}{Z_s} \cos \theta_s - \frac{V \bar{E}_f}{Z_s} \cos(\theta_s + \delta)$$

$P_{in} = \max$ when $\delta = 180 - \theta_s$ but by then stability is to

Neglecting R_a ,

$$Z_s = 0 \times s, \theta_s = 90^\circ$$
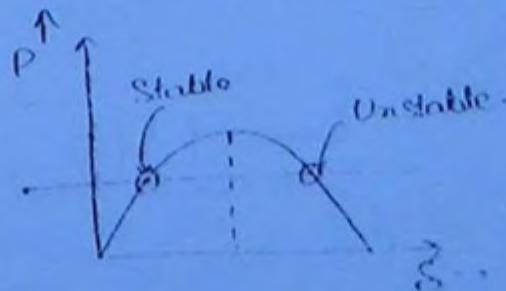
$$\boxed{P_{in} = P_{dev} = P \cdot \frac{\bar{E}_f V \sin \delta}{X_s}}$$



$$Q_{in} = \frac{V}{X_S} (V - E_f \cos \delta)$$

Case 1. $\rightarrow E_f \cos \delta = V$

(258)

Then $Q_{in} = 0$, operating at Unity Pf
normally excited

Case 2. $E_f \cos \delta < V$, Underexcited motor.

$Q_{in} = +ve$, ie taking lagging VARs.

& operating at lagging at lagging H


Case 3. $E_f \cos \delta > V$, overexcited motor.


$Q_{in} = -ve$, ie taking leading VARs.

& operating at leading Pf.

In other words, it is delivering lagging VARs.

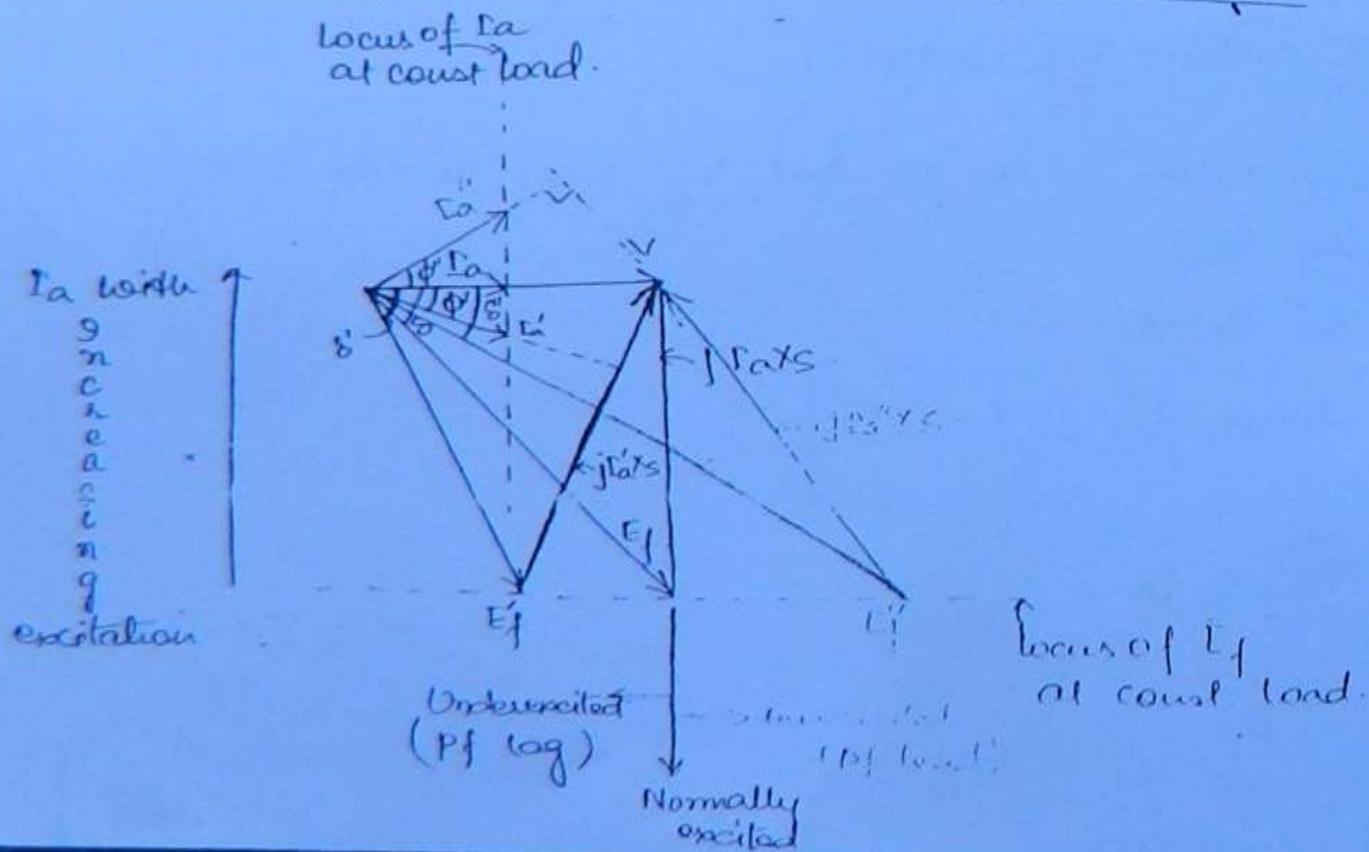
Effect of change in excitation at const (kW) load:-



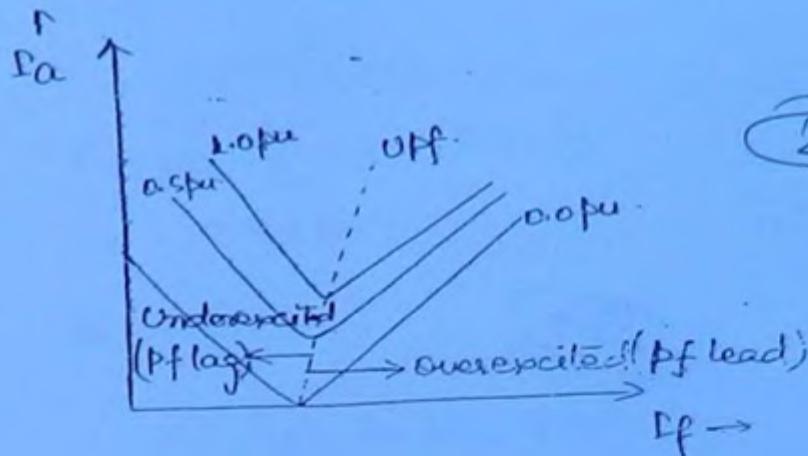

(259)

motor V curves

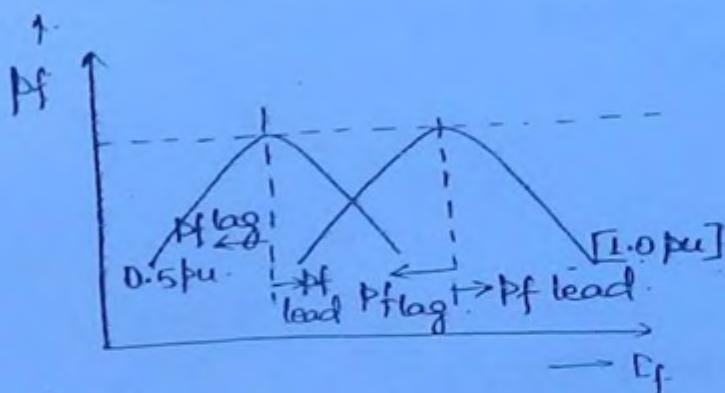

Inverted V curve.

Q. A 3- ϕ star-Y load takes ~~50 A~~^{in 1} at 0.707 lagging P_f with 220 V b/w the lines. A 3- ϕ Y connected round rotor syn. motor having syn. reactance of 1.2732/ ϕ is connected in parallel with the load. Power developed by motor 33 kW at a power angle of 30°. Cal. reactive power of the motor and overall P_f of motor and the load.

L.H.S. $X_S = 1.2732/\phi$

$V = 220 \text{ V}$

P_{dev} = 33 kW

S = 30°

Q_{in} = $\frac{220}{\sqrt{3} \times 1.21} \left(\frac{220}{\sqrt{3}} - 1 \right) \cos 30^\circ$
 $= 45.97.37 = 45.9737 \text{ kVAR}$

~~$P_f = \frac{V^2 S \cos \theta}{X_S}$~~ $\frac{220 \times 1000 \times 30}{1.2732} \times \frac{\cos 30^\circ}{\sqrt{3}}$
 $\times 1.2732$

~~$P_f = \frac{V^2 S \sin \theta}{X_S}$~~ $\frac{220 \times 1000 \times 30}{1.2732} \times \frac{\sin 30^\circ}{\sqrt{3}}$
 $\times 1.2732$

Motor,

$$P = \frac{V E_f \sin \delta}{X}$$

$$\Rightarrow 33 \times 10^3 = \frac{220 \times E_f \sin 30}{1.27}$$

$$\Rightarrow 33 \times 10^3$$

$$\Rightarrow E_f = 381 \text{ volts (L-L.)}$$

260

$$Q_{in} = \frac{V}{X_s} (V - E_f \cos \delta)$$

$$= \frac{220}{1.27} (220 - 381 \cos 30)$$

$$Q_{in} = -19.047 \text{ kVAR.}$$

$$S_{motor} = (33 - j 19.047) \text{ kVA}$$

$$S_{load} = \sqrt{3} \times 220 \times 50 \angle \cos^{-1}(0.707) \text{ VA}$$

$$= 19.053 L45$$

$$S_{total} = S_{motor} + S_{load}$$

$$= 46.806 L - 6.84 \text{ kVA}$$

$$\begin{aligned} \text{Overall pf} &= \cos 6.84^\circ \text{ leading.} \\ &= 0.9929 \text{ leading.} \end{aligned}$$

Q: A 230 V, 4 pole, 50 Hz Y connected syn. motor has $(R_a + j X_s) = (0.6 + j 3) \Omega / \text{phase}$. Its field I_f is so adjusted that the motor draws 60 A at unity pf at rated volt. source. Now with the field current unchanged, the load of the motor is increased till it draws 40 A from the supply.

Find torque developed and now pf.

A.m. P=4

$$V = \frac{230}{\sqrt{3}} V \cdot [L-N]$$

$$R_a + jX_S = (0.6 + j3) \Omega / \phi$$

(Q61)

$$I_a = 10 A \angle 0^\circ$$

$$I_{a_2} = 40 \angle -\phi$$

$$V = E_f + I_a (R_a + jX_S)$$

$$\Rightarrow E_f = V - I_a (R_a + jX_S)$$
$$= 130.29 \angle -13.312^\circ [L-N]$$

$$\therefore \bar{E}_f = \bar{I}_a = \frac{V - E_f}{R_a + jX_S}$$

=

$$40 \angle -\phi = \frac{\frac{230}{\sqrt{3}} \angle 0^\circ - 130.29 \angle -8^\circ}{(0.6 + 3j)}$$

$$\Rightarrow \frac{230}{\sqrt{3}} \angle 0^\circ = 130.29 \angle -8^\circ + 40 \angle -\phi (0.6 + 3j)$$
$$= 130.29 (\cos -8^\circ - j \sin -8^\circ) + 40 (\cos \phi - j \sin \phi) (0.6 + 3j)$$

$$\Rightarrow \left(\frac{230}{\sqrt{3}}\right)^2 = 130.29 \cos 8^\circ +$$

when load is increased,

$$V = \frac{230}{\sqrt{3}} \angle 0^\circ \Rightarrow \bar{I}_a = 140 \angle -\phi \therefore mfc \text{ would become different}$$

$$130.29 \angle -\delta_2 = \frac{230}{\sqrt{3}} \angle 0^\circ - 40 \angle -\phi \times 3.06 / 78.69$$

$$= 132.79 - 122.41 / 78.69 \angle -\phi$$

$$= 132.79 - 122.41 \cos(78.69^\circ - \phi) - j 122.41 \sin(78.69^\circ - \phi)$$

$$\Rightarrow (130.29)^2 = [132.79 - 122.41 \cos(78.69^\circ - \phi)]^2 + [122.41 \sin(78.69^\circ - \phi)]^2$$

$$\Rightarrow (132.29)^2 = 132.79^2 + 122.4^2 - 2 \times 132.79 \times 122.4 \cos(78.69^\circ - \phi)$$

$\therefore \phi = 17.45^\circ$ lagging
 $= 0.954$ lagging.

(262)

$$\begin{aligned} P_{dev} &= P_{in} - 3I_a^2R_a \\ &= \sqrt{3}V_1 I \cos\phi - 3I_a^2R_a \\ &= \sqrt{3} \times 230 \times 40 \times 0.954 - 3 \times (10)^2 \times 0.6 \\ &= 12321.86 \text{ W} \end{aligned}$$

Torque developed : $\frac{P_{dev}}{W_{sm}}$

$$= \frac{12321.86}{\frac{2}{P} \times 2\pi f}$$


$$= 78.44 \text{ N-m}$$

Q) A 2000 V, 3 ϕ Y connected cylindrical rotor sym. motor with syn reactance $X_{sm} = 2 \Omega$ is connected to a同步 generator $X_{sg} = 3 \Omega$ through trans-line of reactance $X_{TR} = 1.5 \Omega$. Sym. motor is drawing 100 A at rated terminal Volt and at unity pf at its terminals.

- compute the alt and motor excitation volt.
- find the power transfer b/w Alt and motor
- With the excitation fed as obtained in part find the power transfer b/w the two m/c. Also find the I_a , V_1 if the motor and its pf under these condition.

$$\mathbf{I}_{ab} = 100\text{A} \angle 0^\circ$$


(263)

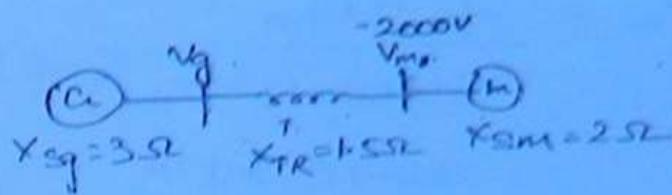

$$\begin{aligned}\mathbf{E}_{fm} &= V_m - j \mathbf{I}_{ab} X_{sm} \\ &= \frac{2000}{\sqrt{3}} - j 100 \angle 0^\circ \times 2 \\ &= 1171.89 \angle -9.826^\circ \text{ [L-N]}\end{aligned}$$

$$\begin{aligned}\mathbf{V}_g &= V_m + \mathbf{I}_{ab} j X_{tr} \\ &= 1164.4035 \angle 7.4015^\circ\end{aligned}$$
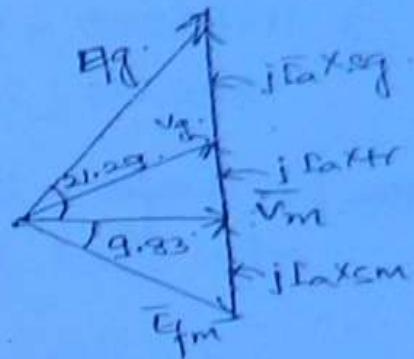
$$\begin{aligned}\mathbf{E}_{fg} &= \mathbf{V}_g + j \mathbf{I}_{ab} X_{sg} \\ &= 1239.287 \angle 21.29^\circ \rightarrow \text{forgen.} \\ &\quad [\text{L-N}]\end{aligned}$$



$$(b) \text{ motor input } P = \frac{V_m E_f \sin 9.826^\circ}{X_{sm}} \quad [\text{L-L}]$$

$$= 346.394 \text{ kW}$$

$$\begin{aligned}\text{Total } S_{gm} &= 21.29 + 9.83^\circ \\ &= 31.12^\circ\end{aligned}$$


$$\begin{aligned}\text{Power transfer} &= 3 \times 1239.287 \times 1171.89 \sin 31.12^\circ \\ &= 346.43 \text{ kW}\end{aligned}$$

$$(c) \mathbf{E}_{fm} = 1171.89 \angle -8^\circ$$

$$\mathbf{E}_{fg} = 1239.287 \angle 8^\circ$$

$$\text{Hence } \mathbf{E}_{fm} = 1171.89 \angle 0^\circ \text{ [L-N]}$$
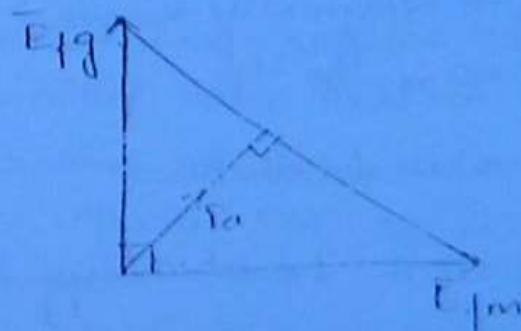
$$\mathbf{E}_{fg} = 1239.287 \angle 30^\circ \text{ [L-N]}$$



$$\begin{aligned}P_{max} &= 3 \frac{\mathbf{E}_{fm} \times \mathbf{E}_{fg}}{X_{sm} + X_{tr} + X_{sg}} \times \sin 30^\circ = 670.19 \text{ kW}\end{aligned}$$

$$\bar{I}_a = \frac{\bar{E}_{fq} - \bar{E}_{fm}}{j(x_{sm} + x_{tr} + x_{sq})}$$

$$= 262.4 \angle 43.4^\circ A$$

(264)

$$V_m = E_{fm} + j I_a x_{sm}$$

$$= 1171.89 \angle 0^\circ + j 262.4 \angle 43.4^\circ \times 2$$

$$= 896.44 \angle 25.17^\circ (L-N)$$


motor pf angle = $18.23^\circ = 43.4^\circ - 25.17^\circ$

Pf. = 0.9498 leading.

Synchronous condenser :— [Rotating VAR compensator
or Synchronous compensator.]

Synchronous capacitor

Synchronous phase Advancee

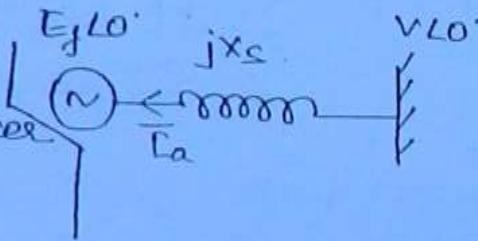

$$Q_{in} = \frac{V}{x_s} (V - E_f \cos \theta)$$

$$= \frac{V}{x_s} (V - E_f)$$

1) $E_f = V \rightarrow$ Normally excited
 $I = 0, Q_{in} = 0$

2) $E_f < V \rightarrow$ Under excited

$Q_{in} = +ve$ i.e. absorbing lagging VARs.


3) $E_f > V \rightarrow$ over excited

$Q_{in} = -ve$ i.e. absorbing leading VARs.

Normally excited →


$$I_a = 0, \quad E_f = V, \quad P_f \rightarrow \text{undefined}.$$

Under excited →

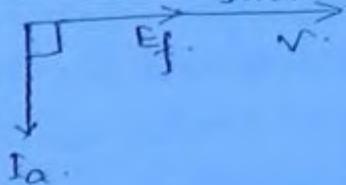


(265)

Over excited →

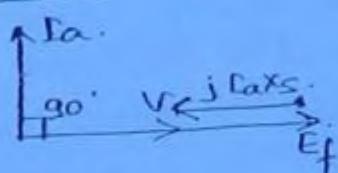

Always on no load.

14/12/11
Starting of Syn. motor :-

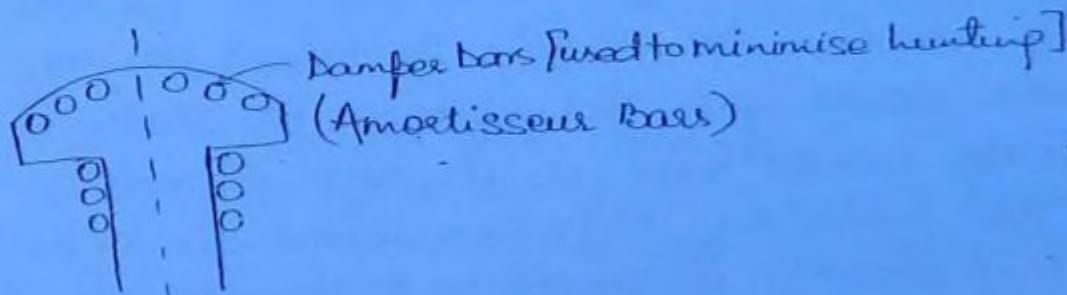

- Syn. motor is not self starting because the rotor M-fld created by the stator wdg at rated freq. rotates at rated syn. speed and an excited rotor that is initially stationary is not able to overcome its inertia and follow the revolving fld. Therefore special arrangement to be made for starting syn. motor.

- One method is auxiliary motor starting where an induction motor or a dc motor is mechanically coupled to rotor of syn. motor. For starting by auxiliary ind. motor, the no. of poles of the ind. motor should be equal to the no. of

poles of syn. motor. However if the no. of poles of syn. motor is large then no. of poles of the ind. motor may be 2 less such that running speed of the induction motor with its operating slip approaches the syn. speed of syn. motor. The induction motor is switched on while its stator wdg and the rotor wdg of syn. motor are unexcited. An excited rotor would make synchronisation necessary while an excited stator with stationary rotor would cause motor overheating an overvoltage in fd wdg during start. Then speed of the shaft correspond to normal value which is near syn. speed, the supply to stator wdg of the syn. motor is switched on. The phase seq. of the supply must be such that the revolving stator fd is in the belt of the rotating shaft. At normal speed, the diff. in the speed of the revolving fd and that of the rotor is very small and therefore excitation to the fd wdg of syn. motor can now be safely switched on. The syn. motor poles would get locked with its stator fd and the motor would run at its syn. speed as a syn. motor. The auxiliary induction motor can now be switched off and if possible it should be preferably be decoupled from the shaft.

(266)

For starting by auxiliary dc motor, the recommended practice is to synchronise the syn. m/c to the supply as a syn. generator, after satisfying all conditions required for synchronisation. This would be possible however the type of suitable dc motor can be varied as per requirement. However if this is not possible then the same procedure has to be followed as with ind. motor starting.

Auxiliary motor starting is obviously starters suited for no load start or low otherwise auxiliary motor rating required would have to be n. $n_{aux} = n_{ind}$

and there is economy in cost. In such cases either damper wdg starting or variable freq. starting may be adopted.


(267)

In damper wdg starting, the supply to syn. motor is switched on at reduced voltage as the damper bars behave like the squirrel cage induction motor. The motor therefore starts as an induction motor on load according to standard starting procedure for induction motor starting. With full voltage applied, when speed reaches its normal value that is slightly less than the syn. speed under this condition, excitation to the fd wdg of syn. motor is switched on. The rotor gets magnetically locked with the revolving stator fd and the motor continues to run at syn. speed as a syn. motor. Such motors are called Synodic-on motor at syn. speed, current in the damper wdg become zero. But if there is any departure from syn. speed during operation, damper wdg restores syn speed quickly and thereby prevents oscillation around the operating points, a phenomenon known as hunting.


It is recommended that the ^{before} shorting on the stator supply, fd wdg may be connected across a resistor having a resistance that is 7 to 10 times the fd resistance. This would prevent damage to the fd wdg insulation due to high induced voltage in the fd wdg at start and would also help in quick acee of the rotor due to induced current in the fd wdg. If the resistor is unavailable, fd wdg should be short circuited and start.

Another method for on load start is called variable freq. starting. Advances in power electronics have provided economically viable variable freq. ^{new} supply which can be used to start the syn. motor on load. Initially the freq. of supply is kept too low keeping ($\frac{V}{f}$) ratio const to avoid over fluxing of stator core. The fd wdg is then excited and the excited motor catches up with the slowly revolving stator fd. Once magnetic locking of rotor

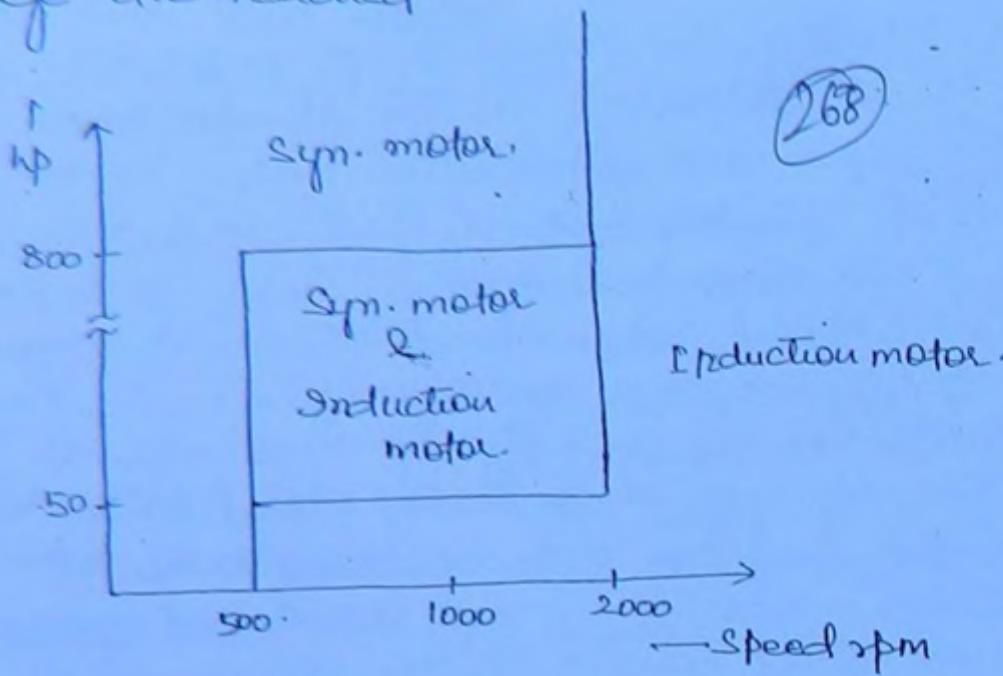
has taken place, supply freq. is gradually inc.
Keeping (f) ratio const until rated freq. and rated voltage are reached.



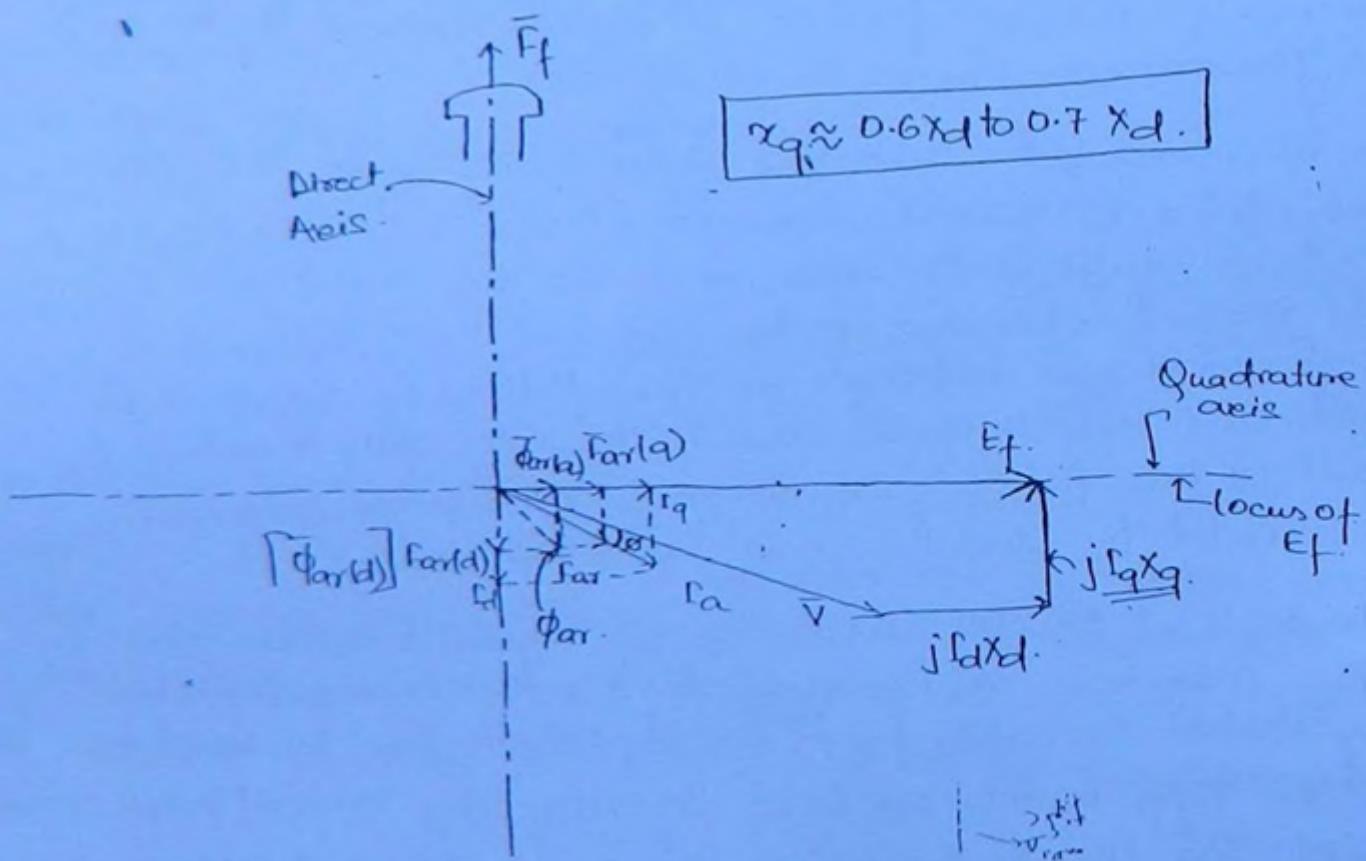Salient pole m/c: → [BLONDEL'S TWO REACTION THEORY]



overexcited gen [lagging pf].

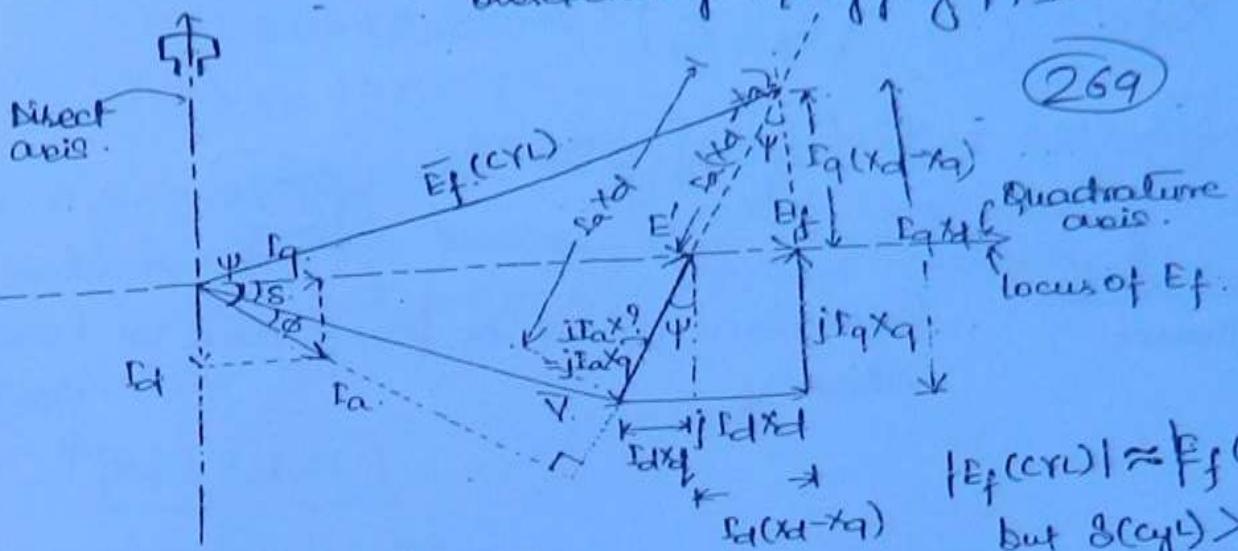

(269)

Quadrature
axis.
locus of E_f .

$$|E_f(CYL)| \approx |E_f^{(cal)}| \\ \text{but } \delta(\text{cal}) > \delta(\text{act})$$

Locating the quadrature axis:

$$I_a X_q = I_a X_d \times \cos\psi.$$

$$\Rightarrow I_a \cos\psi \times q = I_a X_d \times \cos\psi.$$


$$\Rightarrow q = X_d$$

$$I_a X_q \sin\psi \\ = I_a X_d$$

$$X_s = X_d$$

$$E' = V + j I_a X_q$$

$$|E_f| = |E'| + |I_a(X_d - X_q)|$$

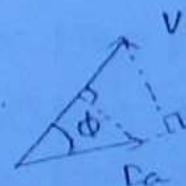

$$P = V I_a \cos\phi$$

$$\begin{aligned} P &= V I_a \cos\phi \\ &= V I_a \cos(\psi - \delta) \\ &= V I_a [\cos\psi \cos\delta + \sin\psi \sin\delta] \\ &= V \cos\delta [I_a \cos\psi] ; V \equiv \text{Supply} \end{aligned}$$

$$\text{Power O/P} = P = V \cos\delta E_q + V \sin\delta I_d$$


$$= \frac{V \cos\delta}{X_q} E_q X_q + \frac{V \sin\delta}{X_d} I_d X_d$$

$$= \frac{V \cos\delta}{X_q} V \sin\delta + \frac{V \sin\delta}{X_d} \{ E_f - V \cos\delta \}$$

$$= \frac{V_{Ef} \sin \theta}{X_d} + V^2 \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \times \sin \theta \cos \theta.$$

$$P = \frac{V_{Ef} \sin \theta}{X_d} + \frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\theta. \quad (29)$$

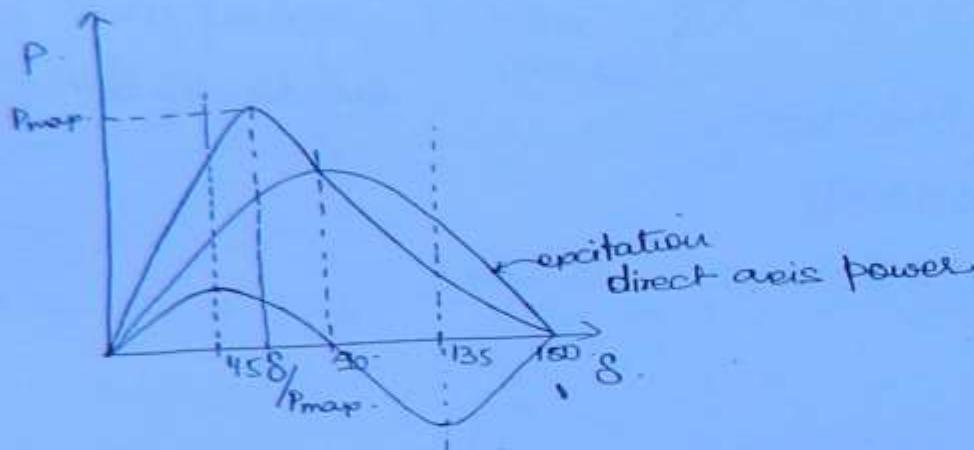↓
Excitation power Reluctance power or power due to Saliency.



The reactances X_d and X_q of salient pole syn. gen. are 1 pu and 0.6 pu. respectively. Amature resistance is negligible. Compute the E_f and θ when gen. delivers rated VA at 0.8 pf lagging current and rated terminal volt.

$$\begin{aligned} E_f' &= V + j I_a X_q \\ &= 110 + j X_1 \angle -\cos^{-1} 0.8 \times 0.6 \\ &= 110 + j 13.67 \\ \therefore I_a' &= \frac{110 + j 13.67}{1.4422 \angle 19.44 \text{ pu} - E_f'} \end{aligned}$$

$|E_f'| = 115.2315 \text{ A}$ $\theta = 19.44^\circ$

$$I_d = I_a \sin \theta$$

$$\begin{aligned} &= 1.0816 (0.687 + j 0.44) \\ &= 0.8211 \text{ pu} \end{aligned}$$

$$E_f = E' + I_d (x_d - x_q)$$

$$= 1.4422 + 0.8321 (1.0 - 0.6)$$

$$= 1.7750 \text{ pu.}$$

(21)

- (b) Cal. excitation volt. and power angle neglecting saliency for the same operating condition as in part a. Also find map off neglect saliency for excitation cal.

Ans * $x_s = x_d = 1$

$$E_f = V + j I_a x_d$$

$$(Cyl) = [1.0 + j 1.0 - \cos^{-1} 0.8 \times 1]$$

$$= 1.7888 \angle 26.56^\circ$$

$$P_{map} = \frac{1.7888 \times 1}{1} = 1.788 \text{ pu. }] S=90^\circ$$

- c) Cal. map power O/P of salient pole gen with the excitation at part (a).

$$\frac{dP}{dS} = 0$$

$$\Rightarrow \frac{x_d}{x_d} E_f \cos S + \frac{V^2}{2} \left(\frac{1}{x_q} - \frac{1}{x_d} \right) 2 \cos S = 0$$

$$\Rightarrow -\cos S \left[\frac{E_f}{x_d} + \frac{V}{x_d} - \frac{V}{x_d} \right] = 0$$

$$\Rightarrow 1.775 \cancel{1.4422} \cos S + 1 \left(\frac{1}{0.6} - 1 \right) \cos S = 0$$

$$\Rightarrow 1.4422 \cos S - 0.667 \cancel{\left(\cos^2 S - 1 \right)} = 0$$

$$\Rightarrow 1.775 \cos S + 0.667 \cos^2 S = 0$$

$$\Rightarrow 1.775 \cos S + 0.667 (\cos^2 S - 1) = 0$$

$$\Rightarrow 1.333 \cos^2 S + 1.775 \cos S - 0.667 = 0$$

$$\begin{aligned}
 P_{\text{max}} &= 1.775 \sin 72.21^\circ + \frac{1}{3} \sin(2 \times 72.21) - \\
 &\Rightarrow 1.6901 + 0.1939 \\
 &= 1.884.
 \end{aligned}$$

272

d) Cal. min excitation emf for the O/P Kw of part a.

$$P_a = 0.8 \text{ kW}$$

$$P = \frac{V E_f \sin \delta}{X_d} + \frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\delta.$$

$$0.8 = \frac{1 \times E_f \sin \delta}{1} + \frac{1}{2} \left(\frac{1}{0.6} - \frac{1}{1} \right) \sin 2\delta.$$

$$\therefore 0.8 - 0.3333 \sin 2\delta = E_f \sin \delta.$$

$$\begin{aligned}
 \frac{dE_f}{d\delta} &= \frac{\sin \delta}{1} \left[-2 \times 0.333 \cos 2\delta \right] - \frac{0.8 - 0.3333 \sin 2\delta}{\cos \delta} \\
 &\stackrel{d\delta = 0}{=} -2 \times 0.333 \cos 2\delta \sin \delta - [0.8 + 0.333 \sin 2\delta] \cos \delta = 0 \\
 &\therefore -0.666 \cos 2\delta \sin \delta - [0.8 + 0.333 \sin 2\delta] \cos \delta = 0.
 \end{aligned}$$

$$\Rightarrow E_f = 0.8 \csc \delta - 0.667 \cos \delta.$$

$$\frac{dE_f}{d\delta} = 0.8 (-\csc \delta \cot \delta) + 0.667 \sin \delta = 0$$

$$\therefore \Rightarrow 0.8 \csc \delta \cot \delta = 0.667 \sin \delta$$

$$\Rightarrow \frac{\csc \delta \cot \delta}{\sin \delta} = \frac{0.667}{0.8333}$$

$$\Rightarrow \cot^3 \delta + \cot^2 \delta - \frac{0.667}{0.8333} = 0$$

$$\delta = 0.6082$$

$$S = 58.69 \text{ MVA}$$

$$E_f = 0.8 \cos \delta - 0.6667 \sin \delta \\ = 0.59 \text{ pu}$$

(273)

- (e) Determine the max power off of salient pole generator when it loses excitation while still connected to infinite bus. What is the corresponding current and Pf.

$$\frac{E_f = 0}{P = \frac{V E_f}{X_d} \sin \delta + \frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\delta} \\ = 0 + \frac{1}{3} \\ = \frac{1}{3}$$

$$\sin 2\delta = 1$$

$$\delta = 45^\circ$$

$$E_q X_q = V \sin \delta \\ E_q = \frac{1.0 \times \sin 45}{0.6} \\ = 1.1785 \text{ pu}$$



$$E_d X_d = V \cos \delta \\ \Rightarrow E_d = \frac{1.0 \cos 45}{1.0} \\ = 0.7071$$

$$\psi = \tan^{-1} \frac{E_d}{E_q} \\ = 30.96^\circ$$

$$\phi = \psi + \delta \\ = 30.96 + 45^\circ \\ = 75.96^\circ \text{ leading}$$

$$P_f = 0.2426 \text{ leading}$$
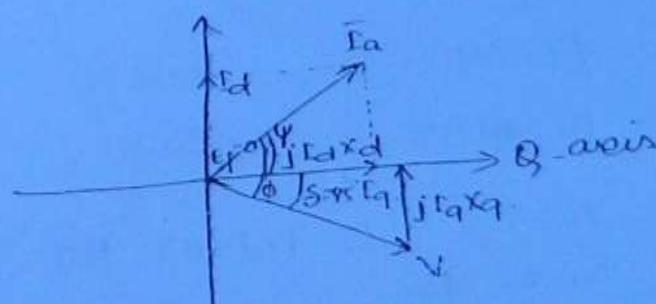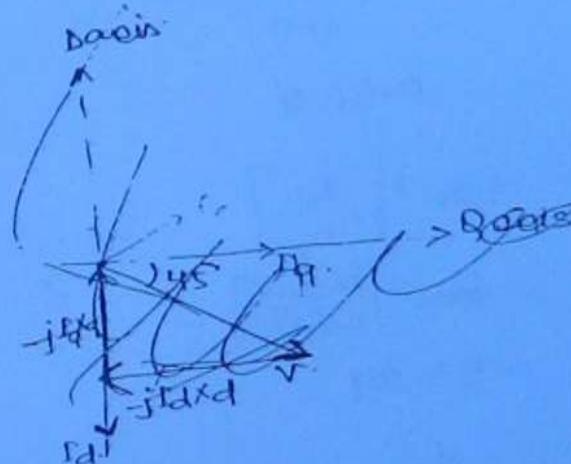
$$I_a = \frac{P_f}{\sin \phi} \propto \frac{1.0}{0.7071} \propto \sqrt{\frac{1}{d^2} + \frac{1}{q^2}} \propto \frac{0.2333}{1.0 \times 0.2426} \approx 1.3746$$



1) Cal. power angle, δ_a , and Pf . When gen. delivers 0.25 pu with its excitation reduced to 8 but still connected to infinite bus at rated volt.

Ans.

P

$$0.25 = \frac{1}{2} \left[\frac{1}{0.6} - \frac{1}{1} \right] \sin 2\delta.$$

$$\Rightarrow 0.5 =$$

$$\Rightarrow \delta = 24.3$$

(274)

$$\Rightarrow E_q = \frac{1.0 \times \sin 24.3}{0.6} = 0.6859.$$

$$\Rightarrow E_d = \frac{1 \times \cos 24.3}{1.0} \\ = 0.9114.$$

$$\Psi = \tan^{-1} \left[\frac{E_d}{E_q} \right] \\ = \tan^{-1} \left[\frac{0.9114}{0.6859} \right] \\ = 53.04.$$


$$\Psi + \delta = \phi$$

$$\phi = 77.34$$

$$\text{Pf} = 0.2192 \quad \text{leading}$$


$$I_a = \frac{0.25}{1.0 \times 0.2192} \approx 1.1407 \text{ pu.}$$

Overexcited sym. motor [leading pf]

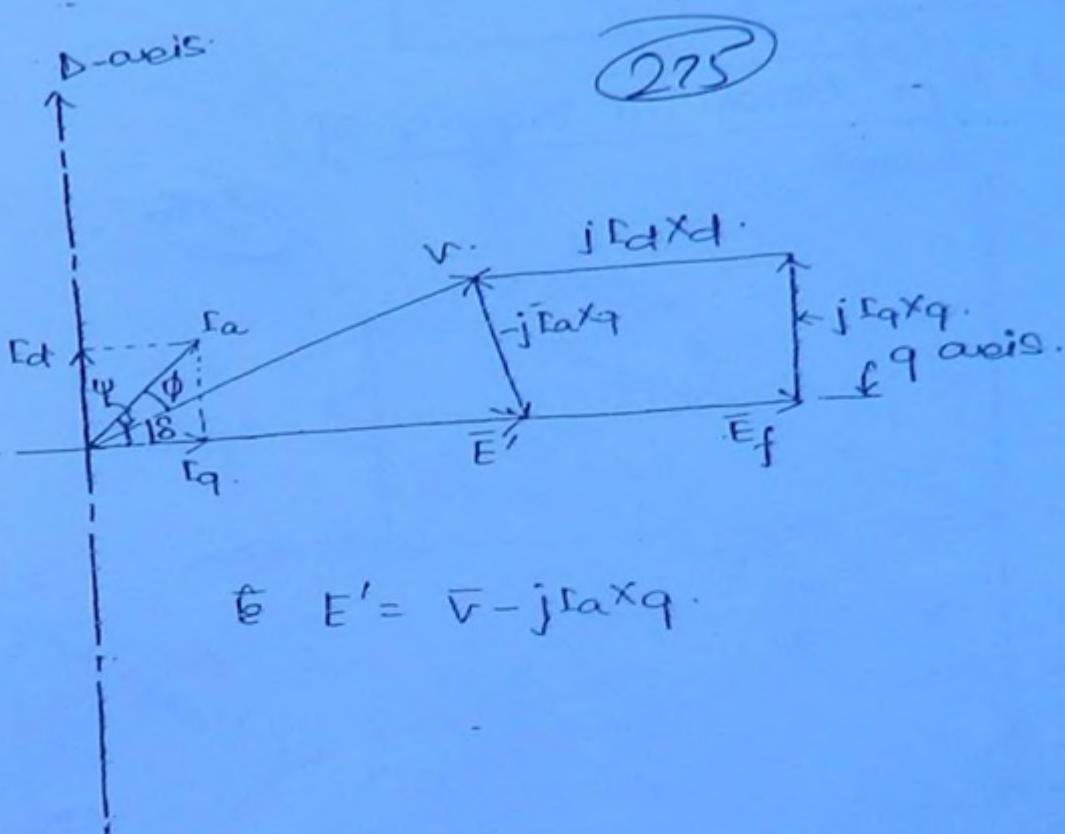

$$\bar{E}' = \bar{V} - jI_a x_q$$

Underexcited sym. gen. [leading pf]

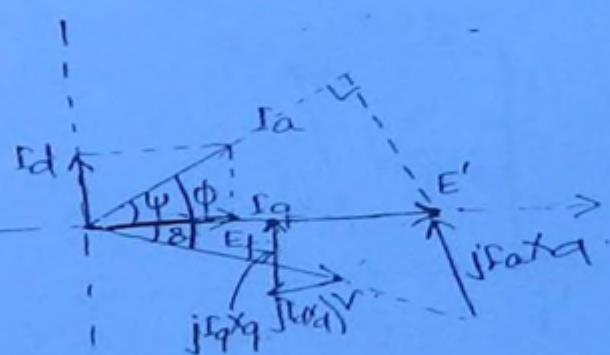

$$V + jI_a x_q = E'$$

$$P = V \cos \delta_{pq} - V \sin \delta I_d$$

$$= V \cos \delta I_a \cos \phi - V \sin \delta$$


$$= \frac{V \cos \delta I_q x_q}{x_q} - \frac{V \sin \delta I_d x_d}{x_d}$$

$$\frac{V \cos \delta V \sin \delta}{x_q} = \frac{V \sin \delta P \cos \delta + f}{x_d}$$


$$P = \frac{V E_f \sin \delta}{X_d} + \frac{V^2}{2} \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\delta$$

Underexcited Syn Motor (At lagging pf)

(276)


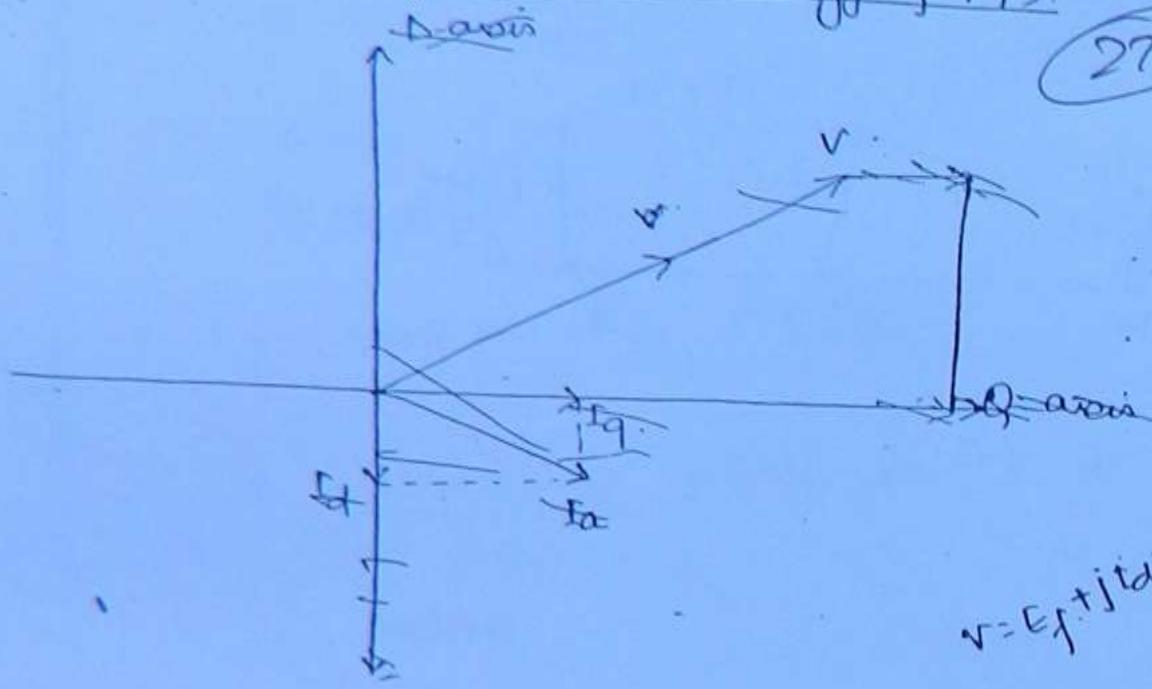


$$V = E_f + j I_d X_d + j I_q X_q$$

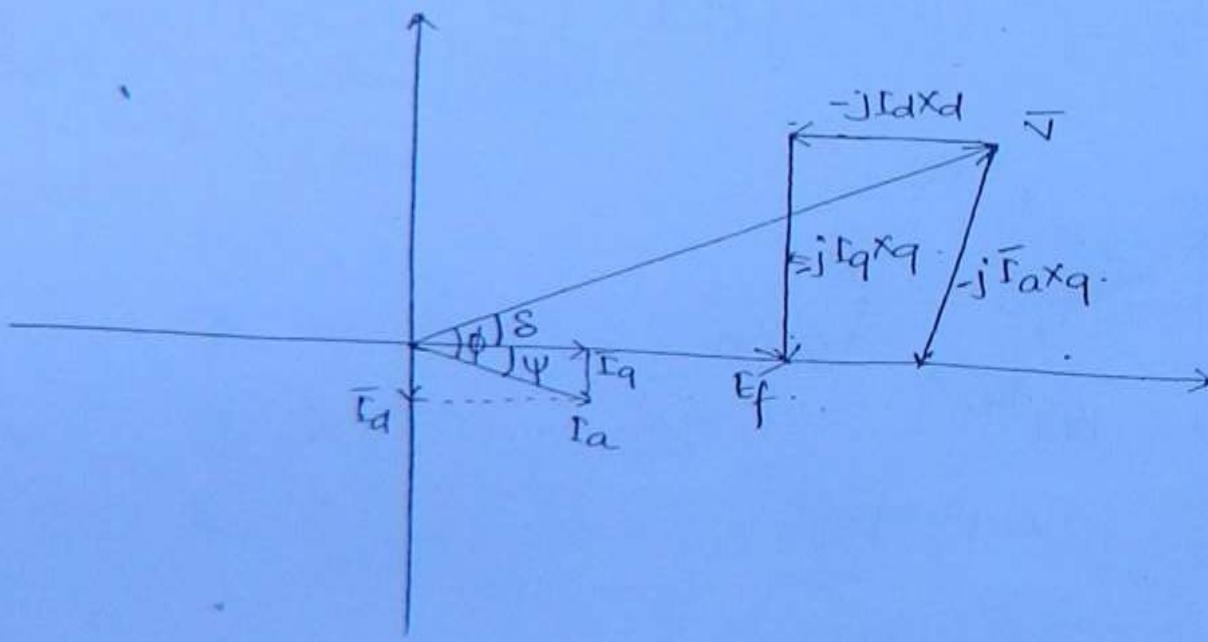

Determination of x_d and x_q by

SLEEP TEST

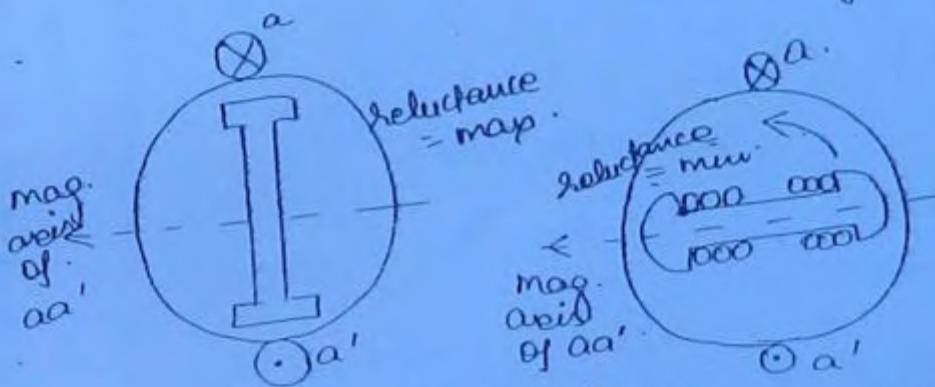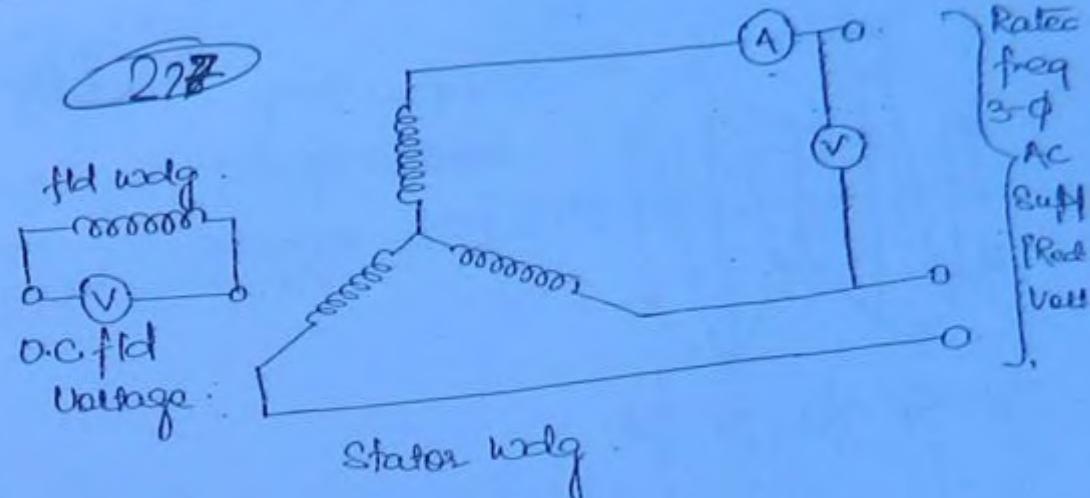

| | | | |
|---|--|---|--|
| X_q max ^m current $\phi = \frac{mmf}{\text{reluctance}}$ | mini flux linkage, $I_{fd} = \frac{\phi}{R}$ | x_d minimum current $I_{fd} = \frac{\text{mini voltage}}{\text{fld volt.} = 0}$ | x_d minimum current $I_{fd} = \frac{\text{mini volt}}{\text{max current}}$ |
|---|--|---|--|


for the given
volt, ϕ const.

$$\text{const} = \phi = \frac{\text{mini volt}}{\text{reluctance}}$$



$$x_d = \frac{\text{Map } m \cdot \text{ Voltmeter reading}}{\text{mini Ammeter reading}}$$

$$x_q = \frac{\text{mini. Voltmeter reading}}{\text{map. Ammeter reading}}$$

for 1 slip cycle \rightarrow

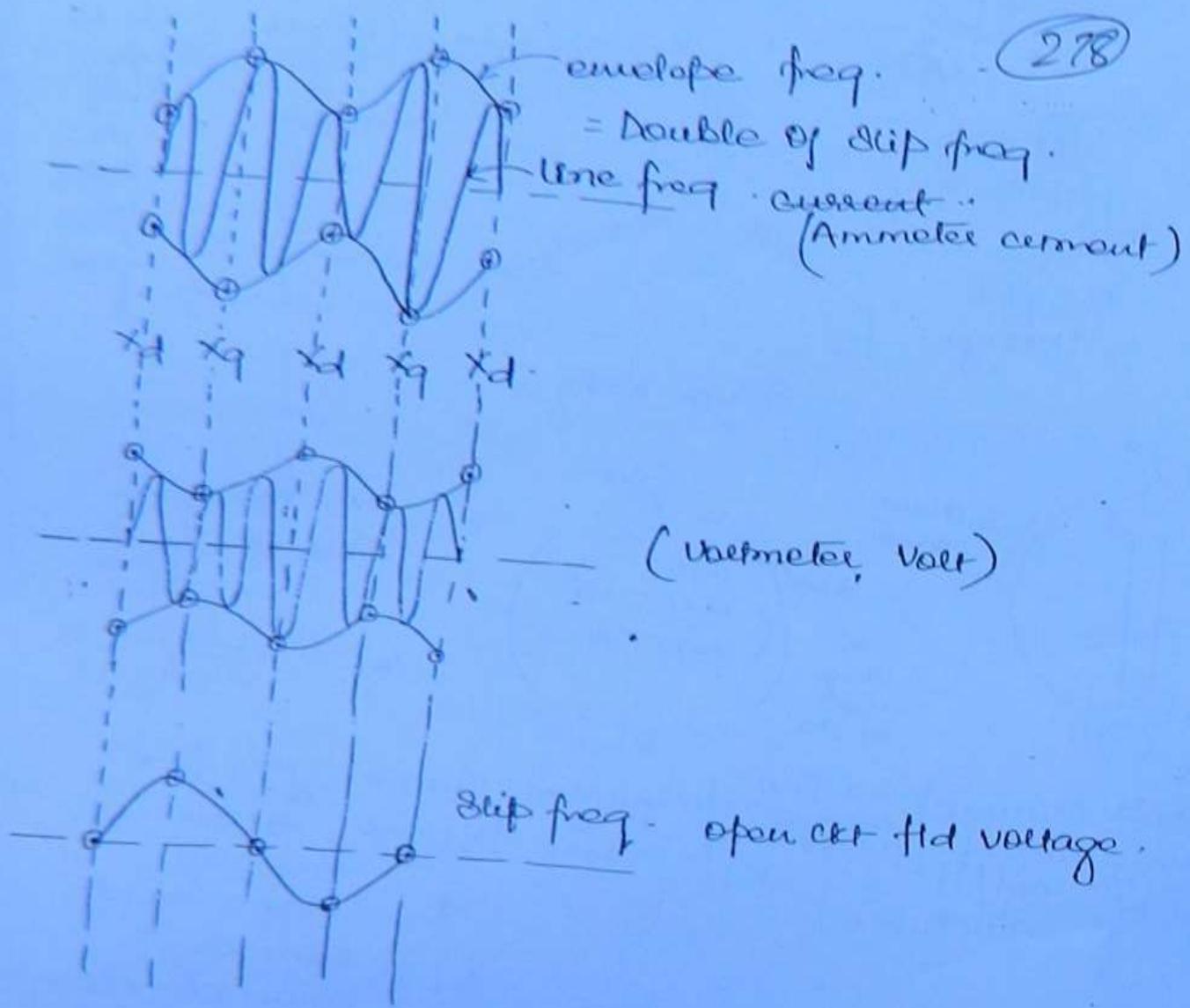

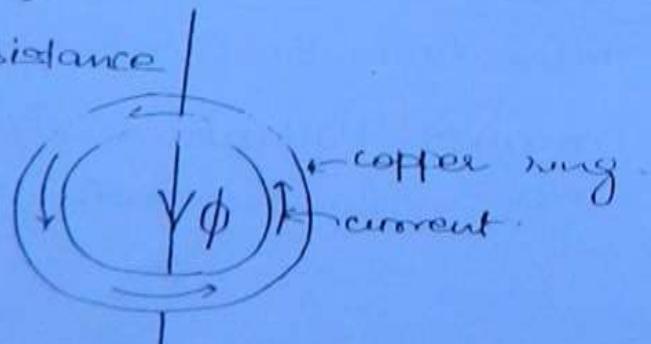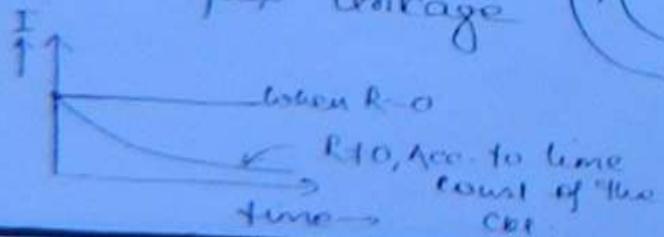Sudden 3- ϕ (Symmetrical) short ckt on the terminals of an unloaded 3- ϕ syn. gen \rightarrow
In a closed ckt having no resistance or voltage source, the mag. voltage can not change. This is called const flux linkage theorem.



Initial flux linkage = 0.

Cmf is max.



damper $\rightarrow R \uparrow, L \downarrow$

$$\frac{L}{R}$$

$x_d'' \rightarrow$ from damper time const.

$x_d' \rightarrow$ from fbd time const.

(279)

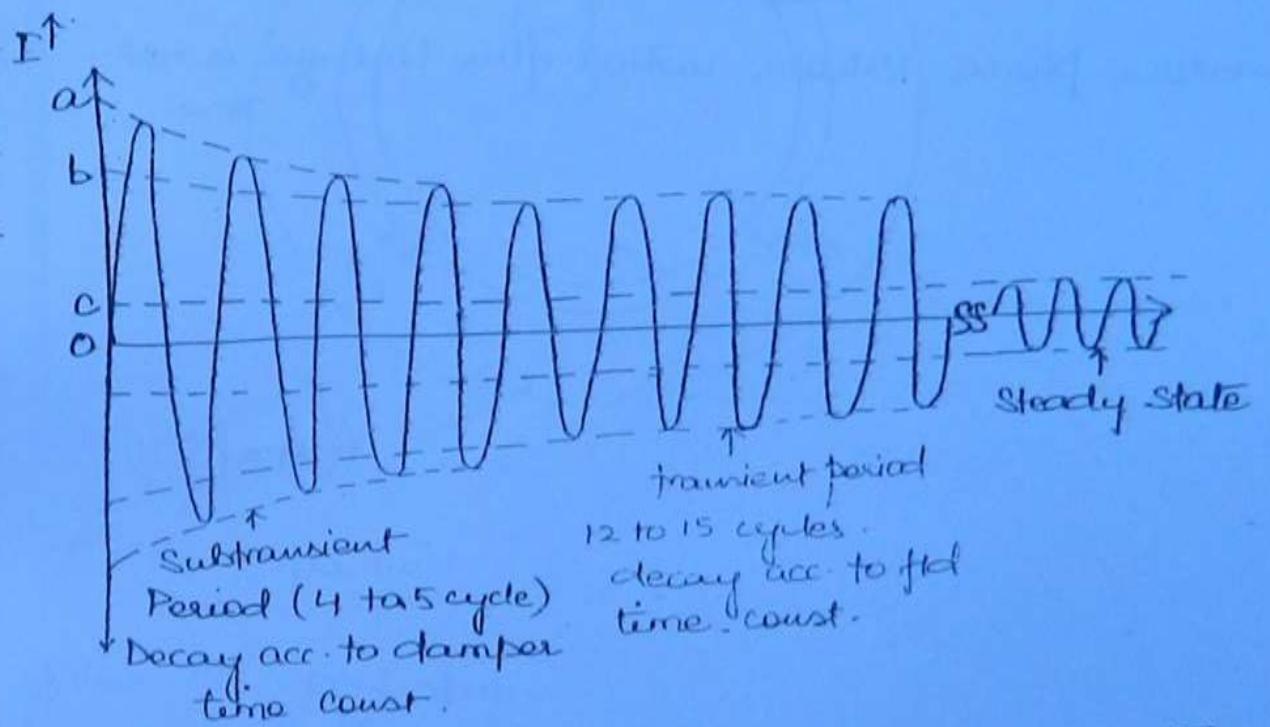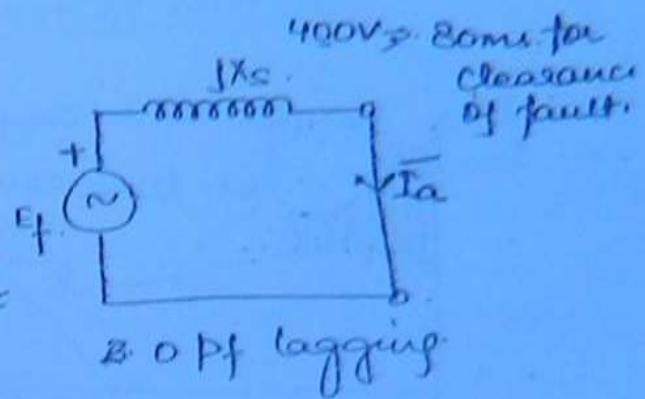



$$\text{Subtransient Reactance} = X_d'' = \frac{E_f}{0a/\sqrt{2}} \approx 0.15 \text{ pu} [\approx X_d]$$

[leakage reactance value]

$$\text{Transient Reactance} = X_d' = \frac{E_f}{0b/\sqrt{2}} \approx 0.20 \text{ pu}$$
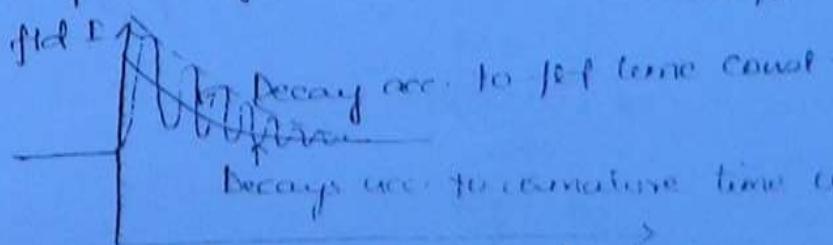
$$(\text{Direct axis}) \text{Syn. Reactance} = X_d = \frac{E_f}{0c/\sqrt{2}} \approx 1.5 \text{ pu}$$





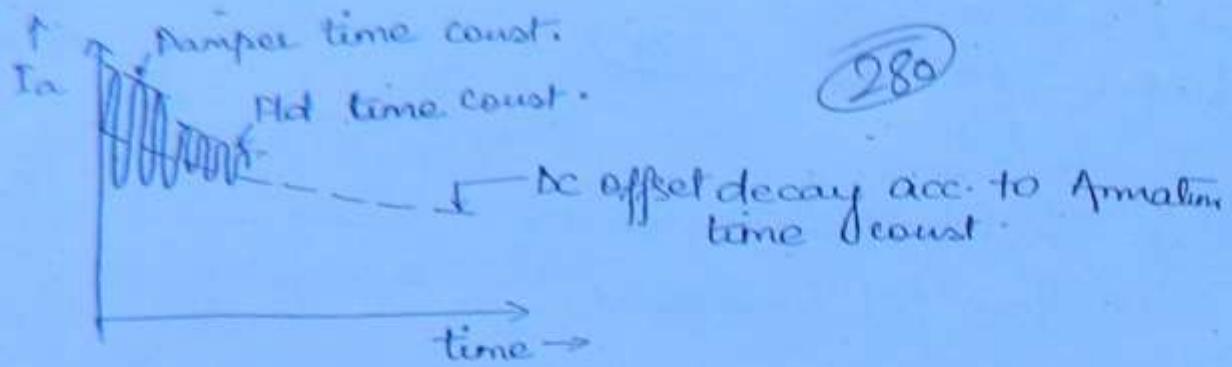

Amature phase whose initial flux linkage is not zero.

THREE PHASE INDUCTION MOTOR

(281)

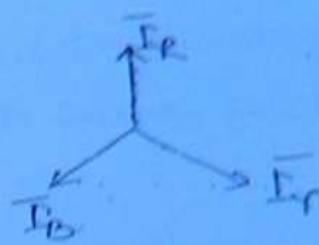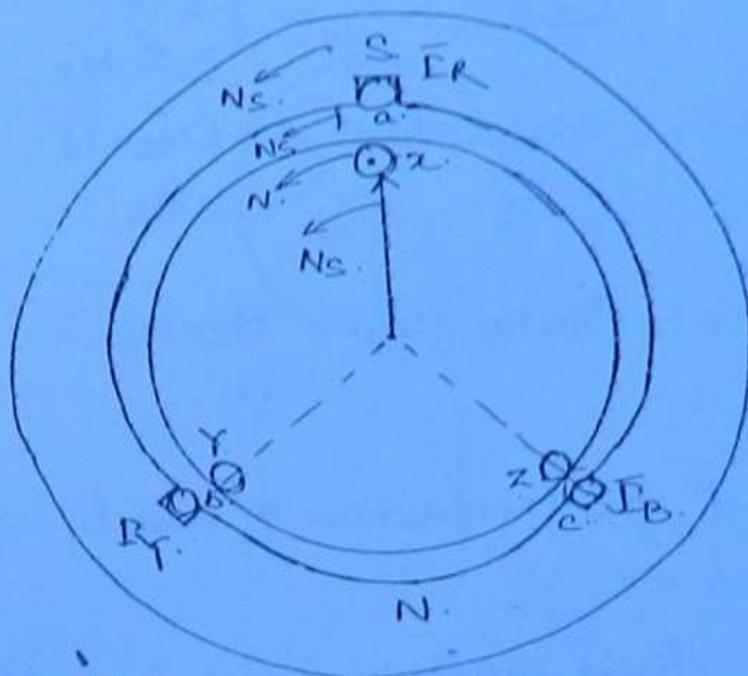

$$S = \frac{N_S - N}{N_S} \text{ per unit}$$

$$\text{Where } N_S = \frac{120f}{P} \text{ rpm.}$$

$$\text{Speed of Stator flux w.r.t. Stator body} = N_S = \frac{120f}{P}$$

$$\text{Speed of Rotor body} = N$$

$$\text{Speed of Stator flux w.r.t. Rotor body} = N_S - N$$

$$\begin{aligned} \text{Rotor freq} &= f_r = \frac{P(N_S - N)}{120} n_2 \\ &= \frac{P(2N_S)}{120} n_2 \end{aligned}$$

$$sf = n_2$$

$$\text{Speed of rotor flux w.r.t. Rotor body} = \frac{\omega_{af_r}}{P}$$

(28)

$$= \frac{f_{0s} sf}{P}$$

$$= S N_S$$

$$\text{Speed of rotor flux w.r.t. Stator body} = S N_S + N$$

$$= N_S$$

$$\text{Speed of rotor flux w.r.t. Stator flux} = N_S - N_S$$

$$= 0.$$


Conditions to be satisfied for production of steady state torque for rotating MLC:-

- > Stator flux and rotor flux must be const in amplitude.
- > Stator flux and rotor flux should be stationary w.r.t. each other.
- > There must be an angular diff. b/w the two.

ol2m

Inverted Induction motor:-

(Rotor fed Induction motor)

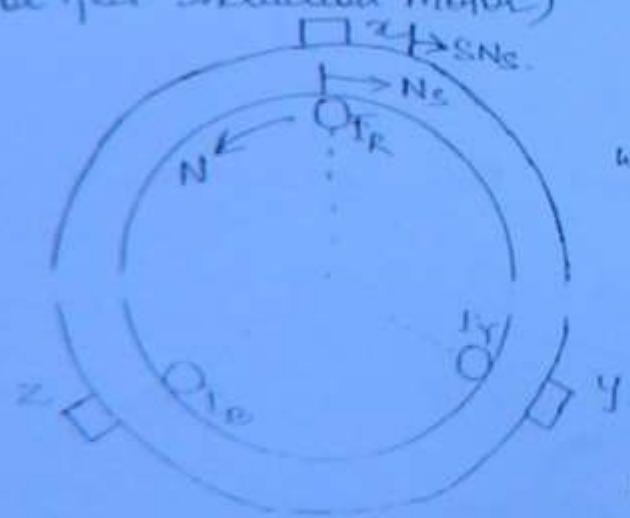

$N_S [R Y B]$

$N_S - N \rightarrow \text{Slip speed}$
w.r.t. Stator $\rightarrow N_S - N$

$2\pi z$


Induced volt per phase

Stator flux w.r.t.
Rotor body $= S N_S + N$
 $= N_S$

Rotor flux w.r.t. rotor
body $= N_S$


DC m/c →

(283)

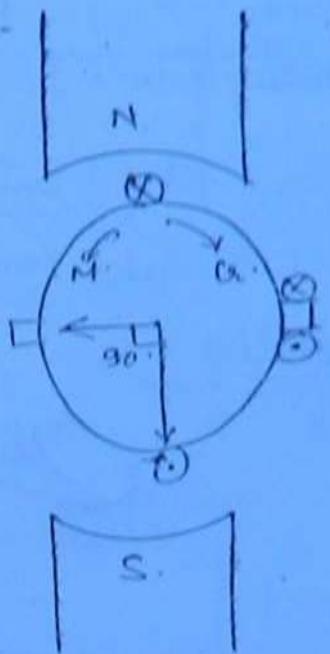

normal torque angle = 90°
most power point m/c

Syn. Gen.

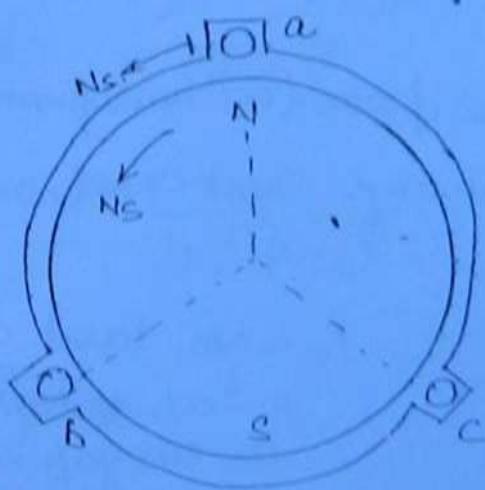


Relative speed = 0

Syn. Gen.

fd wdg on stator -

Revolving Mfd.

wrt. wdg structure
(ie Rotor hole) = n_S

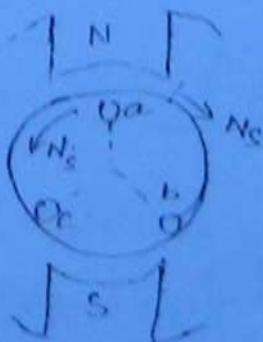

Stator flux = 0

N

S

Rotor flux

N_C

O

EQUVALENT C.R.T OF 3-φ I.M. :→ Flux cuts cond.
 $\phi \rightarrow$ Flux per pole. [Rotating X-mer] → dynamically induced emf
 E_1 , Stator induced emf $\psi = \left(\frac{2}{\pi} B_m \right) \left(\frac{\pi D L}{P} \right)$
 $= k \omega_1 \sqrt{2} \pi f \phi N_1$, $N_1 \rightarrow$ Stator turns / pole.

Rotor induced emf at standstill = E_2

$$= k \omega_2 \sqrt{2} \pi f \phi N_2$$

(284)

$$\therefore \frac{E_1}{E_2} = \frac{k \omega_1 N_1}{k \omega_2 N_2}$$

$$= \frac{N_{e1}}{N_{e2}} \quad \text{where } N_{e1} = \text{No. of eff. stator turns/pole}, \\ N_{e2} = 1, \dots, \text{Rotor "}$$

= a - Reduction factor (or transformation ratio)

Rotor of induction motor is always short circuited:

MMF Balance →

$$N_{e1} \bar{I}_1 - N_{e2} \bar{I}_2 = N_{e1} \bar{I}_0$$

$I_0 \rightarrow$ No. load current

= 30% to 40% of FL


as airgap is high


reluctance is very high

$$\Rightarrow \bar{I}_1 = \frac{\bar{I}_2 + \bar{I}_0}{a}$$

$$\Rightarrow \bar{I}_1 = \bar{I}'_2 + \bar{I}_0$$

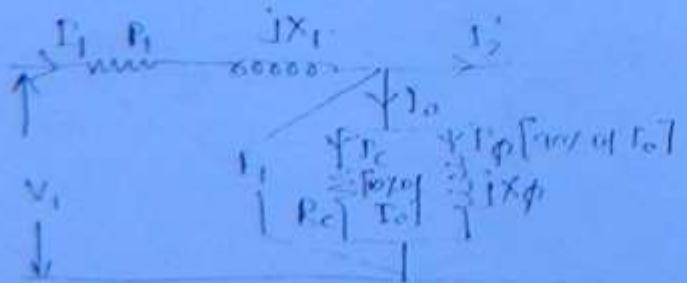$\therefore \frac{\bar{I}_1}{a} = \bar{I}'_2 + \bar{I}_0$ Calculation of magnetization in terms of fluxes



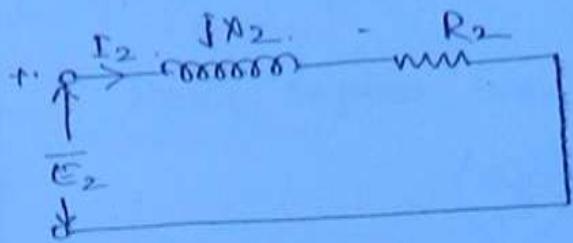


$X_2 \rightarrow$ Rotor leakage reactance
at standstill.

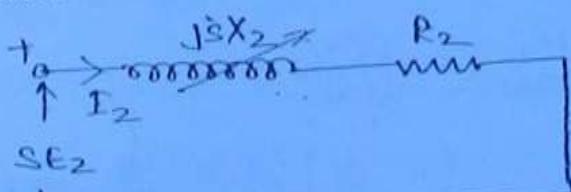(285)

Rotor at standstill.

Starting current is very high because of short circuit of rotor.



[Eq. ckt. at Rotor freq].

* Rotor in motor at slip S.


$$|I_2| = \frac{SE_2}{\sqrt{R_2^2 + (Sx_2)^2}}$$

$$\cos \phi = \frac{R_2}{\sqrt{R_2^2 + (Sx_2)^2}}$$

$$\begin{aligned} \bar{I}_2 &= \frac{SE_2}{R_2 + jSx_2} \\ &= \frac{SE_2 20^\circ}{\sqrt{R_2^2 + (Sx_2)^2}} \angle \tan^{-1} \frac{Sx_2}{R_2} \end{aligned}$$

$$\bar{I}_2 = \frac{SE_2}{\sqrt{R_2^2 + (Sx_2)^2}} \angle -\tan^{-1} \left(\frac{Sx_2}{R_2} \right)$$
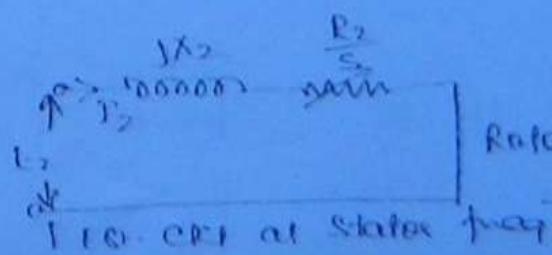
$$\begin{aligned} S\bar{I}_2 &= I_2 R_2 + j I_2 Sx_2 \\ \therefore \bar{I}_2 &= \frac{I_2 R_2 + j I_2 Sx_2}{S} \end{aligned}$$



Rotor in motion
at slip S.


$$\text{Then } \bar{I}_2 = \frac{E_2}{\frac{R_2}{s} + jX_2}$$

$$\Rightarrow I_2 = \frac{s\bar{E}_2}{\sqrt{R_2^2 + (sX_2)^2}} \angle -\tan^{-1}\left(\frac{sX_2}{R_2}\right)$$

$E_2 > \frac{sE_2}{s}$
 $\therefore P_F > P_E$

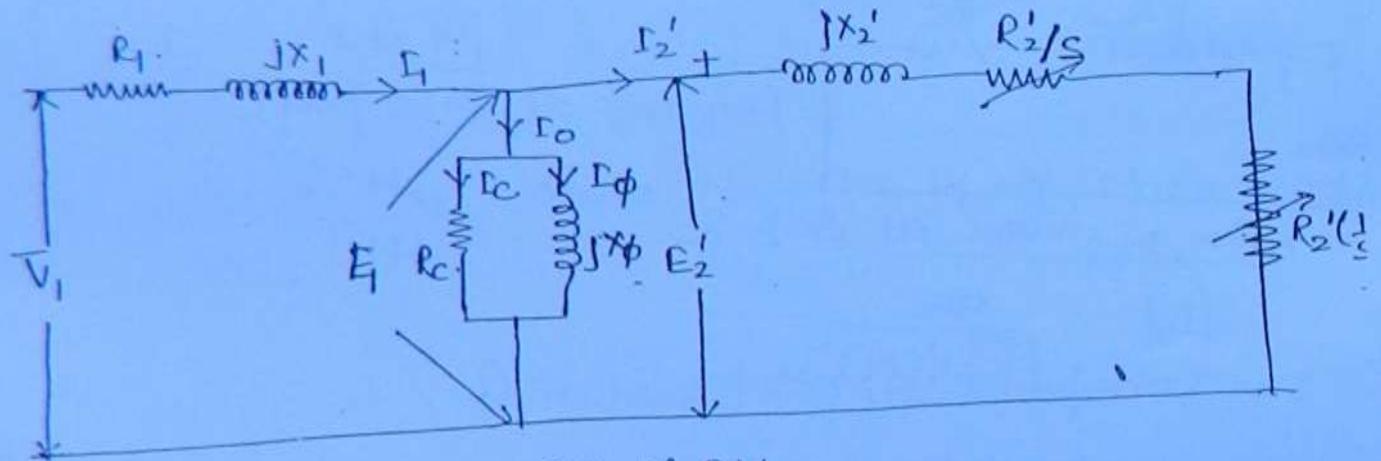(286)

Heav. load Eq. Resistance
 $= R'_2 \left(\frac{1}{s} - 1 \right)$



EXACT EQUIVALENT CIRCUIT OF DM.

$$E'_2 = a^2 E_2$$

$$R'_2 = a^2 R_2$$

$$X'_2 = a^2 X_2$$

Input power $\frac{\text{minus (stator copper loss)}}{\text{+ Stator core loss}}$ Refer EIP or Air gap power $\frac{\text{minus Rotor copper loss}}{\text{+ Rotor core loss}}$

Mechanical no load

Output power $\frac{\text{minus Rotational losses}}{\downarrow P_{friction} + P_{air}}$

$$[\text{magic quantity}] P_g = (I_2')^2 \times \frac{R_2'}{s} \text{ synchronous watts.}$$

$$\text{Rotor copper loss} = (I_2')^2 R_2' \\ = s P_g$$

(287)

$$\text{Mech. power developed} = P_d = P_g - s P_g \\ = P_g (1-s)$$

$$P_d = P_g (1-s) \\ = (I_2')^2 \times \frac{R_2'}{s} (1-s)$$

$$P_d = I_2'^2 \times R_2' \left(\frac{1}{s} - 1 \right).$$

$$S = \frac{N_s - N}{N_s}$$

$$N = N_s - S N_s \\ = N_s (1-s)$$

$$T_d = \frac{P_d}{\omega_m} \text{ NM}$$

$$= \frac{P_d}{\omega_{sm} (1-s)}$$

$$= \frac{P_g (1-s)}{\omega_{sm} (1-s)}$$

$$= \frac{P_g}{\omega_{sm}}$$

$$\therefore T_d$$

$$T = \frac{P_g}{\omega_{sm}}$$

$$\eta_{\text{internal}} [\text{Rotor internal } \eta] : \frac{P_d}{P_g} = \frac{1}{1-s}$$

$$\text{Empirical } \eta = \frac{1-s}{1+s} \text{ [only to be used for obj. Q]}$$

Q. A 6 pole, 50 Hz, 3-φ D.M. running on F.L. develops a useful torque of 160 N-m and Rotor emf is absorbed to make 120 cycles /m. Cal. net magnet mechanical power developed. If the torque loss in windage and friction is 12 N-m. Find the cu loss in rotor wdg,
~~Ans.~~ ~~f_r = 120 cycles / m~~ I/P to the motor and η .

~~120~~

Given \rightarrow total stator losses = 200 W.

(288)

$$\text{In. } T = 160 \text{ NM.}$$

$$\frac{P_g}{W_{sm}} = T = 160 \text{ NM}$$

$$W_{sm} = 2 \pi f \\ = 2 \times \pi \times 50$$

$$P_g = \frac{160 \times 0.25 \pi}{50 \cdot 26.5 \cdot 48} \text{ Sym-well.} \\ = 50.2655 \text{ - Sym. kw.}$$

$$f_r = \cancel{120}$$

$$120 \text{ cycles/m.}$$

$$120 = 5 \times 2 \times 50$$

$$f_r = \frac{120}{60} \text{ cycles / sec.}$$

$$= 2 \text{ Hz.}$$

$$S = \frac{2}{50}$$

$$\Rightarrow S = 0.04 \text{ pu.}$$

$$W_{sm} = \frac{2}{P} \times 2 \times 50.$$

$$\therefore W_{sm} = 104.72 \text{ rad/s.}$$

$$\omega_m = \omega_{sm} (1-s) \\ = 100.53 \text{ rad/s}$$

$$\text{Net power} = 160 \times 100.53 \\ = 16,085 \text{ kW}$$

(289)

$$\text{Gross torque} = 160 + 12 = 172 \text{ Nm}$$

$$P_g = 172 \times \omega_{sm} \\ = 18.01 \text{ kW}$$

$$\text{Rotor copper loss} = S P_g \\ = 720.4 \text{ W}$$

$$\text{D/P power} = P_g + \text{Stator loss} \\ = 18.01 + 0.2 \\ = 18.21 \text{ kW}$$

$$\eta = \frac{16.085}{18.21} = 0.8833 \text{ pu} = 88.33\%$$

Q. A 3φ I.M. has η of 0.9 when load is 37 kW. At this load the stator cu loss and rotor cu loss each equals the iron loss. The mechanical losses are $\frac{1}{3}$ rd of no load loss. Cal. the slip.

$$\underline{\text{Ans}} \quad \eta = 0.9$$

$$P_0 = 37 \text{ kW}$$

$$\frac{R_o}{R_i} < 2$$

$$P_{in} = \frac{37}{0.9} \text{ kW} = 41.11 \text{ kW}$$

$$\begin{aligned}\text{Total losses} &= P_{in} - P_{out} \\ &= 41.111 - 37 \\ &= 4.111 \text{ kW}\end{aligned}$$

Stator cu loss = Rotor copper loss = Iron loss = y

$$\begin{aligned}\text{No load} &= \text{Iron loss} + \text{Mech. loss.} \\ &= y + \frac{\text{No. load loss.}}{3.} \quad \text{(290)}\end{aligned}$$

$$\Rightarrow \frac{2}{3} \text{ No. load loss} = y$$

$$\Rightarrow \text{No. load loss} = \frac{3y}{2}$$

$$\begin{aligned}\text{Mech. loss.} &= \frac{1}{3} \times \frac{3y}{2} \\ &= \frac{y}{2}\end{aligned}$$

$$3.5 y = 4.111 = y + y + y + 0.5y$$

$$\begin{aligned}y &= \frac{4.111 \times 10^3}{3.5} \text{ watts.} \\ &= 1174.6 \text{ watts.}\end{aligned}$$

~~0.1P + 1.5y~~

$$P_g = P_{in} - 2y \text{ or } P_{out} + 1.5y.$$


$$P_g = 38761.8 \text{ watts.}$$

~~Q1/P = $\frac{P_{out} - P_{in} + 1.5y}{P_g}$~~

$$\frac{P_g}{P_g}$$

$$= \frac{1174.6}{38761.8}$$

$$= 0.0303 \text{ pu}$$

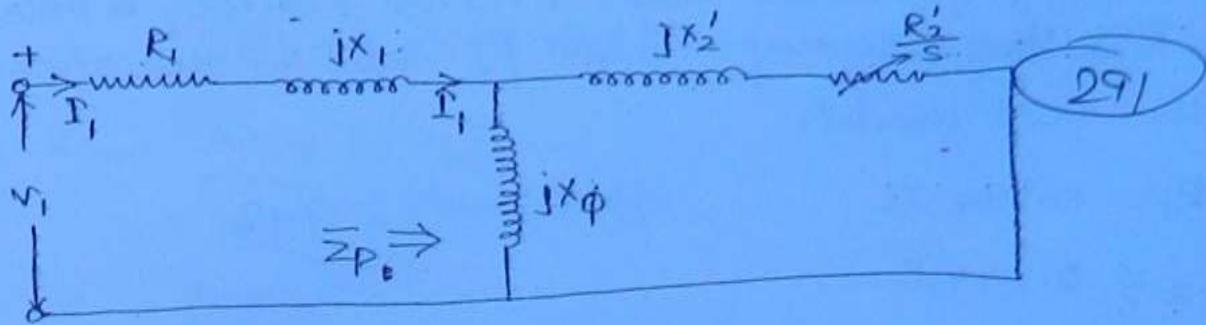

291

IEEE APPROVED STEINMETZ MODEL.

Power flow as per Steinmetz model : →

Input power minus Stator
core loss → P_g i.e. Rotor I/P. minus
Rotor
core loss

O/P power. minus
Rotational
losses minus Mech power de
Pd.


$P_{f+w} + P_{hie} + P_{LL}$
(mech (iron (stray load
loss) loss) loss).

Mathematical computation in convenience

Mathematical convenience in computation : →

Steps →
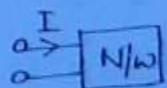
$$1) \bar{Z}_p = (jX\phi) // \left(\frac{R_2'}{S} + jX_2' \right)$$



$$P = I^2 R$$

$$Q = I^2 X$$

$$= R_p + jX_p$$

$$2) \bar{I}_1 = \frac{\bar{V}_1}{(R_1 + jX_1) + \bar{Z}_p}$$

$$3) P_g = \bar{I}_1^2 \times R_p$$

Q: A 3- ϕ Y connected 220V, 7.5 kW, 50 Hz, 6 pole D.M. has the following constants / ϕ refer to the stator in Steinmetz model.

$$R_1 = 0.294 \Omega$$

$$R_2' = 0.144 \Omega$$

$$X_1 = 0.503 \Omega$$

$$X_2' = 0.209 \Omega$$

$$X_\phi = 13.25 \Omega$$

(292)

Total friction, windage and core losses may be assumed to be constant 403 watts independent of load. For a slip of 2%, compute the speed, O/P torque, O/P power, Stator current, Pf and η . With the motor is operated at rated freq and Vol.

$$\begin{aligned} Z_P &= jX_\phi \parallel \left(\frac{R_2'}{s} + jX_2' \right) \quad s=0.02 \\ &= \frac{(jX_\phi) \times \left(\frac{R_2'}{s} + jX_2' \right)}{jX_\phi + \frac{R_2'}{s} + jX_2'} \quad Z_2' = 7.203 \angle 1.66^\circ \\ &= 5.4255 + 3.108i \\ &= 5.43 + 3.11i = P_R R_P + jX_P \end{aligned}$$

$$\begin{aligned} \bar{E}_1 &= \frac{220/\sqrt{3}}{(0.294 + 0.503i) + (5.43 + 3.11i)} \quad Z_{\text{total}} = Z_1 + Z_P \\ &= 16.765 \angle -32.26^\circ \quad - 6.76(32.3i) \end{aligned}$$

$$\begin{aligned} P_{Q1g} &= E_1^2 \times R_P \\ &= 1912.034 \text{ W} \\ &\text{D. } - 5236.12 \text{ rad/s} \end{aligned}$$

$$\begin{aligned} \text{Pf} &= \cos 32.66^\circ \\ &= 0.842 \text{ lagging} \end{aligned}$$

$$\omega_{SM} = \frac{2}{P} \times 2\pi \times 60 \\ = 125.66 \text{ mech rad/s}$$

(293)

$$\omega_m = \omega_{SM} (1-s) \\ = 123.15 \text{ mech rad/s}$$

$$N = \frac{60\omega_m}{2\pi}$$

$$\approx 1176 \text{ rpm}$$

$$\text{torque developed} = \frac{P_g}{\omega_{SM}} = T_d = \text{Air gap torque} \\ = \frac{5740.82}{125.66} \\ = 45.69 \text{ NM}$$

$$P_d = P_g (1-s) \text{ or } P_d = T_d \times \omega_m \\ = 5626 \text{ W}$$

$$\text{O/P power} = P_d - 403 \\ = 5223 \text{ watts}$$

$$\text{O/P torque} = \frac{5223}{10m} \\ = 42.41 \text{ N-m}$$



$$\text{E/P power} = \sqrt{3} \times 220 \times 18.73 \times 0.845 \\ = 6050.3 \text{ watts}$$

$$\eta = \frac{5223}{6050.3} = 86.633\%$$

Thevenin's equivalent of Steinmetz model :-

$$V_{Th} = \frac{V_1}{R_1 + jX_1 + jX_\phi} \times jX_\phi$$

$$Z_{Th} = (jX_\phi) / (R_1 + jX_1)$$

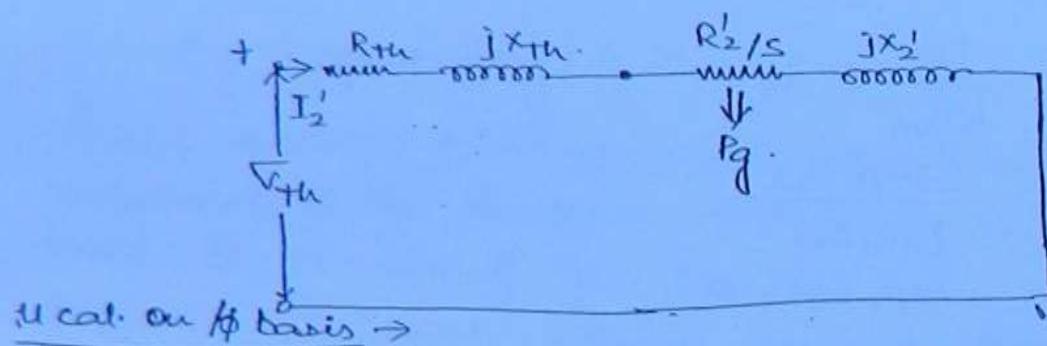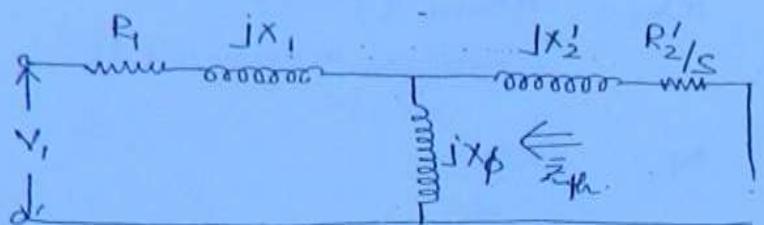

294

Calc. on ϕ basis \rightarrow

$$I_2' = \frac{V_{Th}}{\sqrt{\left(R_{Th} + \frac{R_2'}{S}\right)^2 + (X_{Th} + X_2')^2}}$$

$$T = \frac{P_g}{\omega_{SM}}$$

$$= \frac{1}{\omega_{SM}} \times (I_2')^2 \times \frac{R_2'}{S}$$

$$T = \frac{1}{\omega_{SM}} \times \frac{V_{Th}^2}{\left(R_{Th} + \frac{R_2'}{S}\right)^2 + (X_{Th} + X_2')^2} \times \frac{R_2'}{S}$$

$$\begin{matrix} T \\ \downarrow \\ 0 \end{matrix}$$

$$V_{Th} = V_1, R_{Th} = 0, X_{Th} = 0$$

$$I_2' = \frac{V_1}{\sqrt{\left(\frac{R_2'}{S}\right)^2 + X_2'^2}}$$

T_{max} when $P_g = \text{max}$.
when $\frac{R_2'}{S} = \sqrt{R_{Th}^2 + (X_{Th})^2}$

$$T = \frac{1}{\omega_{SM}} \times \frac{v_1}{\left(\frac{R_2'}{s}\right)^2 + (x_2')^2} \times \frac{R_2'}{s}$$

A) At low slip,

$$\frac{R_2'}{s} \gg x_2'$$

(295)


$\therefore (x_2')^2$ in the denominator may be neglected.

$$\text{i.e. } F_2' = \frac{sv_1}{R_2'} \propto s.$$

$$T = \frac{1}{\omega_{SM}} \times \frac{s(v_1)^2}{R_2'^2}$$

$$[T \propto s]$$

T ~ Speed →

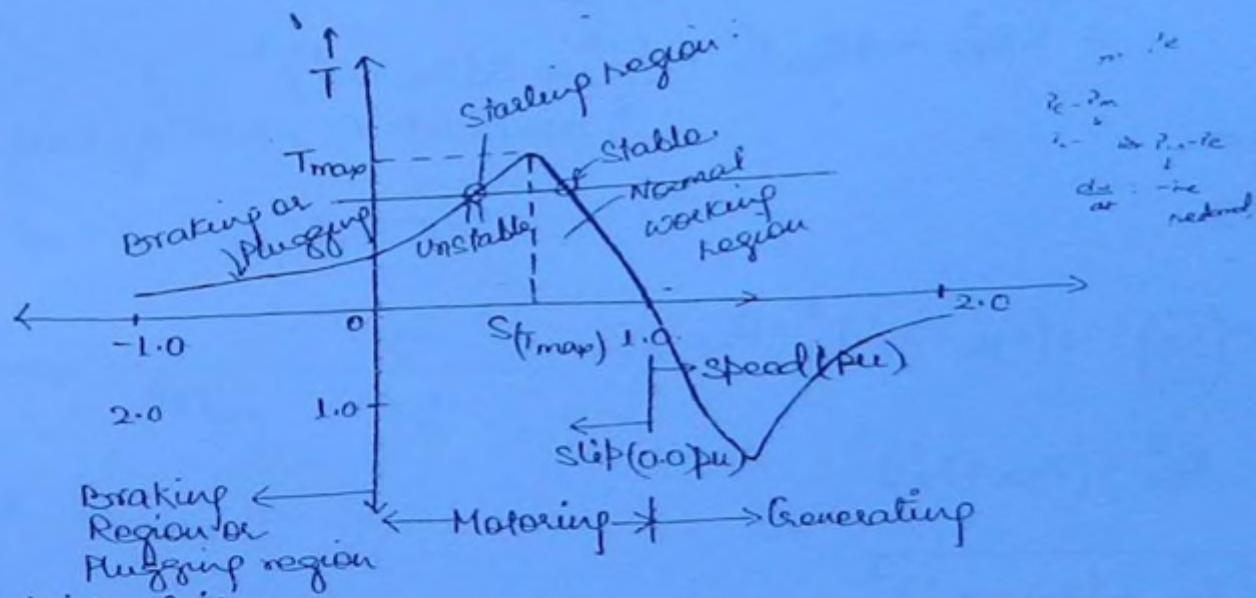

B) At high Slip : →

$$\frac{R_2'}{s} \ll x_2'$$

$\therefore \left(\frac{R_2'}{s}\right)^2$ in the denominator may be neglected

$$\text{i.e. } F_2' = \frac{v_1}{x_2'} \approx \text{const}$$

$$\therefore T = \frac{1}{\omega_{SM}} \times \frac{v_1^2}{x_2'} \times \frac{R_2'}{s} \Rightarrow [T \propto \frac{1}{s}]$$

T_{max} : Max torque or Pull out torque or breakdown torque or Stalling torque.

$$T = \frac{1}{\omega_{sm}} \times \frac{V_{TH}^2}{\left(R_{TH} + \frac{R_2'}{S}\right)^2 + (X_{TH} + X_2')^2} \times \frac{R_2'}{S}$$

(296)

$$= \frac{V_{TH}^2 R_2' / \omega_{sm}}{S \left[\left(R_{TH} + \frac{R_2'}{S} \right)^2 + (X_{TH} + X_2')^2 \right]}$$

Torque is max when denominator is minimum.

$$\begin{aligned} \text{denominator} &= S \left[R_{TH}^2 + \left(\frac{R_2'}{S}\right)^2 + 2R_{TH} \frac{R_2'}{S} \right] + S(X_{TH} + X_2')^2 \\ &= SR_{TH}^2 + 2R_{TH} R_2' + \frac{R_2'^2}{S} + S(X_{TH} + X_2')^2 \end{aligned}$$

For $d^2 = \min$

$$\frac{d}{ds}(d^2) = 0$$

$$\Rightarrow R_{TH}^2 + 0 - \left(\frac{R_2'}{S}\right)^2 + (X_{TH} + X_2')^2 = 0$$

$$\Rightarrow \left(\frac{R_2'}{S}\right)^2 = R_{TH}^2 + (X_{TH} + X_2')^2$$

$$\Rightarrow \frac{R_2'}{S} = \sqrt{R_{TH}^2 + (X_{TH} + X_2')^2}$$

$$S_{T_{max}} = \frac{R_2'}{\sqrt{R_{TH}^2 + (X_{TH} + X_2')^2}} \propto R_2' \text{ if } R_2' \text{ can be varied}$$

$$T_{max} = \frac{1}{\omega_{sm}} \frac{V_{TH}}{\left[R_{TH} + \frac{R_2'}{\sqrt{R_{TH}^2 + (X_{TH} + X_2')^2}} \right]} \times \frac{R_2'}{S_{T_{max}}}$$

$$= \frac{1}{\omega_{sm}} \frac{\frac{V_{th}^2}{R_{th} + \frac{R_2' S_{Tmap}}{S_{Tmap}} + 2 \left(\frac{R_2'}{S_{Tmap}} \right)^2}}{+ \frac{R_2'}{S_{Tmap}}} -$$

297

$$= \frac{1}{\omega_{sm}} \frac{\frac{V_{th}^2}{R_{th} + 2 \frac{R_2'}{S_{Tmap}}}}{+}$$

$$= \frac{1}{\omega_{sm}} \frac{\frac{V_{th}^2}{R_{th} + \frac{R_2'}{S_{Tmap}}}}{+}$$

$$T_{map} = \frac{1}{\omega_{sm}} \frac{\frac{V_{th}^2}{R_{th} + \sqrt{R_{th}^2 + (x_{th} + x_2')^2}}}{=} \boxed{\text{const}}$$


does not vary with
Slip S .

Neglecting stator impedance,

$$V_{th} = V_1, R_{th} = 0, X_{th} = 0$$

$$T_{map} = \frac{1}{\omega_{sm}} \frac{V_1^2}{X_2'} = \text{const}$$
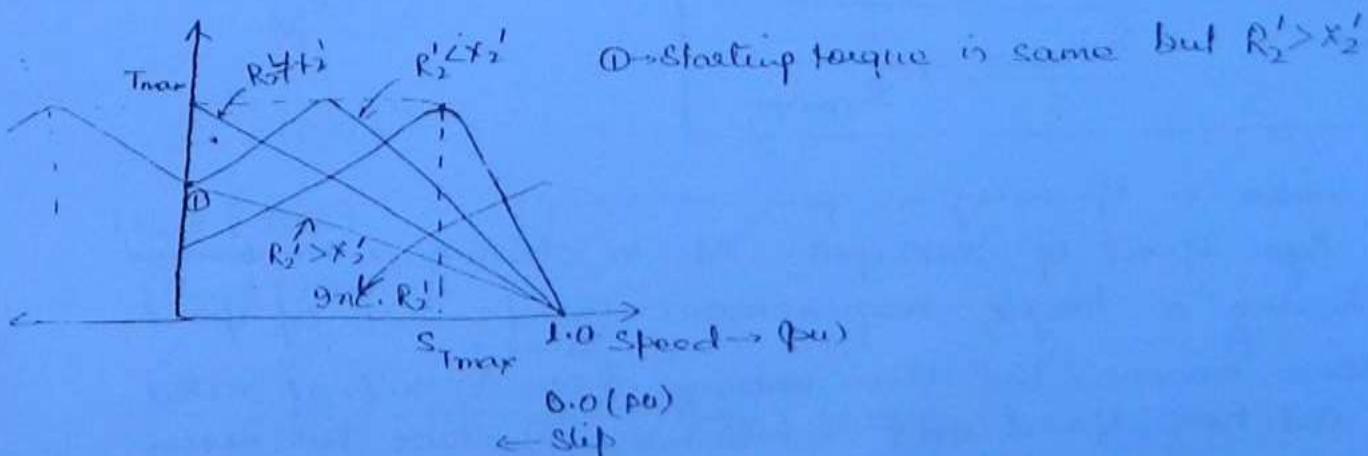
$$\text{at } S_{Tmap} = \frac{R_2'}{X_2'}$$



The ratio of $\frac{T}{T_{max}}$

$$T = \frac{1}{\omega sm} \times \frac{V_1^2}{\left(\frac{R_2'}{S}\right)^2 + (X_2')^2} \times \frac{R_2'}{S}$$

(2.98)

$$T_{max} = \frac{1}{\omega sm} \frac{V_1^2}{X_2'}$$

$$\begin{aligned} \frac{T}{T_{max}} &= \frac{1}{\omega sm} \frac{\cancel{V_1^2}}{\left(\frac{R_2'}{S}\right)^2 + (X_2')^2} \times \frac{R_2'}{S} \times \frac{2\omega sm X_2'}{\cancel{V_1^2}} \\ &= \frac{2}{\frac{S}{R_2' X_2'} \left[\left(\frac{R_2'}{S}\right)^2 + (X_2')^2 \right]} \\ &= \frac{2}{\frac{R_2'}{S X_2'} + \frac{S X_2'}{R_2'}} \\ &= \frac{2}{\frac{(R_2'/X_2')}{S} + \frac{S}{(R_2'/X_2')}} \end{aligned}$$

| | | |
|---------------------|-----|---|
| $\frac{T}{T_{max}}$ | $=$ | $\frac{2}{\frac{S_{T_{max}}}{S} + \frac{S}{S_{T_{max}}}}$ |
|---------------------|-----|---|

Q is motor is operating at full load.

and syn. speed of 1800 rpm. It is driving a mechanical load having a torque requirement independent of speed. For some reason, the line voltage drops to 90% of rated value. Cal. new speed and determine whether the motor would now run hotter or cooler and by how much %. Ignore stator losses.

$$\text{Ans} \quad S = 0.03$$

$$N = 1800 \text{ rpm}$$

$$N = \frac{120f}{P}$$

299

$$T = \frac{1}{\omega_{SM}} \times \frac{SV_1^2}{R_2^1}$$

$$\propto SV_1^2$$

$$S \propto \frac{T}{V_1^2}$$

$$S \propto \frac{1}{V_1^2} \quad \therefore T \rightarrow \text{const}$$

$$\frac{S_2}{S_1} = \frac{1}{(0.9)^2}$$

$$S_2 = \frac{0.03}{0.81} = 0.037 \text{ pu.}$$

$$N_2 = 1800(1 - 0.037) \\ = 1733.4 \text{ rpm}$$

$$N_1 = 1800(1 - 0.03) \\ = 1746.$$

Heat \propto Rotor cu loss

$$\propto SPq$$

$\propto S$. $\therefore Pq \rightarrow \text{const}$ for const torque

$$\propto \frac{1}{V_1^2}$$

$$\propto \frac{1}{(0.9)^2}$$

$$\frac{\text{Heat (90\%)}}{\text{Heat (100\%)}} = \frac{1}{0.81} \\ = 1.2346$$

i.e. H/c runs 23.46% hotter.

A 3-phi D.M. has starting torque equal to 1.5 times full load torque. Max torque = 2.5 times full load torque. Determine the full load slip.

(b) Calc. starting current in pu

$$\text{Ques. } \frac{T}{T_{\max}} = \frac{2}{\frac{s_{T_{\max}}}{s} + \frac{1}{s_{T_{\max}}}}$$

300

$$\frac{1.53}{2.55} = \frac{2}{\frac{s_{T_{\max}}}{s} + \frac{1}{s_{T_{\max}}}}$$

$T = 1.5$

$s = L$

$$3 \left[s_T + \frac{1}{s_T} \right] = 10$$

$$\frac{T_S}{T_{FL}} = 1.5$$

$$\Rightarrow 3 \left[s_T^2 + 1 \right] = 10s_T$$


$$\frac{T_{\max}}{T_{FL}} = 2.5$$

$$\Rightarrow 3s_T^2 - 10s_T + 3 = 0$$

$$\Rightarrow s_T = +0.33 \\ = +3 \Rightarrow X$$


$$s_{T_{\max}} = +0.33 \\ = \frac{1}{3}$$

$$3s_T^2 - 9s_T - s_T + 3 = 0$$

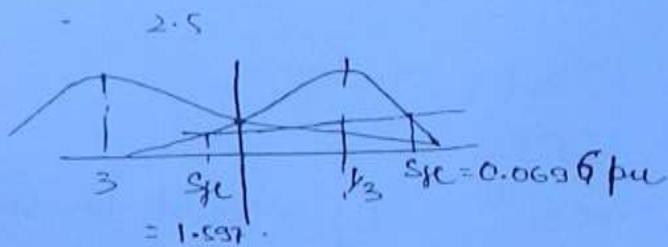

$$\Rightarrow 3s_T(s_T - 3) - 1(s_T - 3) = 0$$

$$\Rightarrow (3s_T - 1)(s_T - 3) = 0$$

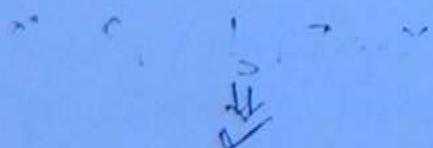

$$\frac{T_{FL}}{T_{\max}} = \frac{2}{\frac{s_{T_{\max}}}{s_{FL}} + \frac{1}{s_{T_{\max}}}}$$



$$\Rightarrow s_{FL} = 0.0697 \text{ & } 1.5$$

Δcopt
ie 6.36%

Because the rotor is short circuited and induced voltage = SE
 at starting $S = 1 \therefore SE_2 = E_2 \cdot S_0$, starting current is very
 high.

301

Starting of I.M.: →

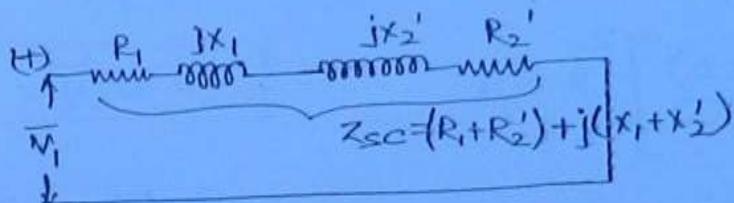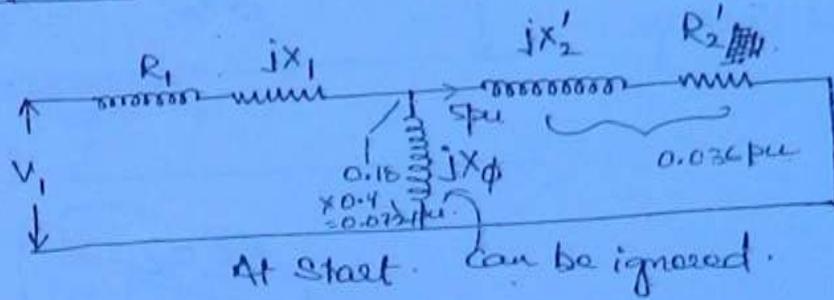

At start

$$T_{fl} = \frac{1}{\omega_m} \times (I_{fl})^2 \times \frac{R_2'}{S_{fl}}$$

$$T_s = \frac{1}{\omega_m} \frac{I_s^2 \times R_2'}{(1-a)}$$

$$\left[\frac{T_s}{T_{fl}} = \left(\frac{I_s}{I_{fl}} \right)^2 \times S_{fl} \right]$$

$$(b) I_s = \left(\frac{I_s}{I_{fl}} \right)^2 \times 0.0697$$

$$I_s = 4.64 (\text{pu})$$

$$\text{After } \frac{I_s}{I_{fl}}$$

$$P_{fl} = \frac{V_1}{(R_2'/S_{fl})} \quad S_{fl} \frac{V_1}{R_2'}$$

$$I_s = \frac{V_1}{R_2'} \rightarrow \frac{I_s}{I_{fl}} = \frac{R_2'/X_2'}{C_{eq}} = \frac{S_{fl \max}}{S_{fl \min}} \Rightarrow \left| \frac{P_s}{P_{fl}} = \frac{S_{fl \max}}{S_{fl \min}} \right|$$


DOL (Direct ON line) \rightarrow Starting of D.M.

$$I_{sc} \triangleq \frac{V_L}{Z_{sc}}$$

When V_L = Rated Voltage.

$$I_S = \frac{V_L}{Z_{sc}}$$


$$\Rightarrow I_S = I_{sc}$$

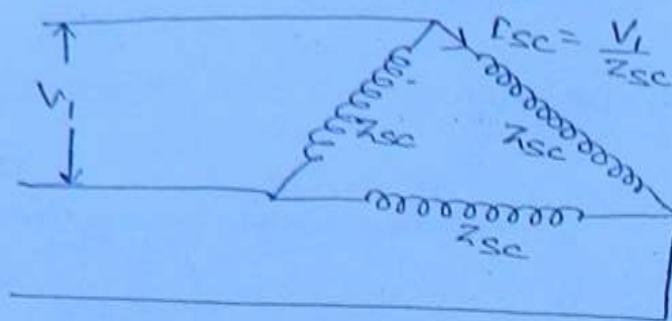

(302)

$$\frac{T_S(DOL\Delta)}{T_{fe}} = \left[\frac{I_S(DOL\Delta)}{I_{fe}} \right]^2 \times S_{fe}$$
$$= \left(\frac{I_{sc}}{I_{fe}} \right)^2 \times S_{fe}$$

Reduced Voltage Starting : \rightarrow

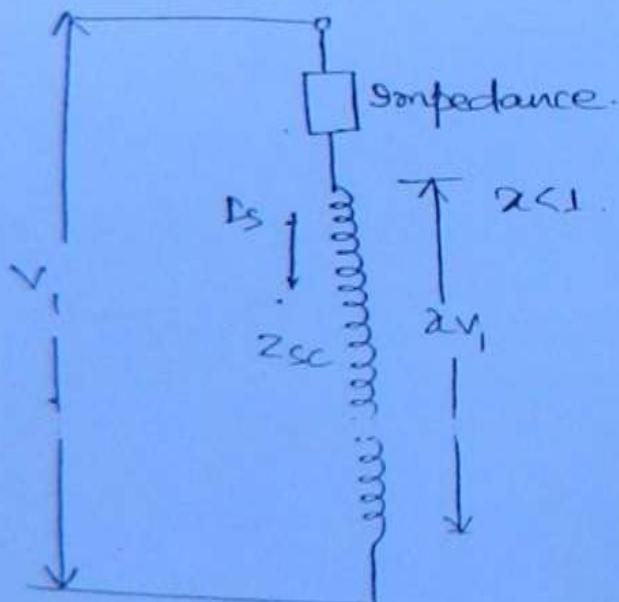

$$I_s = \frac{x v_1}{Z_{sc}}$$

$$\boxed{I_s = x I_{sc}}$$

$$\frac{T_s}{T_{fl}} = \frac{\Gamma_s^2}{\Gamma_{fl}^2} \times S_{fl}$$

$$= \left(\frac{x I_{sc}}{\Gamma_{fl}} \right)^2 \times S_{fl}$$

$$= x^2 \left(\frac{\Gamma_{sc}}{\Gamma_{fl}} \right)^2 \times S_{fl}$$

$$\Rightarrow \boxed{T_s = x^2 T_s (\text{DOL})}$$


(Ans)

Impedance starting

→ Resistance start

→ Inductance or Reactance start

Auto x-mer start →

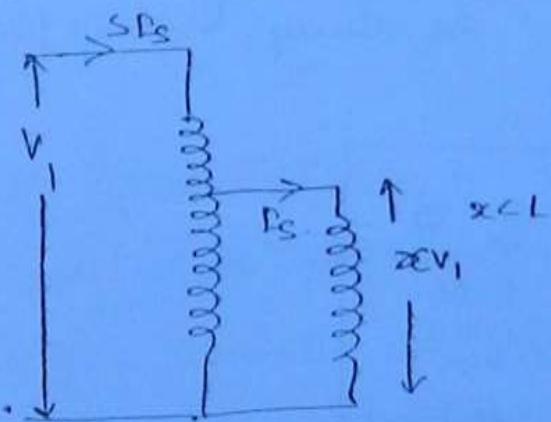

$$I_s (\text{line}) > x I_s$$

$$\boxed{I_{s\text{line}} = x^2 I_{sc}}$$

$$\frac{T_s}{T_{fl}} = \left(\frac{x I_{sc}}{\Gamma_{fl}} \right)^2 \times S_{fl} \propto \boxed{T_s = x^2 T_s (\text{DOL})}$$

Star Delta Starting

$$\frac{I_s(l-\Delta)}{I_s(\text{line } \Delta)} = \frac{1}{3}$$

$$I_s(l-\Delta) = \frac{I_{sc}}{\sqrt{3}}$$

Box

$$\frac{T_s}{T_{fl}} = \frac{1}{3} \left[\frac{D_{sc}/\sqrt{3}}{Z_{fl}} \right]^2 \times \eta_{fl}$$

$\rightarrow T_s = \frac{1}{3} T_s (\Delta \text{ or } \Delta)$

This means that Star Delta starting is equivalent to auto star starting with $X = \frac{1}{\sqrt{3}}$


32/12/12

CIRCLE DIAGRAM :-


Data to be obtained from No load test and blocked rotor test →

w, always leading phase

No load test :-

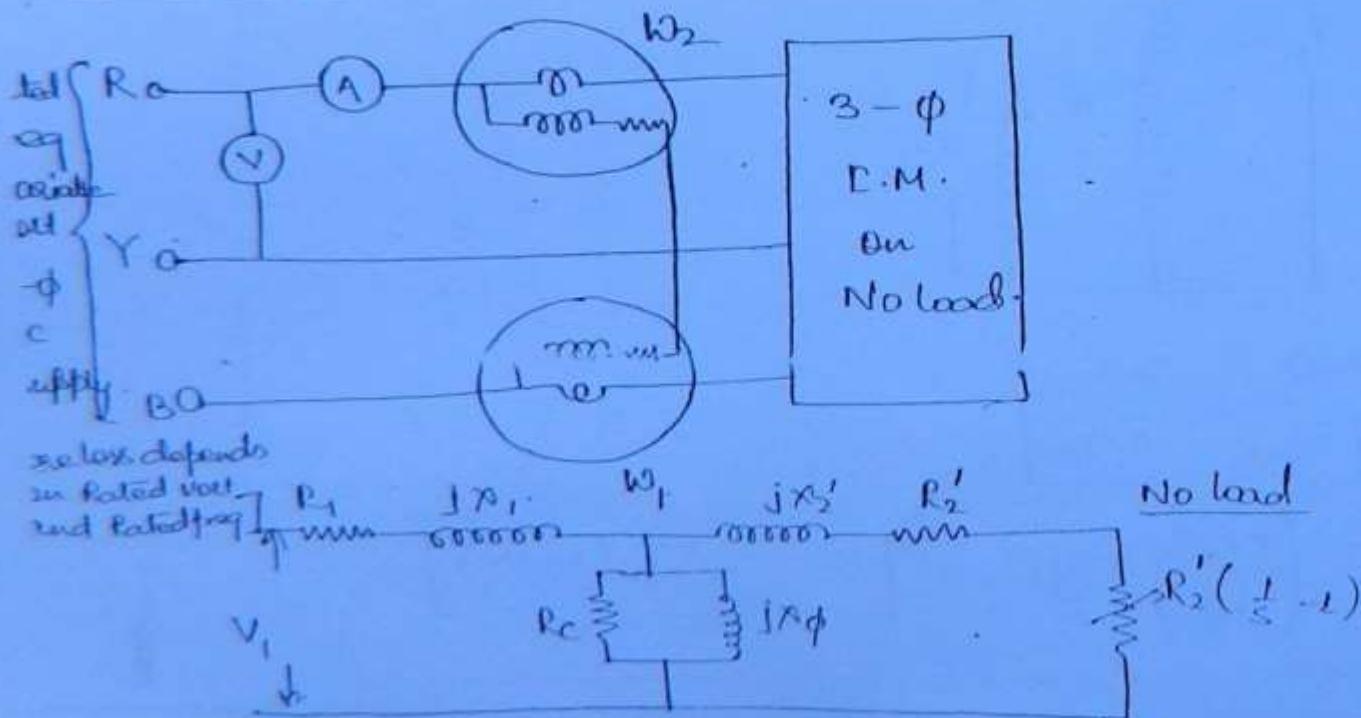

At No load, $S = 0$.

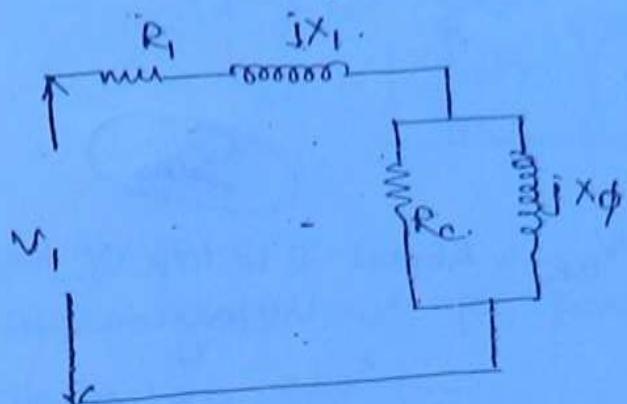

(SOS)


drop in $R_c \rightarrow$ ignored
as $0.036 \times 0.4 = 0.0144$
 $= 1.4\%$ off

V_o , I_o , P_o .

$$P_o \rightarrow (I_1^2 + I_2^2) - I_o^2 R_1$$

$I_o \rightarrow$ No load current

$V_o \rightarrow$ Rated voltage


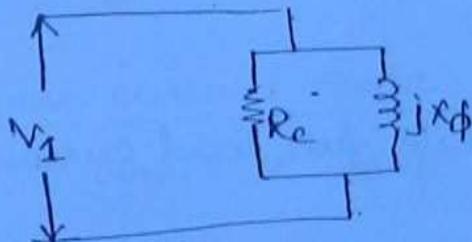


LPT wattmeter is used.


BLOCKED ROTOR TEST →

3- ϕ D.M. with rotor blocked

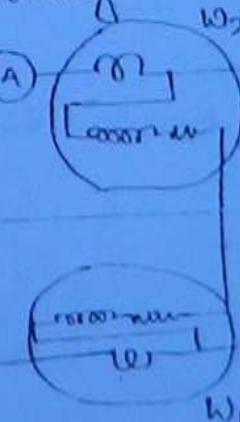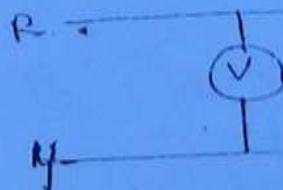Rated freq variable Voltage 3- ϕ AC supply



3- ϕ
P.M.
with
rotor
Blocked

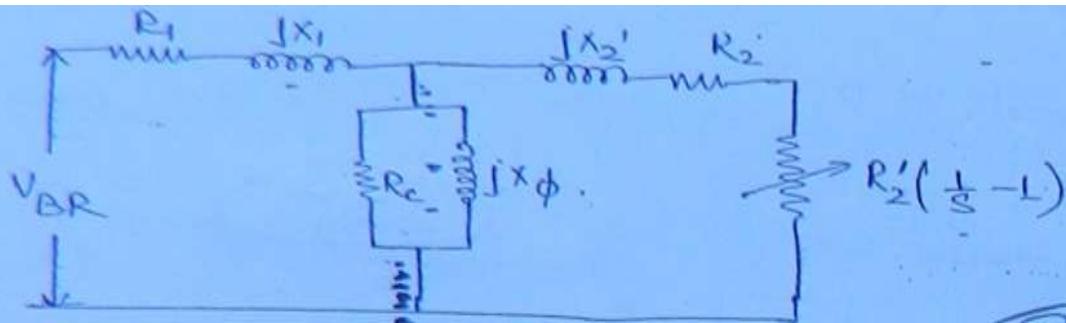


Rotor Blocked
 $S=1$

$V_{BR} \rightarrow$ Almost 8 to 10% of rated Voltage.

(Bob)

terminal short circuited

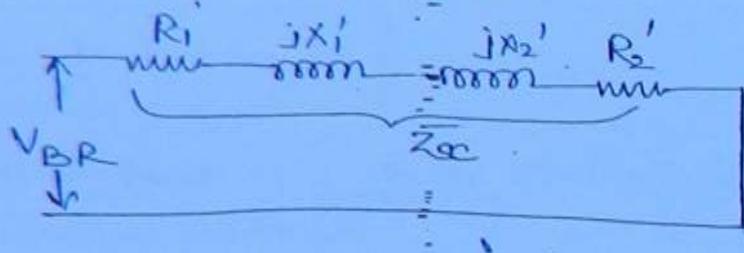

$$V_{BR} > P_{BR} > P_{BR} = \omega_1 + \dot{\omega}_2$$

P_{BR} = full load cu loss

I_{BR} = full load current

V_{BR} = I/P voltage required to circulate full load current with Rotor Blocked.

$$Z_{SC} = \frac{V_{BR}}{P_{BR}} \left[\cos^{-1} \frac{P_{BR}}{V_{BR} I_{BR}} \right]$$

Change \rightarrow

V_{BR} \rightarrow $-$ Arched

$P_{BR} \rightarrow I_{SC}$

$P_{BR} \rightarrow P_{SC}$

Since $Z_{SC} = \text{const}$

Inverted \rightarrow

$\left. \begin{array}{l} \\ \end{array} \right\} \rightarrow \text{for circle diagram}$


$$I_{SC} = I_{BR} \times \frac{V_{rated}}{V_{BR}}$$

$$P_{SC} = P_{BR} \times \left(\frac{\frac{V_{rated}}{V_{rated}}}{\frac{V_{rated}}{V_{BR}}} \right)^2$$

(Pop)

circle diagram →

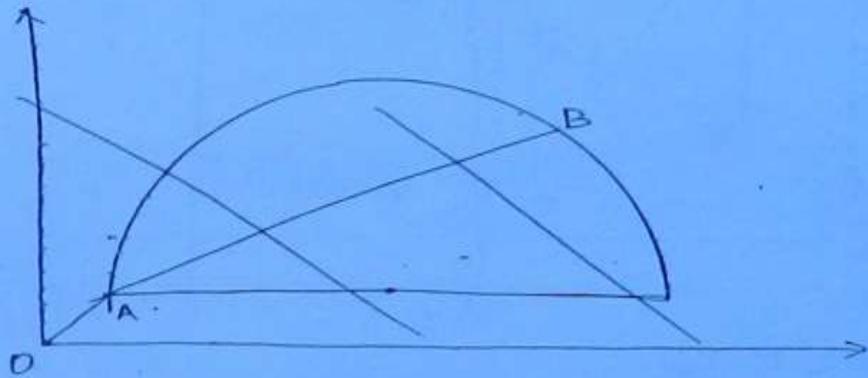An approximate tool for performance prediction using
Cantilever eq. CRF :-



choose current scale :-

$$1 \text{ cm} = x \text{ Amp}$$

The power cycle is

$$1 \text{ cm} = x \times V_{rated} \text{ VA}$$

$$OA \equiv I_0$$

$$\phi_0 = \cos^{-1} \frac{P_0}{V_0 I_0}$$

$$\phi_{SC} = \cos^{-1} \left[\frac{P_{SC}}{V_{SC} I_{SC}} \right]$$

$$= \cos^{-1} \left[\frac{P_{BR}}{V_{BR} I_{BR}} \right]$$

$$OB \equiv I_{SC} \text{ i.e. } I_i \text{ at } S=1$$


No load,

$$S=0$$

stand still,

$$S=1$$

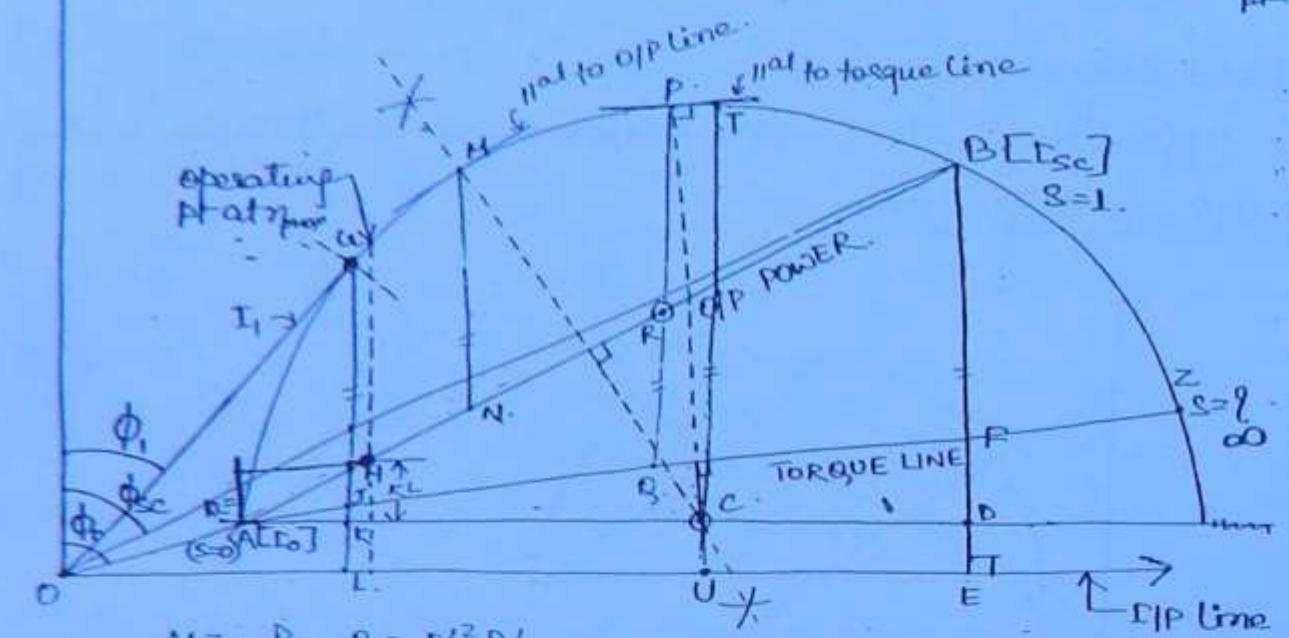For operating pt location,
 take r_1 as radius and
 cut it on half semicircle.
 Pt will be operating pt. Here as
 operating pt



$$\text{At } z, \quad P_g = D + E_2'^2 \frac{R_2'}{S}$$

When $\Gamma_2' = 0$, $S = \infty$

$$AB = \Sigma_2^1 \text{ at } S=1$$

At $S=1$,

$$BE = D/P \text{ power [total loss]}$$

$$DE = \text{fixed losses}$$

BD = total Cu loss

$$\text{Circle diameter} = \sqrt{\text{rated}} \\ [\text{unaffected by the value of } k_2] \quad x_1 + x_2'$$

Br = states cu loss

61 = Range en long.

$$T_s = \frac{BF}{W_{cm}} = \frac{P_g}{W_{cm}}$$

$OC = \text{dia}$.
make circle,
where it touches the semicircle
that it is for map pf.

above torque line,

Get values of line repre
motor E/P

Here $S=1$.

also, $\Delta f = \sin(\omega t)$

When $\mathcal{L} = 1 \rightarrow$ Unstable fit

near $S=0$ → Stable if

$$\frac{R_{ext}}{R_2} = \frac{PR}{RB_1} \text{ for } T_{max} \text{ at } \\ \text{start}$$

At some operating pt \rightarrow

$$G_L = \text{E/I/P Power}$$

$$K_L = \text{Fixed losses}$$

$$I_K = \text{Stator core loss}$$

$$H_I = \text{Rotor core loss}$$

$$G_H = \text{O/I/P power}$$

$$J_{Lr} = \text{Rotor E/I/P or } P_g$$

(309)

on power scale.

On current scale

$$O_{Lr} = \text{E/I/P current } \bar{I}_1$$

~~Slips~~


As performance Index of running D.M. : \rightarrow

$$\text{Slip } S = \frac{H_I}{J_{Lr}}$$


$$\text{Eff. } \eta = \frac{G_H}{G_L}$$

$$\text{E/I/P power factor} = \frac{G_L}{O_{Lr}}$$


Known
E/I/P pf

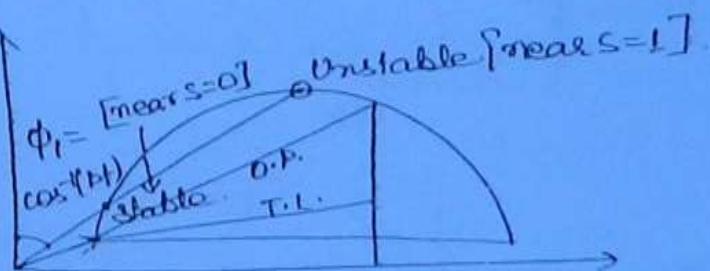


Known O/I/P power \rightarrow

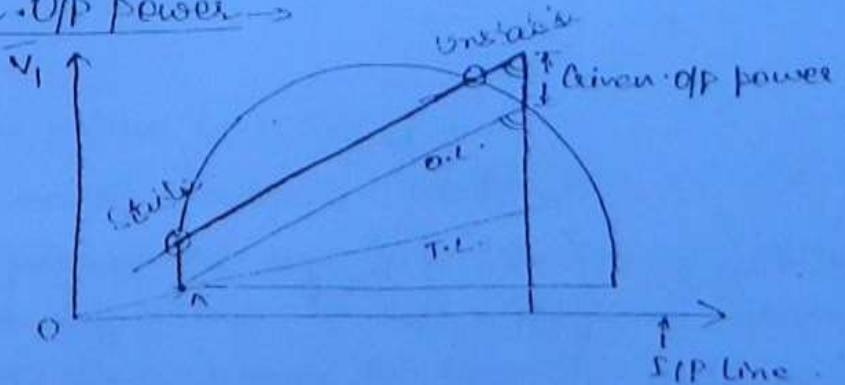

Known torque

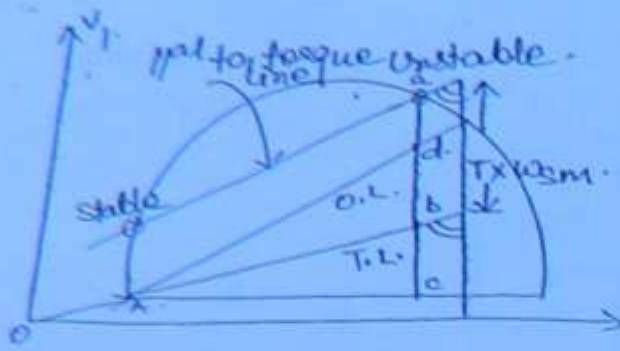


(B10)

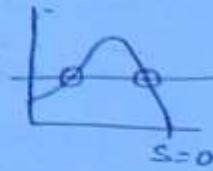

Given torque at start

$$\frac{R_{ext}}{R_2} = \frac{ad}{dc}$$

Known Slip - location of operating pt

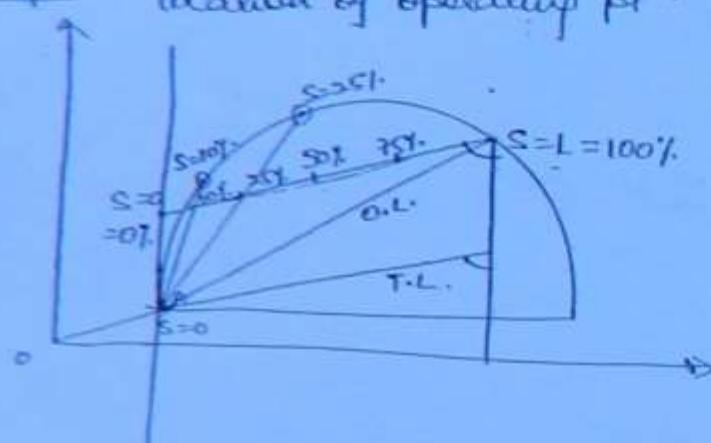

(D1)



Magnet O/P →

$$MN = M_{magnet} O/P$$

$$PQ = T_{magnet} \times w_{sm}$$

$$T_{magnet} = \frac{PQ}{w_{sm}}$$

$$TU = M_{magnet} E/P$$

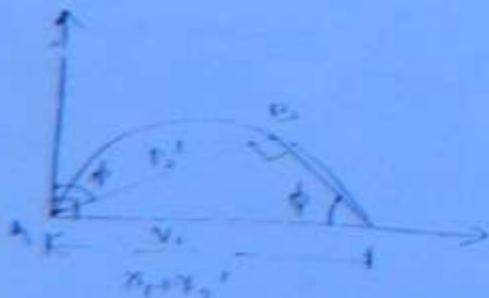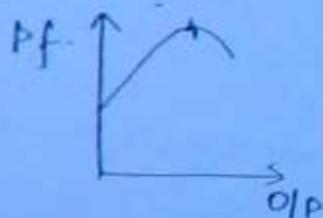

$$I_2' = \frac{V_1}{Z_2}$$

$$= \frac{V_1 \sin \phi}{Z_2 \sin \phi}$$

$$= \left(\frac{V_1}{Z_2} \right) \sin \phi$$


Braking Of 3 ϕ D.M.C. :-

1) Regenerative braking :-



Plugging :-

load torque always opposes
the motion irrespective of
m/c


(31)

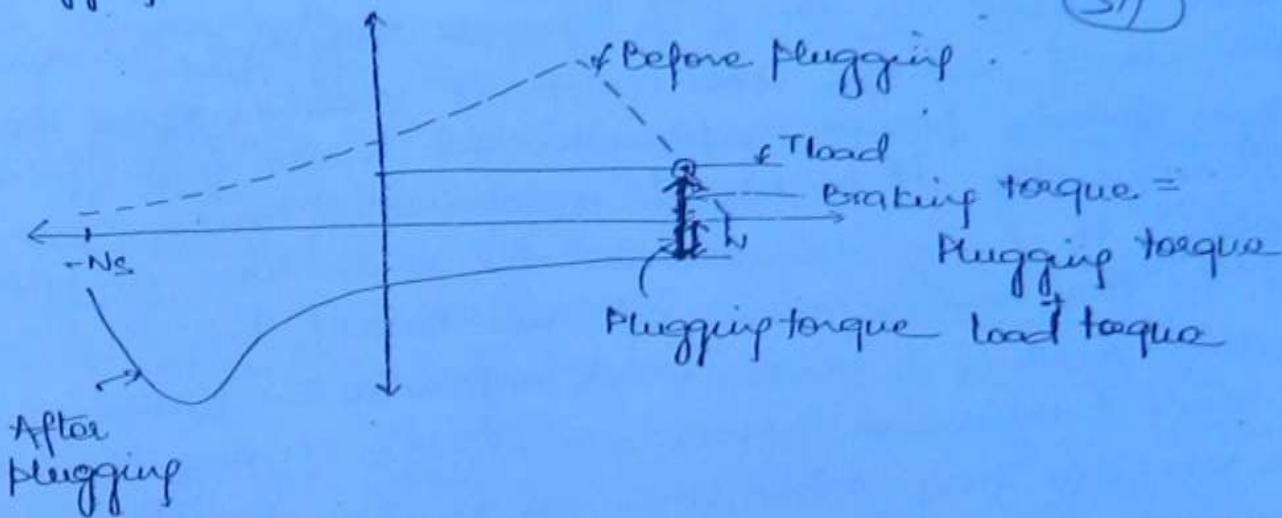

Rheostatic or dynamic braking :-

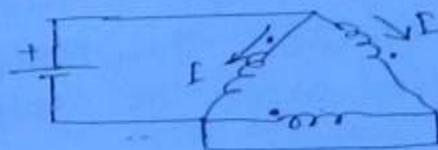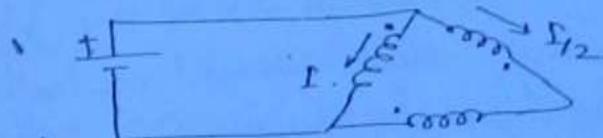

less jerk. compare to above

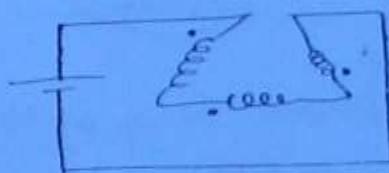

best suited immediately to
rest

1) Regenerative braking :-

This form of braking is possible in stator fed D.M.C. If the no. of poles of the m/c can be changed during running condition by using special switching arrangement. Obviously therefore this would be possible only in squirrel cage D.M.

thus when braking is arrested, the pole no. is increased by a factor of 2. Synchronous speed of revolving field thus become half and therefore the P.M. goes into generating mode as the slip becomes negative. Consequently the speed reduces and when it reaches near the new syn. speed, power supply to the motor is switched off. Subsequently, if required, mechanical braking may be applied to bring the motor to rest. Since el. pow. is fed to the motor mains - at the loss of K.E. to the motor, this method is known as regenerative braking. With much progress in power electronics during the last decade, variable freq. drive are available for I.M of squirrel cage type as well as for slip ring type. Therefore even if the no. of poles remains unchanged, the freq. of supply can be reduced keeping (V) constant to avoid overflusing. This would reduce the syn speed causing regenerative braking as explained above. Thus with variable freq. supplies regenerative braking would be possible to almost standstill and would be applicable to squirrel cage as well as slip ring I.M.

Plugging →

(BJD)

With this form of braking, the phase seq. of stator supply is reversed by interchanging the supply to any two of the motor terminals. This causes a reversal in the direction of the revolving field and therefore the present dir. of rotation is seen by new field at a slip greater than 1. Thus the electromagnetic torque developed by motor now becomes the w.r.t. current dir. of motor rotation. This negative torque called plugging torque together with load torque, may has a braking effect on the rotor than me.

the present forward speed. As the speed reduces, plugging torque and therefore braking torque goes on increasing acc. to standard torque speed char. And thus the red. in speed becomes rapid. When the motor comes to rest, supply to the motor is switched off to prevent its running in the reverse dir.

During plugging, electrical power is taken from the motor and at the same time, mech. power is extracted from the stored k.E. of the rotor. Thus the sum of these two powers is dissipated as heat mainly in the rotor of M.C. Adequate protection must be provided to ensure that the motor not get overheated to the extent of getting permanently damage



(B1B)

DYNAMIC BRAKING:-




Supply to the motor is switched off and immediately thereafter the stator wdg is connected across dc supply of appropriate volt. If coil's stationary M.T. is in the air gap and its presence the moving rotor core and conductors developed induced current which acc to lenz's law oppose motion. This is known as dynamic braking and is similar to eddy current braking. The interconnection of diff. stator coils may be arranged in a no. of ways and the no. of switches to be used would vary accordingly

All methods to start slip ring motors and squirrel cage motors are same.

for slip ring motor.

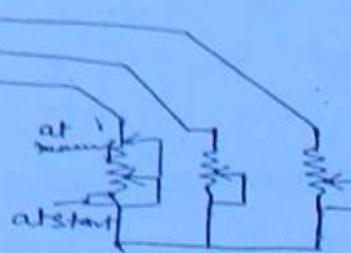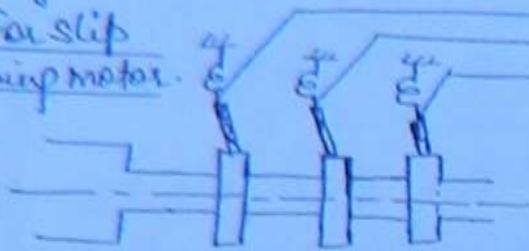

314

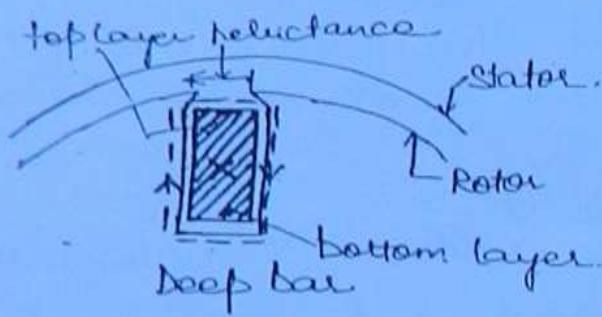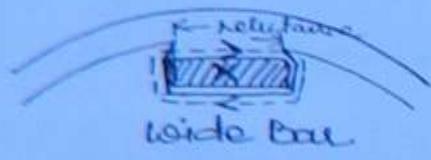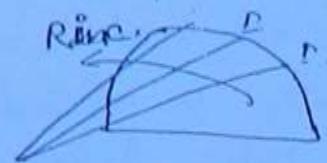

airgap path ↑, reluctance ↑,
mf → same.


$$\phi \propto \frac{1}{\text{resistance}}$$

$$\text{Internal } \eta = 1 - s$$

reluctance in wide bar is high.

$$\therefore \phi_{\text{wide bar}} < \phi_{\text{deep bar}}$$
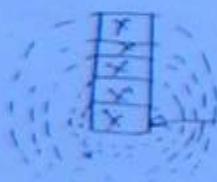
$$X_L \text{ wide bar} < X_L \text{ deep bar}$$




bottom layer has max flux linkage.
as constraint to ...


I_a will feel max opp. in bottom layer.

Double cage Rotor :-

(BIS)

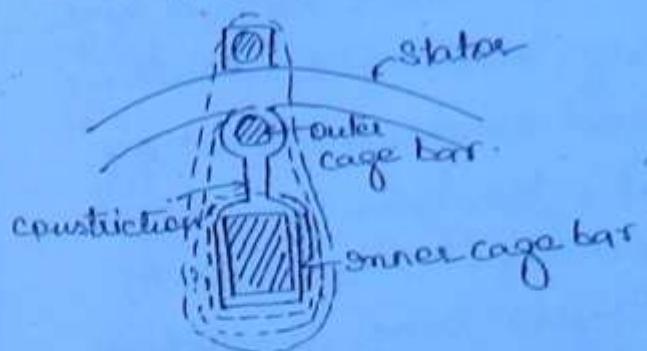

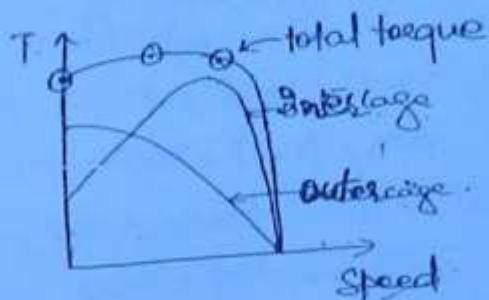constriction is necessary
for the flux linkage of stator
with inner cage bar.



for high starting torque,
this is used. high efficient,
better Pf

Deep bar and double cage rotor :-

Slip Ring I.M. have the provision of an extra insertion ^{part} resistor as the rotor wdg is brought to the slip rings. Insertion of extra resistance reduces their starting current and inc. their starting torque. Unfortunately no such provision is available in squirrel cage I.M. Thus to reduce starting current and to inc. starting torque in squirrel cage I.M., special design rotors have to be used. One of them is the deep bar rotor.


The deep bar rotor consists of narrow but deep slots that accommodate deep rotor bars. The leakage flux linkage of the bottom layer is max and goes on decreasing as one moves towards the upper layer. Thus the top layer of the rotor bar has min leakage reactance while the bottom layer has max. When the motor is started, the rotor freq is equal to the stator freq and at this freq, the lower layer oppose the flow of rotor current as a result of which rotor current is pushed towards the upper layers. Hence the available conductor \times section

For the flow of rotor current is reduced at the time of start. In other words, the motor starts with a high rotor resistance and $\frac{V}{f}$ leakage reactance resulting in reduced starting current and increased starting torque. As the speed picks up, the rotor freq starts reducing and hence the opposition to the flow of rotor current by the lower layers starts receding (gradual slow down). The rotor current therefore starts flowing in the lower layers as well and at normal speed when the rotor freq. is very low, rotor current becomes almost uniformly distributed throughout the layers of rotor bars resulting in improved operating.

(3/6)

The other special design rotor to obtain the desired starting properties is the double cage rotor. As the name suggest two separate cages independent from each other are used. The outer cage consists of small x-sections and therefore has higher bar and cage resistance. The inner cage consists of normal x-section bars separated from outer bars by a small constriction in the slot. It is shown in the fig. The inner cage bars have higher cage flux linkage than the bars than the outer cage bar. In other words, leakage reactance of the inner cage is higher than the leakage reactance of the outer cage. Thus when the motor is started the rotor freq is high and inner cage offers high opposition to the flow of rotor current. Consequently, the rotor current is pushed towards the outer cage and encounters high resistance but low reactance resulting in reduced starting current and increased starting torque. As the speed picks, the rotor freq. starts reducing bypassing the inner cage when the effect of rotor current by the

$S \rightarrow -ive$, Supersyn. speed.

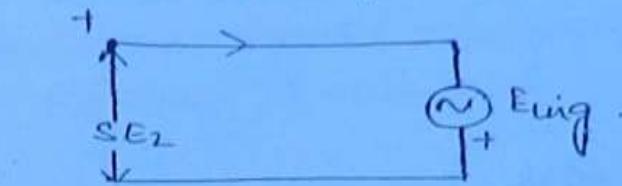

(B12)

$$S E_2 = -E_{inj}$$

$$\boxed{S = -\frac{E_{inj}}{E_2}}$$

→ SCHRADE MOTOR.

$\omega \uparrow$ as motor even in -ive slip.

as SE_2 and E_{inj} both are source for rotor rotation so $\omega \uparrow$.

24/12/11

VVF control

i) speed control below base speed :

$$\frac{v}{f} = \text{const} \quad f < f_{base}$$

2) speed control above base speed

$$v = \text{const} \quad f > f_{base}$$

$$1) T_{max} = \frac{1}{2\omega_m} \times \frac{V_r^2}{X'_2}$$

$$2) S_{T_{max}} = \frac{R'_2}{X'_2}$$

$$3) N_s - N = SN_s$$

$$4) \tan \phi_2 = \frac{S X'_2}{R'_2}$$

$$\Rightarrow \phi_2 = \tan^{-1} \left(\frac{S X'_2}{R'_2} \right)$$

A) $0 < s \leq s_{T_{\max}}$

$$E_2' = \frac{sv_1}{R_2'}$$

$$T = \frac{1}{\omega_{SM}} \frac{sv_1^2}{R_2'}$$

B) $s > s_{T_{\max}}$

$$E_2' = \frac{v_1}{x_2'}$$

$$T = \frac{1}{\omega_{SM}} \frac{v_1^2}{x_2'} \times \frac{R_2'}{s}$$

(318)

i) speed control below base speed : $\rightarrow \frac{v}{f} \rightarrow \text{const}$
 $v \propto f$

$$T_{\max} \propto \frac{1}{f} \times \frac{f^2}{f}$$

$\propto 1$

$$T_{\max} = \text{const}$$

$$s_{T_{\max}} \propto \frac{1}{f}$$

$$N_S - N \propto sf$$

$$\tan \phi_2 \propto sf$$


A) $0 < s \leq s_{T_{\max}}$

$$I_2' \propto sf, I \propto \frac{1}{f} \times sf^2 \\ \propto sf$$

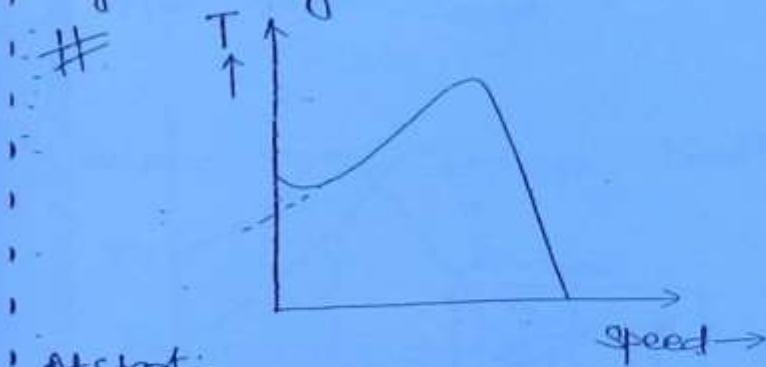B) $s > s_{T_{\max}}$

$$I_2' \propto \frac{f}{s} = \text{const}$$

freq. becomes very low and the rotor current becomes non-distributed resulting in high operating η . The presence of the narrow constriction in the rotor slot is necessary; otherwise with a completely closed slot of inner cage stator flux would completely flux miss linking the inner cage making it redundant.



3/9

At start:

Motor freq 1, current upper layer ↑, eff res ↑, starting torque ↑,
As speed continues to inc, it will have its own char.

Speed control of 3-d T.M.: →

$$N = N_s(1-s)$$

$$= \frac{120f}{P}(1-s)$$

f → Line freq control [vvvf] control


P → By pole changing

s → By slip control

→ By Voltage control [Applicable to SCIM & SRIM]

→ By Rotor resistance control [Applicable]

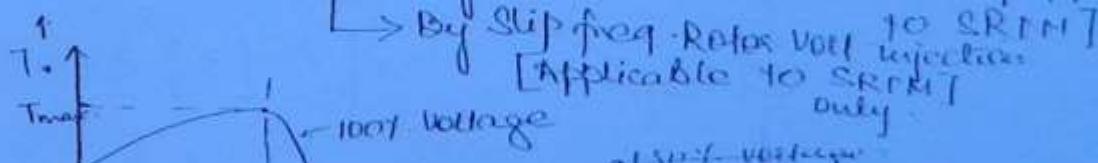→ By Slip freq. Rotor Volt. injection [Applicable to SRIM only]




at 50% voltage

SRIM → Slip ring PM
SCIM → Small capacity
I.H

$$T_{max} = \frac{1}{625m} \times \frac{V_1^2}{R_2}$$

$$S_{T\max} = \frac{R_2'}{X_2'}$$
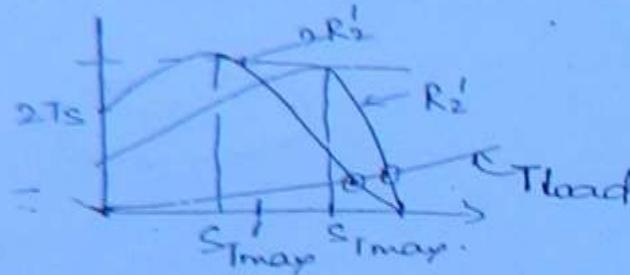
$$T_S = \frac{1}{W_{SM}} \cdot \frac{M_1^2}{X_2'^2} \times R_2'$$




320

$$S_{T\max}' = S_{T\max} \times 2$$

$$\eta = \frac{1-S}{1+S}$$


Applicable to low D.M. only as η becomes low.
Not for large D.M.

freq
Rotors eq. D.C. \rightarrow

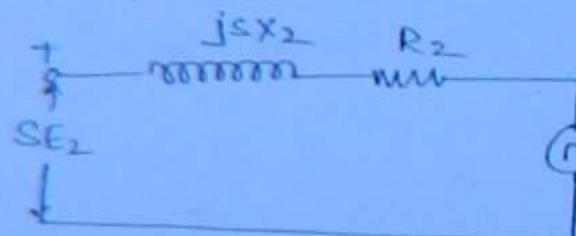

E_mf = same freq as slip freq.

On running condition, $S = 2\gamma$.

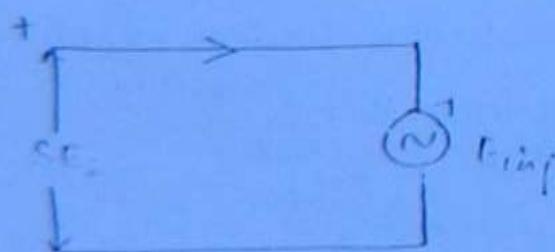


$$SE_2 = E_mf$$

$$\gamma S = \frac{E_mf}{E_2} \quad \therefore \omega \downarrow$$

$$S_{T\max} = \frac{R_2'}{X_2'}$$
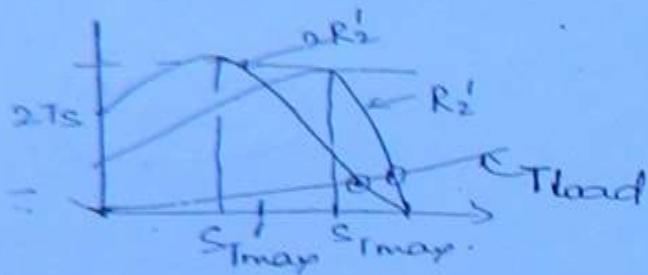
$$T_S = \frac{1}{W_S M} \cdot \frac{M^2}{X_2'^2} \times R_2'$$




320


$$\boxed{S_1' \max = S_{T\max} \times 2} \quad \boxed{\eta = \frac{1-s}{1+s}}$$

Applicable to low I.M. only as η becomes low.
Not for large I.M.

for
Rotating eq. D.C.T. \rightarrow

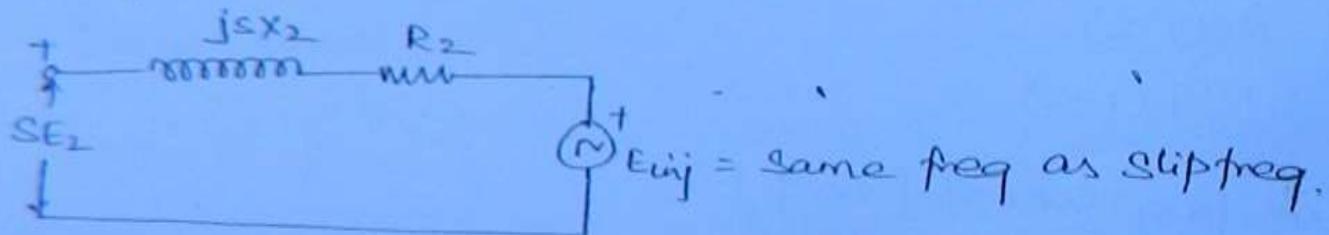

On running condition, $s = 2\%$.

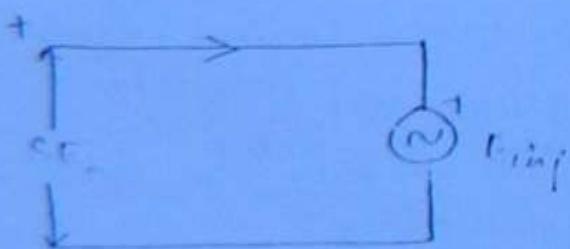

$$SE_2 = E_{1\text{inf}}$$

$$2s = \frac{E_{1\text{inf}}}{L_2} \therefore \omega \downarrow$$

A) $0 < S \leq S_{T\max}$

$$T_2' \propto S, T \propto \frac{S}{f}$$


B) $S > S_{T\max}$

$$T_2' \propto \frac{1}{f}$$

$$T \propto \frac{1}{f} \times \frac{1}{f^2} \times \frac{1}{S}$$

$$\propto \frac{1}{Sf^3}$$

(322)

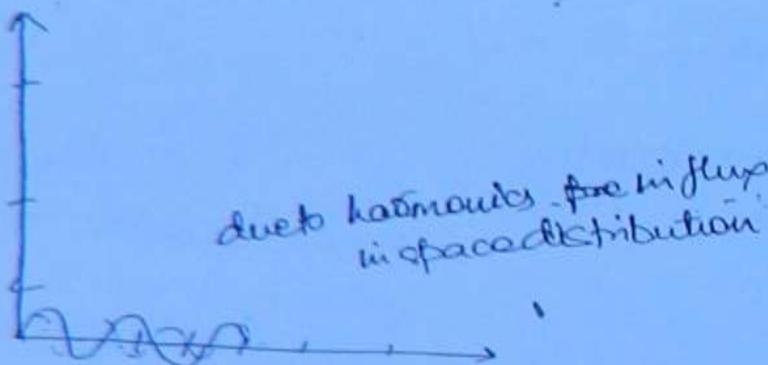

distributing space $\&$ harmonics:-

$6n \pm 1$

at $n=1$,

$$6-1 = 5$$

$$6+1 = 7$$

$$N_S(5) = \frac{1500}{5} : 300 \text{ rpm}$$

[-ive seq]

From other harmonics, $3n120 = 600 - 600 - 360 = 240 \therefore -\text{ive seq}$

$$N_S(7) = \frac{1500}{7} : 214.3 \text{ rpm}$$

[The seq]

[for 7th harmonics, $7n120 = 840 : 120 \therefore +\text{the seq}$]

for 4 pole m/c :-

$$5 \times 4 = 20 \text{ pole}$$


$$7 \times 4 = 28 \text{ pole}$$

even harmonics are absent due to symmetry.

triplet harmonics does not produce any torque as.

3n harmonics are 0° phase distribution $[3 \times 120 = 360 = 0^\circ]$

CRAWLING :-

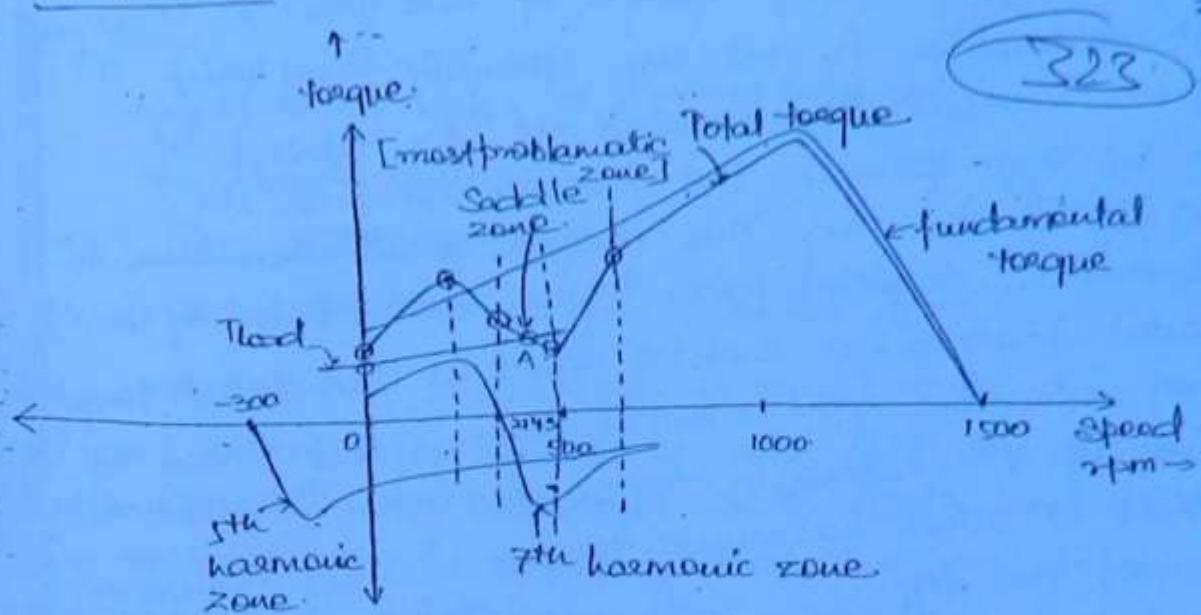

$$\frac{Id\omega}{dt} = T_e - T_{load}$$

At pt A, $T_e = T_{load}$, if motor reaches here slowly then it will remain in pt A and continue to run at a value ω nearly equal to 'I' give rise to low η , high losses etc.

if at no load, Motor is started it will cross the saddle zone

But in many cases, load cannot be removed as it is directly coupled with motor then try to suppress 7th harmonics.

In Synchronous I.M., this problem is not seen as startup torque is high.

The air gap flux in a 3 ϕ I.M. contains, in addition to the fundamental flux wave, space harmonics and out of these $6n+1$ harmonics i.e. non-triplet odd harmonics affect the operation of the I.M. particularly during starting.

Moreover the 5th and 7th space harmonics are of more concern as these amplitude is considerable. 5th space harmonics flux revolves at 5 times sheet or fundamental

syn. speed. The dir. of rotation of this flux is reversed as 5th harmonic is the seq. quantity similarly the space harmonic flux revolves at $\frac{1}{7}$ th speed of fundamental syn. speed in the forward dir. as 7th harmonic is of the seq. The torque speed char due to these harmonics together with torque speed char of the fundamental produce a saddle effect in the total torque speed char. near the 7th harmonic syn. speed. Since the contribution of 7th harmonic torque is more pronounced it compares to other harmonic torque in this region as shown in the fig.

(324)

As the motor is started, acc² torque may be low with the given load torque. The acc therefore would be slow and if the load torque char intersects the saddle point in the negative slope region, the motor become stuck in at a very low speed around the syn. speed of 7th space harmonic, a phenomenon known as crawling. or eg. in a 4 pole, 50 Hz, I.M.

Crawling may take place around 214.3 rpm as shown in fig. During crawling the slip is very high, current very high, losses very high and of very low. Consequently the motor continue to overheat during crawling and may get permanently damage. This phenomenon of crawling is not encountered in slipping I.M as its high starting torque accelerates it rapidly through the saddle point. The prevention against crawling involves reduction in space harmonics by proper selection of no. of stator slots w.r.t. the no. of rotor slots and also by proper distribution and shading of the stator w.r.t. together with measures to increase overall starting torque. Crawling may also be avoided by starting the I.M. on no load, if possible and applying the load when the motor runs. i.e.,

State no load speed

Cogging: →

$$\text{No. of stator slots} = n \times \text{no. of rotor slots}$$

$n \rightarrow$ integral multiple

Avoid this arrangement

325

Skew the rotor slots, cogging avoided.

When the no. of stator slots is equal to or n is an integral multiple of the no. of rotor slots, the alignment forces b/w 1st rotor teeth and stator teeth and at the time of start may be so strong that they may prevent the movement of the rotor. This phenomenon is known as cogging prevention of cogging is possible by avoiding such design and by skewing either the stator slots or rotor slots. This naturally skews the respective teeth as well. However because of practical considerations Rotor teeth instead of stator teeth are skewed and skewing the rotor teeth usually by one slot pitch is sufficient to prevent cogging.

If harmonics in current in time distribution,

$\frac{P_{max}}{P_{avg}}$

No effect in torque.

$n \times$ harmonic

If 7th harmonic flux speed created by 7th harmonic
 $= 2143$

AC Series motor → Universal motor.



(open slot)

& lowest τ_2 .

large airgap


is max. lowest Pf.

airgap max

→ reluctance ↑

$B_d = \text{max} \uparrow \text{current}$

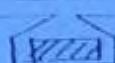$I_d \rightarrow \text{more}, \tau_2 \rightarrow \text{less}$



Semi-closed

slot

(moderate τ_2)

moderate airgap

moderate pf



Closed slot

highest τ_2

airgap

is min.

Highest Pf

$P_f = \frac{P}{\omega}$ increases.

\Rightarrow If AC given in DC Shunt motor

\therefore f.d. and \uparrow , If lag nearly 90° , torque very less.
So, started with less torque.

Domestic \rightarrow L- ϕ series motor
application due to very high starting torque

(326)

AC Sectors \rightarrow Reluctance motor

Hysteresis Motor

Single Phase I.M.: \rightarrow


(2)

$\downarrow \uparrow \phi$ we can see that
 $\downarrow \phi_{\text{par}}$ angle b/w ϕ and
 ϕ_{air} is 180° . Hence
no starting torque is
produced!

\Downarrow 1 ϕ supply creates a stator
mag ϕ as shown in the fig. As
the rotor is sheeted. Hence
current must induce in the
rotor conductors which
opposes the flux by
Lenz's law. Then by applying
right hand thumb rule,
it is of current in rotor
conductors can be found
out. Now applying Fleming's
left hand rule or left hand palm
rule we can find out the motion
of each conductor & here we
can see that the motion of both
conductors are opposite to each other.


Hence 1 ϕ I.M. has no self-starting torque

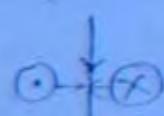Rotating f.d. :— which revolves in
sinusoidal in space but
changes the value w.r.t. time




Not Self Started

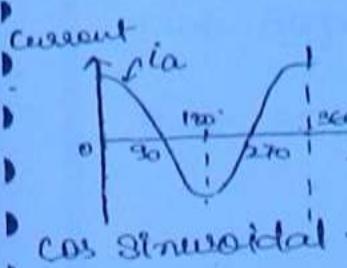Explained by double revolving f.d. theory





327

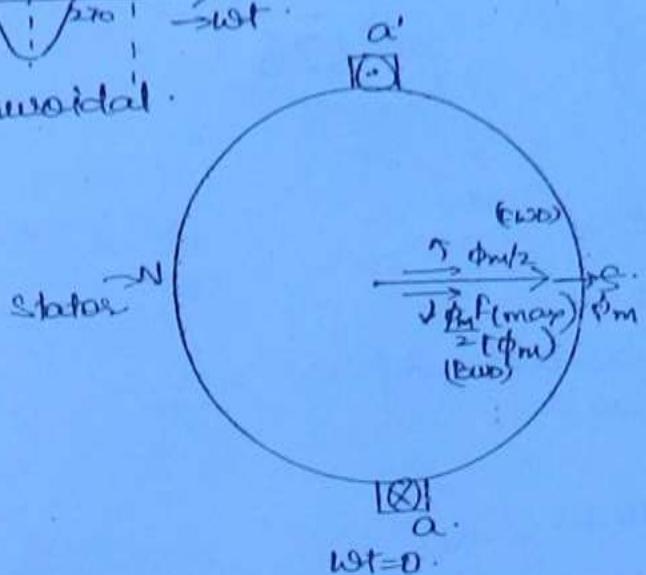


By eq 2 (1).

five M-axes of $a a'$

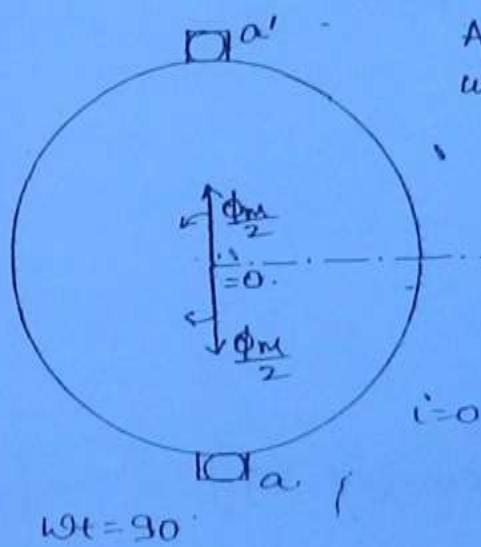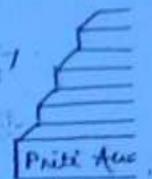

As $i_a = 0$, Hence dir² of sense in conductor is not shown.

Resultant = 0.

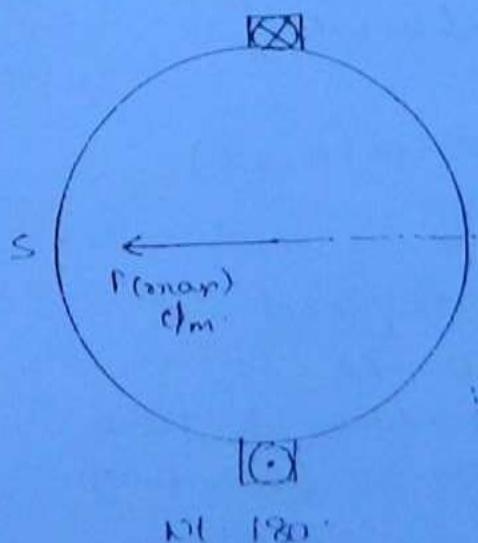

five M-axes of $a a'$

At $\theta = 0^\circ$,

$$f(\theta) = F_{\text{peak}} = F_{\text{max}} \cos \omega t$$

$$= F_{\text{max}} \left(\frac{e^{j\omega t} + e^{-j\omega t}}{2} \right)$$

$$= \frac{F_{\text{max}} e^{j\omega t}}{2} + \frac{F_{\text{max}} e^{-j\omega t}}{2}$$

\uparrow
Forward mag
wave

\uparrow
Background mag
wave.

328

for uniform reluctance,

$$\phi(\theta) = \frac{\Phi_m}{2} e^{j\omega t} + \frac{\Phi_m}{2} e^{-j\omega t} \quad \text{(i)}$$

\uparrow
Front flux
 \uparrow
Back flux.

At $\theta \neq 0^\circ$,

$$f(\theta) = F_{\text{peak}} \cos \theta \cos \omega t$$

$$= F_{\text{max}} \cos \theta \cos \omega t$$

$$f(\theta) = \frac{F_{\text{max}}}{2} 2 \cos \theta \cos \omega t$$

$$= \frac{F_{\text{max}}}{2} [\cos \theta (\omega t + \theta) + \cos (\omega t - \theta)]$$

$$= \frac{F_{\text{max}}}{2} [\cos (\theta - \omega t) + \cos (\theta + \omega t)]$$

$$= \frac{F_{\text{max}}}{2} \cos (\theta - \omega t) + \frac{F_{\text{max}}}{2} \cos (\theta + \omega t)$$

$\theta - \omega t$
at achieve.
if peak
 $\theta = \omega t$ [forward flux]

\downarrow

Background

$\theta = -\omega t$

θ achieve if peak.
 $\theta = -\omega t$ (back flux)

$$\text{Prob. of up } S = \frac{N_S - N}{N_S} = 1 - \frac{N}{N_S} \quad \text{Part - Prob. having up}$$

$$\text{Prob. of } S_1 = \frac{N_S + N}{N_S} = \frac{N_S - (-N)}{N_S} \quad \text{Part - Prob. having up}$$


$$= 1 + \frac{N}{N_S}$$

329

$$(1-S) = \frac{N}{N_S}$$


$$\begin{aligned} S_1 &= 1 + (1-S) \\ \boxed{S_1 &= 2-S} \end{aligned}$$

Prob. Flux \rightarrow

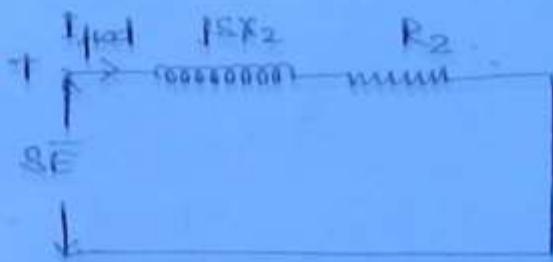


$$\begin{aligned} I_{\text{fout}} &= \frac{S_E}{R_1 + S_E R_2} \\ &= \frac{S_E}{\sqrt{R_1^2 + (S_E R_2)^2}} \quad \left| \tan^{-1}\left(\frac{S_E R_2}{R_1}\right)\right. \\ &\approx \frac{S_E}{\sqrt{R_1^2 + (S_E R_2)^2}} \quad \left| - \tan^{-1}\left(\frac{S_E R_2}{R_1}\right)\right. \end{aligned}$$

Prob. Flux \rightarrow

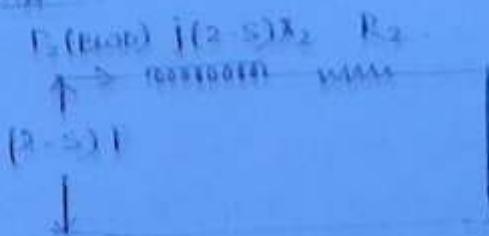

$$\begin{aligned}
 T_2(\text{bwd}) &= \frac{(2-s)E}{R_2 + j(2-s)x_2} \\
 &= \frac{(2-s)E \angle 0^\circ}{\sqrt{R_2^2 + [(2-s)x_2]^2} \angle \tan^{-1} \frac{(2-s)x_2}{R_2}} \\
 &= \frac{(2-s)E}{\sqrt{R_2^2 + [(2-s)x_2]^2}} \angle -\tan^{-1} \frac{(2-s)x_2}{R_2}
 \end{aligned}$$

(330)

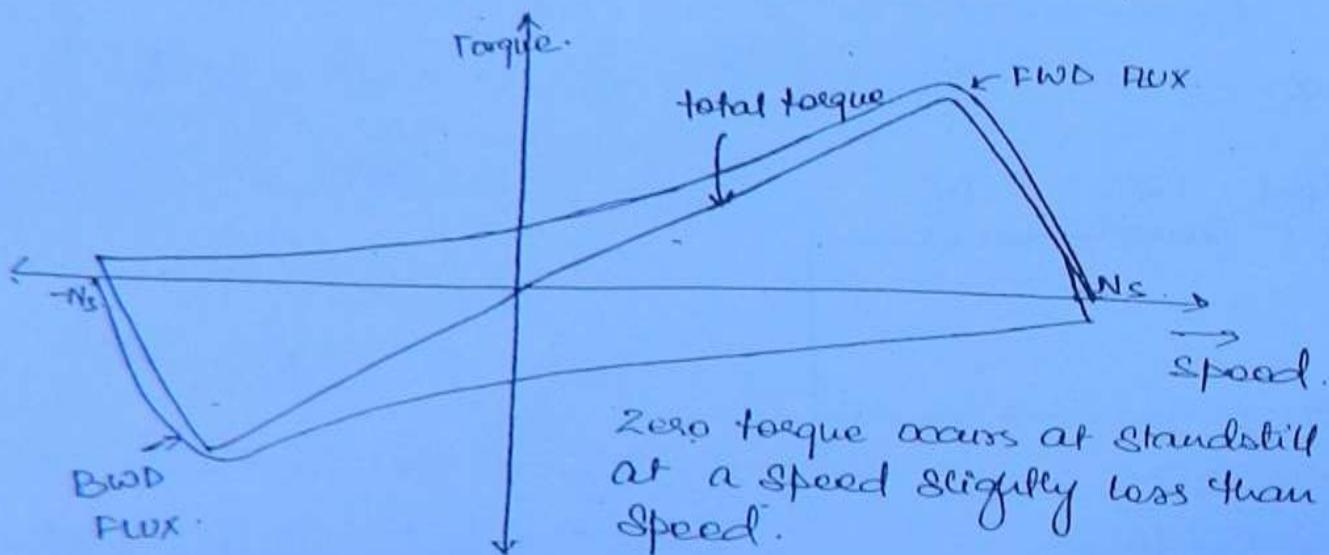

Zero torque occurs at standstill and at a speed slightly less than syn. speed.

Torque does not produce by a single current carrying cond. ictor.

- If there are two cond. with opp./same dir² then it produces attractive/Repulsive torque.
- Torque is produced by the current of one cond. and the flux of other cond.

(Repulsive torque)
By right hand thumb rule

Repulsive torque.
By Fleming's L.H. Rule.

Operation of 1-Φ D.M. acc. to double revolving fld

Theory :-

(331)

Acc. to double revolving fld theory, a sinusoidal pulsating flux can be represented by two revolving flux each having half the amplitude of pulsating flux and rotating in opp. dir²s at syn. speed given by $N_s = \frac{120}{P^2} f$ where f is supply freq. in Hz and P = No. of poles of m/f. At standstill i.e. at time of start, the forward flux and the fact backward flux are equal in magnitude and create equal rotor current at the same pf. Consequently the forward torque at standstill is equal to the back torque resulting in 0 starting torque and therefore the motor fails to start. However if the rotor is given an initial motion in any one dir² by any means then it continues to accelerate in the same dir² till it reaches normal operating speed. This phenomenon can be explained in accordance with the double fld revolving theory.

At any speed N is the so called feld dr², the feld slip $S = \frac{N_s - N}{N_s}$. The back slip therefore = $2 - S$. The rotor current created by the forward flux therefore goes on decreasing as the forward slip decrease with inc. in speed. Also the pf of this current continues to improve as the speed increases. The demagnetising effect of the rotor current on the feld flux therefore goes on decreasing with inc. in speed resulting in a stronger and stronger feld flux.

On the other hand, since the back slip is $2 - S$, the rotor current produced by the back flux contributes to inc. with deteriorating lagging pf, as the speed inc. in the feld dr². This results in opposition to the back flux by its rotor current which goes on inc. as the speed increases making the back flux weaker and weaker as the feld speed continues to inc.

Accordingly therefore, the forward torque contin-


resulting in the total torque being more and more negative as the speed rises towards normal value. However it must be remembered that although the field flux becomes stronger and back flux becomes weaker, their sum remains constant and exactly so the applied voltage is constant requiring constant air gap flux. (332)

Another important aspect of operation is that the field flux licks past to the back mmf wave at the double the syn. speed resulting in a double freq. torque and similarly back flux too glides past the forward mmf wave at double the syn. speed, again resulting in a double freq. torque. The presence of this double freq. torque creates ϕ D.M. noise and more prone to vibration than a comparable 3- ϕ D.M. This again is not unexpected. Since - ϕ instantaneous power always contains double freq. oscillating power component.


The 1- ϕ motor can be placed either on rubber mat or other springy foundation to limit the vibration and noise from spreading to the surrounding.

Equivalent Ckt →

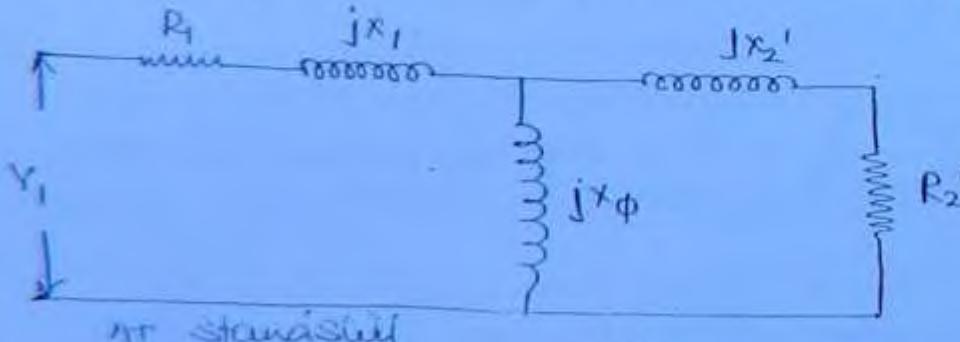(of 1- ϕ I.M. acc. to double revolving field theory)




At standstill

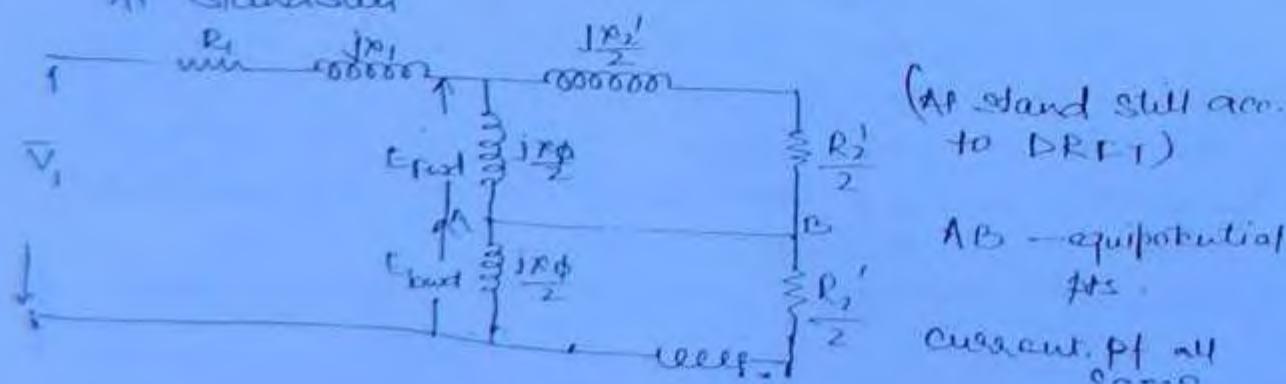

(At stand still acc.
to DRFT)

AB - equipotential
pts.

Current pt. of all

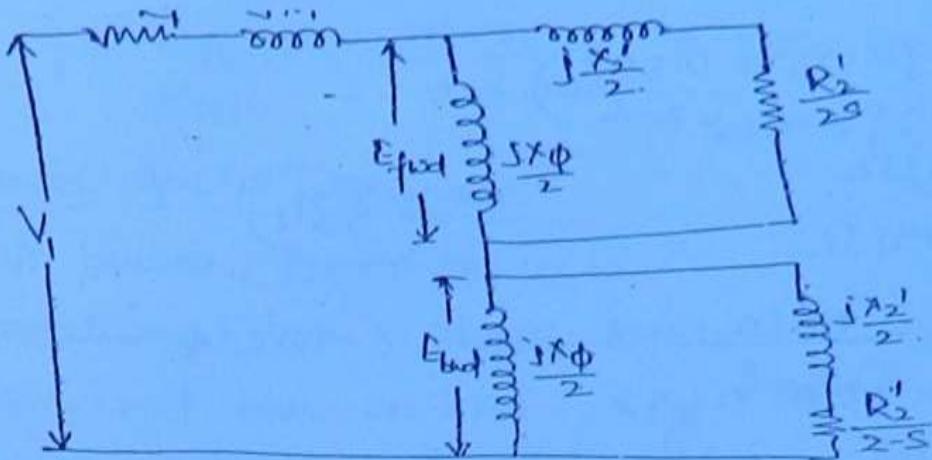

333

In motion slip 's' acc to double revolving fbd theory

$\frac{R_1'}{s} \uparrow, Z_{Fwd} \uparrow, \Rightarrow E_{Fwd} \uparrow, \phi \uparrow$

$\frac{R_2'}{2(2-s)} \downarrow, Z_{Bwd} \downarrow, E_{Bwd} \downarrow, \phi \downarrow.$

Q. A 180 W, 110 V, 60 Hz, 4 pole, 1 φ I.M. has the following constants —

$$R_1 = 2.02 \Omega$$

$$X_1 = 2.73 \Omega$$

$$R_2' = 4.12 \Omega$$


$$X_2' = 2.12 \Omega$$

$$X_\phi = 66.8 \Omega$$

$$\text{core loss} = 24 \text{ W}$$

Friction and windage = 13 W. For a slip of 0.05, determine stator I, P_f , power O/P, speed, torque & η when this motor is running at rated voltage and freq.

Ans.

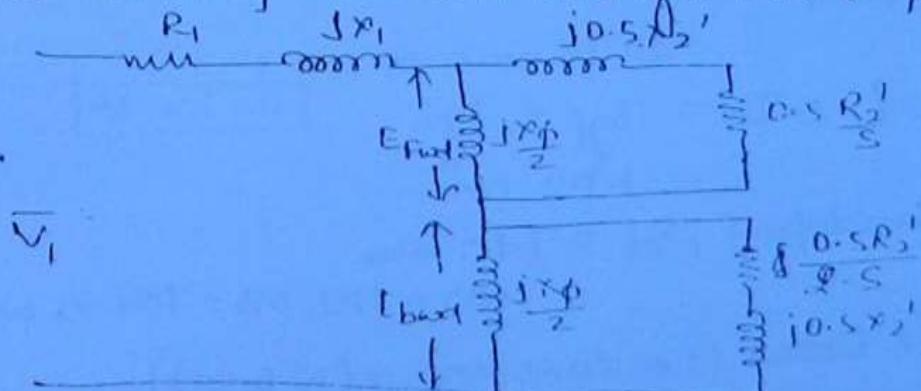

$$Z_f = (j0.5 X_\phi) \parallel ((j0.5 X_2' + \frac{j0.5 R_2'}{s}) / s)$$

$$= (15.9314 + j20.075) \Omega$$

$$Z_B = \left(j0.5x\phi \right) // \left(j0.5x_2' + \frac{0.5R_2'}{2-s} \right)$$

$$= (0.991 + j1.058) \Omega$$

$$R_f = 15.931 \Omega \quad R_b = 0.991 \Omega$$

(334)

$$I_i = \frac{\bar{V}_i}{\bar{Z}_i + \bar{Z}_f + \bar{Z}_b} = \frac{110 L 0^\circ}{\bar{Z}_i + \bar{Z}_f + \bar{Z}_b} = 3.605 \angle -51.63^\circ$$

$$\text{Input pf} = \cos 51.63^\circ$$

$$= 0.6207 \text{ lag}$$

$$\text{Input power} = P_{in} = V_i I_i \cos \phi$$

$$= 110 \times 3.605 \times 0.6207$$

$$P_{gf} = I_i^2 R_f = 207.04 \text{ W}$$

$$P_{gb} = I_i^2 R_b = 12.88 \text{ W}$$

$$\omega_{sm} = \frac{2}{P} \times 2\pi f$$

$$= 188.5 \text{ mech rad/s.}$$

$$\omega_m = (1-s) \omega_{sm}$$

$$= 179.08 \text{ mech rad/s.}$$

$$\nu = \frac{60\omega_m}{2\pi} = 1710 \text{ rpm.}$$

$$T_{gf} = \frac{P_{gf}}{\omega_{sm}} = 1.038 \text{ Nm.}$$

$$T_{gb} = \frac{P_{gb}}{\omega_{sm}} = 0.068 \text{ Nm.}$$

$$\text{Net torque developed} = T_d = T_{gf} - T_{gb}$$

$$= 1.02 \text{ Nm.}$$

$$\text{Net mech power developed, } P_d = T_d \times \omega_m$$

$$= 1.03 \times 179.08 = 184.45 \text{ W.}$$

$$\text{App power} = P_d - (\text{total losses (i.e. core loss + fan loss)})$$

$$= 184.45 - (24.713) = 147.735 \text{ W.}$$

$$\text{Opt torque} = \frac{P_{app}}{\omega_m} = \frac{147.735}{179.08} = 0.823 \text{ Nm}$$

$$\eta = \frac{P_{Op}}{P_{DIP}} = \frac{147.45}{246.14} = 0.5990 \text{ pu}$$

$$= 59.90\%.$$

Power Audit / Balance

(335)

O/P power; $P_{Op} = 147.45 \text{ W}$.

Rotational loss = $24 + 13 = 37 \text{ W}$.



Forward rotor cu loss = $s P_{gf} = 0.05 \times 207.04 = 10.352 \text{ W}$

Back rotor cu loss = $(2-s) P_{gb} = 25.116 \text{ W}$

Stator cu loss = $26.259 \text{ W} = I_r^2 R_1$

Total = $246.1699 \text{ W} = P_{in}$ (satisfied)


Revolving fld in a 2-Φ I.M. →

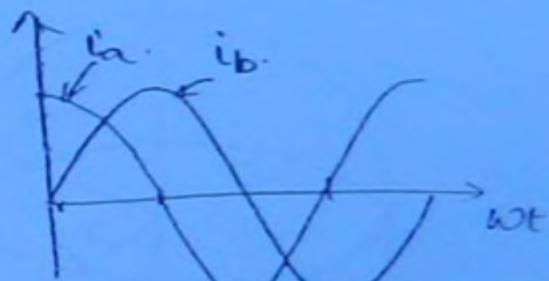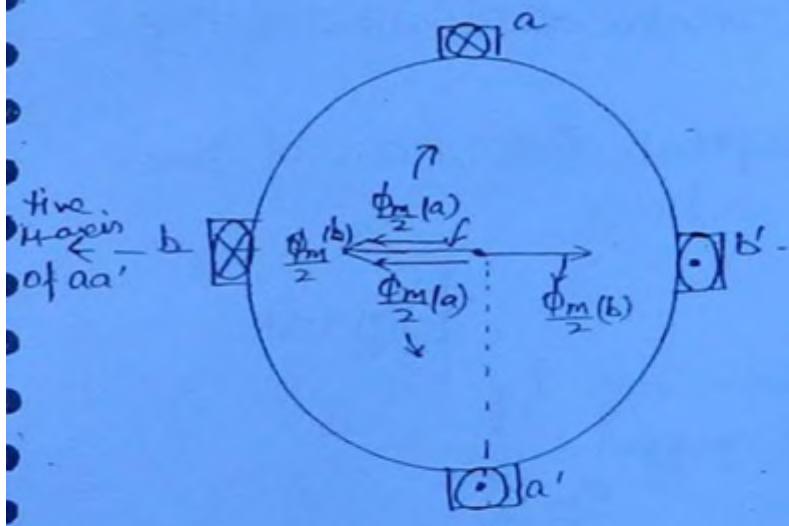

$\frac{\Phi_m}{2}(a)$ cancels $\frac{\Phi_m}{2}(b)$
so,

$$\Phi_{res} = \Phi_m \frac{w}{2} \quad (\text{at } wt = 0)$$

At $wt = 0$

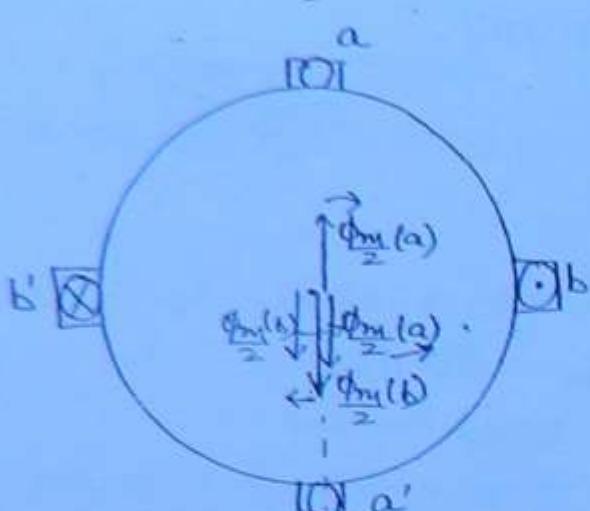


$$\omega t = 90^\circ$$

336

$\frac{\Phi_m}{2}(a)$ cancels $\frac{\Phi_m}{2}(b)$.
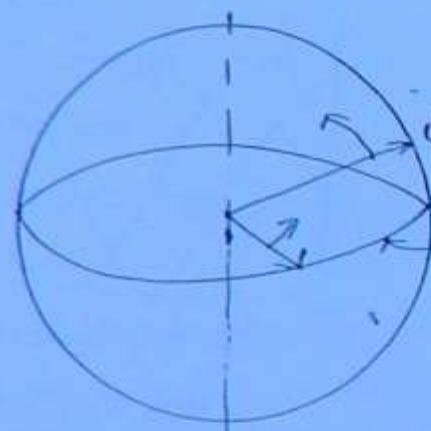
$$\begin{array}{c} \rightarrow \omega \\ \downarrow \\ \Phi_m = \Phi_{res} \\ (\text{at } \omega t = 90^\circ) \end{array}$$



Φ_{res} (Circular distribution of flux)
Elliptical distribution of flux



$\frac{\Phi_m}{2}(a)$
 $\frac{\Phi_m}{2}(b)$
Torque = 0.
as one flux oppo
the other.


Rotating torques

i.e. two torques support each other.

Opposing torque

Resistance start) Split phase 1-Φ I.M. ->

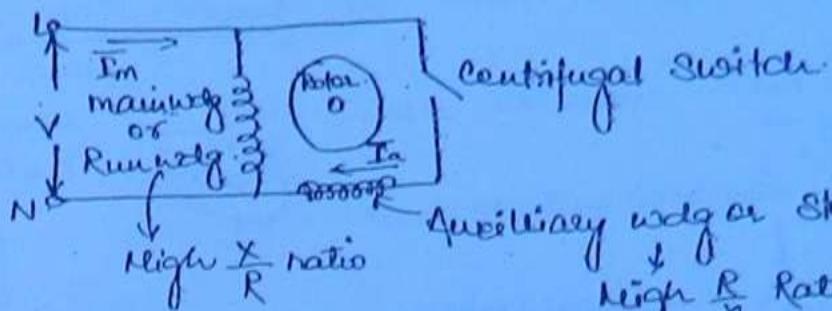Dn = direction of rotation can't be reversed by changing the supply terminals. It can be done by changing or reversing the terminals of any wdg.




337

Auxiliary wdg or Start wdg


High $\frac{X}{R}$ Ratio

[by using thin wires placed in top of the slot.]

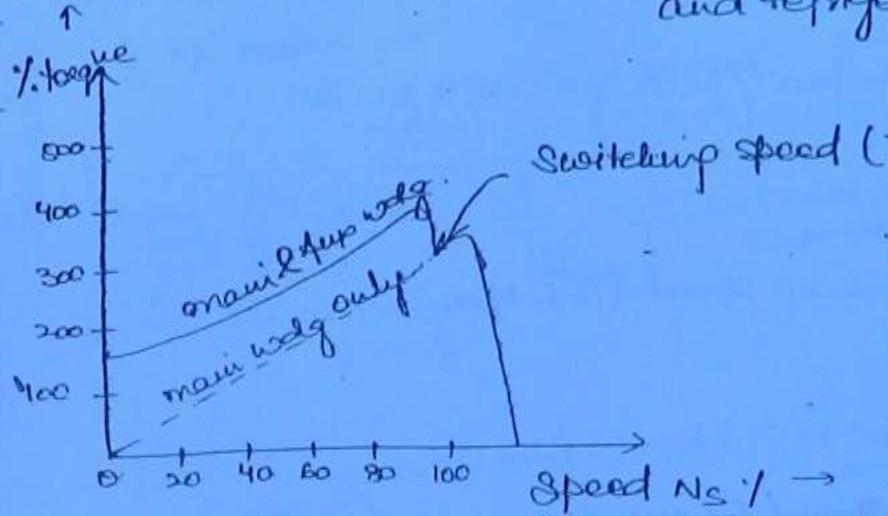Ex-fans, blowers, centrifugal pump and refrigerators (10 to 200W).



Switching speed (75% of Ns)

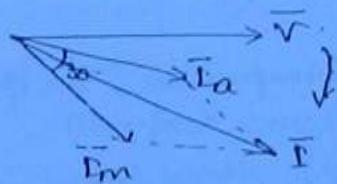

flux rotation from leading phase axis to lagging phase axis.



) flux rotation


(By reversing supply terminal)

(By reversing auxiliary wdg)

Capacitor type motor:


A) Capacitor start motor →

(338)

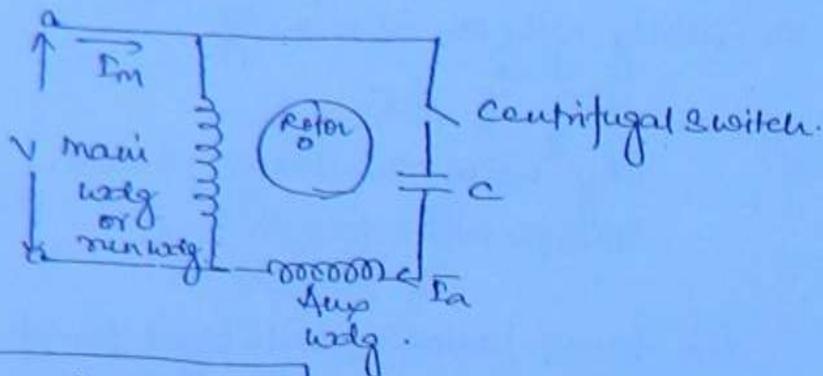


$$Z_{aux} = R - j(x_C - x_L)$$
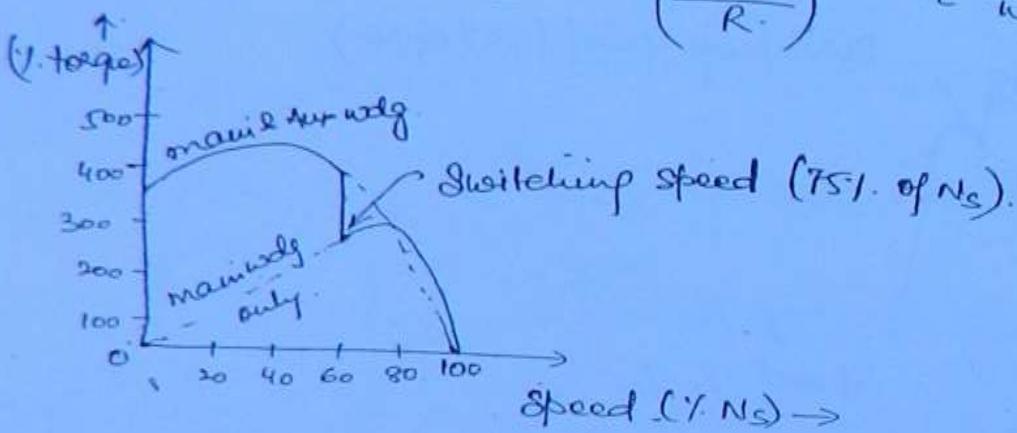
$$Z_{aux} = \sqrt{R^2 + (x_C - x_L)^2} \angle -\tan^{-1}\left(\frac{x_C - x_L}{R}\right) \quad x_C = \frac{1}{\omega C}$$



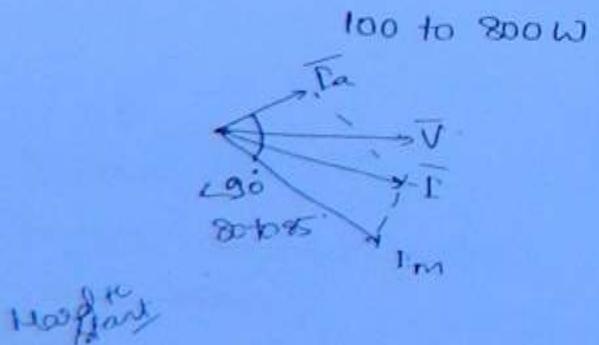Application → Refrigerator, air conditioner, compressor, reciprocating pump




a) at $x_C = x_L$

$|I_{st}| = \text{max.}$


b) $x_C > x_L$

$I_{st} \downarrow$, phase diff b/w V and I_a inc.

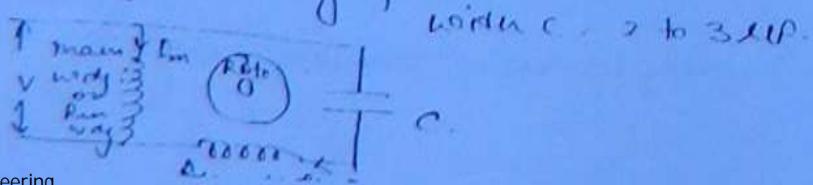b) Permanent split capacitor motor or capacitor run motor
eg - ceiling fans





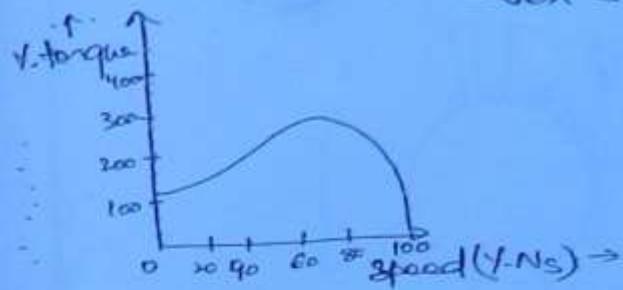It is not meant for hard to start load like compressor,
 - m/c tools.
 Balance 2 φ P.M. hence noiseless and vibration free, Improve
 η and better Pf
 - best starting condition but not best starting condition.




339

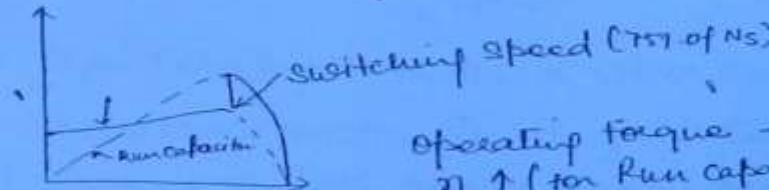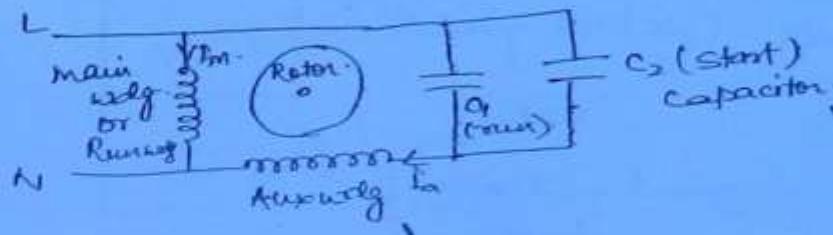→ Capacitor Start & Run motor or Two value capacitor motor →
 $\frac{1}{2}$ hp motor →
 $C_1 = 40 \mu F, C_2 = 300 \mu F$



Operating torque → good (start capacitor)
 $\eta \uparrow$ (for Run capacitor)





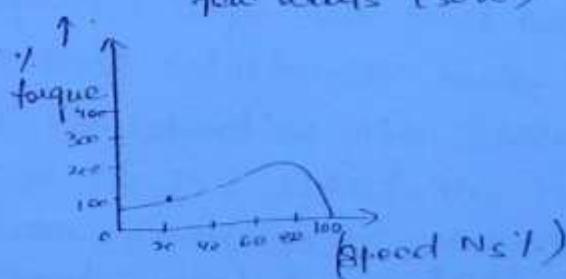
→ Shaded pole :-
 cheapest, small m/c (Hair dryer)
 few watts (50W)



Squirrel cage → Rotor.
 conc. wdg → 20% of slot, we have to short by shading ring.

- In the half, ϕ up to down
- In shading ring, ϕ ↑ up (bottom to up)
- ϕ is lagging in shaded part.
- maximum of flux leading to lagging.

(3) 40

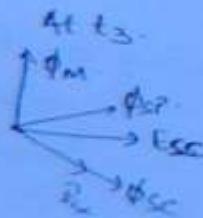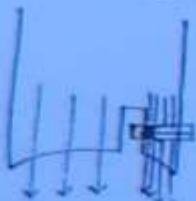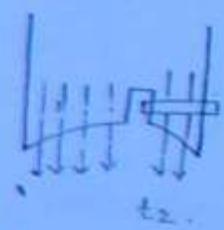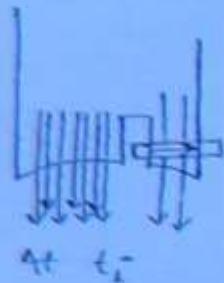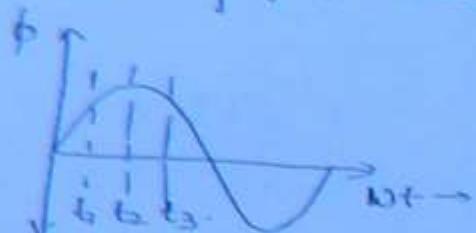

Main flux ϕ_m induces emf e_{sc} in the shading coil by \propto max action due to which I_{sc} flows through the coil which creates per ϕ_{sc} .

So, the shaded pole flux
 $\phi_{bp} = \phi_m + \phi_{sc}$


so, flux ϕ_m leads ϕ_{bp}
unintended pole rotation from leading to lagging phase axis i.e from

Single-phase Syn. Motor :-


1-φ Syn. Reluctance motor :-

(241)

or Self starting Syn. Reluctance motor.

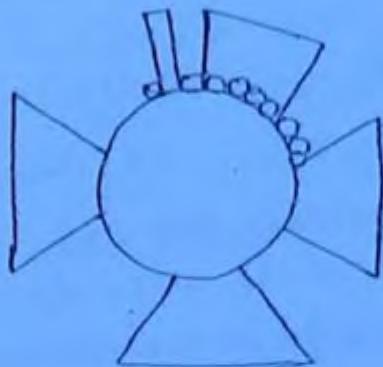

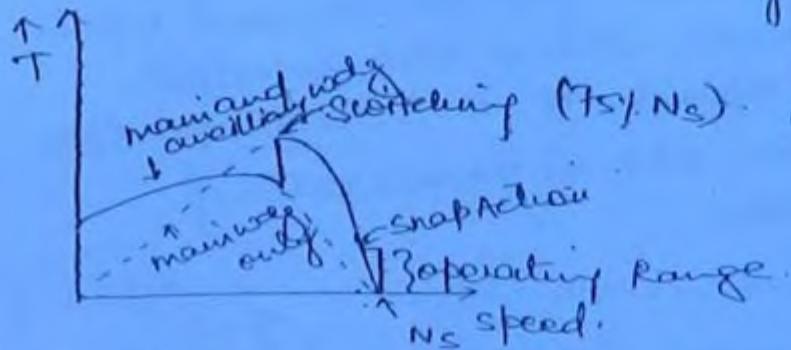Saliency is introduced by cutting some of the rotor teeth.



E.g. Electric clocks, timers, where exact syn. speed is required and is required for small capacity.


1-φ Syn. Reluctance motor is also known as self starting Syn. Reluctance motor. It is just like resistance start split phase I-E I.M. except that some saliency in the rotor structure by removing some rotor teeth at appropriate places to avoid provide the required no. of poles. The squirrel cage bar and end shorting rings are left intact so that reluctance motor can start as I.M. When 1-φ supply is switched on the stator of motor, it starts as 1-φ P.M. At 75% speed, the auxiliary wdg disconnected and motor continues to accelerate the load. As close to syn. speed, reluctance torque causes the rotor to snap into synchronism and henceforth the motor continues to run at syn. speed as a reluctance motor. While operating at syn. speed, the rotor cage becomes redundant but any deviation from syn. speed operation is opposed by the rotor cage and it therefore rotates at similar A.C. as shown under

In Syn. m/c.

The absence of dc excitation greatly reduces the max. torque and hence its size is several times larger than that of regular syn. motor having the same H.P. and the speed rating. The adv. of this motor are that it gives practically maintenance free operation; as there are no slip rings, no brushes and no dc fld wdg. However its pf is very low because it requires a large amount of lagging reactive power for its excitation to be sync. in effective reactive gap consequent upon removal of some rotor teeth. Since the speed of motor is const at syn. speed, it is suitable for like linear timers and their tables etc in small rating.
↓
Rec'd tables.

Hysteresis Motor →

(242)

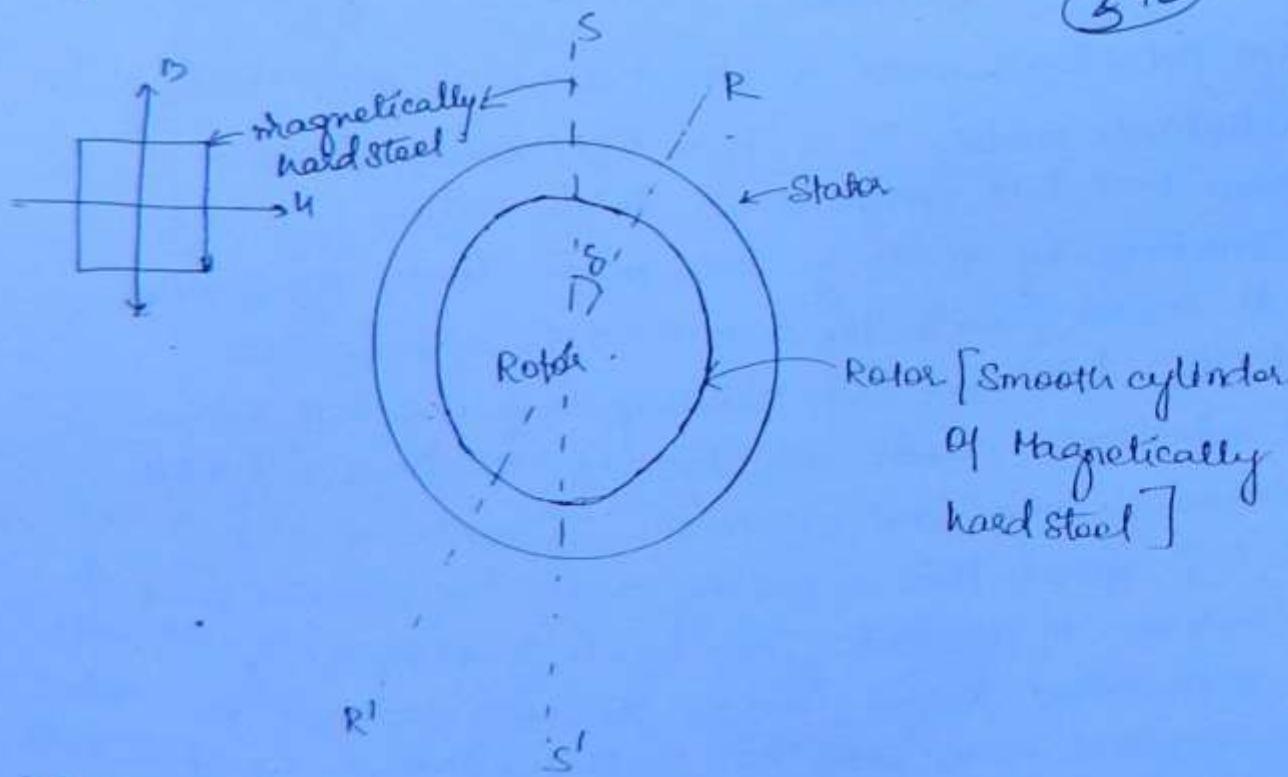

Rotor →



Smooth cylinder of permanent magnet hard steel

By loop → will be square


Shape →

S → decided by property of material and almost const.

∴ const hysteresis torque is produced.

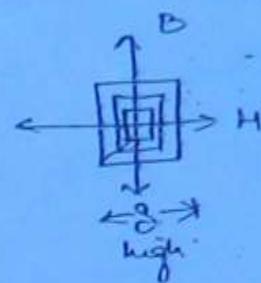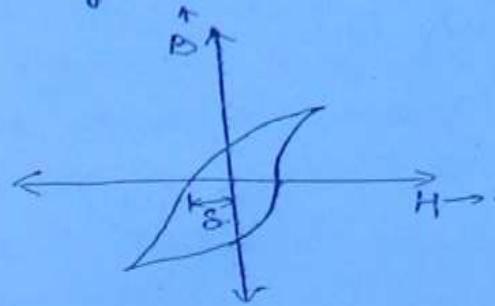

343

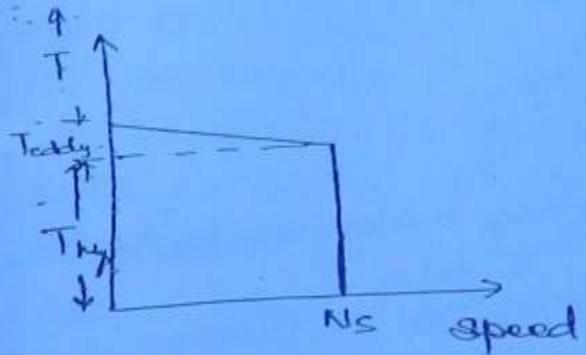

eddy torque :— $P_e = K_{ef}^2 B_m^2$

$P_e = R_e (sf)^2 B_m^2 \rightarrow$ Rotateddy current loss.

air gap power due to eddy current

$$\begin{aligned} P_g(\text{eddy}) &\approx \frac{P_e}{s} \\ \text{air gap power} &= \frac{K_{ef}(sf)^2 B_m^2}{s} \\ \text{due to eddy} &= SK_{ef}^2 B_m^2 \end{aligned}$$

$$T_{\text{eddy}} = \frac{P_g(\text{eddy})}{W_{SM}}$$

$$= \frac{SK_{ef}^2 B_m^2}{W_{SM}}$$

$$T_{\text{eddy}} \propto S$$

Hysteresis loss :-

$$P_h = K_h (Sf) B_m^n \rightarrow \text{Rotor hysteresis loss.}$$

$$\therefore P_g \text{ due to hysteresis} = \frac{P_h}{S}$$
$$= \frac{K_h S f B_m^n}{S}$$
$$= K_h f B_m^n.$$

(344)

$$T_{Hys} = \frac{P_g (hys)}{W_{sm}}$$

$$= \frac{K_h f B_m}{W_{sm}}$$

= const.

$$\frac{Idw_m}{dt} \rightarrow T_e - T_L$$

If $T_e > T_L$, then the motor accelerates or starts for any inertia.
If has a stator similar to that of permanent split capacitor type 1φ I.M.


costlier, less noise, preferable over hysteresis reluctance motor.

It has a stator similar to that of a permanent split capacitor type single φ I.M. Capacitor is chosen to establish approximately balanced two phase condition within the rotor wdg. The rotor is smooth solid cylinder of Magnecilly hard steel like Smax and alnico etc without wdg teeth for cost saving, a thick annular ring can be mounted on a cylinder of Aluminium or other non magnetic material. The axis CC' of stator flux revolves at syn. speed and induces eddy current in the rotor causing hysteresis, magnetization of rotor lags behind inducing it behind and therefore the axis RR' of rotor flux are lags behind the axis of the stator flux wave by hysteric lag angle θ . When the rotor is starting the starting hysteresis torque is $\propto \theta$.

product of stator flux, rotor flux and $\sin \theta$. While the rotor accelerates, θ remains const, being a property of material and it is independent of rate at which hysteresis loop is traversed. Hysteresis motor therefore develops const hysteresis torque right up to syn speed. As the rotor approaches syn speed, the freq of rotor current decreases and at syn speed the rotor material gets permanently magnetised in one dirz as a result of high retentivity of rotor material. In contrast to a syn. reluctance motor that snaps its load into synchronism from induction motor char, a hys. motor can synchronise any load which it can accelerate no matter how great inertia is. After reaching syn speed, motor continues to run with syn speed with 0 eddy current torque with only hysteresis torque. It adjust its torque angle so as to develop the torque required by the load. The hysteresis motor is quite a smooth running motor because of its stator design, smooth rotor periphery. It is suitable for disk and office speed sensitive device like record players, tape recorder and compact disc players etc.

STEPPER MOTOR

345

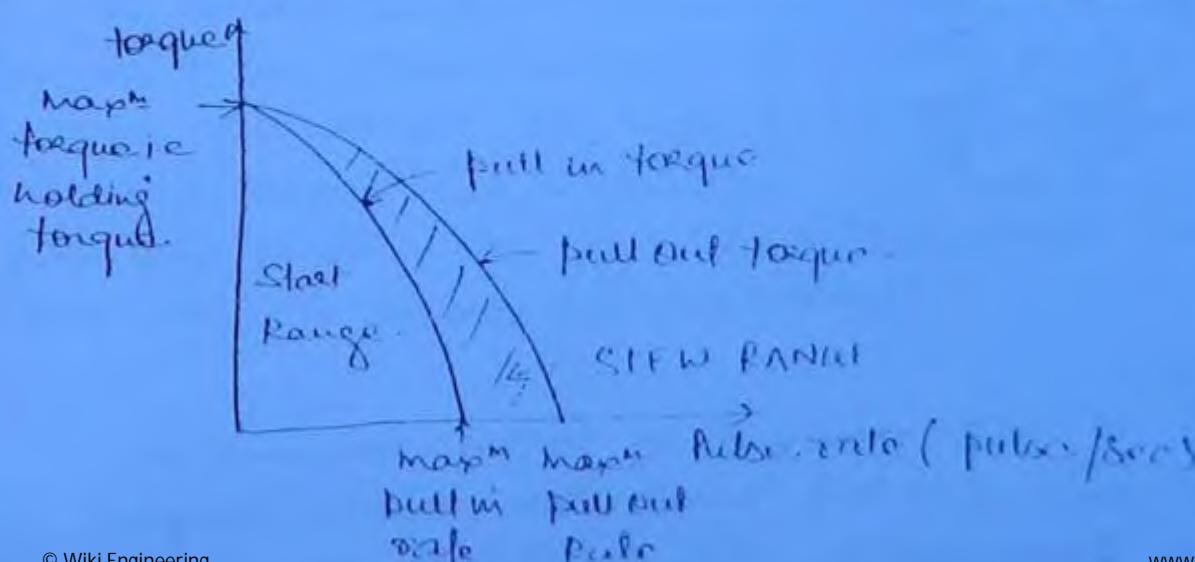

$N_r = N_s$ No. of rotor teeth = No. of stator teeth

No. of rotor teeth = N_r .

Then tooth pitch = $\frac{360^\circ}{N_r}$

If No. of stacks = m .

Then step size, $\Delta\theta = \frac{360^\circ}{m N_r}$

(346)

No. of steps per revolution = $\frac{360^\circ}{\Delta\theta}$
= $m N_r$.

Speed = $\frac{\Delta\theta \times \text{Pulse rate in pulse per sec.}}{360^\circ} \text{ rev/s}$

$$= \frac{\Delta\theta \times \text{pulse rate}}{360^\circ} \times 60 \text{ rpm.}$$

$$\Rightarrow \text{Speed} = \frac{\Delta\theta \times \text{pulse rate}}{6} \text{ rpm.}$$

Then $N_s > N_r$.

Stator tooth pitch = $\frac{360^\circ}{N_s}$

Rotor tooth pitch = $\frac{360^\circ}{N_r}$

Step size = $\frac{360^\circ}{N_r} - \frac{360^\circ}{N_s}$

$$= 360^\circ \left(\frac{N_s - N_r}{N_s N_r} \right)$$

Lubing torque \rightarrow

It is defined as the amount of torque required to move the rotor one full step with the stator energised.
is max torque produced by the motor ad standstly

Detecte torque :-

- It is called residual torque or straining torque.
- It is defined as max load torque that can be applied of an unexcited torque without causing continuous rotation. It is generally 10% of the holding torque in permanent magnet step up motor.

247

Pulling torque :-

- It is defined as torque developed by motor at which motor can start, synchronise, stop or reverse for diff values of load torque. Accordingly in the start range the load position follows the pulses without loosing steps and can start, stop, reverse and on command.

Pull out torque :-

- It is defined as the torque developed by the motor at which motor can run for diff values for load torque if already synchronise. But, it can not start, stop or reverse on command. Accordingly in the slow range pulse rate is very high, the load velo here follows the pulse rate w/o loosing steps but can not start stop or reverse on command.

Comment :-

- It may be realise that increasing pulse rate motor may provide less torque because the stator wdy current pattern gets altered at high pulse rate. Consequently with less torque and within time to climb the load from one position to the next. The rotor fails to start, stop, or reverse on command.

Types of Stepper motor:-

1) Variable Reluctance Stepper Motor:- It has unexcited rotor teeth but excited stator teeth. It can be single stack type or multiple stack type.

Max pulse rate is as high as 1200 pulses per sec and step size may be from 15° down to 2°.

2) Permanent magnet :-


It has PM rotor has higher inertia than that of variable reluctance stepper Motor. Consequently Permanent Magnet Stepper motor has slower acc. and its max pulse rate is 300 pulses per sec. Its step size is 30° to 90°. However, it produces more torque per ampere stator current as compare to a variable reluctance Stepper motor.

Hybrid Stepper motor :-

As the name suggest, it employs a combination of variable reluctance and permanent magnet Stepper motor. It has a rotor made of axial PM & the middle bias and ferromagnetic teeth after sec. A few ferromagnetic teeth acquire the polarity on the pole on which they are mounted. The hybrid motor therefore combines the small step feature of a variable reluctance type Stepper motor with the high torque feature of PM type. Max pulse rate is 2000 pulse per sec. and the possible step size as low as 1.8°. However hybrid motor is more expensive than the variable reluctance motor because of obvious reasons.

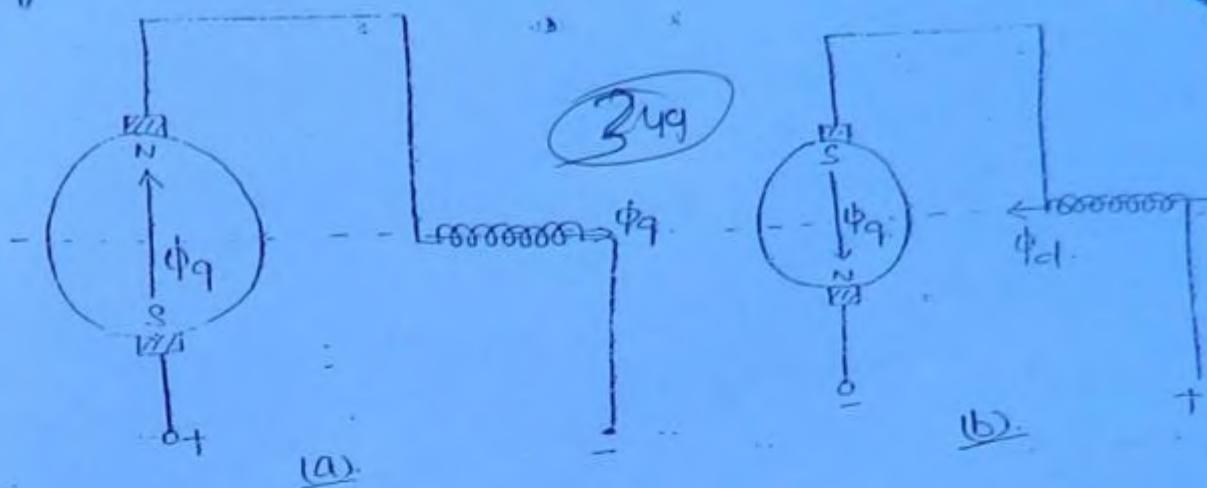(Q48)

Single phase series motor / Universal motor



If an ac is applied to an ordinary dc series motor then for 1 half cycle fig(a) and for other half cycle fig(b) is shown.

The interaction of ϕ_d and ϕ_q results in development of torque. And in fig (a)(b) the torque is in clockwise dir². For ac source, dc series motor produces unidirectional torque. Fractional kw ac series motors make use of salient pole construction. But for large size motors, uniform air gap m/c is used.

The uncompensated or plain series motor is usually constructed in fractional kw sizes. Small 1-φ ac series motors, which can operate satisfactorily both on dc & ac are called universal motors.

Upto about 200 watts → Range.

Applications →

- Drills
- Vacuum cleaners
- Food mixers
- Sewing m/c
- M/c computing m/c

350